

Q1

20/7/22

Electrical circuit

Current - rate of flow of charge

$$\text{Current } \rightarrow I = \frac{dq}{dt}$$

Voltage → Potential difference

↓ Work done / Energy

Potential → Work done / Change

$$V_{ab} = \frac{dw}{dq}$$

$$\text{Power} = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = VI$$

Instantaneous Power

EMF = That charge which creates potential difference

Electric circuit = must have at least one closed path


Electrical network = Connection of elements

Series, Parallel




VDR = Voltage division rule

CDR = Current division rule

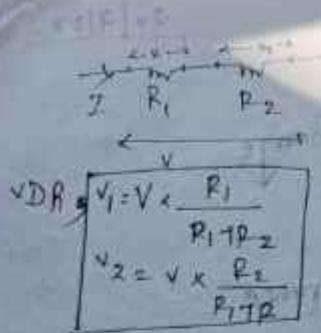

[Eqn no.]
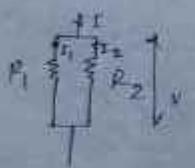
$$\text{VDR} \quad \begin{cases} V_1 = V \times \frac{R_1}{R_1 + R_2} \\ V_2 = V \times \frac{R_2}{R_1 + R_2} \end{cases}$$




$$\text{CDR}, \begin{cases} I_1 = I \times \frac{R_2}{R_1 + R_2} \\ I_2 = I \times \frac{R_1}{R_1 + R_2} \end{cases}$$

- Active devices → that generate S energy
(Voltage current Source, Independent not independent with same)

- Passive devices
(Resistors, Capacitors, Inductances)

- Resistance is distributed
→ wire or conductor
lumped form / distributed form

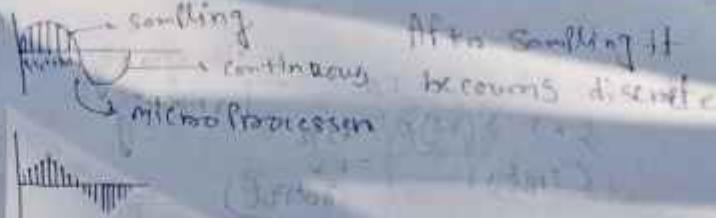- Continuous and discrete signals
A signal is continuous w.r.t time



After Sampling it becomes discrete


22/3/22

Linear elements

conditions - i) Principle of superposition
ii) Principle of homogeneity

i) Superposition - additive property

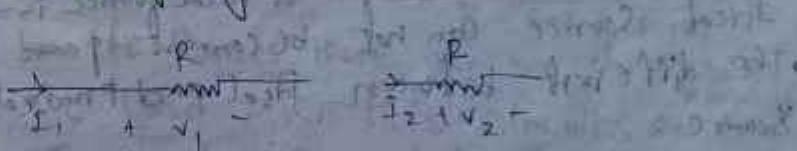ii) Principle of homogeneity - scaling property



$$V_1 = I_1 R \quad V_2 = I_2 R$$

$$(I_1 + I_2) R = I_1 R + I_2 R \quad \left[\begin{array}{l} \text{additive property} \\ (\text{In put}) \end{array} \right]$$

Inputs are not (output)

If

2nd in parallel
is also passive
[means still linear]

$$\begin{array}{l} I \rightarrow v = IR \\ \therefore v = (kV)R = IR \end{array}$$


homogeneity
linearity

(input) (output)

If we multiply any constant in the input we will get the output is also multiplied with the same constant.
Electronics components are non linear.
Components: (Transistor)

Linear components (Resistor)

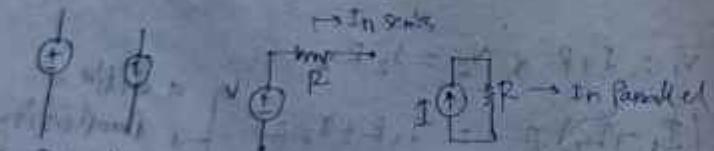- Source transformation [The internal resistance of ideal source is zero]
- Ideal source can not be current source
- The diff. between ideal and practical source



Ideal
current and voltage
source

Practical
voltage and current
source

[R is always in series
with voltage and is
parallel with current]




Source Transformation




Source Transformation

Example

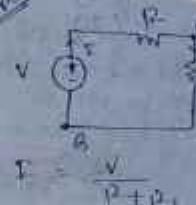

$$I = \frac{V}{R + R_1}$$

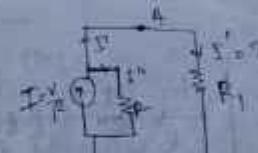

$$I = \frac{V}{R} - \frac{V}{R + R_1} = \frac{V}{R_1}$$


For the sources there are no changes in the load. So this circuits are equivalent. The combination for each of sources (of this picture) to the element R_1 is same. So they are called equivalent.

Dependent Sources

Indicated by diamond

→ Dependent
Vol. Source

→ Current
Source

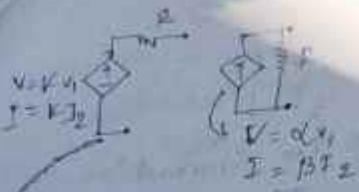

Classification - 4 type of dependent sources

VCCS → Current Control Voltage Source [$\frac{V_{out}}{V_{in}} = k$]

CCCS → Current Control Current Source [$\frac{I_{out}}{V_{in}} = k$]

VCVS → Voltage Control Voltage Source [$\frac{V_{out}}{V_{in}} = k$]

VCCS → Voltage Control Current Source [$\frac{I_{out}}{V_{in}} = k$]

R

$$\begin{array}{l} R \\ \text{---} \\ I = \frac{V}{R} \\ V = IR \\ (DC) \end{array}$$

$$I = \frac{V}{R} \quad (+)$$

$$V = V_m \sin \omega t$$

$$I = I_m \sin \omega t$$

$$\begin{aligned} P_{avg} &= \frac{1}{2\pi} \int_0^{2\pi} P dt = \frac{1}{2\pi} \int_0^{2\pi} V_m I_m \sin \omega t \cdot I_m \cos \omega t dt \\ &= \frac{V_m I_m}{2\pi L} \int_0^{2\pi} (1 + \cos 2\omega t) dt \end{aligned}$$

$$= \frac{V_m I_m}{2\pi L} \left[\omega t + \frac{\sin 2\omega t}{2} \right]_0^{2\pi}$$

$$= \frac{V_m I_m}{2\pi L} \cdot [2\pi - 0 - 0] = 0$$

$$= \frac{V_m I_m}{2\pi L}$$

$$= \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} = \frac{V_m I_m}{2}$$

R = $\frac{V}{I}$

L → EMF

- **Eddy emf** - When we pass ac current through a coil, and we get a varying flux. As this flux is varying, there are no physical change. They cancel out each other and

• **Dynamic emf** -

Eddy emf = when we pass ac current through a coil, as the ac current is varying for one cycle it will give flux and for the another cycle it will give just the opposite flux, these 2 flux cancel out each other. So there will be no physical change, we give static effect.

$$\therefore v = L \frac{di}{dt} \quad [L = \text{Self inductance}]$$

$$= L \frac{d}{dt} (I_m \sin \omega t)$$

$$= WL I_m \cos \omega t$$

$$= WL I_m \cos \omega t$$

$$v = WL I_m \sin(\omega t + \frac{\pi}{2})$$

$$v = V_m \sin(\omega t + \frac{\pi}{2})$$

where $V_m = WL \times I_m$ [$X_L = \text{Inductive reactance}$]

$$\frac{V_m}{\sqrt{2}} = X_L \frac{I_m}{\sqrt{2}}$$

$$V = X_L I$$



$$Q = \frac{q}{V} \rightarrow q = CV = C V_{\text{max}} \sin \omega t$$

$$I = \frac{dq}{dt}$$

$$I = \frac{d}{dt} (CV_{\text{max}} \sin \omega t)$$

$$= \omega C V_{\text{max}} \cos \omega t$$

$$I = \omega C V_{\text{max}} \cos \omega t = \omega C V_{\text{max}} \sin(\omega t + \frac{\pi}{2})$$

$$I = I_m \sin \omega t$$

$$\text{where, } I_m = \frac{\omega C V_{\text{max}}}{R} = \frac{V_{\text{max}}}{R} \times \frac{\omega C}{1} \quad [R > 0 \text{, positive resistance}]$$

$$I = I_m V_{\text{max}} \sin(\omega t + \frac{\pi}{2})$$

$$I = \frac{dq}{dt}$$

$$\Rightarrow I_m \sin \omega t = \frac{dq}{dt}$$

$$\Rightarrow \int dq = I_m \sin \omega t dt$$

$$\Rightarrow q = \frac{I_m \cos \omega t}{\omega}$$

$$\Rightarrow Q = \frac{I_m}{\omega} \sin(\omega t - \frac{\pi}{2})$$

$$V = \frac{q}{C} = \frac{I_m}{\omega C} \sin(\omega t - \frac{\pi}{2}) = \frac{I_m}{\omega C} \sin(\omega t - \frac{\pi}{2})$$

$$V = V_{\text{max}} \sin(\omega t - \frac{\pi}{2})$$

① The total charge entering a terminal is given by $q = \int I \sin \omega t dt$ calculate the current at $t = 0.5s$.

$$I = \frac{dq}{dt}$$

$$= \frac{d}{dt} (5t \sin 4\pi t \times 10^3)$$

$$= 5 \times 10^{-3} [5 \cos 4\pi t \times 4\pi + \sin 4\pi t]$$

$$\text{at } t = 0.5s = 5 \times 10^{-3} [0.5 \cos 4\pi \times 0.5 + \sin 4\pi \times 0.5]$$

Hence

$$[0.5 \times 14] \\ [0.5 \times 100]$$

$$I = 5 \times 0.914 + 5 \sin 4\pi \times 0.5 \\ = 3.44 \times 31.41 \text{ mA} / 1000 \text{ A}$$

② Find the power delivered to an element at $t = 3ms$, if the current entering it's positive terminal is $I = 5 \cos 3600\pi t$ and the voltage is $V = 3 \frac{dI}{dt}$

Find the power delivered

$$\Rightarrow P = VI \\ = 3I \times \frac{dI}{dt} \quad \text{at } t = 3ms \\ = 3 \times (5 \cos 3600\pi t) \times 3 \times 10^{-3}$$

$$= 15 \times 0.0714 \times 3 \times 10^{-3} \\ = 0.0714 \times 6.67 \times 10^{-3} \\ = 53.166 \text{ mW}$$

$$b) N = 3 \text{ A}$$

$$P = VI$$

$$= 3 \frac{dI}{dt} \cdot I$$

$$= 3(5 \cos 60\pi t) \frac{d}{dt}(5 \cos 60\pi t)$$

$$= -15 \times 5 \cos 60\pi t \sin 60\pi t \times 60\pi$$

$$\text{at } t=3 = -15 \times 60\pi t \times \cos 60\pi t \times \sin 60\pi t \times 60\pi$$

$$= -139.5 \text{ kW} \quad [t=180^\circ]$$

$$= -366.45 \text{ kW} \quad [-180^\circ \text{ short circuit}]$$

$$= -150 \times 60\pi \times 3.14 \times 0.5 \times 0.5$$

$$= -6.39 \times 10^3$$

$$= -6.39 \text{ kW}$$

$$\begin{aligned} &= -150 \times 60\pi \times 3.14 \times 0.5 \times 0.5 \\ &= -2260.3 \text{ kW} \quad \text{using red} \end{aligned}$$

• Load \rightarrow deliver/supply = +ve

• load \rightarrow absorb = +ve

2) \downarrow pointers toward +ve end \rightarrow to


• load \rightarrow absorb current with



Behaviour remain

same, whatever we do in?

though
internal

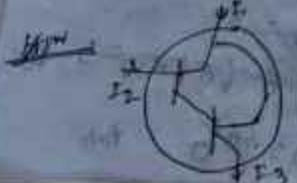

① Current - the fundamental electric quantity
An electric current is a flow of electrical charge \rightarrow electric charge flows when there is voltage present across a conductor

$$I(\text{current}) = \frac{dV}{dt}$$

② Voltage / Potential difference - voltage static
potential difference is the difference in electric potential between two points, which is defined as work needed per unit of charge to move a test charge between the two points.


$$\frac{V}{\text{volts}} = \frac{\text{J}}{\text{coulombs}}$$

③ Power - The rate of doing work or the rate of using energy is called power

$$P(\text{instantaneous power}) = \frac{dW}{dt} = \frac{dW}{dt} \cdot \frac{dI}{dP} = VI$$

④ Instantaneous value - The value of alternating quantity at any particular instant is called instantaneous value. It is denoted by lower letters, such as e for emf, i for current, V for voltage

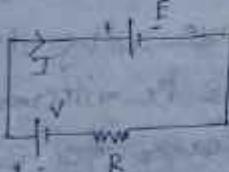⑤ Emf - we define it as the voltage of battery when current is flowing while terminal potential difference is voltage across battery when connected to a resistor and current is flowing through it. Emf is that energy which weak potential difference.



⑥ Electric Circuit - An electronic circuit is composed of individual electronic components such as resistors, capacitors, transistors etc connected by conductive wires through which electric current can flow if must possess one closed path.

⑦ Electric Network - It is connection of electric elements, such as resistors, capacitors, transistors etc.

⑧ Active devices - An active device is only type of circuit component with the ability to electrically control electric charge flow (electricity controlling electricity). In order for a circuit to be properly called electronic, it must contain at least one active device. Active devices generates energy. Ex: Voltage / current source (dependent and independent). Include active devices examples - Battery, generator, transistors, vacuum tubes etc.

⑨ Passive devices - This ~~are~~ do not generate energy, but can store / consume it or dissipate it. Passive devices are the main components used in electronics such as resistors, inductors, transformers, capacitors which together are required to build any electrical or electronic circuit ex - Resistors, capacitors, diodes etc.

⑩ Lumped network - A lumped network is usually a simplification of distributed networks such as a transmission line. A transmission line has built in resistance, inductance and capacitance for every tiny fraction of its length.

It would take a lot of collectors
to do any collection on its own.

(1) Distributed network - A distributed network is a type of computer network that is spread over different networks. This provides a single data communication network, which can be managed jointly or separately by each network. Besides shared communication within the network, a distributed network often also distributes processing.

(2) Continuous signal - A continuous signal is a continuous time signal is a varying quantity (a signal) whose domain, which is often time, is a continuum. That is the function's domain is an uncountable set. The function itself need not be continuous.

(3) Discrete signal - A discrete signal or discrete time signal is a sequence of values that correspond to particular instants in time. The time instants at which the signal is defined are the signal's sample times and the associated signal values are the signal's samples.

(4) Linear elements - These are elements in which the constituent relation i.e. relation between voltage and current, is a linear function. They obey superposition principle. Ex - Resistance, capacitance, inductance etc.

(5) Nonlinear elements - In non-linear circuit, the non-linear elements are an electrical element and it will not have any linear relationship between the current and voltage. Ex - Diode. Some of the nonlinear elements are not there in the electric circuit. It is called a linear circuit.

(6) Principle of Superposition - This is also known as Superposition Property, states that for all linear systems, the net response caused by two or more stimuli is the sum of the responses that would have been caused by each stimulus individually.

(7) Principle of Homogeneity - It states that dimensions of each of the terms of a dimensional equation on both sides should be the same. This helps to convert the principle.

- the units from one form to another.
- (16) Scaling property - The time scaling property of Fourier transform states that if a signal is scaled in time by a quantity (a), then its Fourier transformation is compressed in frequency by the same amount. (no need)
- (17) Additive property - It is a ~~set of~~ (no need)
- (18) Source transformation - It is a process of simplifying a circuit solution especially with mixed sources by transforming voltage source into current sources and vice versa, using Thevenin's theorem and Norton's theorem respectively.
- (19) Ideal Source - These are those imaginary electrical sources that provides constant voltage or current to the circuit regardless of the load current. These ideal sources don't have any internal resistance where it is impossible to build a source with zero internal resistance.

- (20) Practical Source - A practical source is a two terminal device having some resistance connected across its terminals. Unlike ideal current source, the output current of practical source depends on the voltage of the source. The more it is voltage, the less will be the current.
- (21) Diff between ideal and practical source - The ideal source don't have any internal resistance i.e. $R_s = 0$. Again the practical source has internal resistance. The ideal source provides a constant voltage and current regardless of the load current. $R_s \neq 0$. Again the practical source output current of depends on the voltage of the source.
- (22) VCRS - Where the actual source voltage is controlled by the voltage across any element elsewhere in that circuit.
- VCCS - A amplifier that converts a voltage to a current, where the actual source voltage is controlled by the current through any element elsewhere in that circuit.

CCVS - A voltage source that depends on a current input


CCS - A current source that depends on a current input

(2) static emf - when the conductor is stationary and the magnetic field is changing, the induced EMF is such a way is known as statically induced EMF. It is so called because the EMF is induced in a conductor which is stationary. Ex - transformers.

(3) Dynamic emf - when the conductor is moved in a stationary magnetic field so that the magnetic flux linking with it changes in magnitude, as the conductor is subjected to a changing magnetic therefore an EMF will be induced in it. The EMF induced in this way is known as dynamically induced EMF. Ex - DC or AC generators.

(4) Dependent Source - In the theory of electrical networks, a dependent source is a voltage or a current source whose value depends on a voltage or current, elsewhere in the network. Dependent sources are useful, for example, in modeling the behaviour of amplifiers. It is represented by diamond shape.

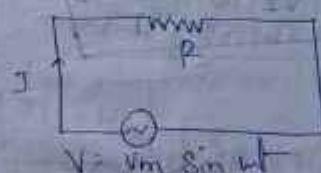(5) pure resistance - The circuit which contains a pure resistance and has negligible inductance is called pure resistive circuit.




For pure resistance,

$$\text{The current in the circuit is } I = \frac{V}{R}$$

$$I = \frac{V_m \sin \omega t}{R} \quad \text{for AC circuit}$$
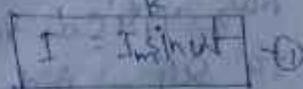
$$I = I_m \sin \omega t \quad \text{for DC circuit}$$



$$[I = I_m = \frac{V_m}{R}]$$

The current will be maximum
 $\omega t = \frac{\pi}{2}$ and $\sin \omega t = 1$ > netone

$$I_m = \frac{V_m}{R}$$


By placing $I_m \sin(\omega t)$ in the J.C.

$$I = I_m \sin \omega t$$

The avg power of a pure resistive circuit

$$P_{av} = \frac{V_m I_m}{2} = \frac{V_m^2}{\sqrt{2}} \times \frac{I_m}{\sqrt{2}} = \frac{V_{rms}^2 I_m}{2}$$

② Pure inductance-

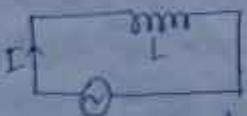

$$V = V_m \sin \omega t$$

The voltage is $V = V_m \sin \omega t$

The self induced emf of the coil is $-L \frac{dI}{dt}$.
 Now applied voltage is equal and opposite to self-induced emf. Therefore,
 $+V_m \sin \omega t$ net emf,

$$+L \frac{dI}{dt} = 0 \quad [R=0, I_P=0]$$

$$\therefore V = L \frac{dI}{dt}$$

$$\Rightarrow V_m \sin \omega t = L \frac{dI}{dt}$$

$$\therefore I = \frac{V_m}{L} \sin \omega t$$

$$\therefore I = -\frac{V_m}{WL} \cos \omega t$$

$$\therefore I = \frac{V_m}{WL} \sin(\omega t + \frac{\pi}{2})$$

The current I will be zero when,
 $\sin(\omega t + \frac{\pi}{2}) = 0 \Rightarrow \omega t + \frac{\pi}{2} = \pi$

$$\therefore I_m = \frac{V_m}{WL}$$

$$I = I_m \sin(\omega t + \frac{\pi}{2})$$

[The voltage is leading
 and the current is
 lagging in the
 case for pure inductive
 circuit]

$$X_L = WL$$

$$[X_L = \text{Inductive resistance}]$$

$$P_{av} = 0$$

The avg power absorbed over a complete cycle in pure inductor is zero

(30) Pure capacitor -



$$V = V_m \sin \omega t$$

The applied voltage is $V = V_m \sin \omega t$

The charge stored in the capacitor is

$$Q = CV = C V_m \sin \omega t$$

$$\text{Now, } I = \frac{dQ}{dt} = \frac{d}{dt}(C V_m \sin \omega t)$$

$$\Rightarrow I = C V_m \cos \omega t$$

$$\Rightarrow I = \frac{V_m}{(1/C)} \cos \omega t$$

$$\Rightarrow I = \frac{V_m}{\frac{1}{C}} \sin(\omega t + \frac{\pi}{2})$$

Now I will be maximum, when $\sin(\omega t + \frac{\pi}{2}) = 1$

$$I_{\text{max}} = \frac{V_m}{1/C}$$

$$I = I_{\text{max}} \sin(\omega t + \frac{\pi}{2})$$

$$X_C = \frac{1}{\omega C} \Omega \quad [X_C = \text{Capacitive reactance}]$$

The average power absorbed over a complete cycle is zero $P_{\text{avg}} = 0$

Hence the current is leading and voltage is lagging by 90°

(31) $P_{\text{avg}} = \frac{1}{2\pi} \int_0^{2\pi} P dt$

$$= \frac{1}{2\pi} \int_0^{2\pi} V_m \sin \omega t \cdot I_m \sin(\omega t + \frac{\pi}{2}) dt$$

$$= \frac{1}{2\pi} \int_0^{2\pi} V_m \sin \omega t \cdot I_m \sin \omega t dt$$

$$= [V = V_m \sin \omega t \quad I = I_m \sin \omega t]$$

$$= \frac{V_m I_m}{2\pi} \int_0^{2\pi} 2 \sin^2 \omega t dt$$

$$= \frac{V_m I_m}{4\pi} \int_0^{2\pi} (1 - \cos 2\omega t) dt$$

$$= \frac{V_m I_m}{4\pi} \left[t - \frac{\cos 2\omega t}{2\omega} \right]_0^{2\pi}$$

$$= \frac{V_m I_m}{4\pi} [(2\pi) - 0] - (0 - 0)$$

$$= \frac{V_m I_m}{4\pi} \times 2\pi$$

$$= \frac{V_m I_m}{4\pi} \times \frac{V_m}{\sqrt{2}} \times \frac{I_m}{\sqrt{2}} = V_m^2 I_m / 8\pi$$

$$P = VI$$

(32) $P_{\text{avg}} = V_{\text{rms}} I_{\text{rms}} \cos \phi$

ϕ : angle between V and I

ϕ : phase diff.

Phase angle also

3/17/22

- C) Calculate the power supplied or absorbed by each element in the given figure.



$$\text{For } 2\text{V}, P = V_I \\ = \frac{2}{2+5} \times 100 = 40\text{W}$$

$$\text{For } 12\text{V}, P = 12 \times 5 = 60\text{W}$$



$$\text{For } 8\text{V}, P = 8 \times 6 = 48\text{W}$$

$$\text{For } 0.2I, P = VI = 8 \times (0.2 \times 3) \\ \Rightarrow 20 = V \times 0.2 \Rightarrow 80 \\ \Rightarrow V = \frac{80}{0.2} = 400 \\ \Rightarrow I = 400/100 = 4\text{A} \\ \text{So, } P = 100 \times 0.2 = 20\text{W}$$


Source is delivering Power Load is absorbing Power

$$\begin{array}{r} 100\text{W} \\ + 60\text{W} \\ + 48\text{W} \\ \hline 108\text{W} \end{array}$$

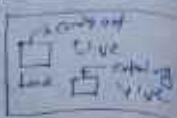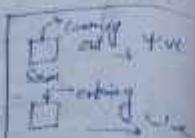In any circuit Source delivers Power > Load absorbs Power



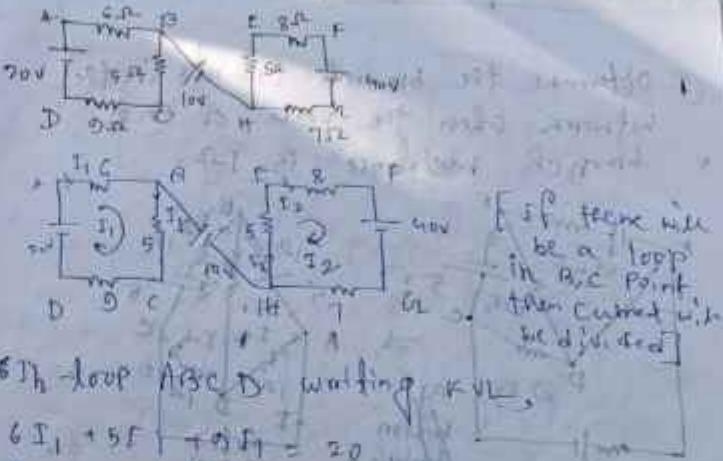- Q) Find V_{CE} and V_{BE} in the given circuit.



In loop ABCD writing KVL,

$$6I_1 + 5F + 7I_1 = 20$$

$$\Rightarrow 13I_1 = 20$$

$$\Rightarrow I_1 = 1\text{A}$$

In loop EFGH writing KVL,

$$8I_2 + 7I_2 + 5I_2 = -40 \quad (+) + (-)$$

$$\Rightarrow 20I_2 = -40$$

$$\Rightarrow I_2 = -2\text{A}$$

CBHE,

CBHG,

$$V_E = -5I_1 + 5I_2 = -5(0) + 5(-2) = -10 - 7I_2$$

$$= -5I_1 - 10 - 7I_2 = -7I_1 - 10 + 7I_2$$


$$= -5 \times 1 + 5 \times (-2) + 7I_2 = -16.5 + 7I_2$$

$$= -5 + 7I_2 = 30\text{V}$$

$$\text{CBHG or FE, } V_M = 6 \times 1 + 10 - 16.5 = 30\text{V}$$

mesh analysis (KVL)

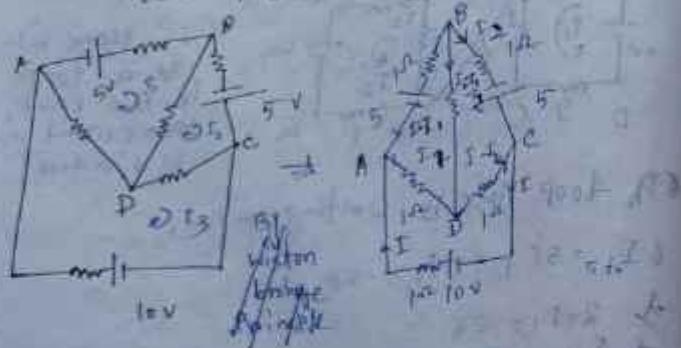- ① determine the branch currents in the network when the value of each branch resistance is 1Ω.



* in loop ABCDA applying KVL,

$$(I - I_1) + (I - I_1 - I_2) - I_1 = 5 \quad \text{---(1)}$$

$$\Rightarrow I - I_1 + I - I_1 - I_2 - I_1 = 5 \quad \text{---(2)}$$

$$\Rightarrow 2I - 3I_1 - I_2 = 5 \quad \text{---(3)}$$

$$\Rightarrow 3I_1 - I_2 - I_3 = 5 \quad \text{---(4)}$$

$$\text{BCDB, } I_1 - (I - I_1 - I_2) + I_2 = 5 \quad \text{---(5)}$$

$$\Rightarrow I - I_1 - I_2 = 5 \quad \text{---(6)}$$

$$ABC \rightarrow ADCA, \quad I_1 - 3I_2 - I_3 = 5 \quad \text{---(7)}$$

$$I_1 - 2I_1 + I_2 + 3I_3 = 10 \quad \text{---(8)}$$

Solve by matrix form -

$$A = \begin{bmatrix} 3 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{bmatrix}, \quad B = \begin{bmatrix} 5 \\ 5 \\ 10 \end{bmatrix}$$

$$X = \begin{bmatrix} x \\ y \\ z \end{bmatrix}$$

$$AX = B$$

$$X = A^{-1}B$$

$$|A| = \begin{vmatrix} 3 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{vmatrix} = 3(9-1) + 1(-3-1) - 1(1+3) = 3 \times 8 - 4 - 4 = 24 - 8 = 16$$

$$= 3(9-1) + 1(-3-1) - 1(1+3)$$

$$= 3 \times 8 - 4 - 4 = 24 - 8 = 16$$

$$= 24 - 4(24 + 8) - (1 - 1 - 1) = 16$$

$$\text{adj } A = \left[\begin{array}{ccc|ccc} 3 & -1 & -1 & -1 & -1 & 1 & 1 \\ -1 & 3 & -1 & 1 & 3 & -1 & -1 \\ -1 & -1 & 3 & 1 & 1 & 3 & -1 \end{array} \right]^T = \left[\begin{array}{ccc|ccc} 3 & 1 & 1 & -1 & -1 & 1 & 1 \\ 1 & 3 & -1 & 1 & 1 & 3 & -1 \\ 1 & 1 & 3 & -1 & -1 & -1 & 3 \end{array} \right]$$

$$= \begin{bmatrix} (2-1) & (-3-1) & (1+3) \\ -(-3-1) & (0-1) & -(-3-0) \\ (1+3) & -(-3-0) & (0+1) \end{bmatrix}$$

$$= \begin{bmatrix} 1 & -4 & 4 \\ 4 & -1 & 0 \\ 4 & 0 & 1 \end{bmatrix}$$

$$= \frac{1}{16} \begin{bmatrix} 1 & -4 & 4 \\ 4 & -1 & 0 \\ 4 & 0 & 1 \end{bmatrix} \times \begin{bmatrix} 8 & & \\ & 8 & \\ & & 8 \end{bmatrix}$$

$$\Delta = \left| \begin{array}{ccc|c} 3 & -1 & -1 & 1 \\ -1 & 3 & -1 & 1 \\ -1 & -1 & 3 & 1 \\ \hline 3 & -1 & -1 & 1 \\ -1 & 3 & -1 & 1 \\ -1 & -1 & 3 & 1 \end{array} \right|$$

$$= -(2-1-1) - (3+3+3) = -8$$

$$= 5 \times \frac{1}{16} \times \begin{bmatrix} 2 & 1 & 1 \\ 1 & 2 & 1 \\ 1 & 1 & 2 \end{bmatrix} \times \begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix}$$

$$= \frac{5}{4} \begin{bmatrix} 2+1+2 \\ 1+2+1 \\ 1+1+4 \end{bmatrix}$$

$$\rightarrow \frac{1}{16} \begin{bmatrix} 40+20+40 \\ 20+40+40 \\ 20+20+80 \end{bmatrix}$$

$$\rightarrow \frac{1}{16} \begin{bmatrix} 100 \\ 100 \\ 120 \end{bmatrix}$$

$$I_1 = \frac{100}{16} = 6.25 \text{ A}$$

$$I_2 = \frac{100}{16} = 6.25 \text{ A}$$

$$(I_3) = \frac{120}{16} = 7.5 \text{ A}$$

$$\text{The current in segment AB} = I_1 = 6.25$$

$$\text{Current in segment BC} = I_2 = 6.25$$

$$\text{Current in segment CD} = I_2 - I_3 = -12.5$$

$$\text{Current in segment DA} = I_1 - I_3 = -1.25$$

$$\therefore \delta = 35 + 12.5 = 47.5$$


$$\text{BD} = I_1 - I_2 = 0$$

④ Galvanic circuit rule

[B] junction bridge principle \rightarrow PT.O
operating

C Find I_0 using mesh analysis.

②

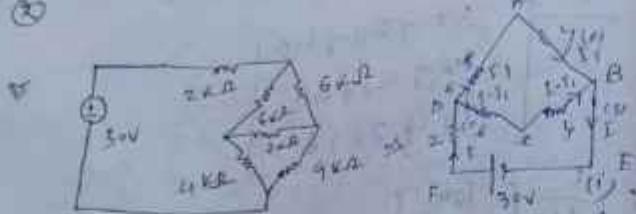

By Weston Bridge Principle we know that

If $\frac{P}{Q} = \frac{E}{S}$ then the middle resistance will be removed. Here, $\frac{E}{S} = \frac{6}{4}$. So the diagram is drawn by us, now.

Applying KVL on ABCDA, $6I_1 + 4I_2 - 4(I_1 - I_2)$

$$-6(I_1 - I_2) = 0$$

$$\Rightarrow 6I_1 - 4I_2 + 4I_1 - 6I_1 + 6I_2 = 0$$

$$\Rightarrow 2I_1 - 10I_2 = 0$$

$$\Rightarrow 2I_1 = 10I_2$$

$$\Rightarrow I_1 = 5I_2$$

$$\Rightarrow I = 2I_1 = 0$$

DCBFFD, $6(I_1 - I_2) + 4(I_1 - I_2) + 2I_2 = \frac{30}{10^3}$

$$\Rightarrow 6I_1 - 6I_2 + 4I_1 - 4I_2 + 2I_2 = 30 \times 10^{-3}$$

$$\Rightarrow 12I_1 - 10I_2 = 30 \times 10^{-3} \quad [From \text{ } ①]$$

$$\Rightarrow 12 \times 2I_1 - 10I_2 = 30 \times 10^{-3} \quad [I = 2I_1]$$

$$\Rightarrow 24I_1 - 10I_2 = 30 \times 10^{-3}$$

$$\Rightarrow 14I_1 = 30 \times 10^{-3}$$

$$\Rightarrow I_1 = 2.143 \times 10^{-3} \text{ A}$$

from ①

$$I = 2 \times I_1$$


$$= 2 \times 2.143 \times 10^{-3}$$

$$= 4.286 \times 10^{-3} \text{ A}$$

$$I = I_0 = 4.286 \times 10^{-3}$$

$$= 4.286 \text{ mA}$$

① Problem ⑦ of KVL

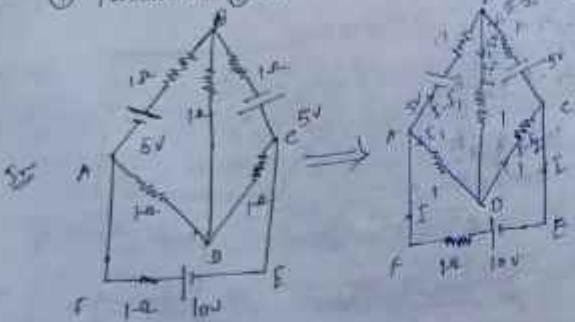

This is not correct.

Applying KVL in ABDA,

$$(I - I_1) + (I - I_1 - I_2) - I_1 = 5$$

$$\Rightarrow I - I_1 + I - I_1 - I_2 - I_1 = 5$$

$$\Rightarrow 2I - 3I_1 - I_2 = 5 \quad \text{--- (i)}$$

Applying KVL in BCDBA,

$$I_2 - (I - I_2) - (I - I_1 - I_2) = 5$$

$$\Rightarrow I_2 - I + I_2 - I + I_1 + I_2 = 5$$

$$\Rightarrow 2I + I_1 + 3I_2 = 5 \quad \text{--- (ii)}$$

Applying KVL in FDCEFA,

$$I_1 + I - I_2 + I = 10$$

$$\Rightarrow 2I + I_1 - I_2 = 10 \quad \text{--- (iii)}$$

From ①, ②, ③ we get a eqn $A\bar{I} = B + 3\bar{I} = 0$


$$\text{Let } A \rightarrow \begin{bmatrix} 2 & -3 & -1 \\ -2 & 1 & 3 \\ 2 & 1 & -1 \end{bmatrix}, B = \begin{bmatrix} 5 \\ 5 \\ 10 \end{bmatrix}$$

$$\begin{aligned} A\bar{I} &= \begin{vmatrix} 2 & -3 & -1 \\ -2 & 1 & 3 \\ 2 & 1 & -1 \end{vmatrix} \bar{I} \\ &= 2(-1-3) + 3(2-(-1)) - 1(-2-2) \\ &= -8 - 12 + 4 \\ &= -16 \end{aligned}$$

$$\text{adj } A = \begin{bmatrix} 1 & 3 & 1 & -2 & 3 & 1 & -2 & 1 \\ 1 & 1 & 2 & 1 & 2 & 1 & 2 & 1 \\ -1 & -3 & 1 & 2 & -1 & 2 & -3 & 1 \\ 1 & 1 & 2 & -1 & 2 & -1 & 2 & -1 \\ -2 & -1 & 2 & 2 & 1 & 2 & -3 & 1 \\ 1 & 3 & 2 & 2 & 3 & 2 & -3 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} (-1-3) - 2(2-6) & (1-2) \\ -(3+1) & -(5-2+2) - (2+6) \\ (2+1) & -(6-2)(2-6) \end{bmatrix}$$

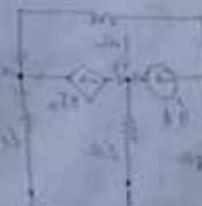
$$\begin{bmatrix} -4 & 4 & -4 & 4 & -8 & -4 & 4 & -8 \\ -4 & 0 & -8 & 0 & -8 & 0 & -8 & 0 \\ -8 & 4 & -4 & 4 & 16 & 4 & -4 & 4 \\ -4 & -4 & -8 & -4 & 16 & -4 & -8 & -4 \\ -4 & -8 & -4 & -8 & 16 & -4 & -8 & -8 \end{bmatrix}$$



$$\begin{aligned} A^{-1}B &= \frac{1}{16} \begin{bmatrix} -1 & -1 & -2 \\ 1 & 0 & 1 \\ -1 & -2 & 1 \end{bmatrix} \times \begin{bmatrix} 5 \\ 5 \\ 10 \end{bmatrix} \\ &= \frac{1}{16} \begin{bmatrix} -5 - 5 - 20 \\ 5 + 0 + 10 \\ -5 - 10 + 10 \end{bmatrix} \end{aligned}$$

not
connected

By Wilson Bridge Principle -

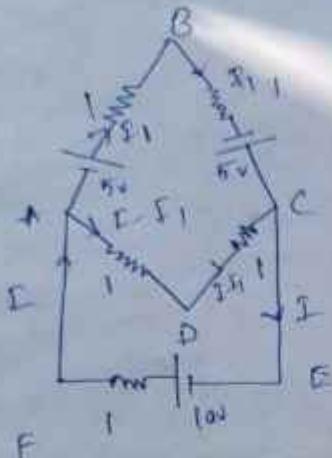

$$\text{At } B \text{ (DA), } I_1 + I_{11} - (I - I_{12}) - (I - I_{21}) = 5 + 5 \\ \Rightarrow 2I_{11} - I + I_{12} - I + I_{21} = 10 \\ \Rightarrow 4I_{11} - 2I = 10 \\ \Rightarrow 2I_{11} - I = 5 \quad \text{--- (i)}$$

At D (CEFA),

$$I - I_1 + I - I_{21} + I = 10 \\ \Rightarrow 3I - 2I_{21} = 10 \\ \Rightarrow -2I_{21} + 3I = 10 \quad \text{--- (ii)} \\ \begin{array}{r} 2I_{11} - I = 5 \quad \text{--- (i)} \\ -2I_{21} + 3I = 10 \quad \text{--- (ii)} \\ \hline \end{array}$$

$$\Rightarrow 2I = 15 \\ \Rightarrow I = \frac{15}{2} = 7.5$$

$$2I_{11} - 7.5 = 5 \\ \Rightarrow 2I_{11} = 6.25$$

A) The branch currents are,

Current on AB = 6.25 A

$$BC = 6.25 A$$

$$CD = 1.25 A$$

$$DA = 1.25 A$$

$$CA = 7.5 A$$



$$\bar{e} + \bar{e} = ((I - I) - (I - I)) - jI + jI \quad (V)$$

$$0I = jL + I - jL + I - jL \quad L$$

$$0I = jL - jL \quad L$$

$$0I = I - I - I \quad L$$

(A + 1) A


$$0I = jL + I - I + I - I$$

$$0I = jL - I \quad L$$

$$0I = 0I - I \quad L$$

Nodal analysis


Ex-① Find v_o by using node analysis

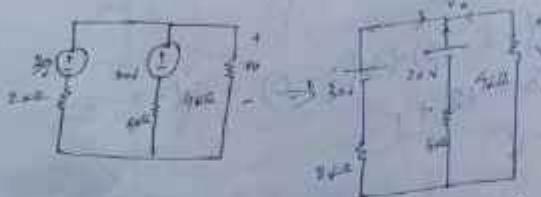

$$\begin{aligned} \frac{v_o - 30}{2 \times 10} + \frac{v_o - 20}{5 \times 10} + \frac{v_o}{4 \times 10} &= 0 \\ \Rightarrow \frac{10(v_o - 30) + 4(v_o - 20) + 5v_o}{20 \times 10 + 30} &= 0 \\ \Rightarrow 10v_o + 4v_o + 5v_o - 300 - 80 &= 0 \\ \Rightarrow 19v_o = 380 \\ \Rightarrow v_o = 20V \end{aligned}$$

Ex-②

Find i_o in the given circuit

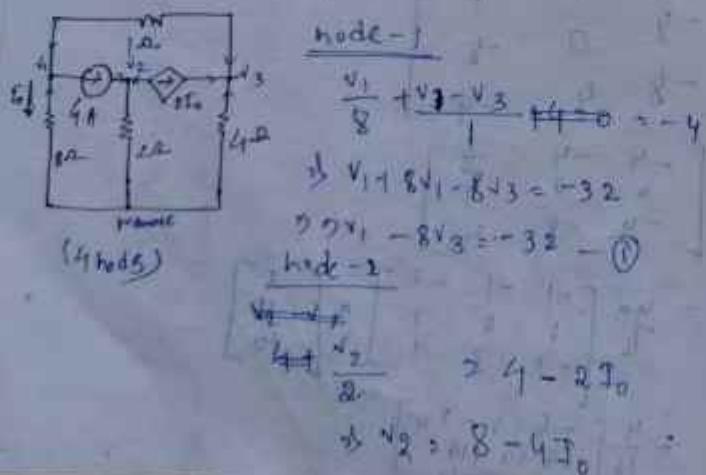

$$2v_2 = 8 - 4i_o \quad | \cdot \frac{1}{2}$$

$$\Rightarrow 2v_2 = 16 - 4i_o$$

$$\Rightarrow 2v_2 + v_1 = 16 \quad | - ①$$

$$1.5i_o = \frac{v_1}{8}$$

node-3

$$\frac{v_3}{4} + \frac{v_3 - v_1}{1} = 230$$

$$\Rightarrow \frac{v_3}{4} + \frac{v_3 - v_1}{1} = 230 + \frac{v_1}{8}$$

$$\Rightarrow v_3 + 4v_3 - 4v_1 = v_1 + 11 - 8$$

$$\Rightarrow 5v_3 - 5v_1 = 0$$

$$\Rightarrow v_1 = v_3 \quad | - ②$$

from ①, ① - ② = 0 - 230 + 230 + 11 - 8

$$8v_1 - 8v_1 = -32$$


$$\Rightarrow v_1 = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

$$i_o = \frac{v_1}{8} = \frac{-32}{8} = -4A$$

$$(4+2)(4+1+2)8 - (9-1) = \begin{bmatrix} 0 & 2 & 1 \\ 0 & 1 & 2 \\ 1 & 2 & 1 \end{bmatrix} = 14$$

$$4 + 1 + 2 = \begin{bmatrix} 0 & 2 & 1 \\ 0 & 1 & 2 \\ 1 & 2 & 1 \end{bmatrix} = 14$$

Method of analysis

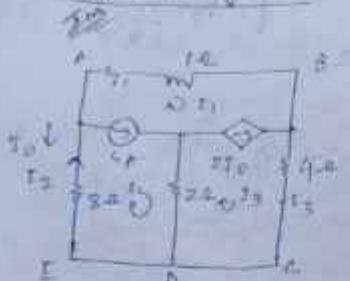

[due to voltage
source here
the sum of the
voltages in the
loop from (1)

In supermesh, we get

$$I_1 + 4I_3 + 8I_2 = 0 \quad (1)$$

$$I_2 - I_1 - 4 = 0 \quad (2)$$

$$I_3 - I_1 + 2I_2 = 0 \quad (3)$$

$$I_3 - I_1 = -2I_2 \quad [\because I_2 = -4]$$

$$I_1 + 2I_2 + I_3 = 0 \quad (4)$$

Let, $A = \begin{bmatrix} 1 & 8 & 4 \\ -1 & 1 & 0 \\ -1 & 2 & 1 \end{bmatrix}$, $B = \begin{bmatrix} 0 \\ 4 \\ 0 \end{bmatrix}$

then, $AI = B$

$$I = A^{-1}B$$

$$|A| = \begin{vmatrix} 1 & 8 & 4 \\ -1 & 1 & 0 \\ -1 & 2 & 1 \end{vmatrix} = 1(1-0) - 8(-1-0) + 4(-2+1) \\ = 1 + 8 - 4 \\ = 5$$

$$A^{-1} = \begin{bmatrix} 1 & 8 & 4 \\ -1 & 1 & 0 \\ -1 & 2 & 1 \end{bmatrix}^{-1} = \frac{1}{5} \begin{bmatrix} 1 & 0 & -4 \\ -1 & 0 & 0 \\ 0 & -2 & 1 \end{bmatrix}^T$$

$$= \begin{bmatrix} (1-0) & -(-1-0) & (-2+0) \\ -(8-8) & +(1+0) & -(2+8) \\ (0-4) & -(0+0) & (1+8) \end{bmatrix}^T$$

$$= \begin{bmatrix} 1 & 1 & -1 \\ 0 & 5 & -10 \\ -4 & -4 & 9 \end{bmatrix}^T$$

$$= \begin{bmatrix} 1 & 0 & -4 \\ 0 & 5 & -10 \\ -1+10 & -1-0 & 9 \end{bmatrix}^T$$

Now, $I = \frac{1}{5} \begin{bmatrix} 1 & 0 & -4 \\ 0 & 5 & -10 \\ -1 & -10 & 9 \end{bmatrix} \times \begin{bmatrix} 0 \\ 4 \\ 0 \end{bmatrix}$

$$= \frac{1}{5} \begin{bmatrix} 0+0+0 \\ 0+20+0 \\ 0-40+0 \end{bmatrix}$$

$$= \begin{bmatrix} 0 \\ 4 \\ -8 \end{bmatrix}$$

$$\therefore I_2 = 4 = 20$$

we know, $I_0 = -I_2 = -4$
 $\therefore I_0 = 4A$

of the
loop like

①

$$I_1 = I_2 - 4 \quad \text{--- IV}$$

From ①, $I_2 - 4 + 4I_3 - 8I_2 = 0$

$$\Rightarrow 3I_2 + 4I_3 - 4 = 0$$

$$\Rightarrow I_3 = 4 - 3I_2$$

From ③, applying ④ and ⑤

$$-I_2 + 4 + 2I_2 + \frac{4 - 3I_2}{4} = 0$$

$$\Rightarrow I_2 + 4 + \frac{4 - 3I_2}{4} = 0$$

$$\Rightarrow 4I_2 + 16 + 4 - 3I_2 = 0$$

$$\Rightarrow -5I_2 = -20$$

$$\Rightarrow I_2 = 4$$

$$\therefore I_3 = I_2 - 4$$

① nodal analysis - the mathematical method for calculating the distribution of voltage between the nodes in a circuit. This is an application of KCL.

② node - junction point [minimum element should be connected in between 2 nodes]

③ mesh analysis - the method in which the current flowing through a planar circuit is calculated. This is an application of KVL.

④ KCL (loop/mesh analysis) - it states that the sum of the currents entering or leaving a junction point at any instant is equal to zero.

$$\Sigma I = 0$$

KCL is also known as Kirchhoff's first law or junction rule. The principle of this law is to conserve the electric charge. The law states that the amount of current flowing into a node is equal to the sum

of current out of it. For performing the nodal analysis, we have to go for KCL.



$$I_1 + I_2 + I_3 = I_5 + I_4$$
$$\Rightarrow I_1 + I_2 + I_3 + (-I_4) + (-I_5) = 0$$

The currents I_1, I_2, I_3 entering the node are considered positive values, while the currents I_4 and I_5 leaving the node are considered negative values.

⑤ KCL (mesh/loop analysis) - KVL is also known as Kirchhoff's second law or Loop Law. The principle of this law is to conserve energy. The law states that the sum of voltages in a closed-loop is zero. The total amount of energy gained is equal to the energy lost per unit charge.

$$\sum V = 0$$
$$\Rightarrow \sum IR = 2E$$

$$\text{also } \sum V = 2E$$

[and E is same]
both of them is $\neq 0$


For loop/mesh analysis, we have
to η for v_{NL} .

- $P = VI \cos\phi$ [Angle between voltage and current = ϕ]

$$P = VI (\text{DC})$$



- AC fundamentals and circuits - (19)

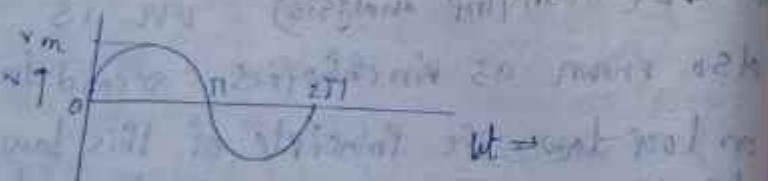

A Sinusoidal wave

The expression for the voltage

$$v = V_m \sin \omega t$$

v = Instantaneous value

V_m = max value

The expression for alternating current

$$I = I_m \sin \omega t$$


I = Instantaneous value


I_m = max value

[ω = angular velocity of the coil]

[$I = I_{rms}$, $V = V_{rms}$]

- Instantaneous value - done
- Amplitude - the amplitude of a sine wave is the maximum vertical distance reached in either direction from the center line of the wave. As a sine wave is symmetrical about its center line, the amplitude of the wave is half of the peak-to-peak value.
- Peak-to-peak value - the peak-to-peak value is the vertical distance between the top and bottom of the wave.
- Volts form a Voltage waveform.
- Peak Value - the peak value of the wave is the highest value the wave reaches above a reference value. The reference value normally used is zero.

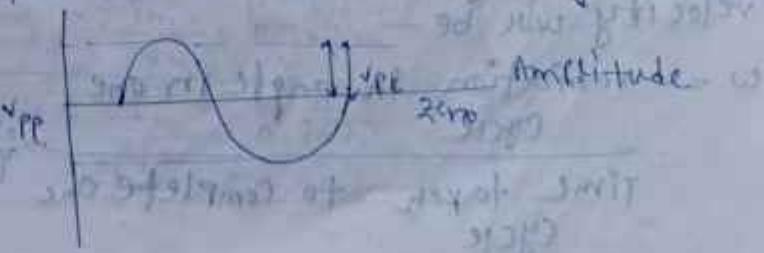

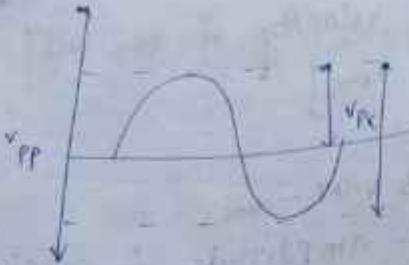

- Cycle and Alternation - When an alternating quantity completes one complete set of positive and negative values, it is called one cycle, whereas when it completes only one set of either positive or negative values, that is half cycle, then it is called one alternation. One alternation corresponds to 180° rad while one cycle is 360° or 2π rad.
- Angular Frequency or angular velocity - An alternating quantity completes one cycle by 2π rad. The angular velocity will be -


$\omega = \frac{\text{Variation in angle in one cycle}}{\text{Time taken to complete one cycle}}$

$$\text{Time taken to complete one cycle} = \frac{2\pi}{\omega}$$

= $2\pi f$ electrical rad/s

- Graphically -

$$V_{AV} = \frac{V_{max} + V_{min}}{2}$$

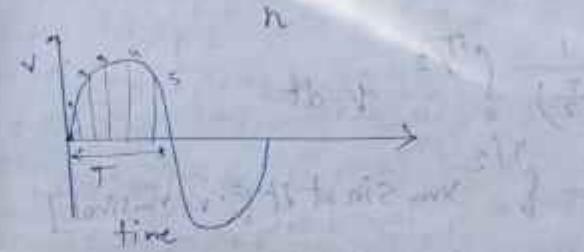

- Analytically -

$$\text{Area of half cycle voltage wave} = 2Vm$$

$V_{AV} = \frac{\text{Height of equivalent rectangle having the same base}}{\text{base}}$

$$V_{AV} = \frac{2Vm}{\pi} = 0.637 V_m$$

$$I_{AV} = \frac{2Im}{\pi} = 0.637 I_m$$

$$V_{avg} = \frac{Vm}{\sqrt{2}} = 0.707 V_m$$

$$I_{avg} = \frac{Im}{\sqrt{2}} = 0.707 I_m$$

$$V_{\text{rms}} = V_{\text{av}} \cdot \frac{1}{2\sqrt{2}}$$

$$\boxed{\frac{V_{\text{rms}}}{V_{\text{av}}} = \frac{1}{2\sqrt{2}}}$$

$$\begin{aligned} V_{\text{av}} &= \frac{1}{(\frac{T}{2})} \int_0^{T/2} v dt \\ &= \frac{2}{T} \int_0^{T/2} V_m \sin \omega t dt \quad [v = V_m \sin \omega t] \\ &= \frac{2V_m}{T} \left[-\frac{\cos \omega t}{\omega} \right]_0^{T/2} \\ &= \frac{2V_m}{T\omega} \times \left[-\cos \frac{\omega T}{2} + 1 \right] \end{aligned}$$

$$\begin{aligned} \frac{V_{\text{av}}^2}{2T} &\times \left(1 - \cos \frac{\omega T}{2} \right) \quad [\because T = \frac{2\pi}{\omega}] \\ &= \frac{2V_m}{\sqrt{2}} \end{aligned}$$

$$\begin{aligned} V_{\text{rms}}^2 &= \frac{1}{T} \int_0^T v^2 dt \\ &= \frac{V_m^2}{T} \int_0^T \sin^2 \omega t dt \\ &= \frac{V_m^2}{2T} \int_0^T 2 \sin^2 \omega t dt \\ &= \frac{V_m^2}{2T} \int_0^T (1 - \cos 2\omega t) dt \end{aligned}$$

$$\begin{aligned} &= \frac{V_m^2}{2T} \left[t - \frac{\sin 2\omega t}{2\omega} \right]_0^T \\ &= \frac{V_m^2}{2T} \left[T - \frac{\sin 2\omega T}{2\omega} \right] \\ &= \frac{V_m^2}{2T} \left[T - \frac{\sin 4\pi}{2\omega} \right] \\ &= \frac{2V_m^2}{T\omega} \times \left[1 - \frac{\sin 4\pi}{2\omega} \right] \\ V_{\text{rms}} &= \frac{V_m}{\sqrt{2}} \end{aligned}$$

- For a DC circuit, the relationship between voltage and current is simple and is expressed as $I = \frac{V}{R}$. However, in the case of an AC circuit, the magnetic effect and the electrostatic effect are also taken into account.

- Calculate the rms and average value of a square wave shown in the fig. If the current is passed through a resistor, find out average power absorbed by it.

$$I_{rms}^2 = \frac{1}{T} \int_0^T I(t)^2 dt = \frac{1}{T} \int_0^T I_m^2 \cos^2(\omega t) dt$$

$I_m = I_{avg}$
= Average
magnitude
of I

$$I_{avg} = \frac{1}{T} \int_0^T I(t) dt + \frac{1}{T} \int_0^T I_m \cos(\omega t) dt$$

For the time interval $0 < t < 0.2$, $I = 10A$
and for $0.2 < t < 0.4$, $I = 0A$. Time period
of the current waveform, $T = 0.4$, the
rms value is given by

$$I_{rms}^2 = \frac{1}{T} \int_0^T I^2(t) dt$$

$$= \frac{1}{0.4} \left[\int_0^{0.2} 10^2 dt + \int_0^{0.4} 0^2 dt \right]$$

$$= \frac{1}{0.4} \left[\int_0^{0.2} 100 dt \right] \times 2 = 100$$

$$= \frac{100}{0.4} \times [0.2 - 0] = 50$$

$$= \frac{100}{2} = 50$$

$$I_{rms} = \sqrt{50} = 7.071A$$

$$I_{avg} = \frac{1}{T} \int_0^T I(t) dt = \frac{1}{0.4} \int_0^{0.2} 10 dt$$

$$= \frac{1}{0.4} \left[\int_0^{0.2} 10 dt + \int_0^{0.4} 0 dt \right]$$

$$= \frac{10}{0.4} [0.2 - 0] = 5A$$

-5

$$\text{Avg power absorbed} = I^2 R$$

$$= 50 \cdot 2$$

$$= 100W$$

- Distinguish between mesh and loop of a network.

Mesh

Loop

1) Loop is any closed path through a circuit where no node more than one is encountered.


2) To find all loops, start at node in the cut, from this node, move back to the same node along a path it does not share that no node is encountered more than once.

A mesh is a closed path in a circuit with no other paths inside it.


In other terms, a loop with no other loops inside it.

- Independent voltage source - An independent voltage source is an idealized circuit component that fixes the voltage in a branch respectively to a specified



value.
Symbol - the middle symbol is for
symbol for a specific type of
independent voltage source known

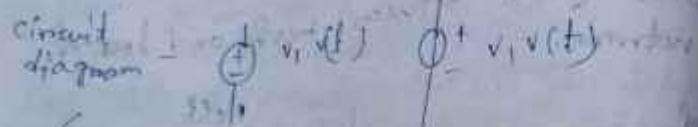circuit diagram - 

- ④  Independent current source - An independent current source is an energy source that pushes a constant flow of electrons through an electrical circuit regardless of the load presented to it. In other words, a lamp current source will maintain a current flow of 1 amp through its terminals if it has an open circuit or short circuit as a load.

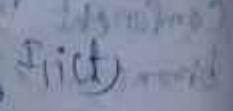Symbol - a circle with an arrow inside is the symbol to indicate the direction of the flow of current. 

• LR circuit

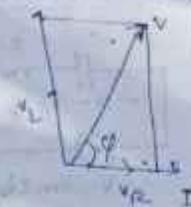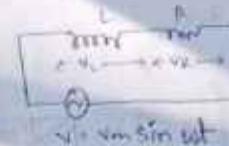

$$V_R = IR$$

$$V_L = IX_L$$

$$\text{net voltage } (V) = \sqrt{V_L^2 + V_R^2}$$

$$= \sqrt{I^2 X_L^2 + I^2 R^2}$$

$$= I \sqrt{R^2 + X_L^2}$$

$$= \sqrt{R^2 + X_L^2}$$

$$Z = \sqrt{R^2 + X_L^2} \quad [Z = \text{impedance}]$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{R^2 + \omega L^2}$$



$$\tan \phi = \frac{V_L}{V_R} = \frac{IX_L}{IR} = \frac{X_L}{R} = \frac{\omega L}{R}$$

$$[\phi = \tan^{-1}\left(\frac{\omega L}{R}\right) = \tan^{-1}\left(\frac{X_L}{R}\right)]$$

ϕ = Phasor angle

In LR circuit current lag behind the voltage by phasor angle $\tan^{-1}\left(\frac{\omega L}{R}\right)$

• CR Circuit

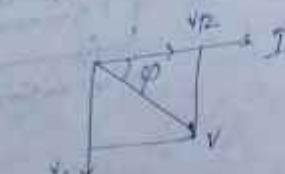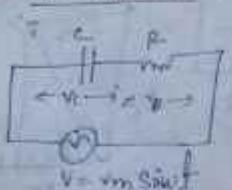

$$V_C = I X_C \quad \text{net voltage } (V) = \sqrt{I^2 + V_C^2}$$

$$V_R = I R$$

$$= I \sqrt{R^2 + X_C^2}$$

$$\frac{V}{I} = \sqrt{R^2 + X_C^2}$$

$$Z = \sqrt{R^2 + X_C^2} = \sqrt{R^2 + \frac{1}{\omega C^2}}$$

$$Z = \sqrt{R^2 + X_C^2} = \sqrt{R^2 + \frac{1}{\omega C^2}}$$

$$\tan \phi = \frac{V_C}{V_R} = \frac{X_C}{R} = \frac{1}{\omega R}$$



$$\phi = \tan^{-1} \left(\frac{1}{\omega R} \right)$$

In CR circuit the voltage lag behind the current by the phasor angle

$$\tan^{-1} \left(\frac{1}{\omega R} \right)$$

it includes for losses factor as well
(i.e.) net values go together

• RL Circuit

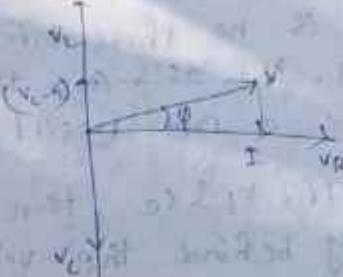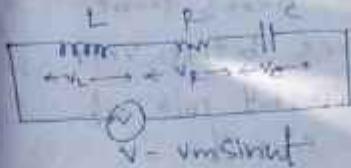

$$V_L = I X_L \quad \text{net voltage } (V) = \sqrt{(V_L - V_R)^2 + V_R^2}$$

$$V_R = I R$$

$$= I \sqrt{R^2 + (XL - \frac{1}{\omega C})^2}$$

$$Z = \sqrt{R^2 + (X_L - \frac{1}{\omega C})^2}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + (XL - \frac{1}{\omega C})^2}$$

$$\tan \phi = \frac{V_L - V_R}{V_R} = \frac{X_L - X_C}{V_R} = \frac{XL - \frac{1}{\omega C}}{R}$$

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right) = \tan^{-1} \left(\frac{XL - \frac{1}{\omega C}}{R} \right)$$

Hence 3 cases are available -
symmetrically balanced or anti-symmetrically balanced

C (i) If $x_L = x_C$, that means there is no phase difference between voltage. In this case the circuit will act like a pure resistive circuit.

(ii) If, $x_L > x_C$, then the voltage will lag behind the current by an angle $\tan^{-1} \left(\frac{wL}{wC} - 1 \right)$. In this case the circuit will act like a pure inductive circuit.

(iii) If, $x_C > x_L$, then the voltage will lag behind the current by an angle $\tan^{-1} \left(\frac{wC - 1}{wL} \right)$. In this case the circuit will act like a pure capacitive circuit.

* The condition of resonance in series RLC circuit -

In a RLC circuit $\omega_0^2 = \sqrt{R^2 + (wL - \frac{1}{wC})^2}$

$$\text{If } \omega_0 = \frac{1}{\sqrt{wL}} \rightarrow R^2 = \text{minimum}$$

In this case $\omega = \omega_{\min} = R$

In this situation the highest current maximum. This is called the resonance.

of series RLC circuit

* Resonance frequency (Natural frequency)

The condition for resonance -

$$\omega_0 L = \frac{1}{\omega_0 C} \quad [\text{For resonance } \omega = \omega_0]$$




$$\Rightarrow \omega_0^2 = \frac{1}{LC}$$

$$\Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

$$3.14 n = \frac{1}{\sqrt{LC}} \quad [n/f = \text{Frequency}]$$

$$n = \frac{1}{2\pi\sqrt{LC}}$$

* Impedance triangle -

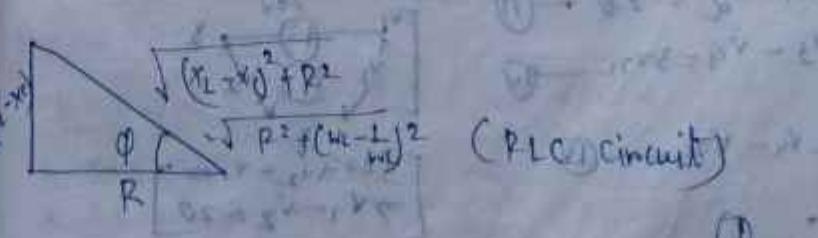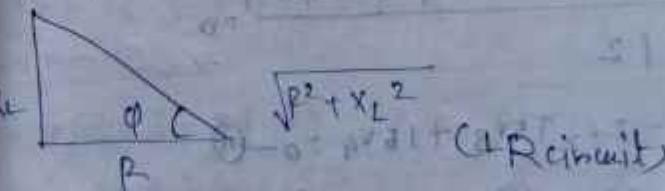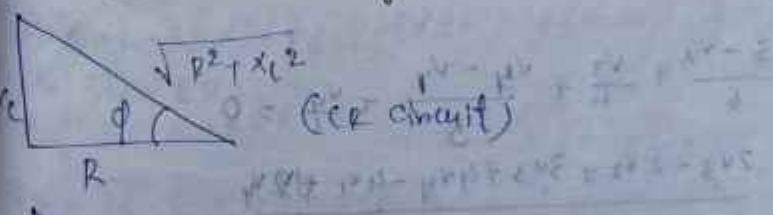

3/8/22

Find the node voltages in the given circuit.



super node

$V_3 - V_4 = 3\text{V}$

$\underline{V_1} \quad \underline{V_4} = 0\text{V}$

$\therefore V_1 - V_3 = 2 \times 2\Omega$

$\therefore V_1 - V_3 = -2(V_1 - V_4)$

$\therefore 3V_1 - V_3 - 2V_4 = 0 \quad \text{--- (V)}$

5 nodes

$$\frac{V_1}{2} + \frac{V_1 - V_4}{3} + \frac{V_2 - V_3}{6} = 10$$

$$\frac{3V_1 + 2V_1 - 2V_4 + V_2 - V_3}{6} = 10$$

$$\Rightarrow 3V_1 + 3V_2 - V_3 = 60 \quad \text{--- (1)}$$

$$\frac{V_3 - V_2}{6} + \frac{V_3}{3} + \frac{V_4 - V_1}{3} + \frac{V_4}{2} = 0$$


$$\frac{7V_3 - 2V_2 + 3V_3 + 4V_4 - 4V_1 + 12V_4}{12} = 0$$

$$\Rightarrow -4V_1 - 2V_2 + 15V_3 + 16V_4 = 0 \quad \text{--- (2)}$$

$$V_1 - V_2 = 20 \quad \text{--- (3)}$$

$$V_3 - V_4 = 3V_2 \quad \text{--- (4)}$$

$$V_1 - V_4 = V_2 \quad \text{--- (5)}$$

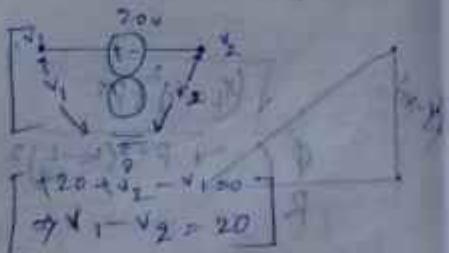

$$V_3 - V_4 = 3\text{V}$$

$$\underline{V_1} \quad \underline{V_4} = 0\text{V}$$

$$\therefore V_1 - V_3 = 2 \times 2\Omega$$

$$\therefore V_1 - V_3 = -2(V_1 - V_4)$$

$$\therefore 3V_1 - V_3 - 2V_4 = 0 \quad \text{--- (V)}$$

from (1)

$$V_1 - V_2 = 20$$

$$3V_2 - V_1 = 20$$

$$\text{from (2)} \quad V_1 = 20 + 3V_2 \quad \text{--- (6)}$$

$$3V_1 + V_2 - 20 = 3V_1 + 2V_2 - 2V_4 = 60$$

$$\therefore 6V_1 - 3V_2 = 60 + 20$$

$$\therefore 3V_1 = 80$$

$$\therefore V_1 = 26.67\text{V}$$

$$V_2 = 26.67 - 20 = 6.67\text{V}$$

from (1),

$$5 \times 26.67 + 6.67 - V_3 - 2V_4 = 60$$

$$\therefore V_3 + 2V_4 = 80.02 \quad \text{--- (V)}$$

from (2),

$$-4 \times 26.67 - 2 \times 6.67 + V_3 + 16V_4 = 0$$

$$\therefore 5V_3 + 16V_4 = 120.02 \quad \text{--- (V)}$$

$$\therefore V_3 + 3V_4 = 24.02 \quad \text{--- (V)}$$

$$\begin{aligned} \sqrt{3}V_2 + 4 &= 80.02 - \textcircled{1} \\ \sqrt{3}V_4 + 4 &= 24.004 - \textcircled{11} \end{aligned}$$

$$V_2 - V_4 = 56.016$$

$$V_2 - V_4 = -56.016V$$

$$V_3 + 2V_4 = 86.016 - \textcircled{12}$$

$$V_3 - 2V_4 = 82.012V$$

$$5V_3 + 16V_4 = 120.02 - \textcircled{13}$$


$$V_3 + 2V_4 = 80.02 - \textcircled{14}$$

$$V_3 - 2(80.02) = -96.68V$$

$$V_3 = 2 \times (-96.68) = 80.02$$

$$V_3 = 123.38V$$

Q Find the V_1, V_2, V_3

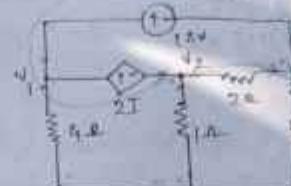

standard analysis

Here when we have
three nodes \rightarrow substitute
then the remaining two
equations of the circuit
with V_1, V_2, V_3 \rightarrow the unknown
variables \rightarrow V_1, V_2, V_3

$$\frac{V_1}{4} + \frac{V_2}{1} + \frac{V_3}{4} = 0 \quad [\frac{V_1}{4} + \frac{V_2}{1} + \frac{V_2 - V_3}{2} + \frac{V_3}{4} = 0]$$

$$\Rightarrow 4V_1 + 6V_2 + 4V_3 = 0$$

$$\Rightarrow V_1 + 1.5V_2 + V_3 = 0 \quad \textcircled{1} \quad V_1 - V_3 = 12 - \textcircled{2}$$

$$V_1 - V_2 = 2I \quad \textcircled{11} \quad V_1 = 12 + V_3 - \textcircled{2}$$

$$I = \frac{V_3}{4} - \textcircled{10}$$

from $\textcircled{10}$ \rightarrow simplified equations \rightarrow $\textcircled{1}$

$$V_1 - V_2 = \frac{2V_3}{4}$$

$$2V_1 - V_2 - 2V_3 = 0 \quad \textcircled{14}$$

from $\textcircled{1}$ and $\textcircled{14}$, $\textcircled{1}$

from $\textcircled{14}$,

~~A~~

$$4V_1 (12 + V_3) \rightarrow V_2 - 2V_3 = 0 - \textcircled{15}$$

$$\Rightarrow 48 + 4V_3 - V_2 - 2V_3 = 0$$

$$\Rightarrow 2V_3 + V_2 = 48 - \textcircled{16}$$

from $\textcircled{1}$,

~~A~~

$$12 + V_3 + 4V_2 + V_3 = 0$$

$$\Rightarrow 4V_2 + 3V_3 = -12 \quad \textcircled{17}$$

$$0 \quad 2v_3 - v_2 = -48 - \frac{\sqrt{11}}{2} \text{ v}$$

$$4v_3 - 4v_2 = -48 - \frac{\sqrt{11}}{2} \text{ v}$$

$$8v_3 - 4v_2 = -19.2$$

$$v_3 + 4v_2 = -12$$

$$\Rightarrow 7v_3 = -24.4$$

$$\Rightarrow v_3 = -2.15 \text{ v}$$

$$2 \times 2.15 \text{ v} = v_1 = -48$$


$$v_2 = 106.28 \text{ v}$$

from ①

$$v_1 + 4v_2 + 106.28 + 25.14 = 0$$

$$\Rightarrow v_1 = -3 \text{ v}$$

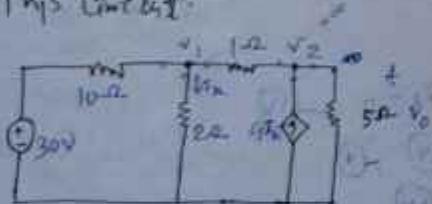② Using nodal analysis determine v_o in this circuit.



$$\frac{v_1 - 30}{10} + \frac{v_1}{2} + \frac{v_1 - v_2}{1} = 0$$

$$\Rightarrow v_1 - 30 + 5v_1 + 10v_1 - 10v_2 = 0$$

$$\Rightarrow 16v_1 - 10v_2 = 30 \quad \text{--- (1)}$$

$$\frac{v_2 - v_1}{1} + \frac{v_2}{5} = -4v_2$$

$$\Rightarrow 5v_2 - 5v_1 + v_2 = 30 \text{ --- (2)}$$

$$v_1 - 5v_1 + 6v_2 = 20 \text{ --- (3)}$$

$$3v_1 = \frac{v_1}{2}$$

$$v_1 - 5v_1 + 6v_2 = 20 \times \frac{v_1}{2}$$

$$v_1 - 15v_1 + 6v_2 = 0 \quad \text{--- (4)}$$

$$\cancel{16v_1} - 10v_2 = 30$$

$$-16v_1 + \cancel{6v_2}$$

from ①

$$\Rightarrow 6v_2 = 15v_1$$

$$\Rightarrow v_2 = \frac{15v_1}{6} \quad \text{--- (5)} \quad \Rightarrow v_2 = \frac{15 \times 3}{6} = 33$$

$$\text{from ④} \quad 16v_1 - 10 \times \frac{15v_1}{6} = 30 \quad \text{--- (6)}$$

$$16v_1 - 10 \times \frac{15v_1}{6} = 30$$

$$\Rightarrow -7v_1 = 30$$

$$\Rightarrow v_1 = \frac{30}{-7} = -3.33 \text{ v}$$

$$v_1 = v_2 = -8.33 \text{ v}$$

$$(1) - (2) = v_1 - 5v_1 + 6v_2 = 30 - 30$$

mesh analysis
independent
current source

Nodal analysis

$$I_2 = \frac{V_1}{2}$$

10

$$\Rightarrow -5V_1 + 6V_2 = 20 \quad (1)$$

$$\Rightarrow -15V_1 + 6V_2 = 0 \quad (1H)$$

$$16V_1 - 10V_2$$

$$V_1 + 4V_2 + V_3 = 0$$

$$\Rightarrow V_3 = V_1 - 12$$

$$\Rightarrow V_3 = V_1 - 12 \quad (II)$$

$$V_1 - V_2 = 2I$$

$$\Rightarrow V_2 = V_1 - 2I$$

$$= V_1 - 2 \times \frac{V_1}{5} \left(\cdot 1, \frac{2}{5} \right)$$

$$= V_1 - \frac{(V_1 - 12)}{2} \quad (\text{from } (II))$$

$$= \frac{2V_1 - V_1 + 12}{2} = \frac{V_1 + 12}{2} \quad (III)$$

$$V_1 + 4 \left[\frac{V_1 + 12}{2} \right] +$$

$$V_1 - 12 = 0$$

$$\Rightarrow V_1 + 24 + V_1 - 12 = 0$$

$$\Rightarrow 4V_1 + 12 = 0$$

$$\Rightarrow V_1 = -3V$$

$$\Rightarrow V_3 = -3 - 12$$

$$= -15V$$

$$V_2 = \frac{-3 + 12}{2}$$

$$= 4.5V$$

mesh analysis - don't consider direction

Nodal \leftrightarrow Axial

5/6/22

① Applying mesh analysis obtain I_1 .



[When there is voltage source, then the Eq. of whole loop will be]

$$\text{ABCDA} \quad I_2 - I_1 = 4 \quad (DC??)$$

A B C D E F G H I

$$4I_1 + 3I_2 + 12 - 12 + 2(I_2 - I_1) + 2(I_1 I_3) = 24 \quad (1)$$

$$I_3 = -2 \quad (2)$$

$$4I_1 + 3I_2 + I_2 + 2I_2 + 2I_4 + 2(I_1 I_2) \quad (3)$$

$$\Rightarrow 4I_1 + 6I_2 - 2I_4 + 2I_1 + 2I_3 + 2I_4$$

$$\Rightarrow 2I_1 + 6I_2 = 2$$

$$\Rightarrow 4I_1 + 6I_2 - 2I_4 = 20 \quad (4)$$

$$2(I_4 - I_2) + 4I_4 + (I_1 + 2) = -3$$

$$\Rightarrow I_1 + 6I_4 = -11 \quad (5)$$

$$(1) \Rightarrow 6I_2 = 2I_1 - 6 \quad (6)$$

$$(5) \Rightarrow I_4 = \frac{2I_1 - 11}{7}$$

put eqn (1) and (5) in (6)

$$6 \times (4 - I_2 - 4) + 6I_2 - 2 \times \left(\frac{2I_1 - 11}{7} \right) = 20$$

$$+ 2I_1 (I_1 - 4) = 20$$

$$\Rightarrow 6I_2 - 24 + 6I_2 - \left(4I_2 + \frac{-22}{7} \right) = 20$$

$$\Rightarrow 42I_2 - 168 + 42I_2 - 4I_2 + 22 = 0$$


$$\Rightarrow 84I_2 = 146$$

$$\Rightarrow I_2 = 1.7825 \approx 1.78$$

$$1.78 - I_1 = 4$$

$$\Rightarrow I_1 = -0.425$$
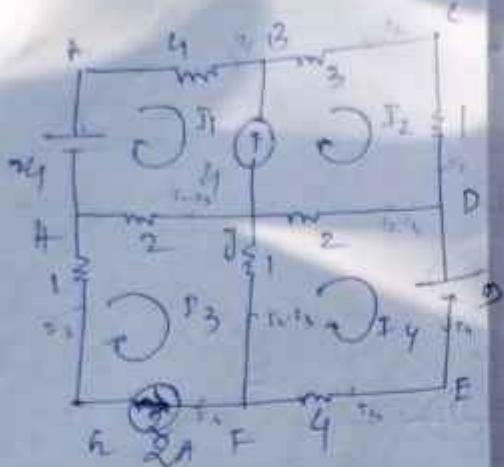
$$I_4 = \frac{2 \times 3.575 - 12}{7} = \frac{4V - 12}{7} = -0.55 \text{ A}$$



Here we cannot divide the current in normal way (the way I_1 is in VVL). So consider I_1, I_2, I_3, I_4 like this way.

As we are not dividing the current in diagram like normal way, so from where we consider a closed loop will be after direction of currents

$$\text{[} \textcirclearrowleft \text{ } \cong \text{ } \boxed{\text{---}} \text{]}$$

[we cannot apply VVL in loop ABJHA, BEGJB, HJFGH as end is present there]

A B C D J H A, VVL,

$$4I_1 + 3I_2 + I_2 + 2(I_2 - I_4) + 2(I_1 - I_3) = 24$$

$$\Rightarrow 6I_2 + 6I_1 - 2I_4 - 2I_3 = 24$$

$$\Rightarrow 6I_2 + 6I_1 - 2I_4 + 4 = 24 \quad [\because I_3 = 2]$$

$$\Rightarrow 6I_2 + 6I_1 - 2I_4 = 20 \quad \text{---(1)}$$


J D E F J, VVL

$$2(I_4 - I_2) + 4I_4 + (I_4 - I_3) = -9$$

$$\Rightarrow 6I_4 - 2I_2 - I_3 - 9$$

$$\Rightarrow 9I_4 - 2I_2 + 2 = -9 \quad [\because I_3 = -2]$$
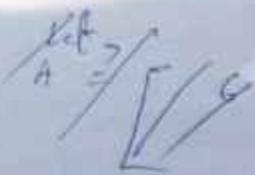
$$\Rightarrow 9I_4 - 2I_2 = -11 \quad \text{---(11)}$$



$$\therefore \text{from } (1), 6I_1 = I_2 - 4$$

$$6I_2 + 6(I_2 - 4) = 2I_4 + 22$$

$$\therefore 12I_2 - 2I_4 = 44 \quad \text{--- (III)}$$

$$6I_2 - 2I_4 = 22 \quad \text{--- (III) } \times 2$$

$$-2I_2 + 9I_4 = 11 \quad \text{--- (1) } \times 6$$

$$12I_2 - 2I_4 = 94$$

$$-12I_2 + 9I_4 = -66$$

$$14I_4 = -22$$

$$\therefore I_4 = -0.55$$

$$\begin{aligned} \text{Now, } I_0 &= I_3 - I_4 \\ &= -2 + 0.55 \\ &= -1.45 \text{ A} \end{aligned}$$

IR range of $I_{0,i}$

$$-0.55$$

~~1.45~~
Hence direction
is in the
negative

$$C = (x^2 - 1)^2 + y^2 + (z^2 - 1)^2$$

$$= x^2 + y^2 + z^2 - 2x^2 - 2z^2 + 2$$


$$= 2(x^2 + y^2 + z^2) - 2$$

$$= 2(C_0) - 2$$


$$\therefore I_0 = I_3 - I_4$$

$$\Rightarrow -2 + (-0.65)$$

$$= -1.65 \text{ A}$$

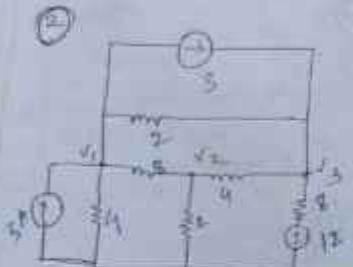

-find-
 v_1, v_2, v_3

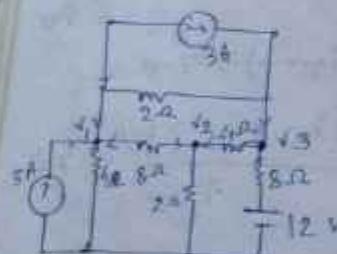

$$v_1 \times v_3$$

$$\begin{vmatrix} 1 & 8 & 2 \\ 2 & 4 & 0 \\ 2 & 4 & 1 \end{vmatrix}$$

$$\frac{v_1}{4} + \frac{v_1 - v_2}{8} + \frac{v_1 - v_3}{2} = 5 - 3$$

$$\Rightarrow \frac{2v_1 + v_1 - v_2 + 4v_1 - 4v_3}{8} = 2$$

$$\Rightarrow 7v_1 - v_2 - 4v_3 = 16 \quad \text{---(1)}$$

$$\frac{v_2 - v_1}{8} + \frac{v_2}{2} + \frac{v_2 - v_3}{4} + \cancel{\frac{v_2}{8}} = 0$$

$$\Rightarrow v_2 - v_1 + 4v_2 + 2v_2 - 2v_3 = 0$$

$$\Rightarrow 7v_2 - v_1 - 2v_3 = 0 \quad ; \quad \Rightarrow -v_1 + 7v_2 - 2v_3 = 0 \quad \text{---(2)}$$


$$\frac{v_3 - v_2}{4} + \frac{v_3 - v_1}{8} + \frac{v_3 + v_1}{2} = 3$$

$$\Rightarrow 2v_3 - 2v_2 + v_3 - v_1 + 4v_3 + v_1 = 24$$

$$\Rightarrow -4v_1 + 2v_2 + 7v_3 = 36$$

[TSS Powers no need]

Source Transformation,

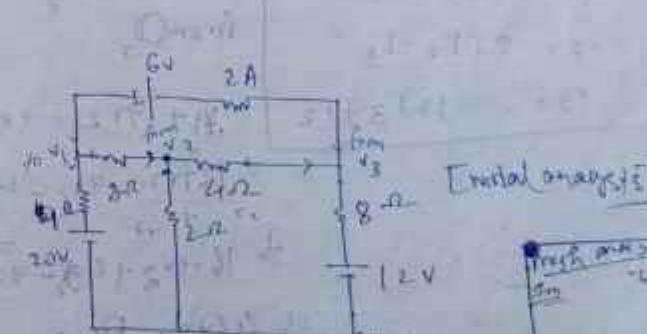

$$\frac{v_2 - v_1}{8} + \frac{v_1}{2} + \frac{v_2 - v_3}{4} = 0$$

$$\Rightarrow v_2 + v_1 + 4v_2 + 2v_3 = 0$$

$$\Rightarrow v_1 + v_2 - 2v_3 = 0 \quad \text{---(1)}$$

$$\frac{v_1 + 6}{2} + \frac{v_1 - 20}{4} + \frac{v_1 - v_2}{8} = 0$$

$$\begin{aligned} & \text{Initial analysis} \\ & \Rightarrow 4v_1 + 2v_2 + 2v_3 = 0 \\ & \Rightarrow (I_1 - I_2) + 2(I_2 + I_3) = 0 \\ & \Rightarrow -20 + 4v_2 = 0 \end{aligned}$$

$$\Rightarrow (I_1 - I_2) + 2I_2 + 2I_3 = 0$$

$$2(I_2 + I_3) = 0$$

$$\Rightarrow 6V_1 + 2V_2 + 2V_3 - 10 + V_2 = 0$$

$$\Rightarrow 7V_1 - V_2 = 16 \quad \text{(1)}$$

$$\frac{V_3 - 4}{2} + \frac{V_2 - 12}{8} + \frac{V_3 - V_2}{4} = 0$$

$$\Rightarrow 4V_3 - 2V_1 - V_2 + 12 + 2V_3 - V_2 = 0$$

$$4V_1 - 4V_3 - 8V_2 = 6 \quad \text{(2)}$$

$$4V_2 - 8V_1 - 2V_3 - 24 = 0 \quad \text{(3)}$$

$$4V_3 - 4V_1 - 2V_2 = 12 \quad \text{(4)}$$

mesh 1
eqn 1
 $V_1 = -4V_2 + 20$

$$V_2 = 2(V_3 - V_1)$$

$$V_3 = 18V_3 + 12$$

$$V_1 - 7V_2 - 2V_3 = 0$$

$$\frac{3(4V_2 - 12V_1 - 24)}{7} + 7V_1 - 2V_3 = 0$$

$$\Rightarrow 16V_2 + 4V_1 - 72 = 0$$

$$\Rightarrow 4V_2 = 56$$

$$\Rightarrow V_2 = 14V$$

$$V_1 = \frac{16V_2 - 33}{7} = 16 \cdot 19V$$

$$V_3 = \frac{36 + 2 \cdot 1 \cdot 33}{7} = 5.52V$$

mesh analysis

(from previous)

$$4V_1 - 4V_3 - 8V_2 = 6$$

$$4V_2 - 8V_1 - 2V_3 - 24 = 0$$

$$4V_3 - 2V_1 - V_2 + 12 = 0$$

$$\Rightarrow -2V_1 - V_2 + 7V_3 = -6 \quad \text{(1)}$$

$$\text{Let } A = \begin{bmatrix} 7 & -4 & -2 \\ -4 & 7 & -1 \\ -2 & -1 & 9 \end{bmatrix}, \quad B = \begin{bmatrix} 3 \\ 1 \\ -6 \end{bmatrix}$$

$$(A) = \begin{bmatrix} 7 & -4 & -2 \\ -4 & 7 & -1 \\ -2 & -1 & 9 \end{bmatrix}$$

$$= 7(45 - 1) + 4(-78 - 2) - 2(4 + 14)$$

$$= 336 - 120 - 36$$

$\therefore |A|$

$$\begin{bmatrix} 7 & -4 & -2 \\ -4 & 7 & -1 \\ -2 & -1 & 9 \end{bmatrix} \rightarrow \begin{bmatrix} 7 & -4 & -2 \\ 1 & 3 & 2 \\ 1 & 3 & 2 \end{bmatrix} \rightarrow \begin{bmatrix} 7 & -4 & -2 \\ 1 & 3 & 2 \\ 0 & 0 & 1 \end{bmatrix}$$

$$\begin{bmatrix} (45 - 1) & (-78 - 2) & (4 + 14) \\ (-78 - 2) & (45 - 4) & (-78) \\ (4 + 14) & (-7 - 8) & (16 + 10) \end{bmatrix} \rightarrow \begin{bmatrix} 48 & 30 & 18 \\ 30 & 45 & 15 \\ 18 & 15 & 33 \end{bmatrix}$$

$$I \cdot A^{-1}B = \frac{1}{180} \begin{bmatrix} 48 & 30 & 18 \\ 30 & 45 & 15 \\ 18 & 15 & 33 \end{bmatrix} \times \begin{bmatrix} 3 \\ 1 \\ -6 \end{bmatrix}$$

$$\Rightarrow \frac{1}{180} \begin{bmatrix} 336 \\ 270 \\ 6 \end{bmatrix} \rightarrow \begin{cases} V_1 = 1.87 \\ V_2 = 1.5 \\ V_3 = 0.03 \end{cases} \quad \begin{cases} V_1 = -0.425 + 1.20 \\ V_2 = 0.54 \\ V_3 = 1.25 \end{cases}$$

$$\frac{v_1 + 6 - v_3}{2} + \frac{v_1 - 2v_2}{4} + \frac{v_1 - v_2}{8} = 0$$

$$\Rightarrow \frac{(v_1 + 6 - v_3) + 2(v_1 - 2v_2) + v_1 - v_2}{8} = 0$$

$$\Rightarrow 4v_1 + 2v_2 - v_1 - 4v_3 - v_2 + 2v_1 - 2v_2 = 0$$

$$\Rightarrow 7v_1 - v_2 - 4v_3 = 16 \quad \text{--- (1)}$$

$$\frac{v_2 - v_1 + v_2 - v_3 + v_2}{8} = 0$$

$$\Rightarrow \frac{v_2 - v_1 + 2v_2 - v_3 + v_2}{8} = 0$$

$$\Rightarrow -v_1 + 4v_2 - 2v_3 = 0$$

$$\Rightarrow -v_1 + 7v_2 - 2v_3 = 0 \quad \text{--- (2)}$$

$$\frac{v_2 - 6 - v_1 + v_3 - v_2}{2} + \frac{v_3 - 12}{4} = 0$$

$$\Rightarrow \frac{(v_3 - 6 - v_1) + 2(v_3 - v_2) + v_3 - 12}{8} = 0$$

$$\Rightarrow 4v_3 + 2v_2 - v_3 - 5v_1 - 2v_2 = 24 - 12 = 0$$

$$\Rightarrow 7v_3 - 4v_1 - 2v_2 = 36$$

$$\Rightarrow -4v_1 - 2v_2 + 7v_3 = 36 \quad \text{--- (3)}$$

$$\text{--- (4)}, \quad v_1 = 7v_2 - 2v_3 \quad \text{--- (4)}$$

$$\begin{aligned} \text{--- (1)}, \quad & 7(7v_2 - 2v_3) - v_2 - 4v_3 = 16 \\ & 49v_2 - 14v_3 - v_2 - 4v_3 = 16 \\ & 48v_2 - 18v_3 = 16 \\ & 24v_2 - 9v_3 = 8 \quad \text{--- (5)} \end{aligned}$$

$$A = \begin{bmatrix} 7 & -1 & -4 \\ -1 & 2 & -2 \\ -4 & -2 & 2 \end{bmatrix} \quad B = \begin{bmatrix} 16 \\ 0 \\ 36 \end{bmatrix}$$

$$\begin{array}{c|ccc} 1 & 7 & -1 & -4 \\ 2 & -1 & 2 & -2 \\ 4 & -4 & -2 & 2 \end{array}$$

$$\Rightarrow 2(49 - 4) + 1(-7 - 8) - 4(2 + 2) \\ = 315 - 15 - 120 \\ = 180$$



$$\text{adj } A = \begin{bmatrix} 7 & -2 & 1 & -4 & -4 & 1 \\ -2 & 7 & 1 & -4 & 7 & 1 \\ 1 & -4 & 7 & 1 & -4 & 1 \\ -1 & 2 & 1 & 3 & -4 & 1 \\ -4 & -2 & 1 & 3 & -4 & 1 \\ 1 & 2 & 1 & 3 & -4 & 1 \end{bmatrix} \uparrow$$

$$\begin{bmatrix} (49 - 4) & -(-7 - 8) & (2 + 2) \\ -(7 - 8) & (49 - 16) & -(-4 - 4) \\ (-2 + 2) & -(-14 - 4) & (2 - 1) \end{bmatrix} \uparrow \quad N = \text{det } B$$

$$\begin{bmatrix} 45 & 15 & 30 \\ 15 & 33 & 18 \\ 30 & 18 & 48 \end{bmatrix} \uparrow \quad \begin{bmatrix} 45 & 15 & 30 \\ 15 & 33 & 18 \\ 30 & 18 & 48 \end{bmatrix} \uparrow \quad \begin{bmatrix} 720 + 1080 \\ 240 + 48 \\ 60 + 1728 \end{bmatrix}$$

$$\begin{bmatrix} 65 & 19 & 30 \\ 15 & 33 & 18 \\ 30 & 16 & 48 \end{bmatrix} \uparrow \quad \begin{bmatrix} 65 & 19 & 30 \\ 15 & 33 & 18 \\ 30 & 16 & 48 \end{bmatrix} \uparrow \quad \begin{bmatrix} 1800 \\ 600 \\ 2208 \end{bmatrix} \quad \begin{array}{l} v_1 = 10 \\ v_2 = 4 \\ v_3 = 12 \end{array}$$

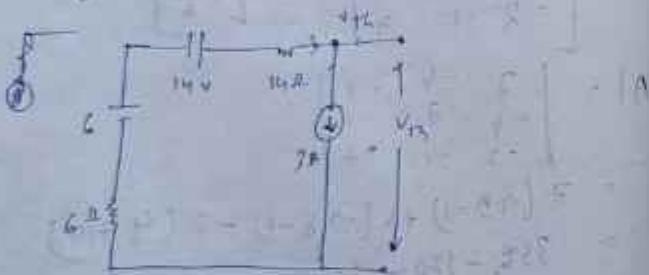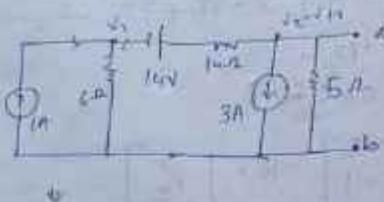
(1) Find Thevenin and Norton's Equivalent
of network from the given circuit.



$$\frac{V_{Th} - 8}{20} = -3$$

$$V_{Th} = -3 \times 20 - 60 + 8$$

$$= -52V - 52V$$

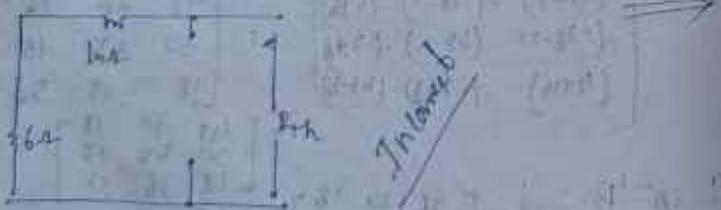

$$R_{Th} = 2.0\Omega$$

$$I_{Th} = \frac{-52}{2.0} = -26A$$

$$\frac{V_1}{6} + \frac{V_1 + 14}{14} = 1$$

$$\Rightarrow \frac{14V_1 + 6V_1 + 84 - 6V_2}{84} = 1$$

$$\Rightarrow 20V_1 - 6V_2 = 84 - 84$$

$$\Rightarrow 10V_1 - 3V_2 = 0$$

$$\Rightarrow V_1 = \frac{3V_2}{10}$$

$$\frac{V_2 - 14 - V_1}{14} + \frac{V_2}{5} = -3$$

$$\Rightarrow \frac{5V_2 - 70 - 5V_1 + 14}{70} = -3$$

$$\Rightarrow 5V_2 - 5V_1 = -210 + 70$$

$$\Rightarrow 5V_2 - 5 \times 3V_2 = -140$$

$$\Rightarrow 12V_2 - 3V_2 = -280$$

$$\Rightarrow 9V_2 = -280$$

$$\Rightarrow V_2 = -31.11V$$

$$\Rightarrow V_1 = \frac{3 \times -31.11}{10}$$

$$= -9.33V$$

$$3 - 5V_1 + 15V_2 = 150$$

$$3 - 5V_1 + 15$$


$$\Rightarrow -5V_1 + 15V_2 = 140$$

$$\Rightarrow -3V_2 + 38V_2 = -280$$

$$\Rightarrow 35V_2 = -280$$

$$\Rightarrow V_2 = -8V$$

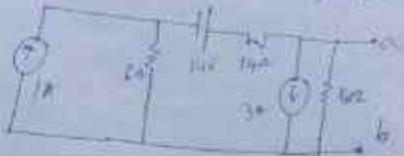Find tensions and polarity of voltage between from the given circuit -



Thévenin's theorem,



As current of 1A enters
to the Source V_1 so,
 $-1 + \frac{V_1}{6} + \frac{V_1 + 14 - V_2}{3} = 0$

$$\Rightarrow -\frac{V_1}{6} + \frac{7V_1 + 94 - 3V_2}{18} = 0$$

$$\Rightarrow V_2 = 42$$

$$\Rightarrow V_1 = 36V$$

As current of 1A

Source V_2 so,
as $\frac{V_2}{5} + \frac{V_2 - 14 - V_1}{14} + 3 = 0$

(Here we will consider the sign when calculating the magnitude)
(i.e. $\sqrt{V_2} = 3V$
but may we take $-3V$ as
it is same as $3V$)

to the right hand side

$$\begin{aligned} & \frac{16V_2 + V_2 - 14 - 210}{10\Omega} = 0 \\ & \Rightarrow 15V_2 - V_1 = 106 \\ & \Rightarrow 15V_2 - \frac{3V_2}{5} = 106 \\ & \Rightarrow 12V_2 = 106 \\ & \Rightarrow V_2 = 19.6 \end{aligned}$$

$$\frac{16V_2 + V_2 - 70 - 210}{10\Omega} = 0$$

$$\Rightarrow 17V_2 - 5V_1 = -160$$


$$\Rightarrow 17V_2 - \frac{3V_2}{5} = -160$$

$$\Rightarrow 38V_2 - 3V_2 = -260$$

$$\Rightarrow 35V_2 = -260$$


$$\Rightarrow V_2 = -8V$$

$$\Rightarrow V_1 = -8V$$

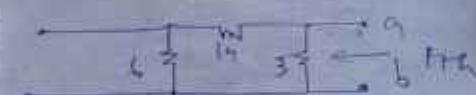


$$6 + 14 = 20$$
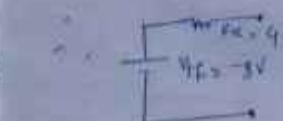
$$R_{eq} = \frac{20 - 8}{26} \Omega = 4 \Omega \parallel 10\Omega$$



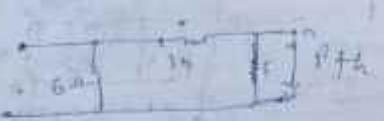for calculating Availat
of the terminals
the R will be placed
when calculating R_{eq}
For calculating the voltage
across the terminals we use





$$I_{Th} = \frac{20 - 2}{2 + 6} = 3 \text{ A}$$

$$I_{Th} = \frac{8}{4 + 15} = 0.38 \text{ A}$$



$$= 0.38 \text{ A}$$

Normal place:

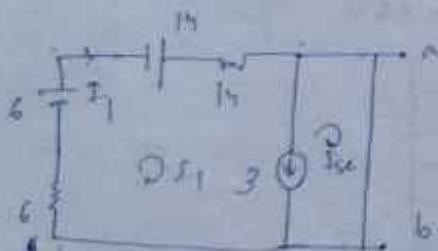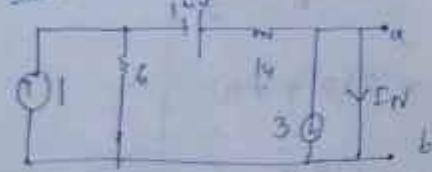

added T.V.L \rightarrow
as if Current Source
has come to that
circuit loop.

$$-6 + 6I_1 - 14 + 15I_2 = 0$$

$$\Rightarrow 20I_1 = 20$$

$$\Rightarrow I_1 = 1 \text{ A}$$

$$I_1 - I_{sc} = 3$$

$$\Rightarrow I_{sc} = I_1 - 3 = 1 - 3 = -2 \text{ A}$$



Req'd. V_{Th}

$$I_{Th} = \frac{-2 + 20}{2 + 4} = \frac{18}{6} = 3 \text{ A}$$

$$= 0.88 \text{ A}$$



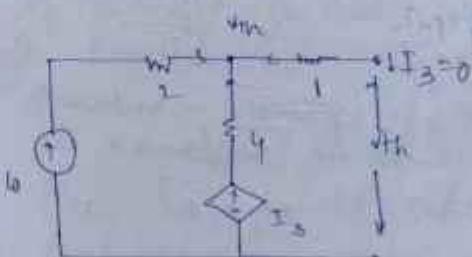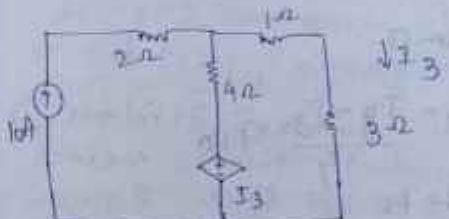③ we determine them to find the
voltage across 3R resistor.




$$3I_3 = \frac{12 - 1}{5}$$

As
 $I_3 = 0$
 I_3 CCVS is a
shunt


$$\frac{\sqrt{V_{Th}} - I_3}{4} > 10$$

$$\Rightarrow \sqrt{V_{Th}} - 0 = 40$$
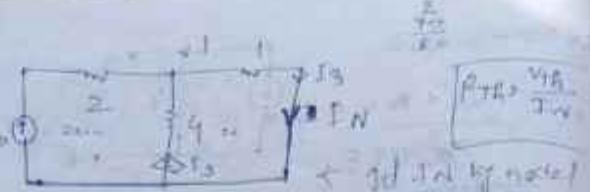
$$\Rightarrow \sqrt{V_{Th}} = 40 \text{ V}$$



$$P_{TH} = 2 \text{ W}$$

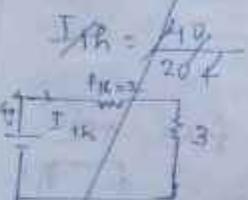

$$R_{TH} = \frac{4\Omega}{5} = 0.8\Omega$$

$$\begin{aligned} & \text{to } \frac{V_1 - I_3}{4} = 10 - I_N \\ & \Rightarrow I_N = 10 - \frac{V_1 - I_3}{4} \quad \text{---(1)} \end{aligned}$$

$$\frac{V_1}{1} = I_N - I_3 \quad \text{from (1)}$$

$$\Rightarrow I_N = I_3 - \frac{V_1}{4} + 10$$

$$\Rightarrow I_N = 10$$

$$P_{TH} = \frac{4\Omega}{10\Omega} = 0.4\text{ W}$$



$$I_{RN} = \frac{40}{7} = 5.71$$

$$\begin{aligned} \text{voltage across } 3\Omega &= V_3 = I_{RN} R_3 = 5.71 \times 3 \\ &= 40 \times \frac{3}{7} \quad P = I^2 R \\ &= \frac{120}{7} = 17.14 \text{ V} \\ &> 17.14 \end{aligned}$$

Thevenin's method
2nd year (EE)

① Thevenin's theorem statement - It states that it is possible to simplify any linear circuit irrespective of how complex it is by one equivalent of how circuit with a single voltage source and a series resistance. Find P_{TH} , then remove it through volt. Procedure - To find out P_{TH} voltage source should be short circuited with its internal resistance - Current source should be open. measure equivalent resistance at (at P_{TH}), viewed from the load terminal.

② Norton's theorem - It states that any linear circuit containing several energy sources and resistance can be replaced by a single constant current generator in parallel with a single resistor.


Procedure - Identify R_{RN} , then short R_N through an ammeter, redraw the circuit diagram, then have to measure 1st short current (I_{RN}), find R_{RN} , redraw the circuit diagram.

③ superposition theorem - It states that a circuit with multiple voltage and current sources, is equal to the sum of simplified circuits using just one of the sources.

only one source will act at one time
More than 1 source should not be present
in the circuit [valve/galvanic source -
more than 1]

- ④ maximum power transformation theorem
more power will flow in load
when load resistance is equal to
the P_{TH} [$P = I^2 R$]. Here cut off voltage
is 50V. [Prove 2nd part - SEE]

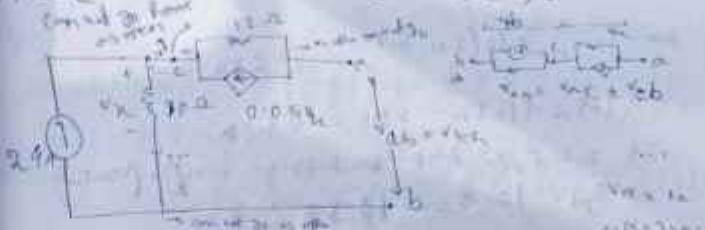⑤ Thevenin's Th at the terminals a, b 10/3/72



$$V_{Th} = 24 \times 10 = 240V = V_{ab}$$


$$V_{RL} = -0.05 \times 12 = 12$$

$$+ 48V$$

$$V_{ab} = V_{RL} + V_{Th}$$


$$= -144 + 240$$

$$= 96V = V_{Th}$$

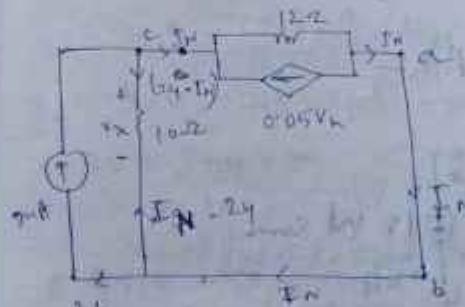

[In incoming
outgoing (in)
outgoing
in incoming (out)]

$$V_R = 10(96 - I_R) - ①$$

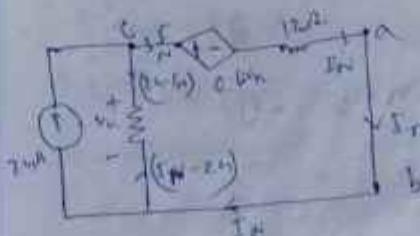

$$= 12V_N + 10(1N - 2) = 6VN$$

$$\Rightarrow 12V_N - 10VN - 240 = -0.6V_N$$

$$\Rightarrow 2.4V_N - 240 + 2.6V_N = 0.6V_N$$


$$\Rightarrow V_N = 10.034 \text{ V}$$

$$V_R = 10(2N - 10.034)$$


$$= 12N - 100.34$$

$$= 1.80 \text{ V}$$
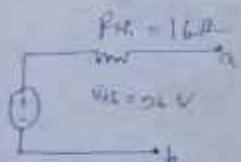
$$R_{TH} = \frac{V_{TH}}{I_N} = \frac{96}{6} = 16 \Omega$$



Other forms to get R_{TH}

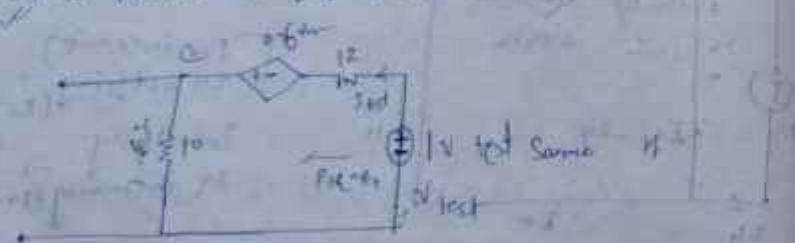

$$R_{TH} = \frac{V_R}{I_N}$$

$$0.6VN - 12I_N + 1 - V_R = 0$$

$$V_R = I_N \times 10 \quad \text{(1)}$$

$$\Rightarrow 0.6VN - 12I_N + 1 - 10I_N = 0$$


$$\Rightarrow -22I_N + 12V_N = 0 \quad \text{(2)}$$

$$\Rightarrow -16V_N = 0 \quad \text{(3)}$$

$$\Rightarrow V_N = \frac{1}{16} \text{ V}$$

$$\text{Hence } R_{TH} = V_R/I_N = 1/(1/16) \\ = 16 \Omega$$

2nd method

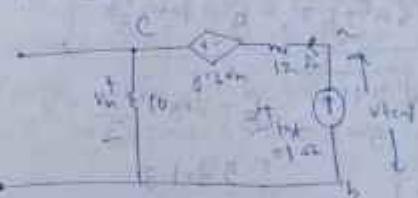

$$0.6VN + -12I_N + V_R = 0$$

$$\Rightarrow 0.6VN - 12I_N + V_R = 0 \quad \text{(1)}$$

$$V_R = I_N \times 10 \quad \text{(2)}$$

$$= 10I_N \quad \text{(3)}$$

$$0.6VN - 12I_N + 10I_N = 0$$

$$\Rightarrow 0.6V_N - 12I_N = 0$$

$$0.6V_N = 12I_N$$

$$V_N = 16V$$

$|A| < 0 \rightarrow$ polar $\times /$

$a+jb \rightarrow$ rectangular form $+ \quad \odot$

AC circuit

Rectangular \rightarrow

$|A| < 0 \rightarrow A[\cos\theta + j\sin\theta]$

Rectangular \rightarrow polar

$$a+jb \rightarrow A = \sqrt{a^2+b^2}, \theta = \tan^{-1} \frac{b}{a}$$

$$3+4j \rightarrow A = \sqrt{3^2+4^2} = 5 \quad \theta = \tan^{-1} \frac{4}{3} = 53.13^\circ$$

$$5 \angle 53.13^\circ \quad (\theta < 0)$$

[in calculator - 1st Pol(3, 4) = 5
then, RCL \rightarrow tan]

$$\text{Pol} = 5 \angle 53.13^\circ \quad (\theta < 0)$$

[in calculator - 1st REC(5, 53.13)
then, pol \rightarrow tan]

$$\text{REC} = 3+4j$$

$$A = 5, \theta = 53.13^\circ$$

$$5 [\cos 53.13^\circ + j \sin 53.13^\circ]$$

$5 \angle 53.13^\circ \text{ ohms}$

$$15 \angle 90^\circ = 150$$



$153.13 + 150 = 203.13$ [rule always added
for multiplication]

$$203.13 / 10 = 20$$

$$20 / 10 = 10$$


$63.13 - (-45)^\circ$ [Angle will subtract
for division]

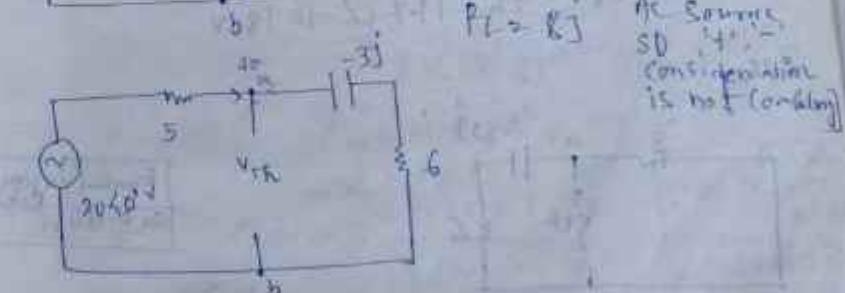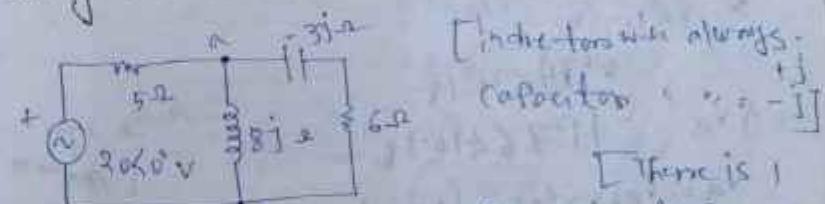- [As if it is added, the sum will be written as 78.13]
① Determine the voltage across and current
through the inductor in the given circuit
using Kirchhoff's theorem.



$$V_{AB} = V_{aB}$$
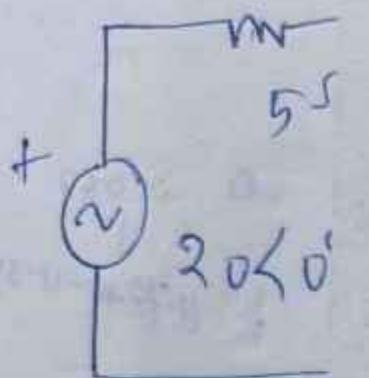
$$\frac{Va - 2.0 + jVb}{5 + j8 - j3} = 0$$



$$v = 35\angle 0^\circ$$

Therefore there will always be a phase difference of 90°

Pol

$$50 \angle 0^\circ =$$

Re

$$50 + 0j$$

$$50 \angle 90^\circ = 0 + 50j$$

Re

$$50 \angle 70^\circ =$$

Pol

$$0 + 50j$$

$$50 \angle 0^\circ =$$

$$50 + 0j$$

$$\sqrt{V_{th}}^2 V_{ab}$$

$$\sqrt{a} = 20 + V_a$$

$$\rightarrow \frac{(V_A + 2j)(6 - 3j)}{5(6 - 3j)}$$

$$\rightarrow V_A \left[\frac{1}{5} + \frac{1}{6-3j} \right] + j$$

$$\rightarrow V_A \left[0.2 + \frac{1}{6+3j} \angle -26.565 \right] + j$$

$$\rightarrow V_A \left[0.2 + 0.159 \angle -26.565 \right] + j$$

$$\rightarrow V_A [0.2 + 0.134 + j0.06] = j$$


From $V_A = [0.336 + j0.06]$ \therefore $33.6 \angle 10.18^\circ$
 $\therefore V_A = [0.34 \angle 10.18^\circ] \text{ V}$

$$\therefore V_A = \frac{j}{0.34 \angle 10.18^\circ}$$

$$\therefore V_A = 11.76 \angle 10.18^\circ$$

$$\therefore V_A = V_{ab} + Th = 11.76 \angle -10.18^\circ \text{ V}$$

Th

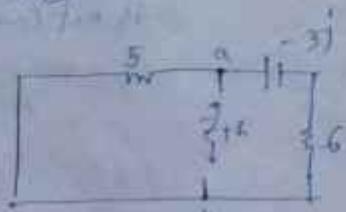

$$Th = 6 - 3j \times 5$$

$$(6 - 3j) + 5$$

$$= \frac{30 - 15j}{11 - 3j}$$


$$30.54 \angle -26.565^\circ$$

$$11.4 \angle -15.255^\circ$$

$$Z_{TH} = 2 \cdot 5 \cdot 4 \cdot 2 \angle -11.27^\circ \Omega$$

$$= 2 \cdot 38 = -0.579 \Omega$$
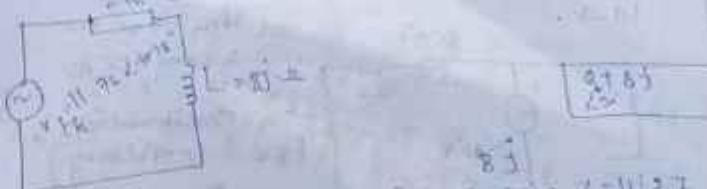
$$= 2 \cdot 38 - 0.579 \angle -90^\circ$$



$$11.76 \angle -10.18^\circ = 2 \cdot 2 \cdot 34.2 \angle -11.27^\circ$$

$$= 34.574 \angle (11.27^\circ - 10.18^\circ)$$

$$34.08 \angle 8.8279.82^\circ$$

$$3.88 \angle 7.43^\circ$$

$$34.08 \angle 79.82^\circ$$

$$7.048 \angle 68.81^\circ$$

$$= 11.81 \angle 11.01^\circ \text{ V}$$

$$I_L = \frac{V_L}{Z_{TH}} = \frac{11.81 \angle 11.01^\circ}{8.9239}$$


Note: Here we can see the voltage across Z_{TH} is V_L .
 I_L is V_L value and current I_L is V_L through Z_{TH} .

$$= 1.476 \angle -78.95^\circ$$

$$= 1.476 \angle -79^\circ \text{ A}$$


Q. 8 2

DDSP

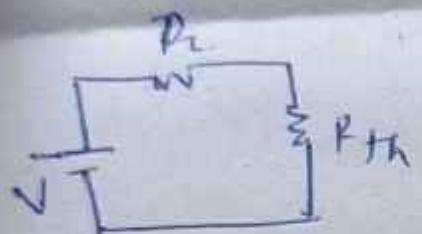

$$I_L = I_R$$

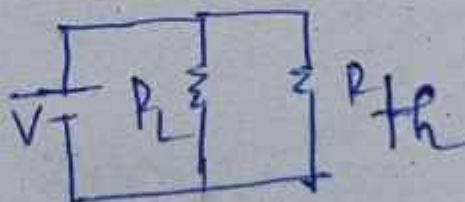~~$V_R \neq V_L$~~ \therefore VDR will be applied



$$V_L = V_R$$


$I_L \neq I_R$? CDR will be applied

$$= 1.476 \angle -78.99^\circ$$


$$= 1.476 \angle -79^\circ A$$

V_{th} is
the v.d.
L is
and
using

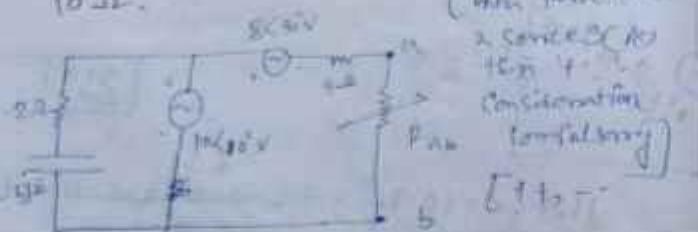- Q In the network shown determine
the variation of current in R_{ab}
when it is varied from 2Ω to
10Ω.



1st find Thevenin's equivalent network

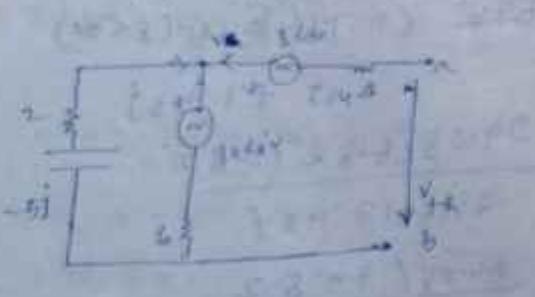

$$\frac{V_{th}}{2-5j} + \frac{V_{th}-10}{6} = 0$$

$$2 \frac{V_{th}}{2-5j} + \frac{V_{th}}{6} = \frac{10}{2+5j} - 10$$

$$2 \frac{V_{th}}{2-5j} \left[\frac{1}{6} + \frac{1}{2-5j} \right] = 10$$

$$2 \frac{V_{th}}{2-5j} \left[0.167 + \frac{1+5j}{2+5j} \right] = 10$$

$$2 \frac{V_{th}}{2-5j} [0.167 + 0.185 \angle 68.2^\circ] = 10$$

$$V_{th} [0.167 + 0.068 + 0.17j] = 10$$

$$V_{th} [0.235 + 0.17j] = 10$$

$$V_{th} = \frac{10}{0.235 + 0.17j}$$

$$= 1.67$$

$$0.167 \angle 35.9^\circ$$

$$v_{th} = 5.76 \angle 35.9^\circ$$

$$v_{th} = V_{ab} = V = 8 \angle 30^\circ$$

$$= 3.75 \angle -35.9^\circ - 8 \angle 30^\circ$$

$$= 4.66 \angle -3.37^\circ$$


$$= 4.66 \angle -3.37^\circ - (6.52 + j)$$

$$= -2.26 - 7.37j \angle -7.16 \angle -68^\circ$$

$$= -(2.26 + 7.37j)$$

$$= -7.916 \angle 72.95^\circ$$

$$= 7.916 \angle -107.05^\circ$$

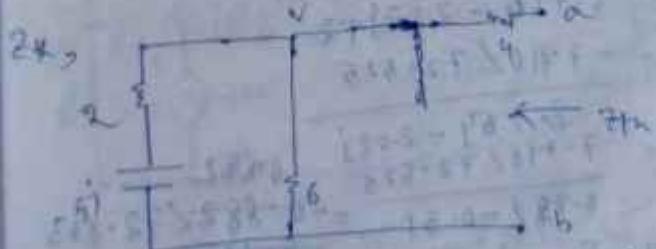

$$\frac{V_{th}}{2+6-5j} + \frac{V_{th}-10}{4} = \frac{10-3j}{2+5j} + j$$

$$\frac{V_{th}}{8-5j} + \frac{V_{th}-10}{4} = \frac{10-3j}{8-5j} + j$$

$$= \frac{12 - 30j + 32 - 80j}{8 - 5j}$$

$$= \frac{44 - 50j}{8 - 5j}$$


$$= 8 - 5j$$

$$= 6.66 \angle -48.65^\circ$$

$$24.3 \angle -32^\circ$$

$$= 7.062 \angle -16.65^\circ$$

$$= (6.765 - 2.02j) \Omega$$

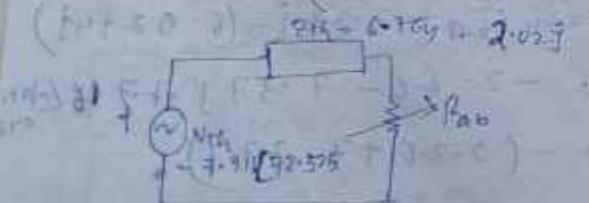

(i) When $R_{AB} > 2.02$

$$Z = 7.716 / 72.525$$

$$= 6.764 - 2.02j + j$$

$$= -7.716 / 72.525$$

$$= -7.764 - 2.02j$$

$$= -7.716 / 72.525$$

(ii) When $R_{AB} = 10.2$

$$Z = \frac{-7.716 / 72.525}{10.2 - j} = -0.75 \angle 86.31^\circ$$

$$= -7.716 / 72.525$$

$$= 16.765 \angle -2.027^\circ$$



$$= -7.716 / 72.525$$

$$= 16.75 \angle -0.55^\circ$$

$$= -0.961 \angle 73.115^\circ$$

$$= 0.961 \angle 106.885^\circ$$

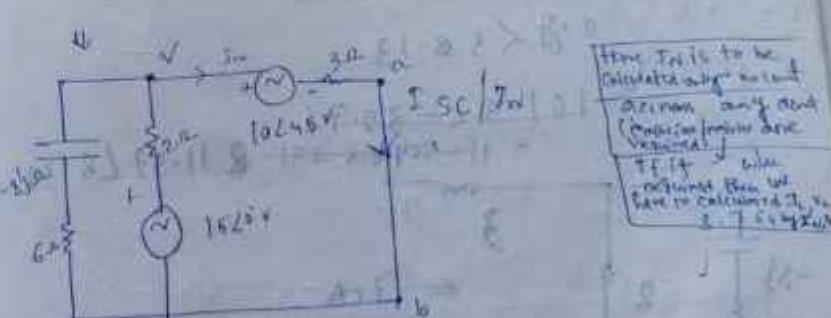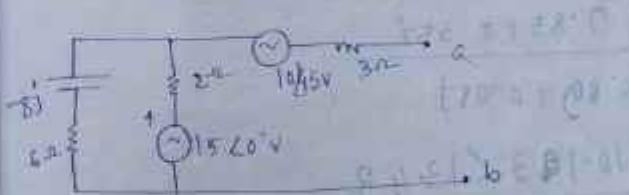③ Obtain the harmonic equivalent circuit at terminals ab of the network.



$$\frac{V}{(6.8j)} + \frac{V - 15}{2} + \frac{V - 10 / 4j}{3} = 0$$

$$\Rightarrow V \left(\frac{1}{6.8j} + \frac{1}{2} + \frac{1}{3} \right) = \frac{15}{2} + \frac{10 / 4j}{3}$$

$$\Rightarrow V \left(\frac{1}{6.8j} + j \frac{1}{3 - 0.5 + 0.3} \right) = 7.5 +$$

$$\Rightarrow V \left(\frac{1}{10 - 5.3 - 1.3j} + j 0.8 \right) = \frac{7.5}{3 + 3.2/1.3}$$


$$\Rightarrow V (0.1453 + j 0.8) = 7.5 + j 2.35 +$$

$$\Rightarrow V (0.06 + j 0.08) = 7.5 + j 2.35 +$$

$$\Rightarrow V (0.06 + j 0.08) = 8.69 + j 2.35$$

$$\begin{aligned} \Rightarrow V &= \frac{9.85 + j 2.35}{0.06 + j 0.08} \\ &= 10.123 \angle 13.42^\circ \end{aligned}$$

$$0.8 \angle 58.13^\circ$$

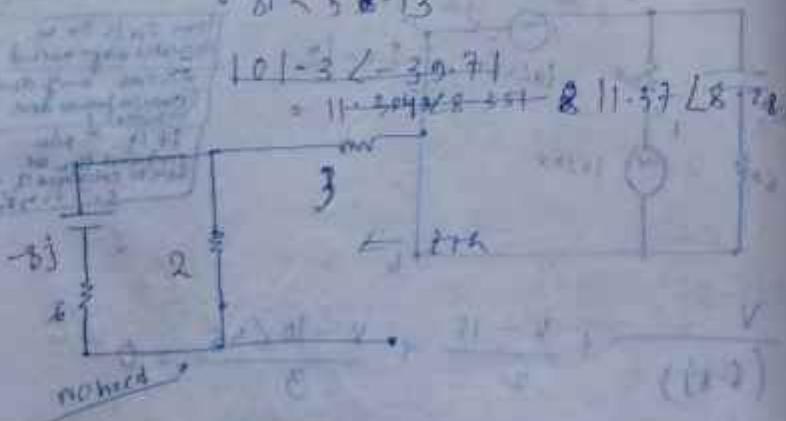

$$\frac{d^2V}{dt^2} + \frac{2}{R} \frac{dV}{dt} + \left(\frac{1}{L} + \frac{1}{C} + \frac{1}{R^2} \right) V = 0$$

$$I_R = \frac{V}{R} = \frac{10.123}{3}$$

$$= 11.304 \angle 8.35^\circ$$

$$\begin{aligned} &= 11.189 + j 1.643 - (7.07 + j 2.35) \\ &\quad + (7.07 + j 2.35) \end{aligned}$$

$$= 4.114 + j 5.453$$

$$= 11.392 \angle 8.78^\circ - 1.645$$

$$\begin{aligned} &= 11.25 + j 1.63j - (7.07 + j 2.35) \\ &\quad + (7.07 + j 2.35) \end{aligned}$$

$$= 4.188 + j 5.29j$$

$$\begin{aligned} &= 6.862 - j 5.294 \\ &= 2.282 \angle 52.46^\circ \end{aligned}$$

$$V \left(\frac{1}{6.8j} + \frac{1}{2} + \frac{1}{3} \right) = \frac{15}{2} + \frac{102.45}{3}$$

$$\Rightarrow V \left(\frac{1}{102.45 - 53.13} + 0.5 + 0.3 \right) = 7.5 + 3.33 \angle 45^\circ$$

$$\Rightarrow V = \frac{7.5 + 3.33 \angle 45^\circ}{0.1 \angle 53.13 + 0.8}$$

$$= \frac{7.5 + 2.35 + 2.35j}{0.06 + 0.088j + 0.8}$$

$$\Rightarrow \frac{9.85 + 2.35j}{0.86 + 0.08j}$$

$$\Rightarrow \frac{10.12 \angle 13.4^\circ}{0.86 \angle 5.31^\circ}$$

$$V_2 = 11.76 \angle 8.1^\circ$$

$$I_{n2} = \frac{V - 102.45}{3}$$

$$= \frac{11.76 \angle 8.1^\circ - 10 \angle 45^\circ}{3}$$

$$\Rightarrow \frac{11.64 + 1.65j - (7.07 + 7.07j)}{3}$$

$$= \frac{11.64 + 1.65j - 7.07 - 7.07j}{3}$$

$$= \frac{4.57 - 5.42j}{3}$$

0.3 1.7
333. 2 7.08 7.18 7.18 < -49.86
7.1 3 2.37 < -49.86

٢٤١٦٥٠١٥

١٤٢٣٢٨٠

٣٣٢٧٤١١

٣٣٢٩١١

٦

13/12/2023

Maximum Power Transfer theorem

- Q) What should be the value of Z_L connected across the terminal a, b so that if we draw maximum power what be amount of maximum power?

A sign - Derivation

Theorem - Maximum power will be transferred to the load Z_L when the load is connected conjugate of the Thevenin's current generator.

$$\text{Complex conjugate} = (A+jB)^* = A-jB$$



$$A < 0 \rightarrow A < 0$$

$$Z = \sqrt{R^2 + (X_L - A)^2}$$

$$Z = R + jX_L$$



Real part \Rightarrow sing part = X_L

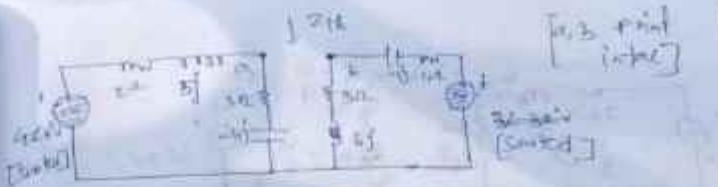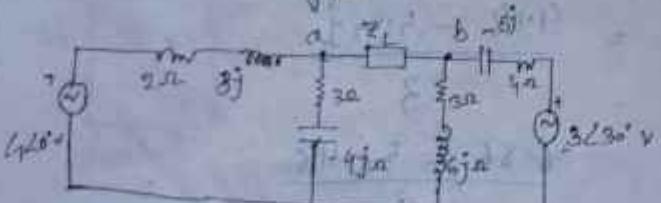

$$\begin{aligned}
 & \text{Reqd. } Z_L = \frac{(2+3j)(3+1j)}{2+3j+3j-4j} + \frac{(4-3j)(6+3j)}{4-3j+3j+4j} \\
 & = \frac{6-8j+7j-12j^2}{5-j} + \frac{12+6j-15j-3j^2}{7+j} \\
 & = \frac{3.61\angle 56.31^\circ - 5j - 53.13}{5.1\angle -11.31^\circ} + 0.4\angle -51.34^\circ \\
 & = \frac{18.05\angle 318^\circ}{5.1\angle -11.31^\circ} + \frac{42.944\angle 12.05^\circ}{7.07\angle 8.13^\circ} \\
 & = 3.54\angle 149.9^\circ + 6.07\angle 3.96^\circ
 \end{aligned}$$

$$= 3.43 + 0.68j + 6.056 + 0.42j$$

$$= 9.486 + 1.1j$$

$$= 9.55\angle 7.8^\circ$$

$$\begin{aligned}
 Z_L &= 2\Omega = \frac{0.47 - 1.3j}{0.47 + 1.3j} \Omega \quad | \quad 5.55^\circ \\
 &= \frac{3.486 + 1.1j}{0.97 - 7.8j} \\
 P_{\max} &= \frac{|V_{th}|^2}{4R_L} \cdot 2\Omega \cdot 2\Omega = \frac{3^2}{4} \cdot 2\Omega \cdot 2\Omega \cdot 0.47 \Omega
 \end{aligned}$$



$$\frac{V_a - 4\angle 0}{(2+j3)} + \frac{V_a}{(3-j)} = 0$$

$$\Rightarrow V_a \left[\frac{1}{2+j3} + \frac{1}{3-j} \right] = \frac{4}{2+j3}$$

$$\Rightarrow V_a \left[\frac{1}{3+4j} + \frac{1}{5-3j} \right] = \frac{4}{3+4j}$$

$$\Rightarrow V_a [0.28 \angle -56.31 + 0.2 \angle 53.13]$$

$$\Rightarrow V_a [0.28 \angle -56.31 + 0.11 \angle -56.31]$$

$$\Rightarrow V_a [0.28 \angle -0.23j + 0.11 \angle -0.16j]$$

$$\Rightarrow V_a [0.28 - 0.07j] = 0.28 \angle -56.31$$

$$\Rightarrow V_a = \frac{0.28 - 0.07j}{3+4j}$$

$$= 0.11 \angle -56.31$$

$$= 0.11 \angle -56.31$$

$$= 0.1288 \angle -14.03$$

$$= 3.85 \angle -42.28$$

$$= 3.85 \angle -22.63$$

$$\frac{V_b - 3\angle 30}{(4-j)} + \frac{V_b}{(3j)} = 0$$

$$\Rightarrow V_b \left[\frac{1}{4-j} + \frac{1}{3j} \right] = \frac{3\angle 30}{4-j}$$

$$\Rightarrow V_b \left[\frac{1}{6.4 \angle -56.34} + \frac{1}{6.3 \angle 63.43} \right] = \frac{3\angle 30}{6.4 \angle -56.34}$$

$$\Rightarrow V_b [0.156 \angle 56.34 + 0.152 \angle -63.43] = 0.47 \angle 81.34$$

$$\Rightarrow V_b [0.097 + 0.12j + 0.067 - 0.13j] = 0.47 \angle 81.34$$

$$\Rightarrow V_b = 0.47 \angle 81.34$$

$$= 0.47 \angle 81.34$$

$$= 0.47 \angle 81.34$$

$$= 0.47 \angle 39.84$$

$$= 0.47 \angle 39.84$$

$$= 0.47 \angle 3.027 + 3j$$

$$V_{ab} = (V_b - V_a)$$

$$= (0.47 \angle 3.027 + 3j) - 0.11 \angle -56.31$$

$$= 0.36 \angle 42.28$$

$$P_{max} = \frac{(-2.58 + 5.6j)^2}{3+4j}$$

$$= \frac{6.96 \times 174.7 - 0.147}{3+4j}$$

$$= 0.33 \angle 7.8$$

<math display

$$S_L = -6.162 \angle 14.7^\circ$$

$$\frac{0.486 - 1.35j + 0.48j}{-0.32 \angle 114.7^\circ}$$

$$P_{out} = (0.32 \angle 114.7^\circ)^2 \times 0.87 L^2 S$$

$$= 0.57 \angle 221.4^\circ$$

(iii)

$$I_1 = \frac{4}{5+j} \quad I_2 = \frac{3/j}{7+j}$$

$$= \frac{3 \angle 30^\circ}{7.07 \angle 28.57^\circ}$$

$$= 0.424 \angle 20.87^\circ$$

$$V_o = I_1 (5-j) = (0.784 \angle 11.81^\circ)(5-j)$$

$$= 3.92 \angle -41.82^\circ$$

$$V_b = I_2 (3+j) = (0.424 \angle 20.87^\circ)(3+j)$$

$$= (0.424 \angle 41.47^\circ)(3+j)$$

$$= (0.624 \angle 14.9^\circ)(6.71 \angle 63.43^\circ)$$

$$= 2.59 \angle 85.3^\circ$$

$$v_o = V_b = V_o - V_D$$

$$= 3.92 \angle -41.82^\circ - 2.05 \angle 28.57^\circ$$

$$= 2.52 \angle -2.61^\circ - (20.87 + 28.57)$$

$$= 2.52 \angle -54.45^\circ$$

$$= 6.75 \angle -63.62^\circ$$

$$P_{out} = \frac{|V_o|^2}{4 R_L}$$

$$= \frac{(6.75 \angle -63.62^\circ)^2}{4 \times 0.47}$$

$$= 0.95 \angle 126.6^\circ$$

$$I_{L1} = \frac{V_{th}}{2 R_L + r_L}$$

$$= \frac{6 \angle -03.6^\circ}{220.47}$$

$$= 0.316 \angle -03.6^\circ A$$


$$P_L = I_{L1}^2 R_L$$

$$= (0.316)^2 \times 12.947$$

$$= 1.95 W$$



R_L : the have
to take the
rest of rest for

R_L : Then sum the
part of *

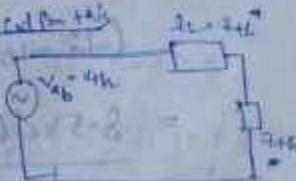

for & since only
one of the mag values
will be used no
angle will come there

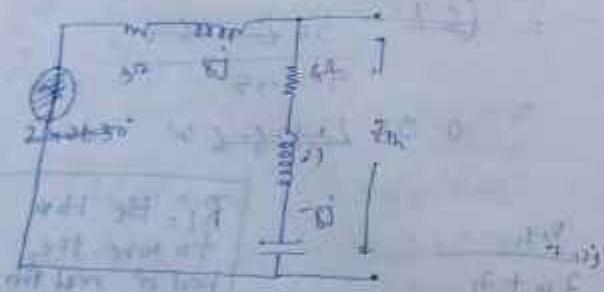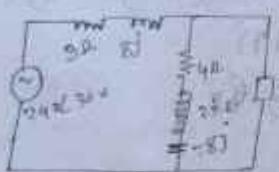① For the circuit show what load
impedance absorbs the max power
and what is the power?



$$R_{th} = \frac{V}{I} = \frac{(3+j4)(4-j6)}{3+j4+8-j6} =$$

$$= \frac{(-12+18j+32j-48)}{3+j4+8-j6} = \frac{-36+50j}{11-j2} =$$


$$= \frac{8.5426544 + j7.21(-.5631)}{11-j2} =$$

$$7.28 \angle 15.54$$

$$= 8.545 \angle -2.81$$

$$= 8.44 - 0.41j$$

$$R_L = 8.44 \quad X_L = 0.41j$$

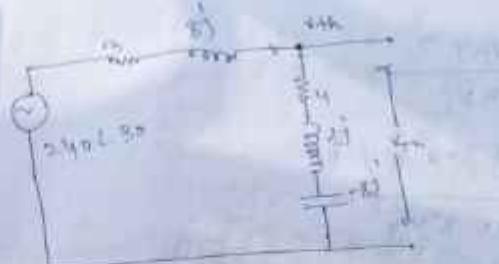

$$\frac{V_{th} - 240 \angle 30^\circ}{(3+j4)} + \frac{V_{th}}{(4-j6)} = 0$$

$$\Rightarrow V_{th} \left[\frac{1}{3+j4} + \frac{1}{4-j6} \right] = \frac{240 \angle 30^\circ}{3+j4}$$

$$\Rightarrow V_{th} \left[\frac{1}{8.54 \angle 65.44} + \frac{1}{7.21 \angle -56.31} \right] = \frac{240 \angle 30^\circ}{3+j4}$$

$$8.54 \angle 65.44$$

$$\Rightarrow V_{th} \left[0.12 \angle -65.44 + 0.142 \angle 56.31 \right]$$

$$= 28.1 \angle -35.44$$

$$\Rightarrow V_{th} \left[0.042 - 0.112j + 0.08 + 0.112j \right] = 28.1 \angle -35.44$$

$$\Rightarrow V_{th} \left[0.122 + 0.004j \right] = 28.1 \angle -35.44$$

$$\Rightarrow V_{th} = \frac{28.1 \angle -35.44}{0.122 + 0.004j} = \frac{28.1 \angle -35.44}{0.122 \angle 1.57} = \frac{230.3 \angle -41.3^\circ}{0.122 \angle 1.57}$$

$$\text{Power} = \frac{Wm^2}{WPL}$$

$$\rightarrow (2.3 + 0.32)^2 \\ \approx 8.04 \\ = 15.07 \text{ W}$$

$$\text{Ansatz: } \frac{1}{Z_{\text{total}}} = \left[\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \frac{1}{Z_4} \right] \text{ A/V} \\ \frac{1}{Z_{\text{total}}} = \left[\frac{1}{1.6 \cdot 10^{-3}} + \frac{1}{1.2 \cdot 10^{-3}} + \frac{1}{0.8 \cdot 10^{-3}} + \frac{1}{0.2 \cdot 10^{-3}} \right] \text{ A/V} \\ \Rightarrow Z_{\text{total}} = 0.2 \text{ JFM C}$$

$$[10 - 2 \cdot 0.2 \cdot 10^{-3} \cdot 0.7 + 0.2 \cdot 10^{-3} \cdot 1.2 \cdot 10^{-3}] \text{ A/V}$$

$$10 \text{ V} = 3.1032 \text{ V}$$

$$1.2 \text{ V} = [0.2 \cdot 10^{-3} + 0.2 \cdot 10^{-3} \cdot 5 \cdot 10^{-3}] \text{ A/V}$$



$$0.002512 \text{ V} = [0.2 \cdot 10^{-3} + 0.2 \cdot 10^{-3}] \text{ A/V} \\ 10 \text{ V} = 3.12 \text{ V} \quad \text{at } 0.2 \text{ A}$$

$$[0.2 \cdot 10^{-3} + 0.2 \cdot 10^{-3}] \text{ A/V}$$

Signal


(is infinite representing physical quantity)
(Temp, p, voice etc)
(electrical I, voltage)

ii) Step function / Step signal -

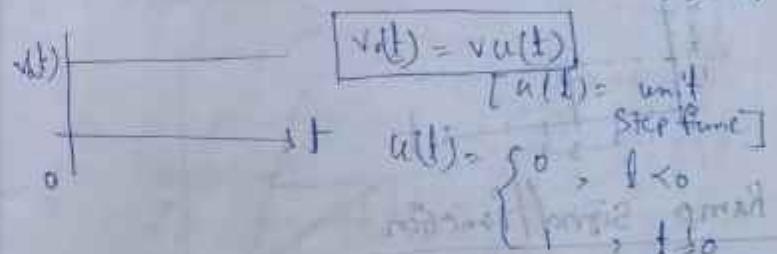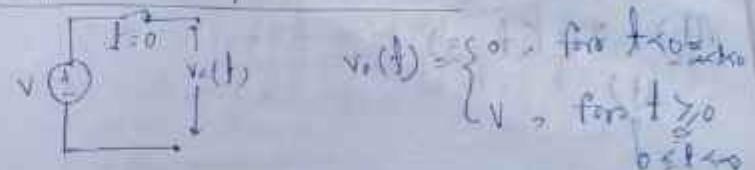

general step function - $f(t) = A \cdot u(t-a) + s^0$

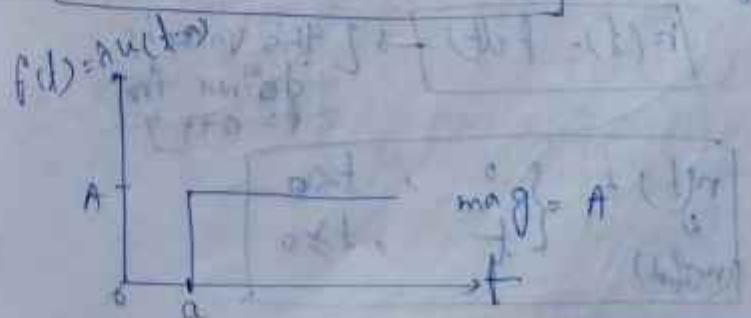
$$f(t) = A \cdot u(t-a) + s^0, \quad t < a \\ f(t) = A, \quad t \geq a \quad [A: \text{general amplitude}, a: \text{delay}]$$



$$f(t) = A u(t+a)$$


[a: progress
here]

$$f(t) = A u(t+a)$$

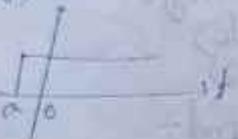

$$f(t) = 2u(t-3)$$

(a)

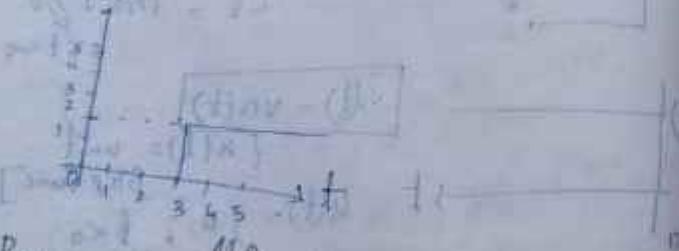

Ramp Signal Function

$$f(t) = \int a u(t) dt = \int 1 dt = t + C$$

but 3rd quadrant has no y-axis


$$\int a u(t) dt$$

$$\int a u(t) dt = t + C$$

$$\int a u(t) dt = t u(t)$$


$$\int a u(t) dt = f(t) \rightarrow [\text{this value is defined for } t = 0+]$$
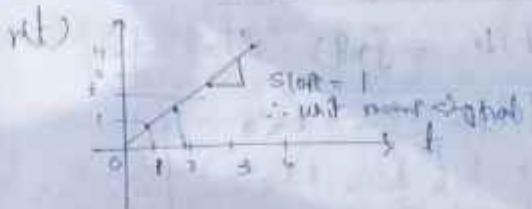
$$r(t) = \begin{cases} 0 & t < 0 \\ t & 0 \leq t < 2 \\ 2 & t \geq 2 \end{cases}$$



General ramp function

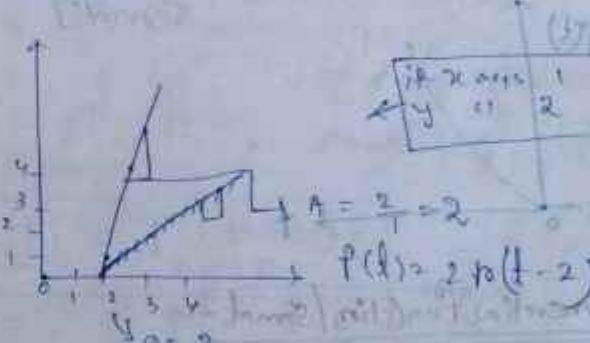
$$r(t) = A u(t-a) = \begin{cases} 0 & t < a \\ At & t \geq a \end{cases}$$



$$r(t) = 2u(t-2)$$

$$\frac{d}{dt}[r(t)] = u(t-2)$$
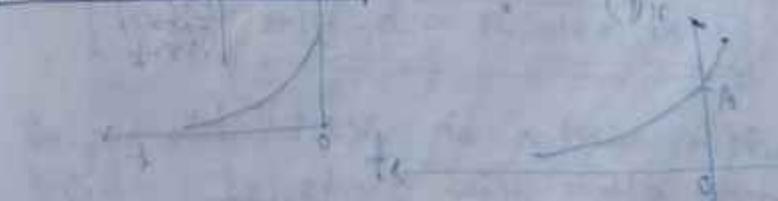
$$u(t-2) = \begin{cases} 0 & t < 2 \\ 1 & t \geq 2 \end{cases}$$




Pointwise & pointwise function

$$\int S(t)dt = s(t) = \left(t + \frac{1}{2} \right)$$

$$f(t) = \begin{cases} 0, & t < 0 \\ \frac{1}{2}, & t \geq 0 \end{cases}$$

$$s(t) = \begin{cases} 0, & t < 0 \\ \frac{t}{2}, & t \geq 0 \end{cases}$$


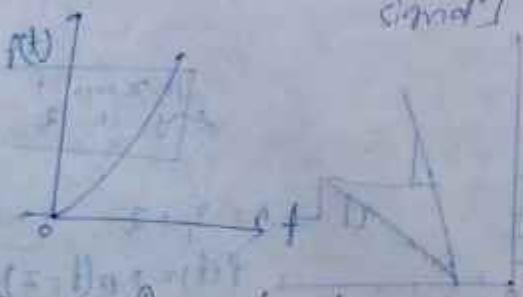
[As constant
don't change
the shape of
signal]



Exponential Function/Signal -

$$n(t) = A e^{-ut}$$

$$n(t) = A e^{-at} u(t)$$

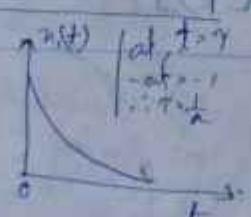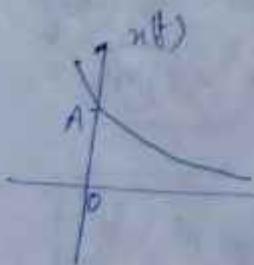


become equal to

Theoretically $s(t)$ can become 0 at $t = \infty$.
But practically $s(t)$ is almost 0 or negligible
with some $s(t) = 0$ at $t = BT$ (long)
Where, $\gamma = \frac{1}{a}$ = time constant [at this
value the exponent is equal to -1]

• Impulsive Signal Function (or) Dirac delta function

Pulse

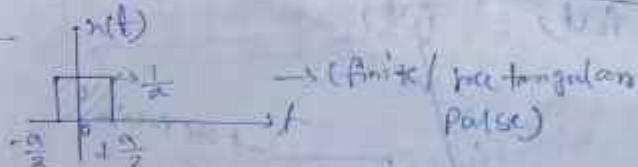

$$n(t) = \begin{cases} \frac{1}{a}, & -\frac{a}{2} < t < \frac{a}{2} \\ 0, & \text{otherwise} \end{cases}$$

now,

$$\delta(t) = \lim_{a \rightarrow 0} n(t)$$

Dirac

$$= \begin{cases} 1, & t=0 \\ 0, & t \neq 0 \end{cases}$$

Base = 0
Height = $\frac{1}{a}$
Area = 1

[For any value of a the area is 1]


So, a unit impulse is a pulse with infinite height, 0 width and area = 1 (that is the uniqueness)

composite signals


$$\textcircled{1} \quad f(t) = \pi t u(t - 3)$$

(with f_1, f_2)


$f_1(t) = \frac{\pi}{2} t$

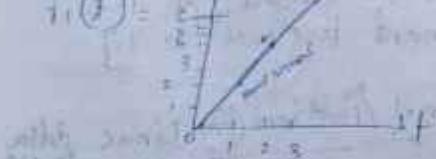
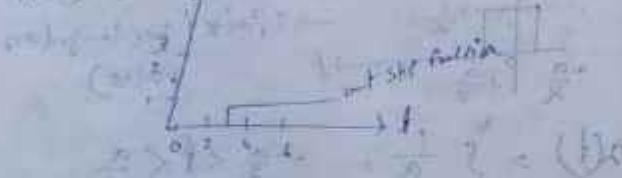
$$f_2(t) = \begin{cases} 1 & 0 \leq t < 3 \\ 0 & \text{else} \end{cases}$$



$$(f_1, f_2, f_3) =$$

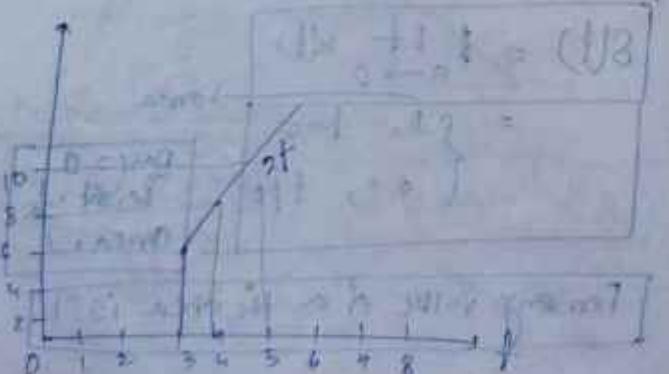

After 20 min $\rightarrow 21$ second time $\rightarrow 0.02$
but this time $0 + 10.8(0.02) = 10.8$
(because $21 \times 0.02 = 0.42$)

$$f(t) = 10e^{-t} + 5 u(t - 3) + 20 u(t - 5)$$

t_1


t_2

t_3

$$f_1(t) =$$







$$f_2(t) =$$

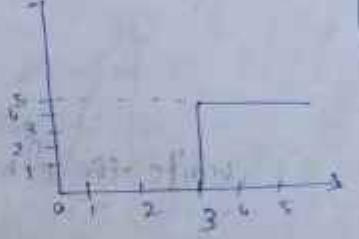

not like
this
($+0$)

$$f_3(t) =$$

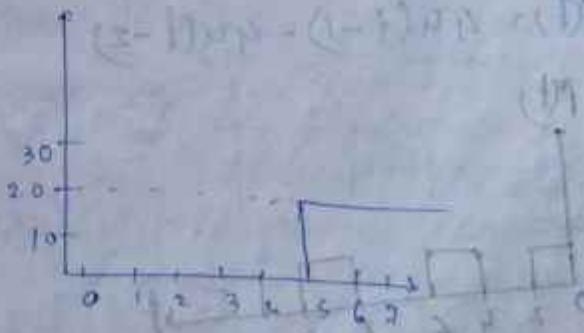

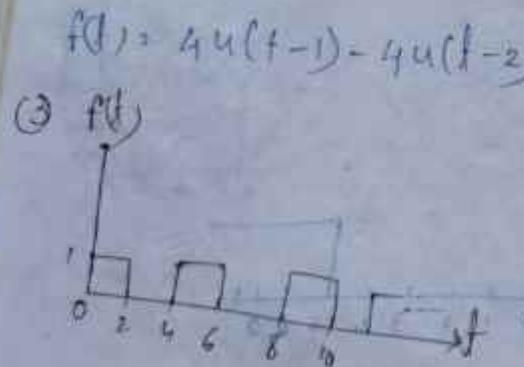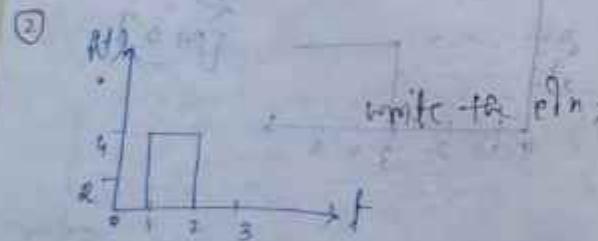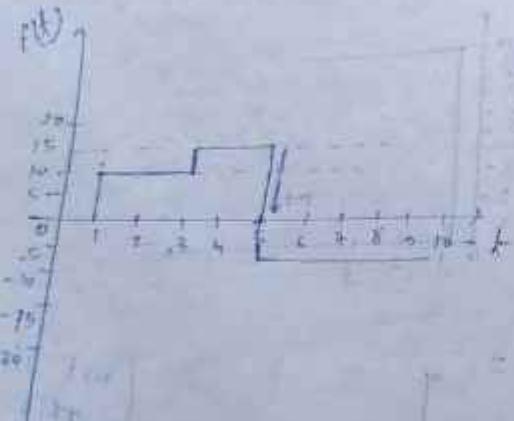


$$f(t) = u(t) - u(t-1) + u(t-2) - u(t-3)$$

$$\begin{aligned} &= u(t) + u(t-1) - u(t-2) - u(t-3) \\ &= \sum_{n=0}^{\infty} (-1)^n u(t-n) \end{aligned}$$

④
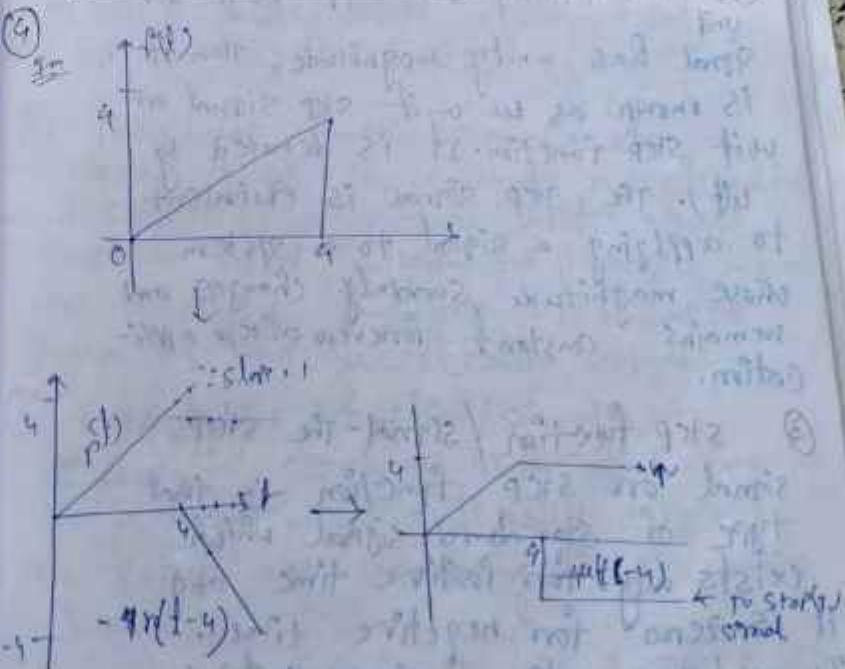
$$\begin{aligned} r(t) &= 1 \cdot u(t) \\ r(t-1) &= (t-1) \cdot u(t-1) \end{aligned}$$



$$\begin{aligned} f(t) &= r(t) - u(t-1) - 4u(t-4) + 4u(t-5) \\ &= t \cdot u(t) - u(t-1)u(t-4) - 4u(t-4) \end{aligned}$$

① signal - In electronics and telecommunications, signal refers to any time varying voltage, current or electromagnetic wave that conveys information. In signal processing, signals are analog and digital representations of analog physical quantities.

② step function / signal - If v is a step unit signal has unity magnitude, then it is known as the unit step signal or unit step function. It is denoted by $u(t)$. The step signal is equivalent to applying a signal to a system whose magnitude suddenly changes and remains constant forever after application.

③ step function / signal - The step signal or step function is that type of standard signal which exists only for positive time and is zero for negative time. In other words, a signal $v(t)$ is said to be step signal if and only if $v(t) = 0$ for $t < 0$ and $v(t) = 1$ for $t \geq 0$.

only if it exists from $t=0$ and ∞ for $t > 0$, the step signal is an important signal used for analysis of many systems.

④ Ramp function / signal - The ramp signal function is a linear among real function, whose graph is shaped like a ramp. It can be expressed by numerous definitions, for example, for negative inputs, output equals input for non-negative inputs.

⑤ Parabolic function / signal - When a signal gives the constant acceleration distinction of actual input signal, such a signal is known as parabolic signal or parabolic function. It is also known as unit acceleration signal.

⑥ Exponential function / signal - An exponential signal or exponential function is a function that literally represents an exponentially increasing or decreasing series.

⑦ Unit impulse function / signal - Continuous-time unit impulse signal. Hence, by


By definition, the unit impulse signal has zero amplitude everywhere except at $t=0$. At the origin, the amplitude of impulse signal is infinity so that the area under the curve is unity.

So there is some way to represent the impulse signal as a rectangular waveform with infinite amplitude & zero width. This is called impulse representation.

(a) Unit Impulse Response (u(t))
interval from $t=0$ to $t=2\pi/3$ having height equal to unity so amplitude is unity. So area is unity or $\int u(t) dt = 1$
So $u(t) = \frac{1}{2\pi/3} \sin(2\pi t/3)$ is the required unit impulse representation.

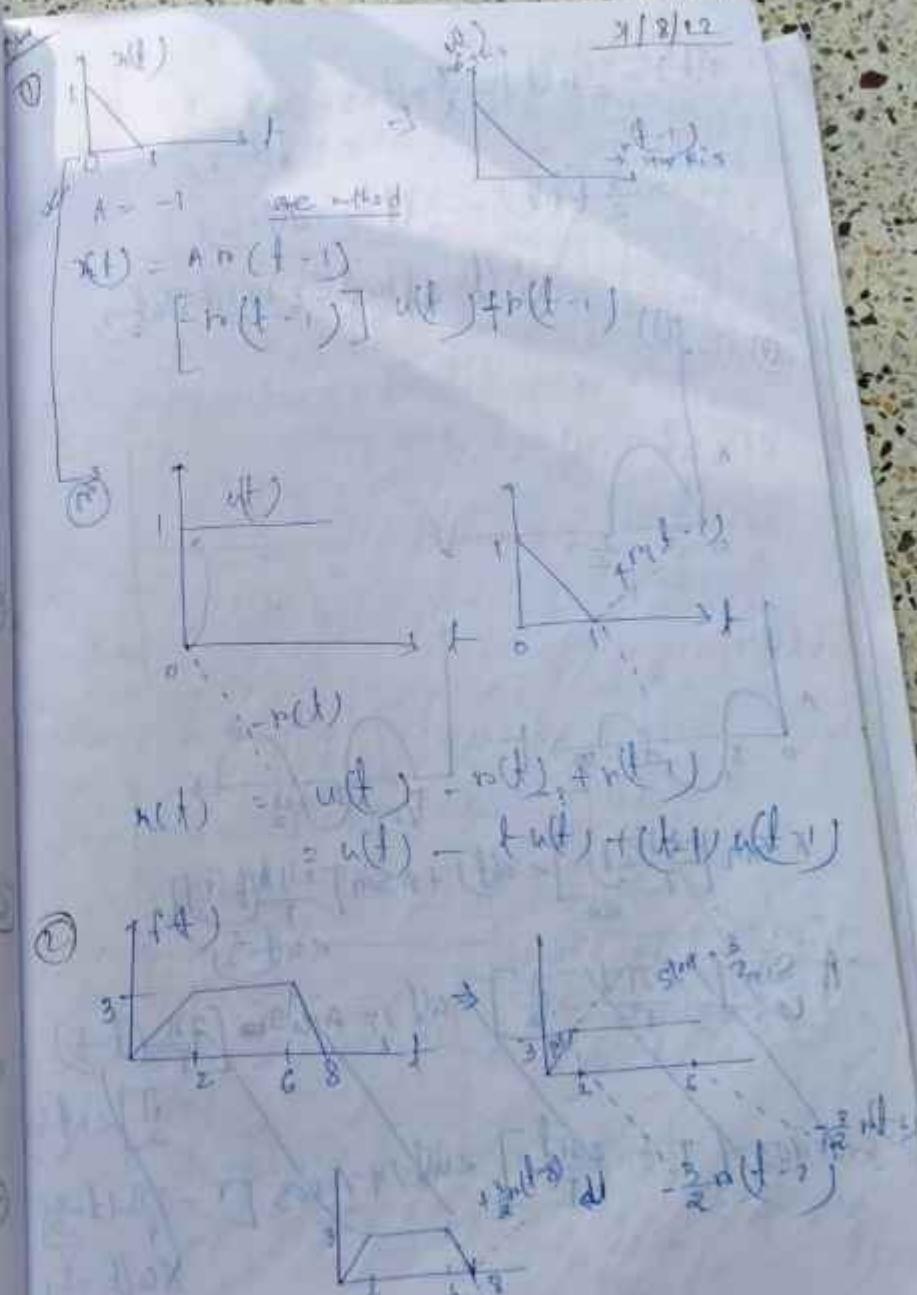(b) Ramp Unit Impulse Response
unit impulse is in basic representation shown in figure but we want to do conversion in general representation so
 $\int u(t) dt = \frac{1}{2} t^2$

Conversion - how to convert general form to standard form
for ramp signal this can be -




$$v(t) = \frac{1}{2} u(t) - \frac{1}{2} u(t-\pi) - \frac{1}{2} u(t-\pi)$$

$$= \frac{1}{2} u(t) - \frac{1}{2} (t - \pi) u(t-\pi)$$

$$- \frac{1}{2} (t - \pi) u(t-\pi) + \frac{1}{2} (8) u(t-\pi)$$

Q)

(d)

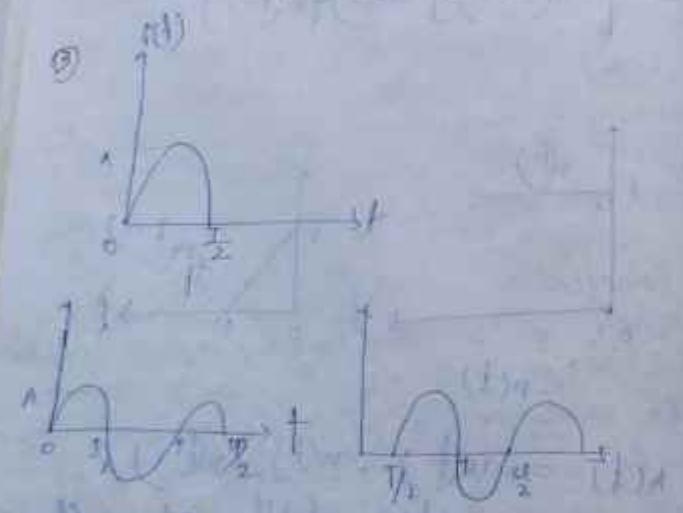

$$\left[A \sin\left(\frac{2\pi t}{T}\right) \right] - u(t) + A \sin\left[\frac{2\pi t}{T}(1-\frac{1}{2})\right]$$


$$A \sin\left[\frac{2\pi t}{T} - \frac{1}{2}\right] - u(t) + A \sin\left[\frac{2\pi t}{T}(1-\frac{1}{2})\right]$$

$$\left[\cos\left(1 - \frac{2\pi t}{T}\right) \right] - u(t) + A \cos\left[T - \frac{2\pi t}{T}(1-\frac{1}{2})\right]$$


$$= b \cos\left[\frac{2\pi}{T}(t - \frac{\pi}{2})\right] + A \cos\left[\frac{2\pi}{T}(t - \frac{\pi}{2})\right]$$

$$= b \cos\left[\frac{2\pi}{T}(t - \frac{\pi}{2})\right] \cdot u(t) + A \cos\left[\frac{2\pi}{T}(t - \frac{\pi}{2})\right]$$

Q)

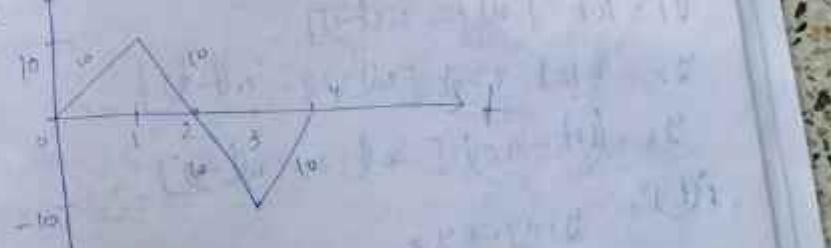


Q)

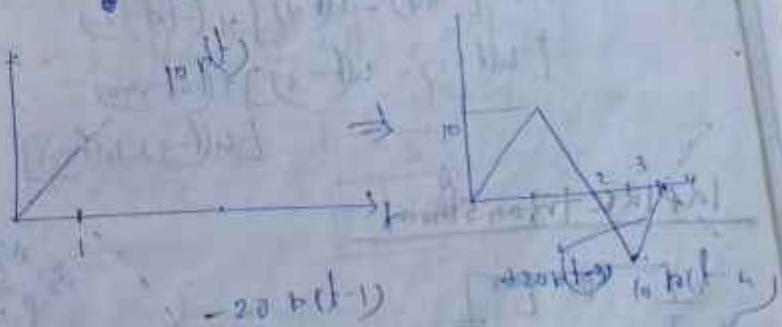

$$10 u(t) - 20 u(t-1) + 20 u(t-2) - 10 u(t-4)$$

Q:

Other method

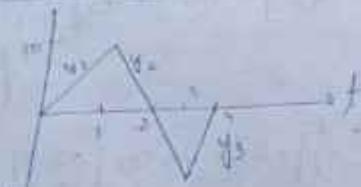

$f = \text{max}(0, (\text{start time}) - wt)$

$$y_1 = 10t [u(t) - u(t-1)]$$

$$y_2 = (10t + 10) [u(t-1) - u(t-2)]$$

$$y_3 = (10t + 40) [u(t-2) - u(t-3)]$$

$$f(t) = y_1 + y_2 + y_3$$

$$= 10t [u(t) - u(t-1)] + (10t + 10)$$

$$[u(t-1) - u(t-2)] + (10t + 40)$$

$$[u(t-2) - u(t-3)]$$

Laplace transform

$$\int_{-\infty}^{\infty} e^{-st} f(t) dt$$

using $\int_a^b f(t) dt = \frac{1}{c} \int_a^{c+b} f(t) dt$ (integral of a function)

$$= \frac{1}{c} \int_0^{\infty} f(t) dt + \frac{1}{c} \int_0^{\infty} \int_0^t f(t') dt' dt$$


(integral of a derivative)

(eg. 1)

$$L[f(t)] = F(s) = \int_{-\infty}^{\infty} f(t) e^{-st} dt$$

$\Rightarrow \int_{-\infty}^{\infty} f(t) e^{-st} dt$ if $t > 0$ is satisfied
 \Rightarrow the initial condition

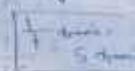Hence $s = \sigma + j\omega$, the complex frequency variable



Inverse Laplace transform

$$f^{-1}[F(s)] = \mathcal{L}^{-1}\left[\frac{e^{s_0 t}}{s - s_0}\right] = \frac{1}{2\pi j} \int_{C-j\infty}^{C+j\infty} \frac{e^{st}}{s - s_0} ds$$

Hence s_0 is a real positive value constant

$$\textcircled{1} f(t) = u(t)$$

$$\text{then, } L[f(t)] = \int_0^{\infty} u(t) e^{-st} dt$$

$$\int_0^{\infty} u(t) e^{-st} dt = \int_0^{\infty} \frac{e^{-st}}{s} dt = \left[-\frac{e^{-st}}{s} \right]_0^{\infty} = \left[+\frac{1}{s} \right]$$

$$\textcircled{2} f(t) = e^{-at}$$

$$L[f(t)] = \int_0^{\infty} e^{-at} e^{-st} dt$$

$$= \int_0^{\infty} e^{-(s+a)t} dt = \left[-\frac{1}{s+a} e^{-(s+a)t} \right]_0^{\infty} = \frac{1}{s+a}$$

$$= \frac{1}{s+a}$$

Q) sin wt

$$\int [sin wt] = \int^{\infty} sin wt e^{-st} dt$$

$$= \frac{1}{2j} \int^{\infty} (e^{(s+jw)t} - e^{(s-jw)t}) e^{-st} dt$$

$$= \frac{1}{2j} \int^{\infty} (e^{(s-jw)t} - e^{-(s-jw)t}) dt$$

$$= \frac{1}{2j} \left[\frac{e^{(s-jw)t}}{(s-jw)} \right]_0^{\infty} + \left[\frac{e^{-(s-jw)t}}{-(s-jw)} \right]_0^{\infty}$$

~~$$\frac{1}{2j} \left[\frac{1}{s-jw} \right]$$~~

$$\frac{1}{2j} \int^{\infty} [e^{-(s-jw)t} - e^{-(s+jw)t}] dt = e^{-(s+jw)t} \Big|_0^{\infty} = (D)$$

$$= \frac{1}{2j} \left\{ \left[\frac{e^{-(s-jw)t}}{-(s-jw)} \right]_0^{\infty} + \left[\frac{e^{-(s+jw)t}}{s+jw} \right]_0^{\infty} \right\}$$

$$= \frac{1}{2j} \left[\frac{1}{s-jw} - \frac{1}{s+jw} \right] = -\frac{1}{2j} = (D)$$

$$= \frac{1}{2j} \left[\frac{s+jw - s-jw}{s^2 - j^2 w^2} \right] = \frac{jw}{s^2 - j^2 w^2} = (D)$$

$$= \frac{1}{j} \cdot \frac{jw}{s^2 - j^2 w^2 (2+jw)} = \frac{jw}{s^2 + j^2 w^2 (2+jw)}$$

$$\rightarrow \frac{w}{s^2 + w^2}$$

Q) cos wt

$$\int [cos wt] = \int^{\infty} cos wt e^{-st} dt$$

$$= \frac{1}{2j} \int^{\infty} (e^{(s+jw)t} + e^{(s-jw)t}) e^{-st} dt$$

$$= \frac{1}{2} \int^{\infty} (e^{(s-jw)t} + e^{-(s-jw)t} - (s-jw)) dt$$

$$= \frac{1}{2} \int^{\infty} [e^{-(s-jw)t} + e^{-(s+jw)t}] dt$$

$$= \frac{1}{2} \left\{ \left[\frac{e^{-(s-jw)t}}{-(s-jw)} \right]_0^{\infty} + \left[\frac{e^{-(s+jw)t}}{-(s+jw)} \right]_0^{\infty} \right\}$$

$$= \frac{1}{2} \left[\frac{1}{s-jw} + \frac{1}{s+jw} \right] = (D)$$

$$= \frac{1}{2} \left(\frac{1}{s-jw} + \frac{1}{s+jw} \right) = \frac{1}{2} \frac{jw}{s^2 + w^2}$$

$$= \frac{1}{2} \left[\frac{s-jw + s+jw}{s^2 + w^2} \right] = \frac{1}{2} \frac{2s}{s^2 + w^2} = (D)$$

$$= \frac{1}{2} \frac{jw}{s^2 + w^2} = \frac{jw}{s^2 + w^2} = \boxed{\frac{jw}{s^2 + w^2}}$$

Few important properties in [derivation]
of transforms

$$\mathcal{L}\{f(t)\}$$

$$F(s)$$

$$\Rightarrow \mathcal{L}\{f(t)\}$$

$$\mathcal{L}\{f_1(t) + f_2(t)\}$$

$$\Rightarrow \frac{d}{dt} f(t)$$

$$\Rightarrow \int_0^t f(t) dt$$

$$\Rightarrow e^{-st} f(t)$$

$$\Rightarrow f(t-a) u(t-a)$$

Few transform pairs

$$\mathcal{L}\{f(t)\} \leftrightarrow F(s)$$

$$\mathcal{L}\{u(t)\}$$

$$\mathcal{L}\{t\}$$

$$\mathcal{L}\{e^{-at}\}$$

$$\mathcal{L}\{\sin wt\}$$

$$\mathcal{L}\{\cos wt\}$$

$$\mathcal{L}\{\sin^2 wt\}$$

$$\mathcal{L}\{\cos^2 wt\}$$

$\lim_{s \rightarrow \infty}$

$$\frac{1}{(s+1)^2}$$

Initial value theorem

$$\lim_{t \rightarrow 0} f(t) = \lim_{s \rightarrow \infty} sF(s) \quad [f'(0) \text{ exists}]$$

Proof

$$\mathcal{L}\left[\frac{d}{dt} f(t)\right] = sF(s) - f(0)$$

$$\Rightarrow \int_0^\infty \frac{d}{dt} f(t) e^{-st} dt = sF(s) - f(0)$$

Applying $\lim_{s \rightarrow \infty}$ on both sides, we get

$$\Rightarrow \lim_{s \rightarrow \infty} \int_0^\infty \frac{d}{dt} f(t) e^{-st} dt = \lim_{s \rightarrow \infty} [sF(s) - f(0)]$$

$$\Rightarrow \lim_{s \rightarrow \infty} \frac{d}{dt} f(t) e^{-st} dt = \lim_{s \rightarrow \infty} [sF(s) - f(0)]$$

$$\Rightarrow 0 = \lim_{s \rightarrow \infty} [sF(s)] - f(0)$$

$$\Rightarrow f(0) = \lim_{s \rightarrow \infty} sF(s)$$

$$\Rightarrow \lim_{t \rightarrow 0} f(t) = \lim_{s \rightarrow \infty} sF(s)$$

Final value theorem

$f(0)$ and $f(\infty)$ should exist

as well as $F(s)$ and $\text{Res}(s)$

$$\underset{t \rightarrow \infty}{\lim} f(t) = \underset{s \rightarrow 0}{\lim} sF(s)$$

$$L\left[\frac{d}{dt} f(t)\right] = SF(s) - f(0)$$

$$\Rightarrow \int_{0}^{\infty} \frac{d}{dt} f(t) e^{-st} dt = SF(s) - f(0)$$

Applying \int_{0}^{∞} on both sides we get

$$\Rightarrow \int_{0}^{\infty} \frac{d}{dt} f(t) e^{-st} dt = \underset{t \rightarrow 0}{\lim} [SF(s) - f(0)]$$

$$\Rightarrow \int_{0}^{\infty} (f'(t)) e^{-st} dt = \underset{s \rightarrow 0}{\lim} [SF(s) - f(0)]$$


$$\Rightarrow [f(t)]_{0}^{\infty} = \underset{s \rightarrow 0}{\lim} SF(s) - f(0)$$

$$\Rightarrow f(\infty) - f(0) = \underset{s \rightarrow 0}{\lim} SF(s) - f(0) = 0$$

$$\Rightarrow [f(t)]_{0}^{\infty} = \underset{s \rightarrow 0}{\lim} SF(s)$$

$$\Rightarrow f(\infty) = \underset{s \rightarrow 0}{\lim} SF(s)$$

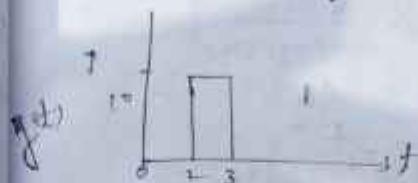① Find the Laplace transform of the given function.



$$f(t) = 10 [u(t-2) - u(t-3)]$$

Applying Laplace on both sides

$$\Rightarrow g(s) = 10 \left[e^{-2s} \cdot \frac{1}{s} - e^{-3s} \cdot \frac{1}{s} \right]$$

using this relation

$$\int [f(t-a)u(t-a)] e^{-st} dt = e^{-as} F(s)$$

$$= \frac{10}{s} [e^{-2s} - e^{-3s}]$$

$$\textcircled{2} \text{ Find } f(t) \text{ if } F(s) = \frac{6(s+2)}{(s+1)(s+3)(s+n)}$$

Let,

$$\frac{6(s+2)}{(s+1)(s+3)(s+n)} = \frac{A}{s+1} + \frac{B}{s+3} + \frac{C}{s+n}$$

$$\Rightarrow 6(s+2) = A(s+2)(s+n) + B(s+3)(s+n) + C(s+1)(s+2)$$

7/9/12

$$Kf(t) \longleftrightarrow Kf(s)$$

$$e^{-st} \longleftrightarrow \frac{1}{s}$$

$$\frac{d}{dt} f(t) \longleftrightarrow sF(s) - f(0)$$

Conversion from t domain to s domain

$$R \longleftrightarrow \frac{\frac{d^2}{dt^2}}{s^2}$$

$$V = RI$$

$$V(s) = R I(s)$$

$$I(s) \longleftrightarrow \frac{V(s)}{R}$$

$$L \longleftrightarrow \frac{dI}{dt}$$

$$V(s) = L \frac{dI(s)}{dt}$$

$$V(s) = L [sI(s) - I(0)]$$


$$V(s) = sI(s) - I(0) \quad [I_0 = I(0)]$$

$$I(s) = \frac{V(s)}{sL} + \frac{I_0}{L}$$

$$I(s) = \frac{V(s)}{sL} + \frac{I_0}{L}$$

$V_{out} = V_{in}$
Series - parallel


$$\begin{aligned} & \text{Given: } B(-1) = 0 \\ & \Rightarrow B(-2) = 0 \\ & \Rightarrow B=3 \\ & S = -1 \\ & A(1) \times (-3) = -1 \\ & \Rightarrow A = \frac{1}{-3} = -\frac{1}{3} \\ & S_2 = \frac{1}{2} \\ & C(-3)(-2) = 6 \\ & \Rightarrow C = 6 \\ & R = 4 \\ & L = 1 \\ & \therefore (S+4)(S+3) \\ & \text{On, } (S+3)(S+4) \text{ is } S = -4 \\ & \Rightarrow (S+4) = (2) = 2 \\ & (F(s))_s = \frac{3}{s+1} + \frac{4}{s+2} \quad (\text{by partial fraction}) \\ & \text{In next, } 2 \left[e^{-t} + 3e^{-2t} - 4e^{-4t} \right] \quad (\because e^{-at}) \\ & \text{Distribution: } \left[e^{-t} + 3e^{-2t} - 4e^{-4t} \right] u(t) + [\text{transient}] \\ & \text{On, } 2 \left[(e^{-t} + 3e^{-2t} - 4e^{-4t}) u(t) \right] \\ & \quad (e^{-t})(12) \end{aligned}$$

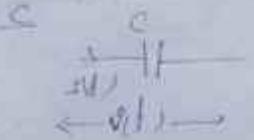


$$I(t) = C \frac{dV(t)}{dt}$$

$$I(s) = C [sV(s) - v_0]$$


$$I(s) = C s V(s) - C v_0$$

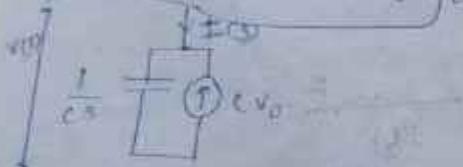

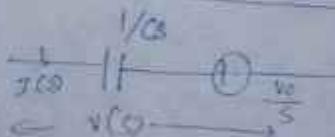
$$v(s) = \frac{I(s)}{Cs} + \frac{v_0}{s}$$



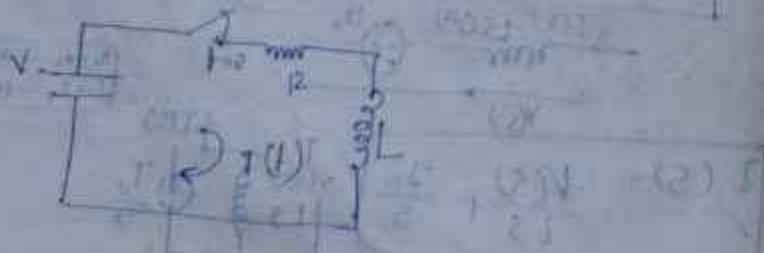① Consider the given circuit and
at $t=0$ find $i(t)$.
when switch is closed



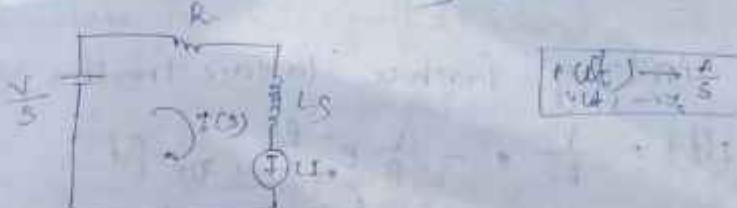transforming it's cut into (from left to right)
+ to laplace (s-domain) form



$$\frac{V}{s} = R I(s) + L I(s) - L i_0$$

$$\Rightarrow \frac{V}{s} + L i_0 = I(s) [R + L]$$

$$\begin{aligned} \Rightarrow I(s) &= \frac{V}{s(R+L)} + \frac{L i_0}{R+L} \\ &= \frac{V/L}{s(R+L)} + \frac{L i_0}{R+L} \end{aligned}$$

$$\frac{V/L}{s(R+L)} = \frac{A}{s} + \frac{B}{s+R/L}$$

$$\therefore A(s+R/L) + B s$$

$$\begin{aligned} A &= \frac{s/V_L}{s+R/L} \quad \Big|_{s=0} \quad B = \left(s + \frac{R}{L} \right) \frac{V_L}{s+R/L} \\ &= \frac{V_L}{L+R} \quad \therefore B = \frac{-V_L}{L+R} \end{aligned}$$

$$I(s) = \frac{V}{R} - \frac{V}{R(s+P)} e^{-\frac{t_0}{s+P}}$$

Applying inverse laplace transform


$$i(t) = \frac{V}{R} - \frac{V}{R} e^{-\frac{t}{\gamma}} e^{-\frac{t_0}{\gamma}}$$

[we can write $\frac{V}{R} e^{-\frac{t}{\gamma}} + V e^{-\frac{t+t_0}{\gamma}}$
Here $\gamma = \frac{L}{R}$ = time constant
of this circuit]

$$i^0, t_0 = 0$$

$$\text{then, } i(t) = \frac{V}{R} \left[1 - e^{-\frac{t}{\gamma}} \right]$$
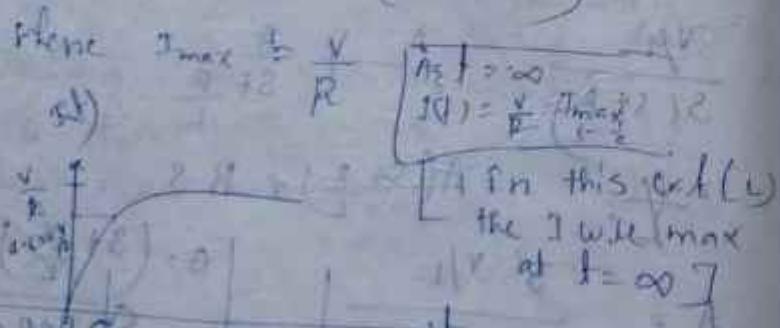
$$= i_{\max} \left(1 - e^{-\frac{t}{\gamma}} \right)$$




$$i_{\text{cd}} \cdot t_0 = 0.632 \frac{V}{R}$$


time constant or value of R

$$i_{\text{cd}} \text{ will increase } 0.632 \frac{V}{R}$$

Q2 Similar for RC circuit (Previous)
RC

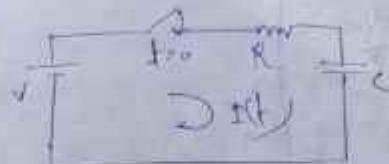

Transforming this into laplace form

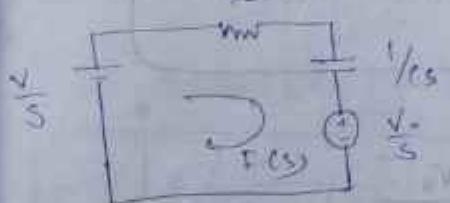

$$\frac{V}{s} = \frac{V_0}{s} - sR + I(s) \cdot \frac{1}{sC}$$

$$\Rightarrow \frac{1}{s} [V/V_0] = \frac{V}{s} - \frac{V_0}{s} = I(s) [R + \frac{1}{sC}]$$

$$\Rightarrow I(s) = \frac{V}{s(R + \frac{1}{sC})} = \frac{V_0}{s(R + \frac{1}{sC})}$$

$$\frac{V}{s(R + \frac{1}{sC})} = \frac{A}{s} + \frac{B}{s + \frac{1}{sC}} = \frac{\frac{V}{s}}{s + \frac{1}{sC}} = \frac{\frac{V}{s}}{\frac{sC + 1}{sC}} = \frac{V}{s^2 + sC + 1}$$

$$I(s) = \frac{V}{R s + \frac{1}{C}} = \frac{V}{R s + \frac{1}{C}} \cdot \frac{s + \frac{1}{L}}{s + \frac{1}{L}} = \frac{V(s + \frac{1}{L})}{(R s + \frac{1}{C})(s + \frac{1}{L})} = \frac{V(s + \frac{1}{L})}{R s^2 + R s + \frac{1}{C} s + \frac{1}{C L}}$$

Applying inverse laplace transform

$$i(t) = \frac{V}{R(s + \frac{1}{C})} - \frac{V_0}{R(s + \frac{1}{L})}$$

$$\frac{V}{R(s + \frac{1}{C})} = \frac{A}{s + \frac{1}{C}} + \frac{B}{s + \frac{1}{L}}$$

Applying inverse laplace transform


$$i(t) = \frac{V}{R} e^{-\frac{t}{C}} - \frac{V_0}{R} e^{-\frac{t}{L}} = \frac{V}{R} e^{-\frac{t}{C}} - \frac{V_0}{R} e^{-\frac{t}{L}} = \left(\frac{V-V_0}{R}\right) e^{-\frac{t}{C}}$$

we can write $\frac{V-V_0}{R} = \text{constant}$
if no initial charge, $T = \frac{L}{R}$

If $V_0 = 0$

then $i(t) = \frac{V}{R} e^{-\frac{t}{C}}$ [In this case $i(t)$ will be max when $t=0$ at $t=0$ $i(t) = V$]
i.e., if $t = \infty$, then $i(t) = T_{\max} = \frac{V}{R}$

$$i(t) = T_{\max} e^{-\frac{t}{T}}$$

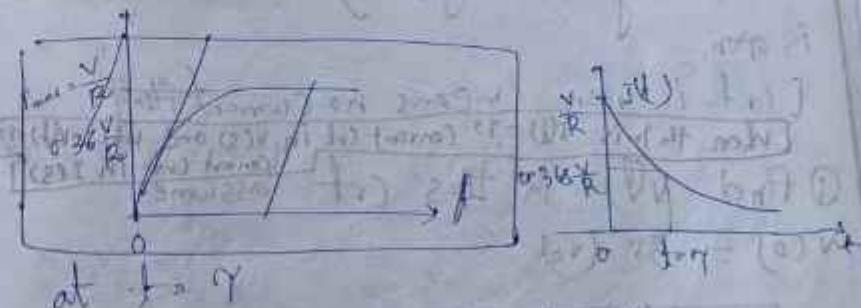

at $t = T$

$$i(t) = 0.368 \frac{V}{R}$$

i.e. at time (constant T), value will increase
decrease

$$0.368 \frac{V}{R}$$

$$L \cdot I(t) = \frac{V}{R} (1 - e^{-\frac{t}{T}})$$

$$I(t) = \frac{V}{R} e^{-\frac{t}{T}}$$

$$L \rightarrow I(0) = 0, I(\infty) = \frac{V}{R}$$

$$C \rightarrow I(0) = \frac{V}{R}, I(\infty) = 0$$

In initial the induction is open.

At infinity (steady point) the induction is short [As. $\frac{V}{R}$, there are no effects of inductance]

In capacitor the initial it is short.


At infinity (steady point) the capacitor is open.

[Ckt is open means no current flow]


When this is $I(t) = 0$ (current cut in VCS) and when $V(t) = 0$ (current cut in LGS)

① Find $V(t)$ if this ckt assume

$$I_V(0) = 0.5V \neq 0$$

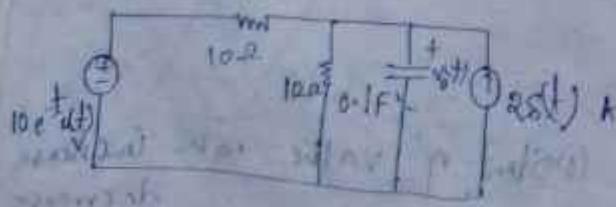

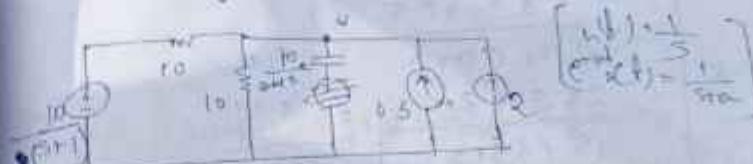transforming this into the laplace domain



VCRs

$$\frac{V}{10} + \frac{1}{10} + \frac{0.01(s+10)}{10} = 0.5 + 2$$

$$\Rightarrow V \left[\frac{1}{10} + \frac{1}{10} + \frac{1}{100} + \frac{1}{10} \right] = 2.5$$

$$\Rightarrow \frac{V}{10} \left[1 + \frac{1}{10} + 1 + \frac{1}{10} \right] = 2.5$$

$$\Rightarrow \frac{V}{10} \left[\frac{S+1+10}{S+1} + 1 + S \right] = 2.5$$

$$\Rightarrow \frac{V}{10} \left[\frac{1}{10} + \frac{1}{10} + \frac{1}{10} + \frac{1}{S+1} \right] = 2.5$$

$$\Rightarrow V \left[0.1^2 + \frac{1}{10} \right] - \frac{1}{S+1} = 2.5$$

$$\Rightarrow \frac{V}{10} (S+2) - \frac{1}{S+1} = 2.5$$

$$\Rightarrow \frac{V = 0}{S+2} - \frac{1}{S+1} = 2.5$$

$$\Rightarrow V = \left[2.5 + \frac{1}{S+1} \right] \times 10$$

$$= 2.5(S+1) + 1$$

$$\frac{(S+1)(S+2)}{(S+1)(S+2)}$$

(r)

$$V_{CS} \rightarrow V - \frac{V_0}{5}$$

10
V

$$\frac{V_0}{10} - \frac{1}{5\pi} + \frac{V_0}{10} + \frac{VS}{10} = 2.5$$

V

$$\Rightarrow \frac{2V}{10} + \frac{VS}{10} - \frac{1}{5\pi} = 2.5$$

V

$$\Rightarrow V\left(\frac{2}{10} + \frac{S}{10}\right) - \frac{1}{5\pi} = 2.5$$

V

$$\Rightarrow \frac{V}{10}(S\pi/2) - \frac{1}{5\pi} = 2.5$$

V


$$\Rightarrow \frac{V}{10} = \left[\frac{2.5 + \frac{1}{5\pi}}{S\pi/2} \right]$$

V

$$\Rightarrow \frac{V}{10} = \frac{2.5}{S\pi/2} + \frac{1}{(5\pi)(S\pi/2)}$$

$$\Rightarrow V_2 = \frac{2.5}{S\pi/2} + \frac{10}{(5\pi)(S\pi/2)}$$

when N
in ICS

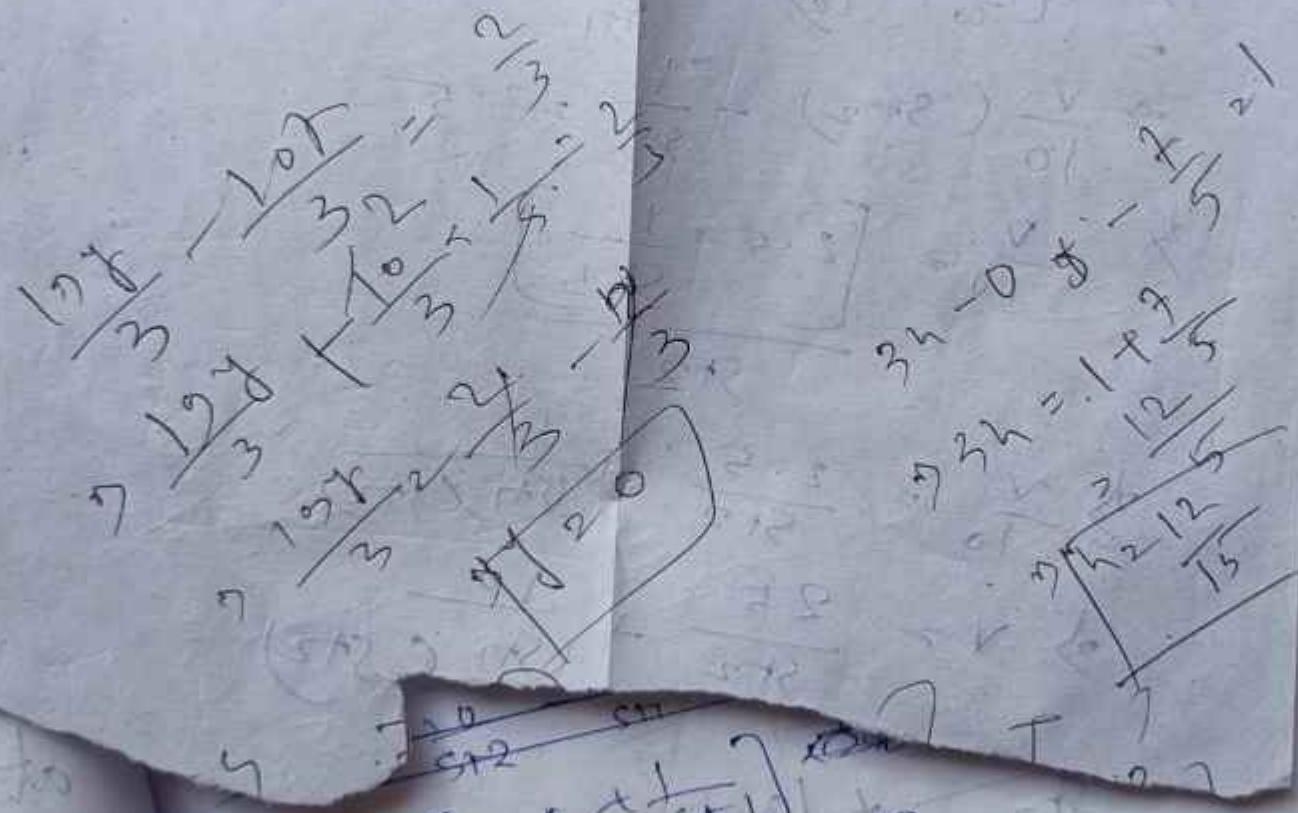

$$\Rightarrow V = \left[\frac{2.5 + 1}{2} \times 10 \right] \times 10$$
$$= \frac{2.5(5\pi) + 1}{5\pi} \times 10$$

$$V = \frac{2.5s + 2.5 + 1}{(s+1)(s+2)} = \frac{2.5s + 3.5}{s^2 + 3s + 2} = \frac{2.5(s + \frac{3.5}{2.5})}{s^2 + 3s + 2}$$

$$= \frac{2.5}{s+2} + \frac{10}{(s+1)(s+2)}$$

$$A = \frac{10}{(s+1)(s+2)} \Big|_{s=0} = \frac{10}{1 \cdot 2} = 5$$

$$B_2 = \frac{10}{(s+1)(s+2)} \Big|_{s=-2} = -10$$

Hence

$$V \text{ for } V(s) = \frac{2.5}{s+2} + \frac{10}{s+1} - \frac{10}{s+2}$$

$$\therefore \frac{15}{s+2} + \frac{10}{s+1}$$

$$V(t) = (3e^{-2t} + 10e^{-t}) u(t) - 10$$

10/12

- Q) Find the unit step response for I_2 in the given network. It is given that $I(0^-)$




Selection / main source: V_s [As we have to find the unit step response]

$$\text{From the fig: } I_s = V_s$$

Transforming the given net into laplace domain

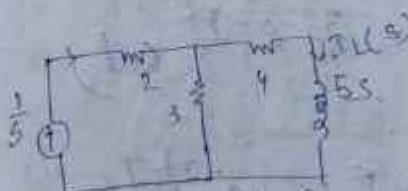[Hence point 1(b)
But initial time $\Rightarrow t=0^-$ from fig]



$$I_s(s) = \frac{1 \cdot 3}{s \cdot 3s + 5s} \quad [\text{from } 1(b)]$$

$$= \frac{1}{s} \cdot \frac{3}{3s + 5} \Rightarrow \frac{3}{s(5s + 3)}$$

$$\frac{3}{s(5s + 3)} = \frac{A}{s} + \frac{B}{5s + 3}$$

$$A = \frac{3}{s(5s + 3)} \Big|_{s=0}$$

[As in my fig
need to find unit
response for I_2 ,
so no need one
 $u(t)$ less diff]

$$\frac{3}{2} \cdot \frac{2}{2}$$

$$B_2 = \frac{3+5t+1}{8(50)} / 50 \cdot \frac{2}{5}$$

$$\frac{3+5t}{40}$$

$$\Rightarrow \frac{3}{7.5} - \frac{15}{7(50t)}$$


$$\Rightarrow \frac{3}{7.5} - \frac{15t^3}{7.5(50t^2)}$$

rounding to one place

$$I_L(t) = \frac{3}{7.5} u(t) - \frac{3}{7} e^{-\frac{7t}{5}} u(t)$$

$$= \frac{3}{7} u(t) - \frac{3}{7} e^{-\frac{7t}{5}}$$

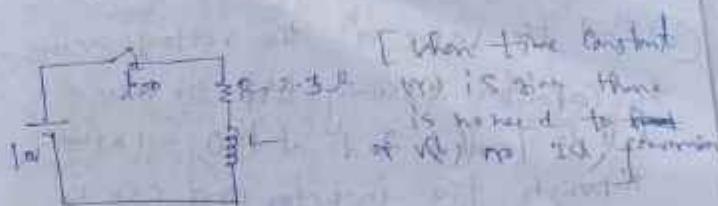- Q) A coil has a resistance of 2.5Ω and its time constant is 1.6s. Determine a) the current over 1s after 10V is applied b) the time taken for the current to attain half its final value.



$$I(t) = \frac{V}{R} (1 - e^{-\frac{t}{\tau}}) \quad [t = \frac{V}{R}]$$

$t = \frac{1}{2} \times 1.6 \text{ s}$

$$\therefore I_L(1) = \frac{10}{2.5} (1 - e^{-\frac{1}{1.6}})$$

$= 1.858 \text{ A}$ [no info about t , so assume $t = 1$]

$\approx 1.66 \text{ A}$ [measured]

by final value of current = $\frac{10}{2.5} = 4 \text{ A}$ [as final value is given]

Half of final value = 2 A

$$2 = \frac{10}{2.5} (1 - e^{-\frac{t}{1.6}})$$

$$\Rightarrow \frac{1}{2} = 1 - e^{-\frac{t}{1.6}}$$


$$\Rightarrow e^{-\frac{t}{1.6}} = 1 - \frac{1}{2} = \frac{1}{2}$$

$$\rightarrow \frac{1}{1.6} \cdot \ln\left(\frac{1}{t}\right) \quad \left[v_o = -2.5 + 1.6 \ln\left(\frac{1}{t}\right) \right]$$


$$\rightarrow t_{1.6} = 10.692 \quad \left[\frac{1}{t} = 1.6 \right]$$

$$\rightarrow t = 1.1$$

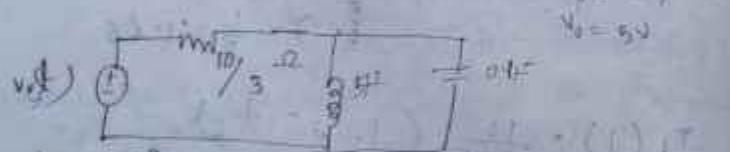③ find the value of the voltage across the capacitor assuming that the value of $v_s(t) = 10\sin(t)$ and at $t=0$, -1 flows through the inductor and $+5V$ is across the capacitor. $i_0 = -1V$



transforming the circuit by replacement

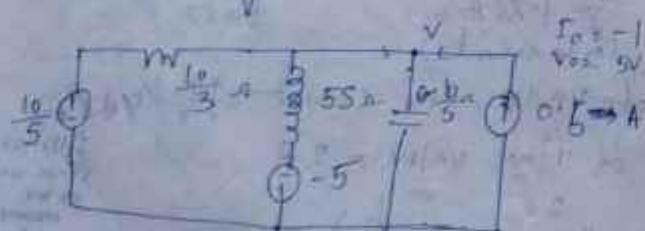

$$\frac{2}{3} + \frac{v_o}{53} + \frac{v_o}{10/3} = 0.5$$

$$\rightarrow \frac{3v_o}{10} - \frac{2}{53} + \frac{v_o}{53} + \frac{1}{10} + \frac{v_s}{10} = 0.5$$

$$\rightarrow \frac{3v}{10} - \frac{2}{53} + \frac{43}{10} - 0.5 + \frac{1}{53} + \frac{1}{10}$$

$$\rightarrow v \left[\frac{3}{10} + \frac{1}{53} + \frac{5}{10} \right] = 0.5 + \frac{1}{5}$$

$$\rightarrow \frac{v}{105} [35 + 2 + 5] = 0.5 + \frac{1}{5}$$

$$\rightarrow \frac{v}{105} (52 + 35) = 0.5 + \frac{1}{5}$$

$$\rightarrow v = \frac{55v_0}{5^2 + 35 + 2}$$

$$= \frac{55v_0}{(5+1)(5+2)}$$

$$\frac{55v_0}{(5+1)(5+2)} = \frac{A}{5+1} + \frac{B}{5+2}$$

$$A = \frac{55v_0}{(5+1)(5+2)} \quad | \quad s = -1$$

$$-5 < -1 \quad \cancel{\frac{55v_0}{5+1}} \quad | \quad s = -1$$

$$-5 < -1 \quad \cancel{\frac{55v_0}{5+2}} \quad | \quad s = -1$$

$$\frac{55v_0}{(5+1)(5+2)} = \frac{A}{5+1} + \frac{B}{5+2}$$

$$A = \frac{(55v_0) \cdot (-1)}{55 \cdot 1 \cdot (5+2)} \quad | \quad s = -1$$

$$= \frac{55v_0 \cdot (-1)}{55 \cdot 7} = -5v_0$$


$$B = \frac{(55v_0) \cdot 1}{55 \cdot 1 \cdot (5+2)} \quad | \quad s = -2$$

$$= -10 + \frac{10}{7} = -\frac{60}{7} = -8.57$$

$$\frac{43 \text{ mho}}{(s+1)(s+2)} \cdot V(s) = \frac{35}{s+1} - \frac{30}{s+2}$$

Taking inverse Laplace transform
 $V(t) = [35e^{-t} - 30e^{-2t}] \text{ volt}$

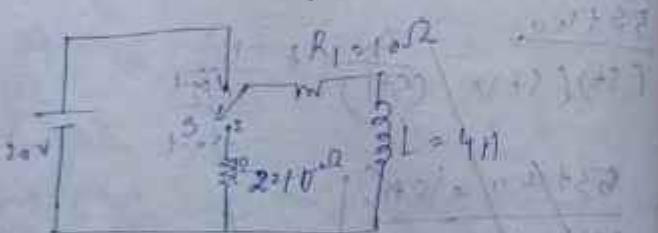- ④ This circuit in the figure is initially under steady state condition. The switch is moved from position 1 to position 2 at $t=0$. Find the current after switching.



Before switching the inductances in steady state, I_0


$$I_L(0^-) = \frac{V}{R} = \frac{20}{10} = 2 \text{ A} \quad [0 \text{ A}]$$

After switching

$$I_L(0^+) = I_0 = 2 \text{ A} \quad [\text{As the values of inductors will not change so quickly}]$$

[As before switching the value of I is initial and it is I_0]

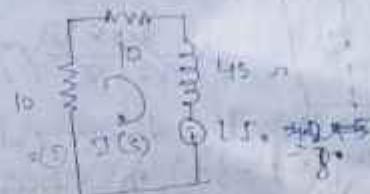
Connecting the "off" or switched off circuit to inverse domain.



$$X(s) = \frac{s}{s+3} = \frac{2}{s+5} \text{ (V/V)}$$

Taking inverse Laplace transform
 $I(t) = 2e^{-5t} \text{ A}$

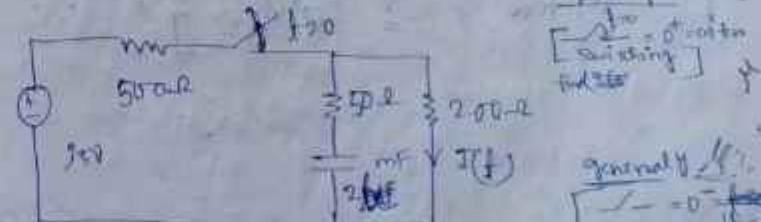- ⑤ Consider this circuit shown the switch was in closed position for a long time. It is opened at $t=0$. Find the current $I(t)$ for $t>0$ (after switching).




Before switching, $I = 0$

generally $I(t) = 0$
 $\therefore I = 0$
 Before switching
 [Switching]


Switching:
 we move the
 switch from
 one state/position to
 another state/position

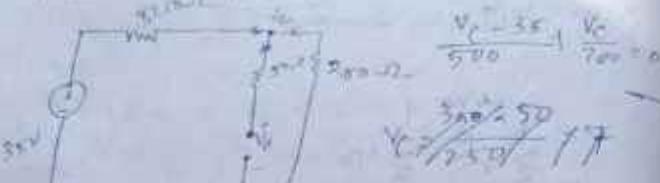A.C before switching ($t = 0^-$) there was no effect of capacitor in circuit i.e. circuit contains source + load.



[Let's find the V_o at $t = 0^-$ after cutting off the switch.]

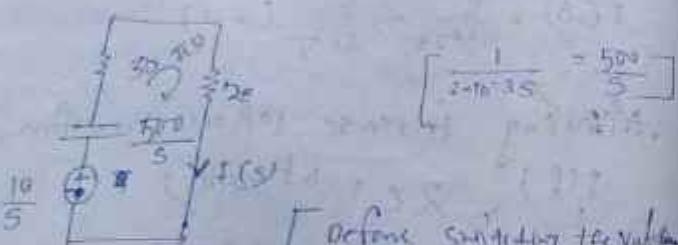After switching ($t = 0^+$), in steady state



[Define switching frequency
After switching
Initial voltage]

[Hence before switching
After]



$$\begin{aligned} & \Rightarrow \frac{V_c}{50} + \frac{V_o}{250} = \frac{35}{50} \\ & \Rightarrow \frac{1}{50} + \frac{1}{250} = \frac{35}{50} \\ & \Rightarrow \sqrt{\left[\frac{1}{50} + \frac{1}{250} \right]} = \frac{35}{50} \\ & \Rightarrow \sqrt{\left[2 - 10^{-3} + 5 \times 10^{-3} \right]} = \frac{35}{50} \\ & \Rightarrow \sqrt{\frac{35}{50}} = \frac{35}{50} \end{aligned}$$

Before switching the value of this cut is $\omega_0 = 10\text{ rad/s}$.
Initial voltage of this cut is $V_0 = 5\text{ V}$.

$$= \frac{10}{5(50, 50+250)}$$

$$= \frac{10 \times 5}{5(50+250+5)} < 10$$

$$= \frac{1}{50+250}$$

$$= \frac{1}{25(5+2)}$$

$$I(1) = 0.04 e^{-2t} \text{ A}$$

① Laplace transform - In mathematics, the Laplace transform, named after its discoverer Pierre-Simon Laplace, is an integral transform that converts a function of a real variable to a function of a complex variable s . The transformation has many applications in science and engineering because it is a tool for solving differential equations.

② Inverse Laplace transform -
The inverse Laplace transform is the transformation of a Laplace transform into a function of time. If then $f(t)$ is the inverse Laplace transform of $F(s)$, the inverse being written as:-

[13] The inverse can generally be obtained by using standard techniques.

③ Shifted function - A shift is an addition or subtraction to the x of $f(x)$ component & when you shift a function, you're basically changing the position of the graph of the function. A vertical shift raises or lowers the function as it adds or subtracts a constant to each y coordinate while the x coordinate remains the same.)

④ Initial and final value theorem - Initial and final value theorem are basic properties of Laplace transform. These theorems were given by French mathematician and physicist Pierre Simon Marquis de Laplace. Initial and final value theorem are collectively called limiting theorems.

⑤ Introduction to transient - Transient analysis calculates a circuit's response over a period of time defined by the user. The accuracy of the transient analysis is dependent on the size of internal time steps, which together make up the complete simulation time than as the run time or stop time. X

⑥ Transient disturbance or the term transient usually originates from electric circuit theory where it describes voltage and current variation from its present steady state to next steady state.

↳ In the power system, the term the transient is usually used in a different way. It denotes abrupt change in voltages and currents for short duration.

↳ Usually for duration less than the period of power system voltage and current signal (50-60 Hz).

⑦ Cause of transient disturbances
↳ switching operation, faults, and other disturbances like lightning

↳ Shutdown of heavily loaded units

↳ necessary communication of high-powered network (e.g. pf connection)

↳ short circuit fault with initial overvoltages, harmonics at 90°, 180°, 270°, 360° with 30°

⑧ How can it be measured for better power quality assessment we have to define new indices (other than conventional) based on signal processing techniques as present indices for transient disturbance analysis have limitations.

↳ Indices can be also defined on basis of time frequency analysis.

↳ Indices based on time domain analysis are crest factor, peak and rms value.

↳ Indices based on frequency domain are THD Distortion Index, r factor. These indices are defined in terms of Fourier Series Coefficient.


23/9/22

1)

two port networks

Terminal - It is a pair where a connection can neither can be fixed nor it is free. The pair of terminals where the connection between two port network is the basic building block of any electrical or electronic circuit.

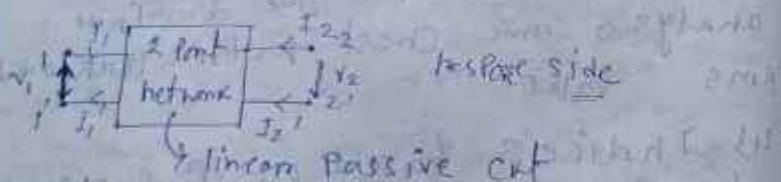Two port network - 4 terminals, 1 input, rest of them outputs.



Source /

excitation = this positions can be interchanging

Port condition is that the current entering the port i_1 is equal to the current coming out of the port i_2 .

$$\text{ie } i_1 = i_2 \quad i_1 = i_2'$$

$$V_1 \quad i_1 \quad V_2 \quad i_2$$

2-independent variables \rightarrow 2 variables
2-dependent variables \rightarrow 2 different parameters

So, that we can have 20ns.
4 variables in group of 2.
So, there are $4c_2 = 6$ possible set of

- ① Z-parameters
- ② Y-Parameters
- ③ T-parameters
- ④ A-parameters
- ⑤ Inverse T mat-parameters
- ⑥ Inverse A (or g) parameters

① Open circuit parameters or Z-parameters

Impedance parameters or open circuit impedance parameters

$$(V_1 \rightarrow V_2) = f^o(i_1, i_2)$$

The defining $V_1 = 2i_1 + 3i_2$
Ans $V_2 = 3i_1 + 2i_2$
of 2-parameters

matrix form

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2 & 3 \\ 3 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

transient condition

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} \quad [i_2 \text{ is independent}]$$

$$[Z_{11}, Z_{22} = \text{Driving point}] \quad [i_2 \text{ is taken to find}]$$

$$[Z_{11}, Z_{21} = \text{transf. fcn.}] \quad Z_{11} \text{ (dependent parameter)}$$

[i_{12} = fixed driving point] [i_1, i_2 are two port. i_{22} = output] we can get any condition

$$[Z_{12}, Z_{21} = \text{IP off} \Rightarrow \text{Reciprocity law}]$$

if $\text{IP} / \text{IP} = \text{Forward transmission}$


$$Z_{11} = \frac{v_1}{I_1} \mid I_2=0 \rightarrow \text{1/p driving point admittance}$$

$$Z_{21} = \frac{v_2}{I_1} \mid I_2=0 \rightarrow \text{Forward transfer impedance}$$

$$Z_{12} = \frac{v_1}{I_2} \mid I_1=0 \rightarrow \text{reverse transfer impedance}$$

$$Z_{22} = \frac{v_2}{I_2} \mid I_1=0 \rightarrow \text{output driving point impedance}$$

Equivalent circuit of Z-parameters

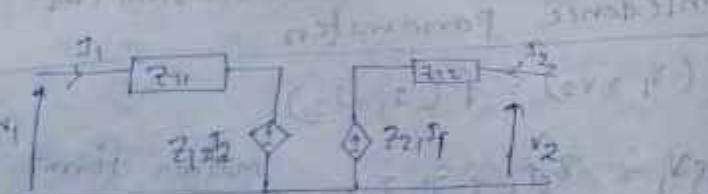

② short cut of Parameters w.r.t
Parameters on Admittance Parameters

$$(I_1, I_2), f(v_1, v_2)$$

$$I_1 = Y_{11}v_1 + Y_{12}v_2 \quad \text{matrix form}$$

$$I_2 = Y_{21}v_1 + Y_{22}v_2 \quad \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

then we can get $\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \text{matrix solution}$


$$V_1 = \frac{I_1}{Y_{11}} \mid I_2=0 \rightarrow \text{1/p driving point admittance}$$

$$Y_{21} = \frac{I_2}{Y_{11}} \mid V_1=0 \rightarrow \text{Forward transfer admittance}$$

$$Y_{12} = \frac{I_1}{Y_{22}} \mid V_1=0 \rightarrow \text{Reverse transfer admittance}$$

$$Y_{22} = \frac{I_2}{Y_{22}} \mid V_1=0 \rightarrow \text{1/p driving point admittance}$$


Equivalent circuit of y-parameters

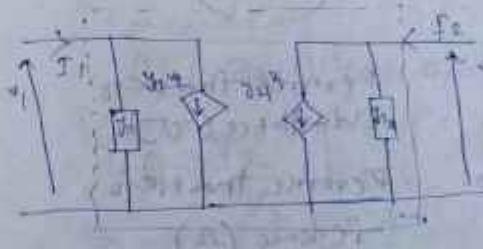

The change will be into the network the ports will be same.

$$V = I_2$$

$$\Rightarrow Z = \frac{1}{Y} V = YV$$

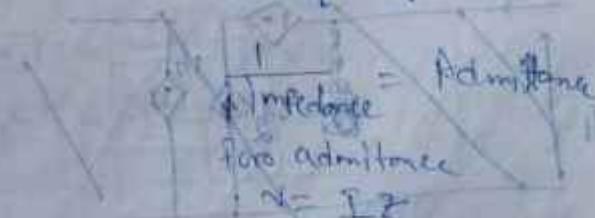

③ ABCD parameters on transmission
line parameters or T-parameters
chain parameters.

$$(V_1, I_1) = T(V_2, -I_2)$$

$$V_1 = A V_2 + B (-I_2)$$

$$I_1 = C V_2 + D (-I_2)$$

matrix form


$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \cdot \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$A = \frac{V_1}{V_2} \mid I_2=0 \quad \text{forward voltage, } \text{impedance } (Z_1)$$

$$B = \frac{I_1}{V_2} \mid I_2=0 \quad \text{reverse transfer admittance } (Y_1)$$

$$C = \frac{-V_1}{I_2} \mid V_2=0 \quad \text{reverse transfer admittance } (Y_2)$$
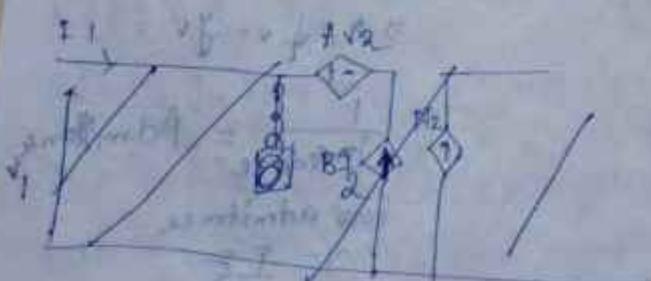
$$D = \frac{-I_1}{I_2} \mid V_2=0 \quad \text{reverse current gain } (\text{units})$$



equivalent and is not possible because
no relation between V_1, I_2

④ Hybrid parameters on h-parameters

$$(V_1, I_2) = T(V_2, -I_2) \quad \text{matrix form}$$

$$V_1 = h_{11} V_2 + h_{12} (-I_2) \quad \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$h_{11} = \frac{V_1}{V_2} \mid I_2=0 \quad \text{I/P driving point impedance } (Z_1)$$

$$h_{21} = \frac{I_2}{V_2} \mid V_2=0 \quad \text{For word transfer impedance } (Z_2)$$


$$h_{12} = \frac{V_1}{I_2} \mid I_2=0 \quad \text{reverse gain } (Y_1)$$

$$h_{22} = \frac{I_2}{V_1} \mid V_1=0 \quad \text{forward gain } (Y_2)$$

$$h_{11} = \frac{V_1}{V_2} \mid I_2=0 \quad \text{I/O P driving point admittance } (G_{11})$$

$$h_{22} = \frac{I_2}{V_1} \mid V_1=0 \quad \text{point admittance } (G_{22})$$

equivalent circuit -

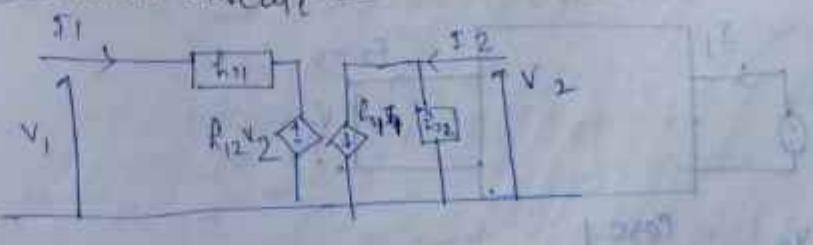



conditions for symmetry and reciprocity

A 2 port network will be called reciprocal if there is no change in response when the two ports are interchanged.

$$\frac{V_{21}}{I_1} = \frac{V_{22}}{I_2} \quad (\text{Response ratio is same, not means } x_1 = y_{21}, y_{12})$$

If the ports are interchanged, then the behavior of the network remains the same. The impedance seen by I/P side is same to the impedance seen by O/P side, that type of network is called symmetric.

Symmetry

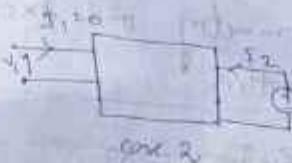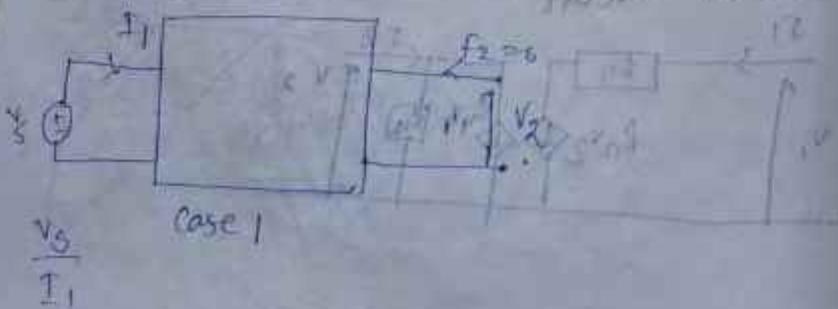

$$\frac{V_2}{I_2}$$

$$f_1^0$$

$$\frac{V_2}{I_1} = \frac{V_2}{I_2}$$

then Π is symmetric


Reciprocity



case - 3

$$\frac{V_2}{I_2}$$


$$f_1^0$$

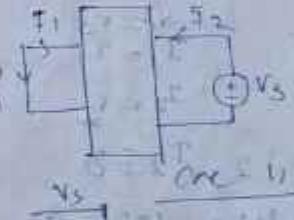

case - 4

$$\frac{V_2}{I_1} = \frac{V_2}{I_2}$$

then it is reciprocal

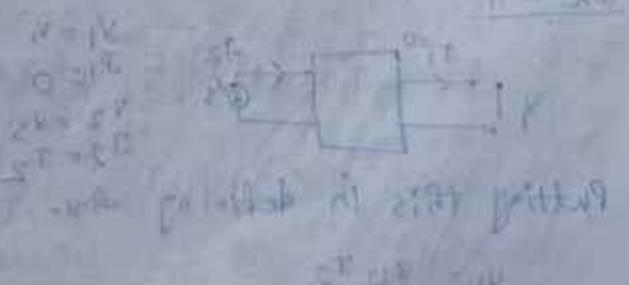

case 5 is also reciprocal

Condition for Symmetry and Incidence
for π -parameters

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \quad (A)$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \quad (B)$$

for symmetry

Case - I.



$$V_1 = V_3$$

$$I_1 = I_3$$

$$Z_2 = V_3$$

$$I_2 = 0$$

Condition




Putting this in defining terms

~~$$\frac{V_5}{I_1} = Z_{11}$$~~

$$\frac{V_5}{I_1} = Z_{11} \quad (A)$$

Case - II

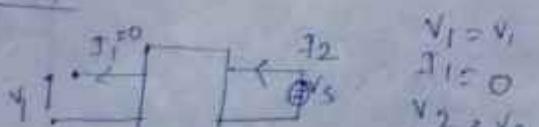

$$V_1 = V_1$$

$$I_1 = 0$$

$$V_2 = V_3$$

$$I_2 = I_2$$

Putting this in defining terms

$$V_1 = Z_{12}I_2$$

$$\begin{aligned} V_5 &= Z_{11}I_1 \\ \Rightarrow \frac{V_5}{I_1} &= Z_{11} \end{aligned} \quad (B)$$

For the network to be symmetrical

eqn (A) must be equal to eqn (B)

$$\text{i.e. } \frac{V_5}{I_1} = \frac{V_5}{I_2}$$

The condition for the π to be
symmetrical in terms of π -parameters

$$\therefore Z_{11} = Z_{22}$$

for Incidence

Case - I



$$I_1 = I_1$$

$$V_1 = V_5$$

$$I_2 = I_2$$

$$V_2 = 0$$

$$\therefore V_5 = Z_{11}I_1 + Z_{12}I_2 \quad (I)$$

$$\frac{V_5}{I_1} = Z_{11}$$

$$0 = Z_{12}I_1 + Z_{12}I_2$$

$$\therefore Z_{11} = \frac{Z_{12}I_1}{I_1} \quad (II)$$

from eqn ①

$$V_S = Z_{11} \frac{I_1 + I_2}{Z_{11}} - Z_{12} I_2$$

$$\therefore V_S = \left(Z_{11} Z_{21} - Z_{12} \right) I_2$$

$$\therefore \frac{V_S}{I_2} = \frac{Z_{11} Z_{21} - Z_{12}}{Z_{11}}$$

$$\text{cox - 11} \quad \frac{V_S}{I_2} = \frac{A_2}{Z_{11}} = \frac{A_2}{Z_{11}} \left[Z_{11} \frac{Z_{21} - Z_{12}}{Z_{11}} \right] \quad ②$$



$$I_1 = -I_1'$$

$$V_1 = 0$$

$$I_2 = I_2$$

$$V_2 = V_S$$

$$0 = Z_{11}(-I_1') + Z_{12}I_2$$

$$\therefore I_2 = \frac{Z_{11}I_1'}{Z_{12}} \quad ③$$

$$V_S = -Z_{21}I_1' + Z_{22}I_2$$

$$\therefore V_S = -Z_{21}I_1' + Z_{22}I_2 - \frac{Z_{21}Z_{11}I_1'}{Z_{12}} \quad (\text{from } ③)$$

$$\therefore V_S \cdot \left(Z_{22}Z_{11} - Z_{21}Z_{12} \right) I_1' = 0$$

$$\therefore \frac{V_S}{I_1'} \cdot \frac{A_2}{Z_{12}} = 0 \quad ④$$

for reciprocity condition
the condition is $\frac{V_S}{I_2} = \frac{V_S}{I_1}$

$$= \frac{A_2}{Z_{12}} = \frac{A_2}{Z_{21}}$$

28/9/22


Find the conditions for reciprocity and symmetry for $\frac{1}{2}$ -port networks

$$V = AV_2 + B(-I_2) \quad ①$$

$$I_1 = CV_2 + D(-I_2) \quad ②$$

Symmetry

Cox 1 -

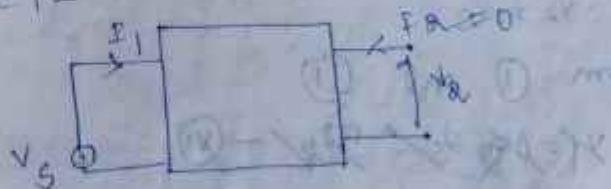

$$V_1 = V_S$$

$$I_1 = I_1$$

$$V_2 = V_2$$

$$I_2 = 0$$

$$\text{From } ① \text{ and } ② \\ I_1 = CV_2 + D \cdot 0 \quad \text{and} \quad V_2 = \frac{I_1}{Z_{21}} + ⑤$$

$$V_S = MR \quad \text{--- (IV)}$$

(V) & (VI)

$$\frac{V_S}{I_1} = \frac{Bf_2}{C}$$

$$\frac{A}{C} = \frac{B}{C} \quad \text{--- (V)}$$

Case - I



$$V_1 = V_S$$

$$I_1 = 0$$

$$I_2 = f_2$$

$$V_2 = V_S$$

from (I) and (II)

$$Y_1 = A \quad V_S \rightarrow Bf_2 - (I_1) \quad 0 \quad V$$

$$0 = (V_S - Df_2)$$

$$\Rightarrow CV_S = DF_2$$

$$\Rightarrow \frac{V_S}{I_2} = \frac{D}{C}$$

$$\text{--- (VI)}$$

$$\text{--- (VII)}$$

The condition is

$$\frac{V_S}{I_1} = \frac{V_S}{I_2}$$

$$\Rightarrow \boxed{\frac{A}{C} = \frac{B}{C}} \Rightarrow \boxed{A=B}$$

for nullarity

Case - I



$$I_1 = I_2$$

$$V_1 = V_S$$

$$I_2 = f_2$$


$$V_2 = 0$$

from (I) and (II)

$$V_S = Bf_2$$

$$\Rightarrow \frac{V_S}{I_2} = B$$

Case - II

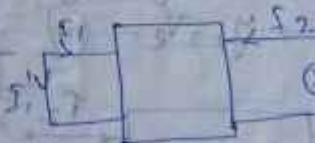

$$V_2 = V_S$$

$$I_2 = f_2$$

$$I_1 = -I_2$$

$$V_1 = 0$$

from (I) and (II)

$$0 = AV_S - BF_2$$

$$\Rightarrow I_2 = \frac{AV_S}{B}$$

$$-I_1 = CV_S + DF_2$$

$$\Rightarrow -I_1 = CV_S - \frac{DAV_S}{B}$$

$$\begin{aligned} & \Rightarrow v_s \left(c - \frac{AD}{B} \right) = -i_1 \\ & \Rightarrow v_s \left(\frac{B_1 - AD}{B} \right) = -i_1 \\ & \Rightarrow v_s \left(\frac{(AD - B_1)}{B} \right) = i_1 \quad | \quad \boxed{A = 3} \\ & \Rightarrow \frac{v_s}{i_1} = \frac{B}{AD - B_1} \end{aligned}$$

the condition is


$$\begin{aligned} \frac{v_s}{i_1} &= \frac{v_s}{i_2} \\ \frac{B}{AD - B_1} &= B \\ \Rightarrow \frac{1}{AD - B_1} &= 1 \quad | \quad \boxed{\text{AD} - B_1 = 1} \end{aligned}$$

find the conditions for reciprocity
and symmetry for y -parameters

$$I_1 = j_{11}v_1 + j_{12}v_2 \quad | \quad \boxed{1}$$

$$I_2 = j_{21}v_1 + j_{22}v_2 \quad | \quad \boxed{2}$$

Symmetry

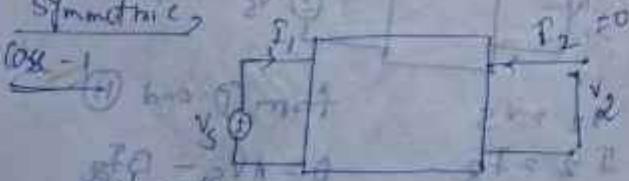

$$\begin{aligned} v_1 &= v_s \\ i_1 &= I_{12} \\ i_2 &= 0 \\ v_2 &= v_s \\ i_2 &= I_2 \end{aligned}$$

from ①,

$$0 = y_{11}v_1 + y_{12}v_2 \quad | \quad \boxed{3}$$

$$\Rightarrow y_{12}v_2 = -y_{11}v_1 \quad | \quad \boxed{4}$$

$$\Rightarrow v_2 = -\frac{y_{11}}{y_{12}}v_1 \quad | \quad \boxed{5}$$

from ②,


$$I_1 = y_{11}v_1 - \frac{y_{12}v_2}{y_{12}} v_s \quad | \quad \boxed{6}$$

$$\Rightarrow I_1 = v_s \left(\frac{y_{11}y_{12} - y_{12}^2}{y_{12}} \right)$$

$$\Rightarrow \frac{v_s}{I_1} = \frac{y_{12}}{y_{12}y_{11} - y_{11}y_{12}}$$

$$= \frac{y_{12}}{y_{12} - y_{11}} \quad | \quad \text{where } \Delta y = \begin{vmatrix} y_{11} & y_{12} \\ y_{12} & y_{11} \end{vmatrix}$$

Case - II

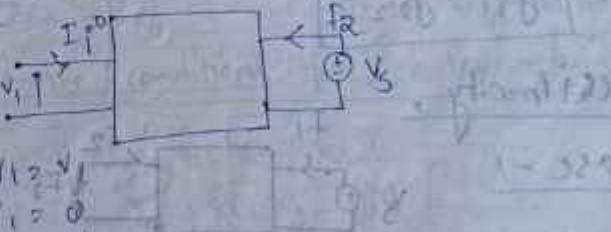

$$\begin{aligned} v_1 &= v_s \\ i_1 &= 0 \\ v_2 &= v_s \\ i_2 &= I_2 \end{aligned}$$

from ①,

$$0 = y_{11}v_1 + y_{12}v_s \quad | \quad \boxed{6}$$

$$\Rightarrow y_{11}v_1 = -y_{12}v_s \quad | \quad \boxed{7}$$

$$\Rightarrow v_1 = -\frac{y_{12}}{y_{11}}v_s \quad | \quad \boxed{8}$$

from (1)

$$J_2 = -\frac{y_{11} + y_{12}}{y_{11}} V_S + y_{12} V_S$$

$$\Rightarrow J_2 = V_S \left(y_{11} - \frac{y_{11} + y_{12}}{y_{11}} \right) \quad (2)$$

$$\Rightarrow J_2 = V_S \left(\frac{y_{11} y_{12} - y_{11}^2}{y_{11}} \right) \quad (2)$$

$$\Rightarrow \frac{V_S}{J_2} = \frac{y_{11}}{y_{11} + y_{12}} = \boxed{\text{where } y_{11} = \frac{y_{11} y_{12}}{y_{12} + y_{11}}} \quad (3)$$

The condition is


$$\frac{V_S}{J_1} = \frac{V_S}{J_2}$$

$$\Rightarrow \frac{y_{11}}{y_{11} + y_{12}} = \frac{y_{11} + y_{12}}{y_{12}}$$

$$\Rightarrow \boxed{y_{11} = y_{12}}$$

Reciprocity,

case - I

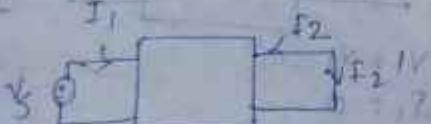

$$V_1 = V_S$$

$$J_1 = I_1$$

$$J_2 = -I_2$$

$$V_2 = 0$$

$$\text{from (1), } -I_2 J_2 - y_{21} V_S = 0$$

$$\Rightarrow \frac{V_S}{I_2} = -\frac{1}{y_{21}} \quad \boxed{(1)}$$

CASE - II



$$J_1 = -I_1$$

$$V_1 = 0$$

$$J_2 = I_2$$

$$V_2 = V_S$$

from (1),

$$-I_1 = y_{12} V_S \quad (2)$$

$$\Rightarrow \frac{V_S}{I_1} = -\frac{1}{y_{12}} \quad \boxed{(2)}$$

The condition is

$$\frac{V_S}{I_1} = \frac{V_S}{I_2}$$

$$\Rightarrow -\frac{1}{y_{12}} = -\frac{1}{y_{12}}$$

$$\Rightarrow \boxed{y_{12} = y_{21}}$$


symmetry and reciprocity
find the conditions for R-parameters

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad (1)$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad (1)$$

for symmetry,

case - I

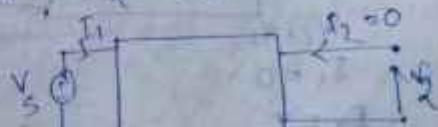

$$v_1 = v_s$$

$$I_1 = I_1$$

$$I_2 > 0$$

$$v_2 < v_s$$

from (1),

$$0 = h_{11} I_1 + h_{21} I_2$$

$$\rightarrow h_{11} v_2 - h_{21} I_1$$

$$\rightarrow v_2 = -\frac{h_{21}}{h_{11}} I_1 \quad (1)$$

$$v_s = h_{11} I_1 - \frac{h_{11} h_{21}}{h_{22}} v_2 \quad (2)$$

$$\rightarrow v_s + \frac{h_{11} h_{21}}{h_{22}} v_s + h_{22} I_1 \quad \rightarrow v_s \left(1 + \frac{h_{11} h_{21}}{h_{22}} \right) = h_{22} I_1$$

$$\rightarrow v_s \left(\frac{h_{11} h_{21}}{h_{22}} \right) = h_{22} I_1$$

$$\rightarrow \frac{v_s}{I_1} = \frac{h_{22}}{h_{11} h_{21}} \quad (3)$$



$$V_1 = V_s$$

$$I_1 = 0$$

$$I_2 = I_2$$

$$V_2 = V_s$$

from (1)

$$I_2 = h_{22} I_1$$

$$\rightarrow \frac{v_s}{I_1} = \frac{1}{h_{22}} \rightarrow (B)$$

the condition is

$$\frac{v_s}{I_1} = \frac{v_s}{I_2}$$

$$\begin{cases} h_{11} h_{21} \\ h_{22} / h_{11} h_{21} \end{cases} \Rightarrow \frac{\Delta h}{h_{22}} = \frac{1}{h_{22}} \Rightarrow \boxed{\Delta h = 1}$$

for oscillation,

Case - I



$$V_1 = V_s$$

$$I_1 = I_1$$

$$I_2 = -I_1$$

$$V_2 = 0$$

$$\text{from (1)} \quad I_2 = h_{22} I_1$$

$$\rightarrow I_1 = -\frac{I_2}{h_{22}} \quad (V)$$

$$\text{from (2)} \quad V_s = -\frac{h_{11}}{h_{22}} I_2 \quad \text{[from (V)]}$$

$$\rightarrow \frac{V_s}{I_2} = -\frac{h_{11}}{h_{22}} \quad (A)$$

Box - 1



$$I_1 = -I_2$$

$$V_1 = 0$$

$$I_2 = I_1$$

$$V_2 = V_s$$

from Q,

$$0 = h_{11} I_1 + h_{12} V_s$$

$$\Rightarrow h_{12} V_s = h_{11} I_1$$

$$\therefore \frac{V_s}{I_1} = \frac{h_{11}}{h_{12}} \quad \text{--- (1)}$$

The condition is

$$\frac{V_s}{I_1} = \frac{V_s}{I_2}$$

$$\therefore \frac{h_{11}}{h_{12}} = -\frac{h_{11}}{h_{12}}$$

$$\therefore h_{12} = -h_{11}, \quad \text{--- (2)}$$

④ **h-parameters** - Hybrid parameters are known as 'hybrid' P, as they use **Z_{in}**, **V_{out}**, **voltage ratio**, and **current ratios** to represent the relationship between **voltage** and **current** in a two port network.

① **terminal** - In electronics or electrical it is a coil where a connection can be given. A two-port network (a kind of four-terminal network or quadrupole) is an electrical network (circuit) or device with two pairs of terminals to connect to external circuits.

② **Port** - In electrical circuit theory, a port is a pair of terminals connecting an electrical network or circuit to an external circuit, as a point of entry or exit for electrical energy.

③ **Z-parameters** - one they are also known as open-circuit impedance parameters as they are calculated under open circuit conditions. i.e. $I_x = 0$, where $x=1, 2$ refers to input and output currents flowing through the ports (of a two port network in this case) respectively.

④ **Y-parameters** - 4 parameters of two port network is a 2×2 admittance matrix. Since admittance is the ratio of circuit current and voltage, therefore this admittance matrix gives the relationship between the input and output current and voltage of the network. It is also known as short circuit admittance parameters.

⑤ **T-parameters** - They are called inverse transmission parameters or **A B C D** parameters. The parameters **A** and **D** do not have any units, since those are dimension less.

The result of summation is 0 and it shows that
the relationship between the parallel
metres.

2 in terms of T

$$V_1 = A, I_1 + B, I_2 - \textcircled{1}$$

$$V_2 = C, I_2 - D, I_1 - \textcircled{2}$$

$$V_1 = AV_2 + BC - I_2 - \textcircled{3}$$

$$I_1 = C, I_2 - D, I_1 - \textcircled{4}$$

$$\text{2 in terms of } T = Z = f(A, B, C)$$

from $\textcircled{4}$

$$T_1 = CV_2 - DI_2$$

$$\Rightarrow I_1 + DT_2 = C, V_2$$

$$\Rightarrow Y_2 + \frac{1}{C} (I_1 + DT_2) \rightarrow \textcircled{5}$$

from $\textcircled{3}$

$$V_1 = AV_2 + B, I_2$$

$$\Rightarrow Y_1 = \frac{A}{C} (I_1 + DI_2) - B, I_2 \quad [\text{from } \textcircled{4}]$$

$$\Rightarrow Y_1 = \frac{A}{C} I_1 + \frac{AD}{C} I_2 - B, I_2$$

$$\Rightarrow Y_1 = \frac{A}{C} I_1 + \left(\frac{AD}{C} - B \right) I_2 - \textcircled{6}$$

Comparing $\textcircled{5}$ and $\textcircled{6}$ we get,

$$\boxed{Y_{12} = \frac{AD}{C} - B, \quad \frac{AD - BC}{C} = \frac{AT}{C}}$$

from $\textcircled{1}$

$$I_1 = CV_2 - DI_2$$

$$\Rightarrow -CV_2 = I_1 - DI_2$$

$$\Rightarrow CV_2 = I_1 + DI_2$$

$$\Rightarrow V_2 + \frac{1}{C} I_1 + \frac{D}{C} I_2 - \textcircled{7}$$

Comparing $\textcircled{7}$ and $\textcircled{2}$ we get

$$\boxed{Z_{21} = \frac{1}{C}, \quad Z_{22} = \frac{D}{C}}$$

3 in terms of Y

$$V_1 = h_{11} Y_1 + h_{12} Y_2 - \textcircled{8}$$

$$I_2 = h_{21} Y_1 + h_{22} Y_2 - \textcircled{9}$$

$$I_1 = Y_1, V_1 + Y_2, V_2 - \textcircled{10}$$

$$Y_2 = Y_1, V_1 + Y_2, V_2 - \textcircled{11}$$

from $\textcircled{8}$

$$I_1 \rightarrow \textcircled{10} \quad V_1 + Y_2, V_2$$

$$\Rightarrow -Y_{11} V_1 = -I_1 + Y_{12} V_2$$

$$\Rightarrow Y_{11} Y_1 = I_1 - Y_{12} V_2$$

$$\Rightarrow Y_{12} = \frac{1}{Y_{11}} I_1 - \frac{Y_{12}}{Y_{11}} V_2 - \textcircled{12}$$

Comparing $\textcircled{12}$ and $\textcircled{9}$ we get,

$$\boxed{h_{11} = \frac{1}{Y_{11}}, \quad h_{12} = -\frac{Y_{12}}{Y_{11}}}$$

Comparing (i) and (ii)

$$h_{11} = y_{11}$$

$$h_{12} = y_{12}$$

Ans (iii)

$$x_1 = y_{11} v_1 + y_{12} v_2$$

$$\Rightarrow x_1 - y_{12} v_2 = y_{11} v_1$$

$$\Rightarrow v_1 = \frac{1}{y_{11}} (x_1 - y_{12} v_2) \quad \text{(iv)}$$

Put (iv) in (i)

$$x_2 = y_{21} \frac{1}{y_{11}} (x_1 - y_{12} v_2) + y_{22} v_2$$

$$\Rightarrow \frac{y_{21} x_1}{y_{11}} - \frac{y_{21} y_{12} v_2}{y_{11}} + y_{22} v_2$$

$$= \frac{y_{21} x_1}{y_{11}} + \left(y_{22} - \frac{y_{21} y_{12}}{y_{11}} \right) v_2$$

$$\Rightarrow x_2 = \frac{y_{21}}{y_{11}} x_1 + \left(\frac{y_{21} y_{12} - y_{22} y_{11}}{y_{11}} \right) v_2 \quad \text{(v)}$$

Comparing (v) and (i) we get

$$h_{21} = \frac{y_{21}}{y_{11}}$$

$$h_{22} = \frac{y_{21} y_{12} - y_{22} y_{11}}{y_{11}}$$

$$\text{or } = \frac{h_{12} v_2}{y_{11}}$$


$$\frac{h_{12} v_2}{y_{11}}$$

$$[\text{from eqn } (i)]$$



T	A	B	C	D
T	$\frac{\partial f_{11}}{\partial x}$	$\frac{\partial f_{12}}{\partial x}$	$\frac{\partial f_{11}}{\partial y}$	$\frac{\partial f_{12}}{\partial y}$
A	$\frac{\partial f_{11}}{\partial x}$	$\frac{\partial f_{12}}{\partial x}$	$\frac{\partial f_{11}}{\partial y}$	$\frac{\partial f_{12}}{\partial y}$
B	$\frac{\partial f_{21}}{\partial x}$	$\frac{\partial f_{22}}{\partial x}$	$\frac{\partial f_{21}}{\partial y}$	$\frac{\partial f_{22}}{\partial y}$
C	$\frac{\partial f_{21}}{\partial x}$	$\frac{\partial f_{22}}{\partial x}$	$\frac{\partial f_{21}}{\partial y}$	$\frac{\partial f_{22}}{\partial y}$
D	$\frac{\partial f_{21}}{\partial x}$	$\frac{\partial f_{22}}{\partial x}$	$\frac{\partial f_{21}}{\partial y}$	$\frac{\partial f_{22}}{\partial y}$

12/10/22

① Find Z parameters

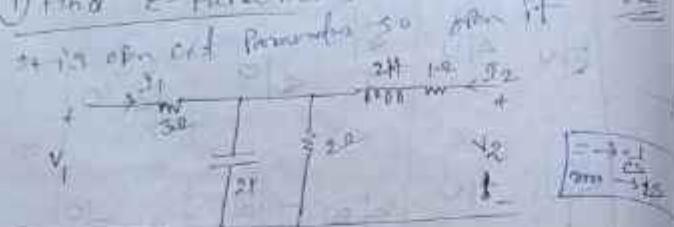

Transform into S domain

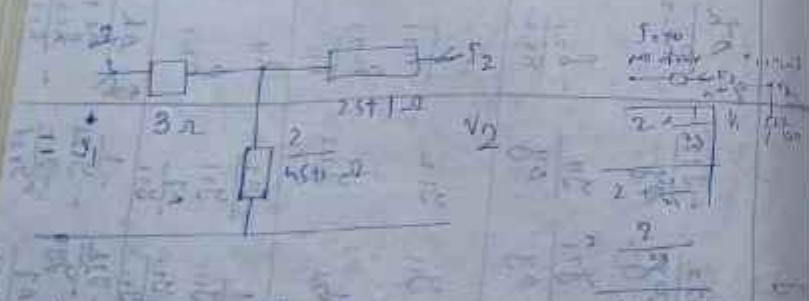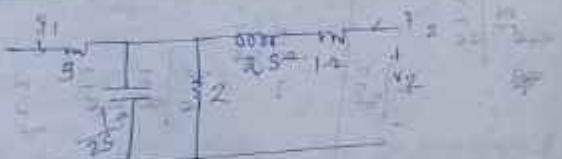

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}, \quad Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}, \quad Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

Circ 1

$$I_2=0$$



$$V_1 = 3 + \left(\frac{2}{4s+1} \right) V_2$$

$$\Rightarrow \frac{V_1}{V_2} = 3 + \frac{2}{4s+1}$$

$$\Rightarrow \frac{Z_{11}}{Z_{22}} = \frac{12s+5}{4s+1}$$

$$\Rightarrow Z_{11} = \frac{12s+5}{4s+1}$$

$$V_2 = \frac{2}{4s+1} I_1$$

$$\Rightarrow \frac{V_2}{I_1} = \frac{2}{4s+1} \cdot 4s+1 = 2$$

$$\Rightarrow Z_{22} = \frac{2}{4s+1}$$

Circ 2:

$$I_1=0$$



$$\frac{V_1}{I_2} = \frac{2}{4s+1}$$


$$\Rightarrow Z_{21} = \frac{2}{4s+1}$$

$$\begin{array}{r} \text{Nodal Analysis} \\ \text{Step 1: Node 1} \\ \text{Step 2: Node 2} \\ \text{Step 3: Node 3} \end{array}$$

$$\begin{aligned} &= \frac{3+4s}{4s+1} - 1/s \\ &= \frac{3+4s + s^2 + 2s^2 + 2s}{4s+1} \\ &= \frac{8s^2 + 6s + 3}{4s+1} \end{aligned}$$

$$Z_{eq} = \frac{8s^2 + 6s + 3}{4s+1}$$

② Find γ -parameters

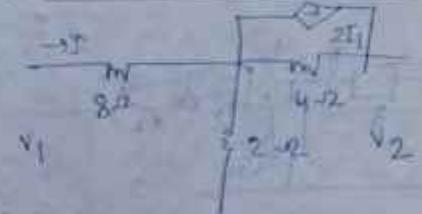

Source transformation



$$\begin{aligned} V_1 &= I_1 + V_1 + V_2 + V_2 \\ V_2 &= V_1, V_1 = V_2 \end{aligned}$$

It is short-circuit parameter or adm.

Case 1: $V_2 = 0$



$$\begin{aligned} V_1 &= 8I_1 + 2(I_1 + I_2) \\ V_1 &= 10I_1 + 2I_2 \quad \text{--- (1)} \end{aligned}$$

$$\begin{aligned} V_1 &= 8I_1 + 4I_2 - 8I_1 \\ V_1 &= -4I_2 \end{aligned}$$

$$\Rightarrow \frac{I_2}{V_1} = 8 + \frac{1}{2}$$

$$3 + I_2 = -\frac{V_1}{4} \quad \text{--- (2)}$$

from (1),


$$I_1 = 2V_1 \quad V_1 = 10I_1 - \frac{V_1}{2}$$

$$3 + I_2 = -\frac{V_1}{4} \quad \Rightarrow \frac{3}{2}I_1 = 10I_1 - \frac{V_1}{2}$$

$$I_1 = \frac{V_1}{20} \quad \Rightarrow \frac{3}{2} \cdot \frac{V_1}{20} = 10V_1 - \frac{V_1}{2}$$

$$(12V_1) \Rightarrow V_1 = \frac{3}{20}$$

Ans 2
 $v_1 = 0$

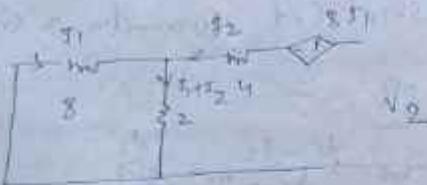

$$v_2 = 4i_2 + 2(i_1 + i_2)$$

$$\therefore 4i_2 + 2i_1 \quad \text{---} \quad \textcircled{1}$$

$$v_2 = 8i_1 + 8i_2 + 2(i_1 + i_2)$$

$$8i_1 + 8i_2 + 6i_2 + 2i_1 \quad \text{---} \quad \textcircled{1}$$

$$v_2 = 8i_1 + 4i_2 + -8i_1 \quad 0 \rightarrow 0$$

$$8i_1 + 4i_2 + -8i_1 \quad \text{---} \quad \textcircled{2}$$

$$\therefore 4v_2 = 8i_1 + 4i_2 + -8i_1$$

$$4i_2 = v_2 + 8i_1$$

$$i_2 = \frac{1}{4}(v_2 + 8i_1)$$

From $\textcircled{1}$

$$v_2 = 8i_1 + 6i_2$$

$$v_2 = 8i_1 + 4i_2 + 2i_2$$

$$v_2 = 8i_1 + 4i_2$$

$$\frac{v_2}{i_2} = 15 \quad i_2 = \frac{v_2}{15} \quad \boxed{\frac{i_2}{v_2} = \frac{1}{15}}$$

$$\text{From } \textcircled{1}, \quad v_2 = 10i_1 + 6 \frac{v_2}{15}$$

$$\Rightarrow v_2 = 3i_1 + 10i_1$$

$$\Rightarrow i_1 = \frac{v_2}{18} = 10i_1$$

$$\Rightarrow \frac{v_2}{18} = 10i_1$$

$$\Rightarrow \frac{v_2}{18} = 10i_1$$

$$\Rightarrow \frac{v_2}{18} = 10i_1$$

$$\Rightarrow i_1 = \frac{v_2}{180}$$

$$\Rightarrow i_1 = \frac{v_2}{180}$$

from (9)

$$v_1 = 2s_1 + 2s_3 + 2s_1 - v_1 \\ \rightarrow s_3 = \frac{1}{2}(2s_1 - v_1) \quad \textcircled{1}$$

Putting in (6),

$$2 = -3v_1 + 2s_1 - \frac{3}{2}(2s_1 - v_1)$$

$$\rightarrow 2 = -3v_1 + 2s_1 - 3s_1 + \frac{3}{2}v_1$$

$$\rightarrow 2 = -3v_1 + \frac{3v_1}{2} - s_1$$

$$\rightarrow s_1 = \frac{3v_1}{2} - 2$$

$$\rightarrow s_1 = -\frac{3v_1}{2} - 2 \quad \textcircled{2}$$

Comparing \textcircled{1} with \textcircled{2}

$$\left\{ \begin{array}{l} Y_{11} = -\frac{3}{2}, \quad Y_{12} = -1 \end{array} \right.$$

from \textcircled{2},

$$v_2 = -3s_1 + 2s_1 - 2s_3 - s_2 \\ \rightarrow -3s_1 + (s_1 - 2s_3) - \frac{1}{2}(2s_1 - v_1) \quad (\text{from } \textcircled{1}) \\ \rightarrow -3s_1 + s_1 - s_3 + \frac{v_1}{2} \quad (\text{from } \textcircled{2}) \\ \rightarrow -2s_1 - s_3 + \frac{v_1}{2} \quad (\text{from } \textcircled{3}) \\ \rightarrow 2s_1 + \frac{v_1}{2} - s_3 \quad \textcircled{4}$$

\textcircled{1} - 2\textcircled{4}

$$v_1 - 2s_1 = 2s_1 + s_2$$

$$\rightarrow -v_1 = 2s_1 + s_2 \quad ; \rightarrow v_1 = -(2s_1 + s_2)$$

from \textcircled{5}

$$v_2 = -3(2s_1 + s_2) + 2s_1 - \frac{3}{2}(2s_1 - v_1) \\ \rightarrow v_2 = 4s_1 + 3s_2 + 2s_1 - 3s_1 + \frac{3}{2}v_1$$

⑥ Determine the z and y parameters
for the network form




$$V_1 = 2s_1 + 2s_3 - s_2 \quad \textcircled{1}$$

$$V_2 = 2s_2 - s_1 - s_3 \quad \textcircled{2}$$

$$s_1 = 3s_1 - v_1 + s_3 - v_2 \quad \textcircled{3}$$

$$s_2 = s_2 + v_1 - s_3 - v_2 \quad \textcircled{4}$$

defining equations

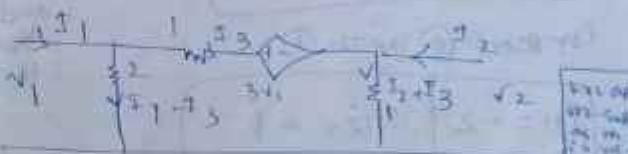

base case
no voltage
no current
no gain
no feedback

$$V_1 = 2s_1 - 2s_3 \quad \textcircled{5}$$

$$V_1 = s_3 + 3s_1 + s_2 + s_3$$

$$s_1 = 2s_1 + 3s_1 + s_2 + s_3 \quad \textcircled{6}$$

$$s_2 = 2s_1 + s_3 + s_2$$

$$s_3 = 2s_1 + s_2$$

$$s_3 = \frac{1}{2}(2s_1 + s_2) \quad \textcircled{7}$$

In this case
there are
2 unknowns
s_1, s_3
so we can't
determine
s_2 - 1 eqn is still there

Hence KVL relation
on dependent
source is
independent
of s_3 as
it is intermediate

$$V_2 = (I_2 + I_3)s_1 \quad \textcircled{8}$$

$$V_2 = -3V_1 - s_3 + 2s_1 - s_2 \\ = -3s_1 + s_3 + 2s_1 - s_2 \\ = -s_1 + s_2 - 3s_3 \quad \textcircled{9}$$

$$v_1 = 3(v_1 - v_3)$$

$$\rightarrow 2v_1 - 2v_3 = 0 \quad (1)$$

$$v_1 + v_3 + 3v_1 + v_2 + v_3$$

$$\rightarrow 2v_1 + 2v_3 = v_2 + 2v_3 - (1) \quad /$$

$$0 + 0$$

$$3 - v_1 = 2v_1 + v_2$$

$$2v_1 + v_2 = 2v_1 + v_2$$

$$\boxed{v_{11} = -1, v_{12} = -1}$$

$$2 = v_2 + v_3 - (1) \quad /$$

$$v_2 = -3v_1 - v_3 + 2(v_1 - v_3)$$

$$\rightarrow v_2 + 3v_1 = -v_3 + v_1 - 2v_3$$

$$\rightarrow v_2 + 3v_1 = -3v_3 + 2v_1 - (1) \quad /$$

$$\rightarrow v_2 + 3\left(\frac{1}{2} - v_3\right) = -3v_3 + 2v_1$$

$$\rightarrow v_2 - \frac{3}{2}v_3 - 6v_3 = -3v_3 + 2v_1$$

$$\rightarrow v_2 = 2v_1 + \frac{3}{2}v_3$$

$$\boxed{v_{21} = 2, v_{22} = \frac{3}{2}}$$

$$(1) \times 2 + 0$$

$$\cancel{2v_1 + 2v_3 = 2v_2 + 2v_3 + 2v_1 - 2v_3} \\ \cancel{3v_1 + 2v_3 = 2v_1 + 2v_2}$$

$$(1) - 2(v_1)$$

$$3 - 2v_1 - 2v_2 = v_2 + 2v_3 - 2v_2 - 1v_3$$

$$\rightarrow 2v_1 + v_2 = v_2$$

$$\rightarrow v_2 = 2v_1 + 0v_2$$

$$\boxed{v_{21} = 2, v_{22} = 0}$$

$$\text{from } (1) \rightarrow v_1 + 2v_3 = 2v_1 - (1) \quad / -v_1$$

$$\text{from } (1), \text{ putting } (1) \rightarrow v_1 + 2v_3 = 2v_1 - v_1$$

$$\rightarrow v_2 + 3v_1 = -2v_3 + v_1 + 2v_3$$

$$\text{from } (1), \rightarrow v_2 + 2v_3 = v_1 - (1) \quad / -2v_3$$

$$\text{from } (1), \text{ putting } (1),$$

$$v_2 + 3v_1 = +\frac{3}{2}(v_1 - 2v_3) + 2v_1$$

$$\rightarrow v_2 + 3v_1 = \frac{3v_1}{2} - 3v_1 + 2v_1$$

$$\rightarrow v_2 + 3v_1 - \frac{3v_1}{2} = -v_1$$

$$\rightarrow v_2 = \frac{3v_1}{2} - v_2, \boxed{v_{11} = -\frac{3}{2}, v_{12} = -1}$$

from

$$3 - 2T_3 + 2v_1 - T_2$$

$$3T_3 = -\frac{1}{2}(2v_1 + T_2)$$

Putting it in ⑤

$$v_1 = 2T_1 + 2T_2 \quad (2v_1 + T_2)$$

$$= 2T_1 + 2v_1 + T_2$$

$$\boxed{3v_1 = -(2T_1 + T_2) - ⑥}$$

Corr. ⑥ with ①

$$\boxed{T_{11} = -2 \quad T_{12} = -1}$$

$$⑦ + 2 \times ⑥$$

$$2T_1 + 2T_3 = 2T_2 + 2T_3$$

$$T_1 + T_{12} = T_2 + 2T_2 + 2v_1 = 1^*$$

$$3 - 2T_1 - T_2 + 2v_2 = 3T_2 \quad (\text{from } ④)$$

$$3T_2 = 4v_1 + 3T_2 \quad \cancel{+ v_1} = 1^* \rightarrow$$

~~$$3v_2 = 2T_{11} + \frac{3}{2}T_{12}$$~~

$$\boxed{T_{21} = 2 \quad \boxed{T_{11} = \frac{3}{2}}}$$

[Now after solving all eqns, then calculate all forward
by $v_1, T_1 = 1$,
and v_2 and T_2
start]

[After Solv.

all eqns
you can
also
combine
them with
defining eqn
and
then calculate
the parameter

⑦ for ⑧

$$3 - 2v_1 = 2T_1 + T_2$$

$$\Rightarrow v_1 = -(2T_1 + T_2)$$

$$3v_1 = -2T_1 - T_2$$

$$\boxed{3(v_1 + T_2)} = T_1$$

$$\text{for } ⑨, -\frac{1}{2}(v_1 + T_2) = -\frac{3v_1}{2} - v_2$$

$$\Rightarrow -\frac{v_1}{2} - \frac{1}{2}T_2 = -\frac{3v_1}{2} - v_2$$

$$\Rightarrow -\frac{1}{2}T_2 = -\frac{3v_1}{2} + \frac{v_1}{2} - v_2$$

$$\Rightarrow -\frac{1}{2}T_2 = -v_1 - v_2$$

$$\Rightarrow T_2 = 2v_1 + 2v_2$$

$$\boxed{y_{11} + 2 = y_{12}}$$

from ⑩,

$$2T_{12} - 2T_3 - 2T_2 \quad | \quad 2$$

$$3 - 2T_3 = -2T_2 - 2v_1$$

$$3T_3 = -\frac{1}{2}(T_2 + 2v_1) - ⑩$$

Putting ⑩ in ⑧

$$v_2 = -3v_1 + 2v_2$$

Solving
Com
0
be
with
ng eqn.
calculate
parametry

$\lambda - m$


$$\begin{bmatrix} -2 & -1 \\ 2 & \frac{3}{2} \end{bmatrix}$$
$$\frac{y_{11} - 2}{\lambda}$$

$$y_{12} = \frac{-(-1)}{-1} = -1$$
$$= -\frac{3}{2}$$

$$y_{21} = \frac{-2}{-1} = 2$$

$$y_{22} = \frac{-2}{-1} = 2$$

R. Parameters

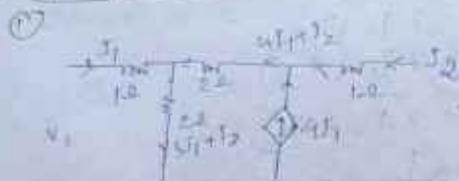

$$v_1 = I_1 + 2(R_1 + R_2) \quad \text{--- (1)}$$

$$v_1 = R_1 I_1 + R_2 v_2$$

$$\frac{v_1}{2} = R_1 I_1 + R_2 v_2$$

$$v_2 = 2(4I_1 - 2I_2) + 2(3I_1 + I_2) + I_2 \\ = 8I_1 + 4I_2 + 2I_2 + 2I_2 + I_2$$

$$v_2 = 18I_1 + 5I_2 \quad \text{--- (2)}$$

$$\therefore v_2 - 5I_2 = 18I_1 \rightarrow I_2 = \frac{1}{5}(v_2 - 18I_1)$$

$$\therefore I_1 = \frac{1}{18}(-5I_2 + v_2) \quad \text{--- (3)}$$

$$\begin{bmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{bmatrix} = \begin{bmatrix} \frac{1}{18} & \frac{1}{5} \\ \frac{1}{5} & \frac{1}{10} \end{bmatrix}$$


$$\text{from (1)} \quad v_1 = 18I_1 + \frac{1}{5}(v_2 - 18I_1) \quad \text{--- (4)}$$

$$\text{from (2)} \quad v_1 = 11I_1 + \frac{2}{5}(v_2 - 8I_1) \\ = 11I_1 - \frac{2}{5}R_1 + \frac{4}{5}v_2 \\ = \frac{13I_1}{5} + \frac{4}{5}v_2$$

14/10/13

$$R_{11} = \frac{1}{5} \times \frac{10}{18} = \frac{2}{9} \quad R_{12} = \frac{2}{5}$$

FIND Z and T parameters

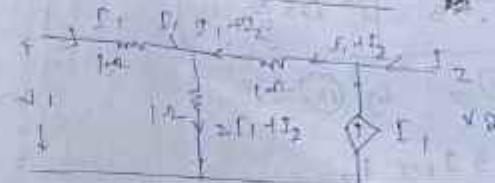

$$v_1 = I_1 + 2I_1 - I_2$$

$$v_1 = 3I_1 + I_2 \quad \text{--- (1)}$$

$$v_2 = R_1 I_2 + 2I_1 + I_2$$

$$\text{from (2)} \quad v_2 = 3I_1 + 2I_2 \quad \text{--- (2)}$$

$$\text{from (1)} \quad v_1 = 2I_1 + I_2 + 2I_2 = 3I_1 + 3I_2$$

$$v_2 = I_{21} + I_{22} + I_{23} + I_2 = 3I_1 + 3I_2$$

$$\text{from (2)} \quad \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 3 & 1 \\ 3 & 2 \end{bmatrix}$$

$$v_1 = A v_2 + B I_2$$

$$\text{from (1)} \quad v_1 = 3I_1 + 2I_2$$

$$\text{from (2)} \quad v_2 = 3I_1 + 2I_2 \\ A = 3I_{12} = v_2 - 2I_2$$

$$v_1 = h_{11}I_1 + h_{12}v_2 \quad \text{--- (1)}$$

from (111),

$$\begin{aligned} v_1 &= 11I_1 + 2I_2 \\ &= 11I_1 + \frac{2}{5}(v_2 - 18I_1) \\ &= 11I_1 - \frac{36}{5}I_1 + \frac{2}{5}v_2 \end{aligned}$$

$$v_1 = \frac{19}{5}I_1 + \frac{2}{5}v_2 \quad \begin{matrix} 55 \\ -36 \\ \hline 19 \end{matrix}$$

$$\therefore h_{11} = \frac{19}{5}, \quad h_{12} = \frac{2}{5}$$

$$\text{from (1)} \quad 5 - 2 \quad \Rightarrow h_{22} = \frac{1}{5} + \frac{1}{5} \cdot 8^{\frac{3}{2}}$$

$$Z = \begin{bmatrix} 3 & 1 \\ 3 & 2 \end{bmatrix}$$

$$T = \begin{bmatrix} I_{11} & \frac{A+2}{2} \\ I_{21} & \frac{A+2}{2} \end{bmatrix}$$

T in Z

$$A = \frac{3}{3}$$

$$B = \frac{6-3}{3} = 1, C = \frac{1}{3} = \frac{1}{3}$$

$$D = \frac{2}{3}$$

$$= \frac{3}{3} - \frac{2}{3}$$

$$T = \begin{bmatrix} 1 & 1 \\ \frac{1}{3} & \frac{2}{3} \end{bmatrix}$$

Z in T

$$Z_{11} = \frac{A}{C} = 1 \times 3 = 3$$

$$Z_{12} = \frac{AT}{C} = \frac{2}{3} - \frac{1}{3}$$

$$= \frac{\frac{1}{3}}{\frac{2}{3}} = 1$$

$$T_{21} = \frac{1}{C} = 3$$

$$Z_{22} = \frac{D}{C} = \frac{2}{3} \times 1 = 2$$

T in I

$$V_1 = A V_2 + B (-T_2) \quad \text{--- (i)}$$

$$I_1 = C V_2 - D F_2 \quad \text{--- (ii)}$$

$$V_1 = I_{11} T_1 + I_{12} T_2 \quad \text{--- (iii)}$$

$$V_2 = I_{21} T_1 + I_{22} T_2 \quad \text{--- (iv)}$$

from (iv)

$$V_2 = I_{21} T_1 + I_{22} T_2$$

$$\Rightarrow V_2 - I_{21} T_2 = I_{22} T_1$$

$$3 T_1 = \frac{1}{I_{21}} (V_2 - I_{22} T_2) \quad \text{--- (v)}$$

Comparing (i) with (v)

$$C = \frac{1}{I_{21}}, D = \frac{I_{22}}{I_{21}}$$

From (ii),

$$V_1 = I_{11} (V_2 - I_{12} T_2) + I_{12} T_2$$

$$= \frac{I_{11}}{I_{21}} V_2 - \frac{I_{11} I_{12}}{I_{21}} I_{22} T_2$$

$$\therefore R = \frac{I_{11}}{I_{21}} B + \frac{I_{12}}{I_{21}} V_2 - \frac{I_{11} I_{12}}{I_{21}} \frac{I_{22}}{I_{21}} I_{22} T_2$$

$$\Rightarrow 3I_1 = V_2 - 2I_2$$

$$\Rightarrow I_1 = \frac{1}{3}V_2 - \frac{2}{3}I_2 \quad (1)$$

$$\boxed{C = \frac{1}{3}v_2 \quad D = \frac{2}{3}}$$

for (1) > (2)

$$V_1 = 3I_2 + I_2$$

$$3V_1 = 3\left(\frac{1}{3}V_2 - \frac{2}{3}I_2\right) + I_2$$

$$= V_2 - 2I_2 + I_2$$

$$\Rightarrow V_1 = V_2 - I_2$$

$$\boxed{A = 1 - v \quad B = 1 + v}$$

(2) The A, B, C parameters of this 2-point network are given like this

$$T = \begin{bmatrix} \frac{5}{2} & \frac{1}{2} - v \\ \frac{1}{2}v & \frac{1}{2} \end{bmatrix}$$

Determine Z, Y and parameters.

$$T = \begin{bmatrix} \frac{5}{2}(A) & \frac{1}{2}(B) \\ \frac{1}{2}(C) & D \end{bmatrix}$$

for Z

$$Z = T = \frac{5}{2} \times 5 \Omega$$

$$Z = \frac{AD}{C} = \frac{(AO - BC)}{C} = \frac{\frac{5}{2} - \frac{1}{2}}{\frac{1}{2}} = 12 \Omega$$

$$Z_{21} = \frac{1}{C} = 2 \Omega$$

$$Z_{22} = \frac{B}{C} = 1 \Omega$$

$$Z = \begin{bmatrix} 5 & 2 \\ 2 & 1 \end{bmatrix}$$

for Y

$$Y_{11} = \frac{B}{A} = \frac{1}{5} \Omega$$

$$Y_{12} = -\frac{A}{C} = \frac{AO - BC}{C} = \frac{\frac{5}{2} - \frac{1}{2}}{\frac{1}{2}} = 2 \Omega$$

$$Y_{21} = -\frac{C}{B} = -\frac{1}{2} \Omega$$

$$Y_{22} = \frac{A}{C} = \frac{5 - v}{2} \Omega = 5 \Omega$$

$$Y = \begin{bmatrix} 1 & 2 \\ 2 & 5 \end{bmatrix}$$

$$h = \frac{B}{D} = 1 \Omega$$

$$L_{112} = \frac{B}{C} = \frac{AO - BC}{C} = 2$$


$$L_{212} = \frac{1}{D} = -\frac{1}{2}$$




$$L_{122} = \frac{1}{D} = 1 \Omega \text{ with } \begin{bmatrix} 1 & 2 \\ 2 & 1 \end{bmatrix}$$

Graph Theory

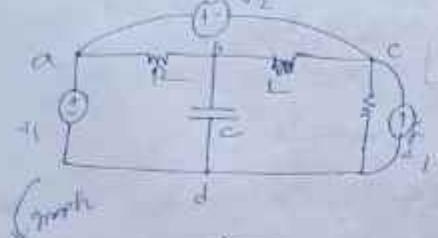Graph is nothing but a skeleton / structure.



Significance of
graph theory

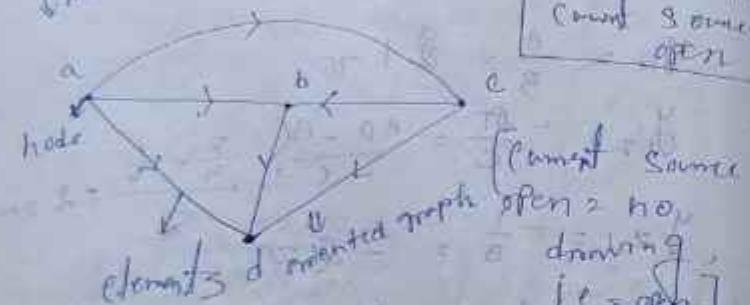


The line segments are elements hence
the junctions are vertices of the
segment are elements one node here

If assign direction. oriented graph
All the directions are arriving.



An edge
if it crosses = planar graph
If it is possible to draw a graph where

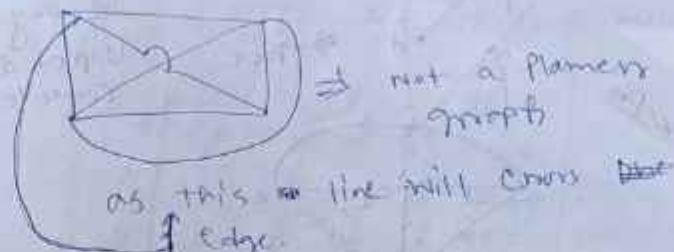
there are no edges crossing, then
this type of graph is called Planar
graph



NON planar graph



not planar

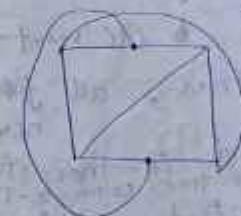


Tree

Connected graph - is a graph where there
exist at least one path between
any two nodes of that graph

Tree

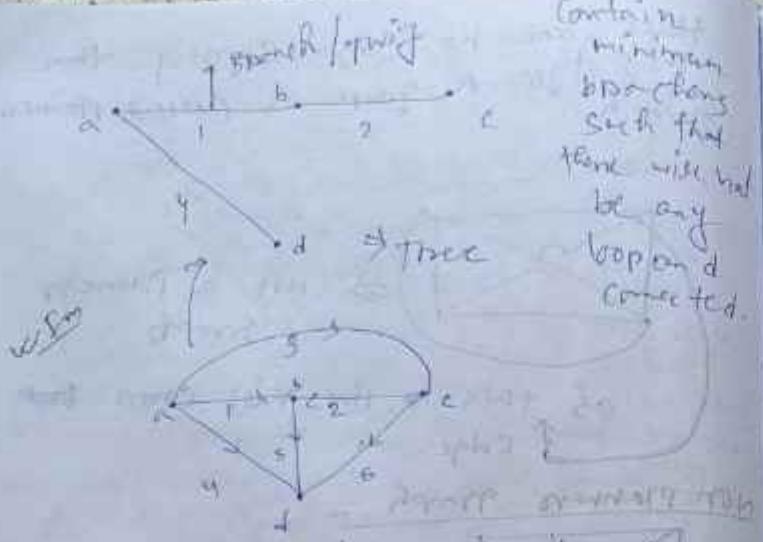Tree of a Connected Graph is a
graph that contains all the nodes of original
graph but not contains L.L.S or R.R.P.



the elements / line segments of a tree = Branch / twig

co-tree - except those elements that need to form a tree, all the remaining elements are called co-tree of the graph. Co-tree is the complement of tree. $e_{\text{tree}} = n - e_{\text{co-tree}}$

No. of elements of a graph = $e_{\text{tree}} + \text{nodes}$

$b = h - 1$ (where b = no. of twigs, h = no. of trees)

thus, $b = h - 1$

$$b = h - 1$$

In incidence and incident matrix

In a graph if an element is connected to a node then it is incident on the node.

Augmented incidence (complete incidence matrix)

$$A_a = \begin{bmatrix} a & 1 & 2 & 3 & 4 & 5 & c \\ b & -1 & 0 & +1 & 0 & 0 & \\ c & 0 & +1 & -1 & 0 & 0 & +1 \\ d & 0 & 0 & 0 & -1 & -1 & -1 \end{bmatrix}$$

$$a_{ij} = +1$$

$$-1$$

$$= 0$$

incoming = -ve
outgoing = +ve

column sum = 0 (always)

If we want to element one how we can simply do that, nothing will be change


Reduced incidence matrix:

$$A_a = \begin{bmatrix} a & 1 & 2 & 3 & 4 & 5 & c \\ b & -1 & 0 & +1 & +1 & 0 & \\ c & 0 & +1 & -1 & 0 & 0 & +1 \\ d & 0 & 0 & 0 & -1 & -1 & -1 \end{bmatrix}$$

not in main diag

eliminate now d

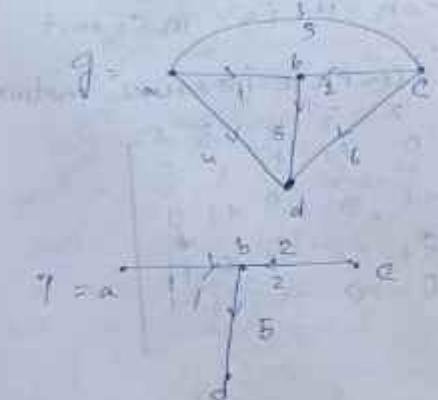Fundamental loops and fundamental matrix on tie set matrix



Fundamental loop

loop 1: $\{v_1, v_2, v_3\}$
loop 2: $\{v_2, v_3, v_4\}$
loop 3: $\{v_3, v_4, v_5\}$

Condition of Fundamental loop subset

In that loop there must be 1 fundamental loop. In the loop there must contain only one link. Furthermore the direction of that loop will be in the direction of this defining link.

$$B = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 \\ 1 & -1 & 1 & 1 & 0 & 0 \\ 1 & 0 & 0 & 1 & 1 & 0 \\ 1 & 0 & -1 & 0 & 0 & 1 \end{bmatrix}$$

where $v_1 = 1$, $v_2 = 0$, $v_3 = 1$, $v_4 = 1$, $v_5 = 0$, $v_6 = 1$

Branch voltages
 $v_1 = 1$, $v_2 = 0$, $v_3 = 1$, $v_4 = 1$, $v_5 = 0$, $v_6 = 1$

$$\begin{aligned} l_1: v_3 + v_2 - v_1 &= 0 \Rightarrow v_1 + v_2 + v_3 = 0 \\ 0 + 0 + 1 &= 0 \\ l_2: -v_1 - v_5 + v_4 &= 0 \Rightarrow -v_1 + v_4 - v_5 = 0 \\ -1 + 0 + 1 &= 0 \\ l_3: v_6 + v_5 - v_2 &= 0 \Rightarrow -v_2 - v_5 + v_6 = 0 \\ 0 + 0 + 1 &= 0 \end{aligned}$$

$$\rightarrow \begin{bmatrix} -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 & 0 & 0 \\ 1 & 0 & 0 & 1 & 0 & 0 \\ 0 & -1 & 0 & 0 & 1 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$


intrinsic bound [left] \rightarrow units

$$\rightarrow [L_B] [v_b] = 0 \quad [\text{if the branch } b \text{ is any one of } E]$$

\Rightarrow Cut set matrix & branch volt. matrix = 0

Cut set matrix

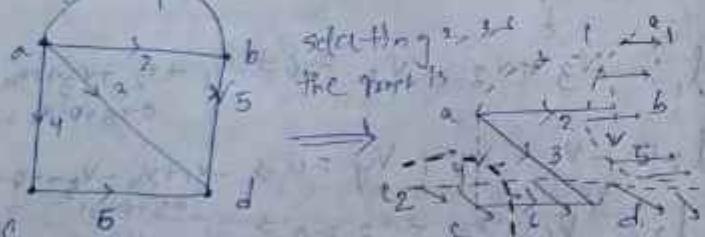cut set - it is such a set of elements which may remove any cut that divides the graph into two parts. write the condition that the element should set must contain max. 1 branch.



$$[f] = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 \\ 1 & 0 & 0 & 1 & 0 & 0 \\ 0 & 1 & 0 & 0 & 1 & 0 \\ 0 & 0 & 1 & 0 & 0 & 1 \\ 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \end{bmatrix} \quad [I_b] = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix}$$

Directions defining branch direction

$$C_1: I_1 + I_2 + I_5 = p \quad (\text{at } b) \quad \begin{matrix} I_1 + I_2 + I_5 = 0 \\ I_3 + I_4 + I_6 = 0 \end{matrix}$$

$$I_4 - I_C = 0 \quad (\text{at } c)$$

$$I_3 + I_5 + I_C = 0$$

$$C_3: I_4 - I_C = 0 \quad (\text{at } c)$$

$$I_3 + I_5 + I_C = 0 \quad (\text{at } c)$$

$$\begin{bmatrix} 1 & 1 & 0 & 0 & -1 & 0 \\ 0 & 0 & 1 & 1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix} \quad \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \\ I_C \end{bmatrix} = 0$$

$$\Rightarrow [A] [I_b] = 0$$

Hint: $I_b = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix}$

$$[A] [I_b] = 0$$

$[A] = \text{Incidence matrix}$

$\{(A)E\} f_b = \text{zero} \Rightarrow \text{solution to eqn (i)}$

i) The reduced matrix of an oriented graph is given as.

$$A = \begin{bmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

ii) Draw the graph.


iii) How many trees are possible for this graph?

iv) Write the tie-set matrix.

v) Write the cut-set matrix.

Ans

	0	1	2	3	4	5	
a	0		2	3	4	5	
b	0	-1	0	0	0	0	
c	0	0	-1	0	0	0	
d	1	1	0	-1	0	0	

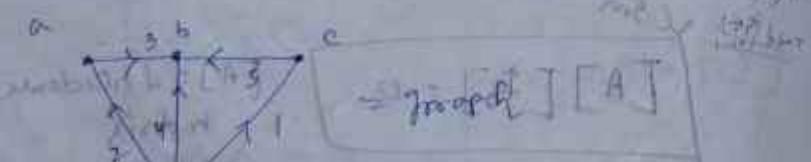

vi) No of possible trees = $\det \begin{bmatrix} A & I \\ I & A^T + \text{diag}(A) \end{bmatrix}$

$$A^T$$

$$\begin{bmatrix} 0 & 0 & -1 & 0 & 0 \\ -1 & 0 & 0 & 0 & 0 \\ 1 & -1 & 0 & 0 & 0 \\ 0 & -1 & 0 & 0 & 0 \\ 0 & -1 & 1 & 0 & 0 \end{bmatrix} \times \begin{bmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ 1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

$$A \cdot A^T = \begin{bmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix} \times \begin{bmatrix} 0 & 0 & -1 & 0 & 0 \\ -1 & 0 & 0 & 0 & 0 \\ 1 & -1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \end{bmatrix}$$

$$\begin{bmatrix} 0+1+1+0+0 & 0+0-1+0+0 & 0+0+0+0+0 \\ 0+0-1+0+0 & 0+0+1+1+1 & 0+0+0+0-1 \\ 0+0+0+0+0 & 0+0+0+0-1 & 1+0+0+0+1 \end{bmatrix}$$


$$\begin{bmatrix} 2 & -1 & 0 \\ -1 & 3 & 0 \\ 0 & -1 & 2 \end{bmatrix}$$

$$\begin{bmatrix} 2 & -1 & 0 \\ -1 & 3 & 0 \\ 0 & -1 & 2 \end{bmatrix} = 2(2-1)+1(1-0) = 10+2 = 12$$

No of Possible trees = 8




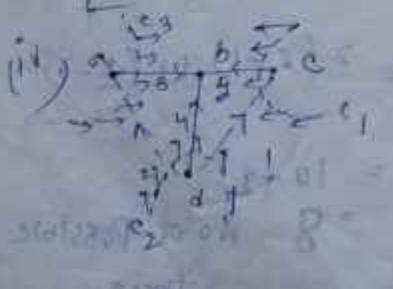$B = \begin{bmatrix} 0 & 1 & 0 & 0 & 0 \\ 1 & 0 & -1 & 0 & 0 \\ 0 & -1 & 0 & 1 & 0 \\ 0 & 0 & 1 & 0 & -1 \\ 0 & 0 & 0 & -1 & 0 \end{bmatrix}$



$$G = \begin{bmatrix} 0 & 1 & -1 & 0 & 0 \\ 1 & 0 & -1 & 0 & 0 \\ -1 & 0 & 0 & 1 & 0 \\ 0 & 0 & 1 & 0 & -1 \\ 0 & 0 & 0 & -1 & 0 \end{bmatrix}$$

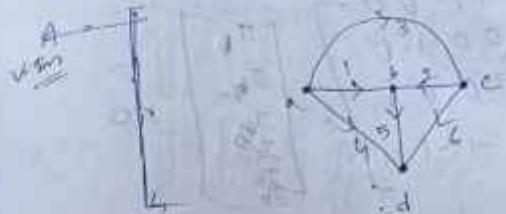~~$\nabla^T A_3 [I_b] = 0$~~ (at b) Incident matrix



Branch currents = I_1, I_2, I_3, I_4

a: $-I_3 - I_1 - I_4 = 0$ (at a)

b: $I_1 + I_3 + I_4 = 0$

$\Rightarrow I_1 + 0I_2 + 0I_3 + I_4 + 0I_5 + 0I_6 = 0$

b: $I_1 - I_2 + 0I_3 + 0I_4 + 0I_5 + 0I_6 = 0$
 $\Rightarrow I_1 - I_2 + 0I_3 + 0I_4 + 0I_5 + 0I_6 = 0$
 $\Rightarrow -I_1 + I_2 + 0I_3 + 0I_4 + 0I_5 + 0I_6 = 0$

c: $I_3 - I_2 - I_6 = 0$ (at c)

$\Rightarrow -I_2 + I_3 - I_6 = 0$

$\Rightarrow I_2 - I_3 + I_6 = 0$

$\Rightarrow 0I_1 + I_2 - I_3 + 0I_4 + 0I_5 + I_6 = 0$

d: $I_4 + I_5 + I_6 = 0$ (at d)

$\Rightarrow -I_4 - I_5 - I_6 = 0$



$\Rightarrow 0I_1 + 0I_2 + 0I_3 - I_4 - I_5 - I_6 = 0$

$$\begin{bmatrix} 1 & 0 & 1 & 0 & 0 \\ 0 & -1 & 0 & 0 & 1 \\ 0 & 1 & -1 & 0 & 0 \\ 0 & 0 & 0 & -1 & -1 \end{bmatrix} \cdot \begin{bmatrix} T_1 \\ T_2 \\ T_3 \\ T_4 \\ T_5 \end{bmatrix} = 0$$

$$\Rightarrow [A] \begin{bmatrix} T_5 \end{bmatrix} = 0$$

→ augmented incident matrix
branch current matrix

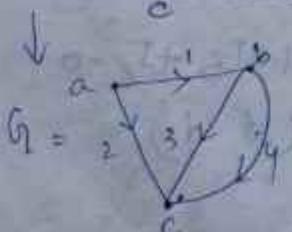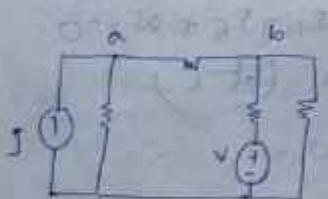- Q2
- (i) Draw the graph of the network and draw and indicate the no. of all possible trees of the network.



$$\text{No. of trees} = \frac{1}{4!} \begin{bmatrix} 1 & 2 & 3 & 4 \\ -1 & +1 & 0 & 0 \\ -1 & 0 & +1 & +1 \\ 0 & -1 & -1 & -1 \end{bmatrix}$$

$$= \frac{1}{4!} \begin{bmatrix} 1 & -1 & 0 & 0 \\ 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \end{bmatrix}$$




No. of possible trees =

$$\text{No. of trees} = A^{-1} \begin{bmatrix} 1 & 1 & 0 & 0 \\ -1 & 0 & 1 & 1 \end{bmatrix} \cdot \begin{bmatrix} 1 & -1 \\ 1 & 0 \\ 0 & 1 \\ 0 & -1 \end{bmatrix}$$


$$= \begin{bmatrix} 1+1+0+0 & -1+0+0+0 \\ -1+0+0+0 & 1+0+1+1 \end{bmatrix}$$

$$= \begin{bmatrix} 2 & -1 \\ -1 & 3 \end{bmatrix}$$
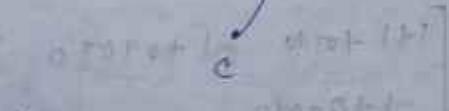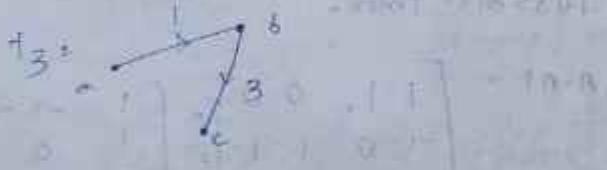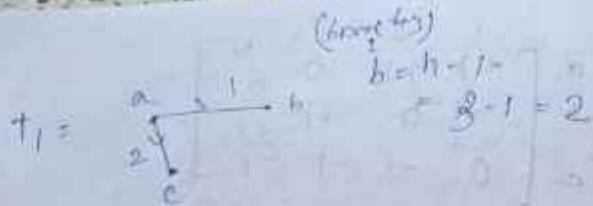
$$\begin{aligned} \text{No. of trees} &= \begin{vmatrix} 2 & -1 \\ -1 & 3 \end{vmatrix} \\ &= 6 - 1 \\ &= 5 \end{aligned}$$




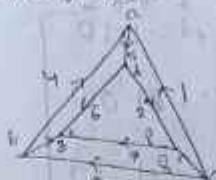- ③ For the oriented graph shown in figure and for the tree indicated obtain all the tie-set and cut-set matrices.



Tree : {5, 6, 7, 8, 9}

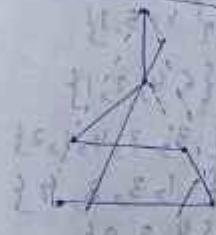$b = n - 1 = 6 - 1 = 5$ = no. of fundamental loops,
 $c = e - b - n = 9 - 5 - 6 = 4$ = no. of fundamental cuts



$I_1 : \{1, 5, 6, 7, 8\}$ primary tie-set

$I_2 : \{2, 6, 7\}$

$I_3 : \{3, 7, 8, 9\}$ cut-set

$I_4 : \{4, 5, 6, 7, 8, 9\}$

max $\rightarrow 8$

$$\begin{cases} l_1 : v_1 + v_5 + v_6 - v_4 - v_8 = 0 \\ l_2 : v_2 + v_7 + v_6 - v_5 - v_8 = 0 \\ l_3 : v_3 + v_9 - v_8 + v_7 - v_6 = 0 \end{cases}$$

$$\begin{cases} l_1 : v_1 + v_5 + v_6 - v_4 - v_8 = 0 \\ l_2 : v_2 + v_7 + v_6 - v_5 - v_8 = 0 \\ l_3 : v_3 + v_9 - v_8 + v_7 - v_6 = 0 \end{cases}$$

$$\begin{cases} l_1 : v_1 + v_5 + v_6 - v_4 - v_8 = 0 \\ l_2 : v_2 + v_7 + v_6 - v_5 - v_8 = 0 \\ l_3 : v_3 + v_9 - v_8 + v_7 - v_6 = 0 \end{cases}$$


$$I_4: v_6 + v_8 + v_6 - v_2 - v_0 \xrightarrow{v_6} 3 \xrightarrow{v_4 + v_2} 0 \xrightarrow{v_4 + v_2} 0 \xrightarrow{v_3} 0$$

$$B = I_1 \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 & 9 \\ 1 & 0 & 0 & 0 & 1 & 1 & -1 & 0 & 0 \end{bmatrix}$$

$$I_2 \begin{bmatrix} 0 & 1 & 0 & 0 & 0 & -1 & 0 & 0 & 0 \end{bmatrix}$$

$$I_3 \begin{bmatrix} 0 & 0 & 1 & 0 & 0 & 0 & -1 & 0 & 0 \end{bmatrix}$$
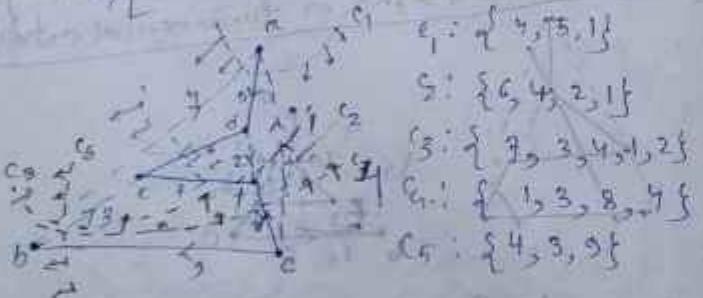
$$I_4 \begin{bmatrix} 0 & 0 & 0 & 1 & 0 & 1 & -1 & -1 & 0 \end{bmatrix}$$



[a] is coming towards

b [a], c [a]'s direction
should be towards

b]

$$\text{method 2} = C = I_1 \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 & 9 \\ -1 & 0 & 0 & -1 & 1 & 0 & 0 & 0 & 0 \end{bmatrix}$$



$$I_2 \begin{bmatrix} -1 & 1 & 0 & -1 & 0 & 1 & 0 & 0 & 0 \end{bmatrix}$$

$$I_3 \begin{bmatrix} -1 & 1 & -1 & 1 & 0 & 0 & 1 & 0 & 0 \end{bmatrix}$$

$$I_4 \begin{bmatrix} 1 & 0 & 1 & 1 & 0 & 0 & 0 & 1 & 0 \end{bmatrix}$$

$$I_5 \begin{bmatrix} 0 & 0 & 1 & -1 & 0 & 0 & 0 & 0 & 1 \end{bmatrix}$$

(Method 2)

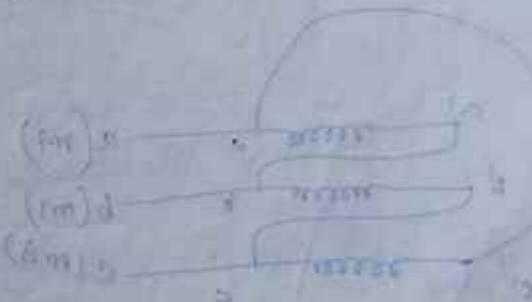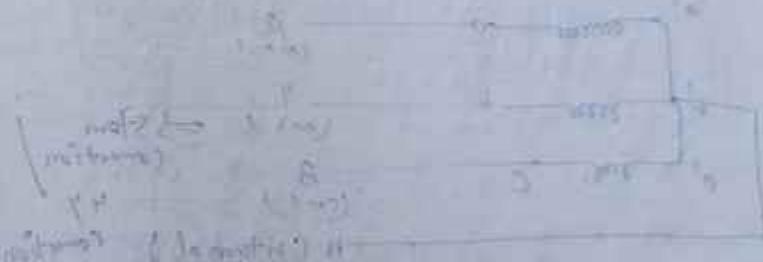

3-phase (Poly phase)


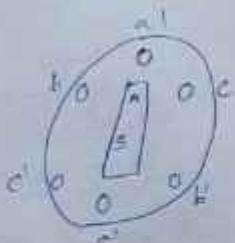
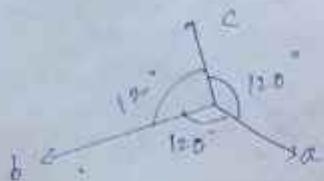
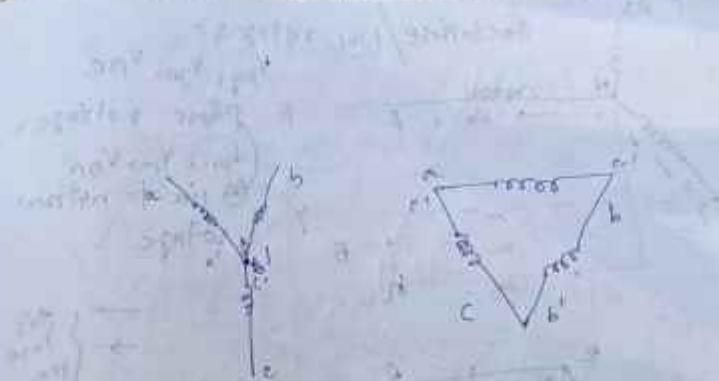
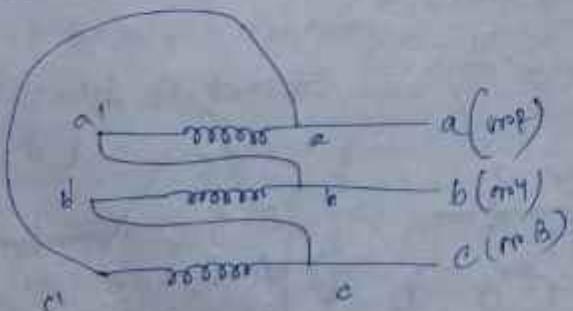


Fig B on ABC
phase diff = 120° [$\frac{2\pi}{3}$]

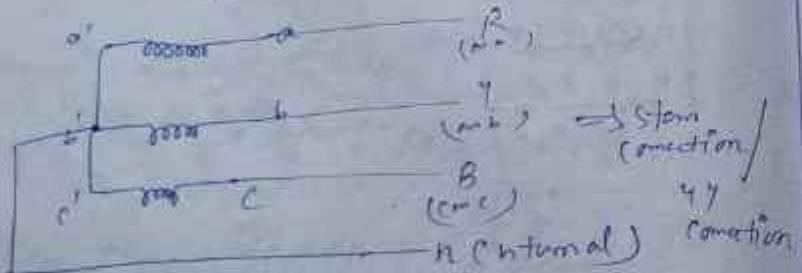


$$E_a = |E| \angle 0^\circ = E$$

$$E_b = |E| \angle -120^\circ = E \angle 120^\circ$$


$$E_c = |E| \angle -240^\circ = E \angle 120^\circ$$

[E = emf]

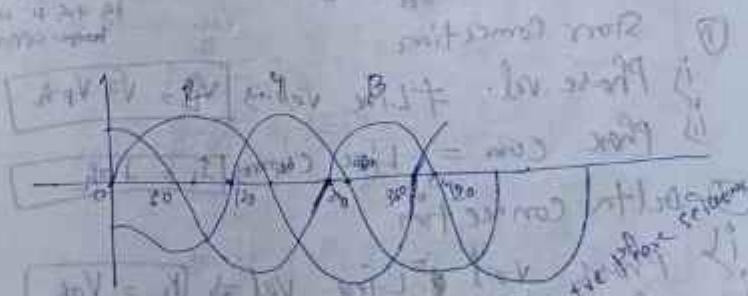

After Phase sequence $\rightarrow A + B + C$ 2 Possibilities

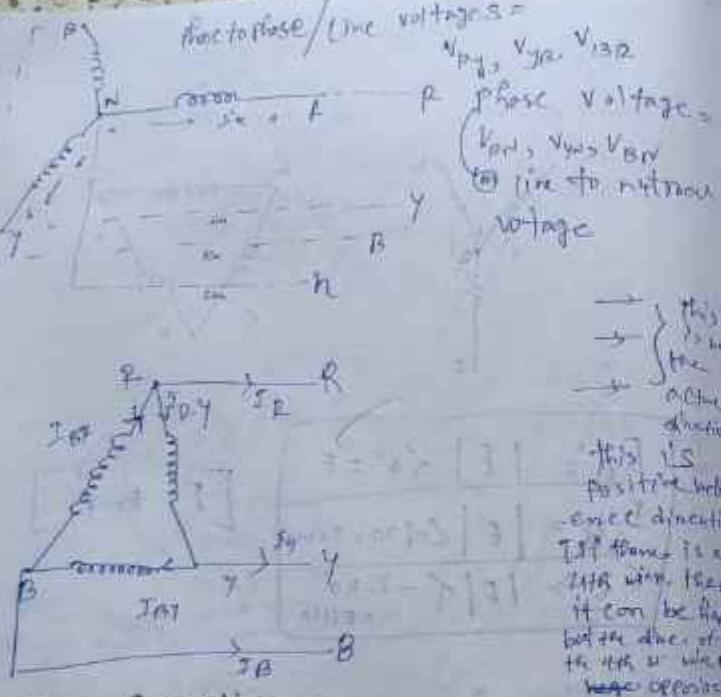$\rightarrow A + C + B$ only one phase sequence



① Star Connection

i) Phase vol. + line vol $\Rightarrow V_L = \sqrt{3} V_{ph}$


ii) Phase curr. = Line curr. $[I_L = I_{ph}]$

② Delta Connection

i) Phase vol. = Line vol $\Rightarrow V_L = V_{ph}$

ii) Phase curr. + line curr. $[I_L = \sqrt{3} I_{ph}]$

H.W Same, solve (ii)
 methods

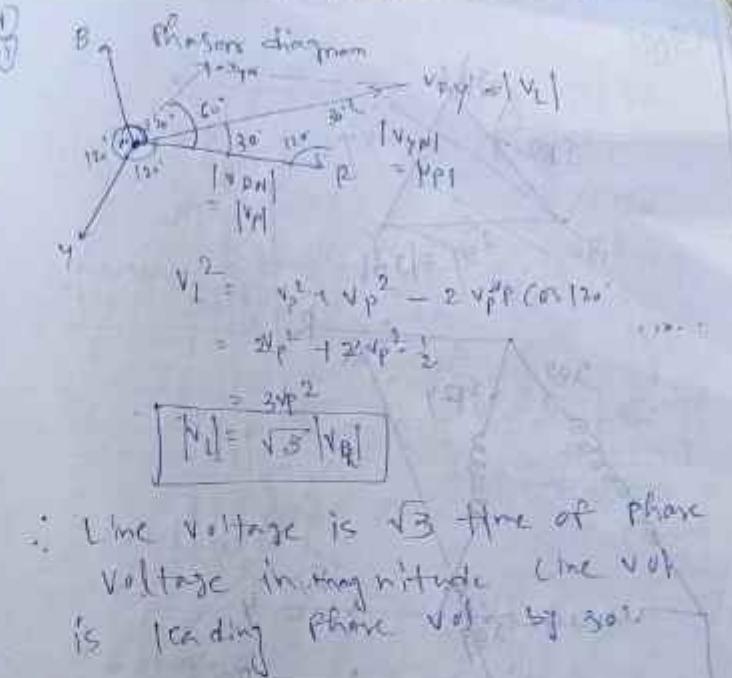

$$E_{ab} = E_a - E_b$$

$$= E \angle 0^\circ - E \angle 120^\circ$$

$$= E [1 - 1 \angle 120^\circ]$$

$$\rightarrow E [1 - (-0.5 - 0.86j)]$$

$$\rightarrow E [1 + (\frac{1}{2} + \frac{\sqrt{3}}{2}j)]$$

$$= E \left(\frac{3}{2} + \frac{\sqrt{3}}{2}j\right)$$


$$= \frac{1}{2} E (3 + \sqrt{3}j)$$

$$= \sqrt{3} E \angle 30^\circ$$


$$\rightarrow 1.73 E \angle 20.9^\circ$$

$$E_{ab} \angle 30^\circ$$


(Q3)

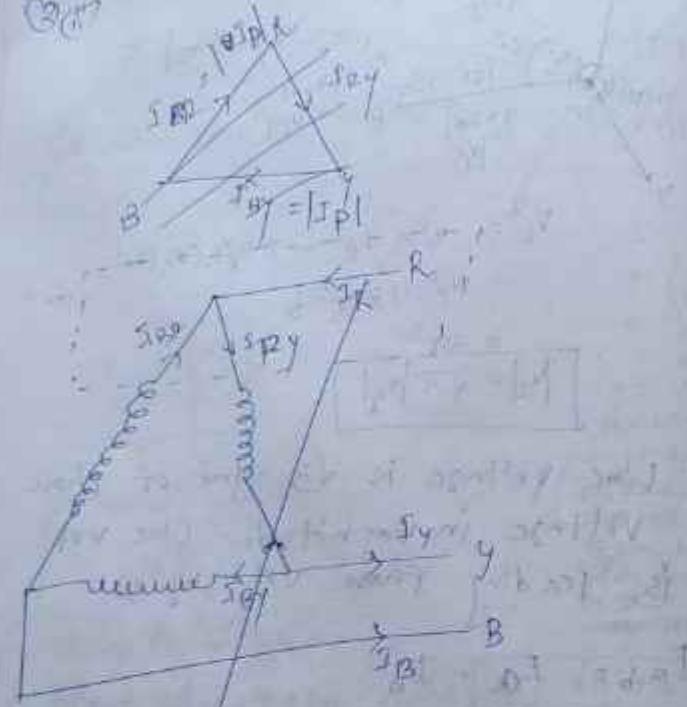

I_R is resultant of I_{B1} and I_{B2}

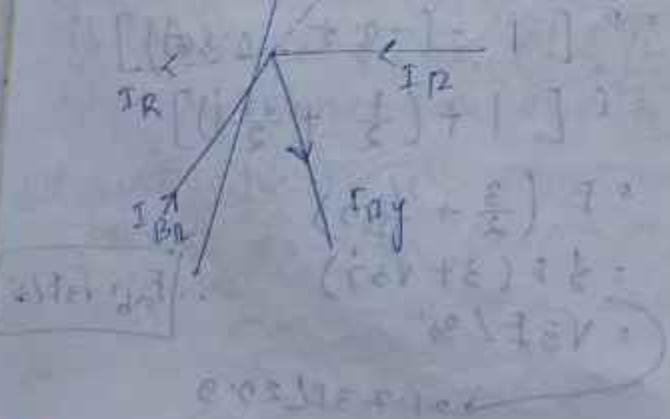

coherency

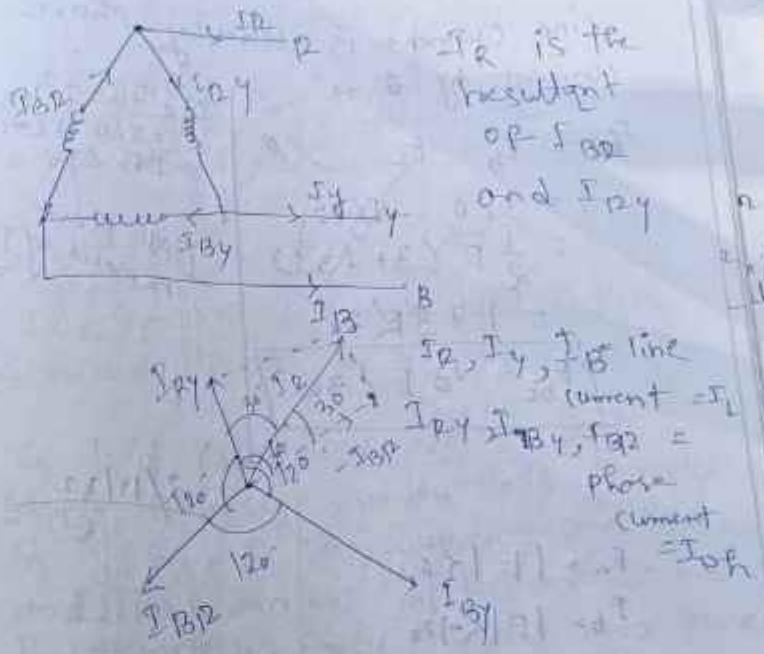

I_R is the resultant of I_{B1} and I_{B2}

I_R, I_Y, I_B line current = I_L
 I_B, I_B1, I_B2 phase current = I_{ph}

NOW,

$$I_R = \sqrt{(I_{B1})^2 + (I_{B2})^2 - 2 I_{B1} I_{B2} \cos 60^\circ}$$

$$\Rightarrow I_L = \sqrt{2 I_{ph}^2 + 2 I_{ph}^2 \times \frac{1}{2}}$$

$$= \sqrt{3 I_{ph}^2} \quad [I_L = I_{ph}]$$

∴ Line current is $\sqrt{3}$ times of phase current in magnitude.

line current is leading phase current by 60°

$$\begin{aligned} F_{bc} &= F_b - F_c \\ &\sim E/0^\circ - E/120^\circ \\ &= \frac{1}{\sqrt{3}} E (3 + \sqrt{3} j) \\ &= 1.73 E / 30^\circ \\ F_{bc} &= \sqrt{3} E / 30^\circ \end{aligned}$$

$$\begin{aligned} B &= I_B \angle -72^\circ \\ &= 120 \angle -12^\circ \\ &= 123 \angle 30^\circ \end{aligned}$$

[All Four
represent of T]

2/11/12

$$F_a = 1E / 0^\circ$$

$$F_b = 1E / -120^\circ$$

$$F_c = 1E / +120^\circ$$

$$I_a + I_b + I_c$$

$$> |I| [120 \angle 0^\circ + 120 \angle -120^\circ]$$

$$\begin{aligned} &> |I| [1 + (-0.5 - j0.86)] + (-0.5 + j0.86) \\ &> |I| [1 - j1.0] \\ &= 0 \end{aligned}$$


Sum of 3ph balance quantity = 0

Sum = 0


To 2nd part, we will be moving to 3rd part
of question in tomorrow's class

If sum isn't 0 then we need the 4th wire and that is neutral = n

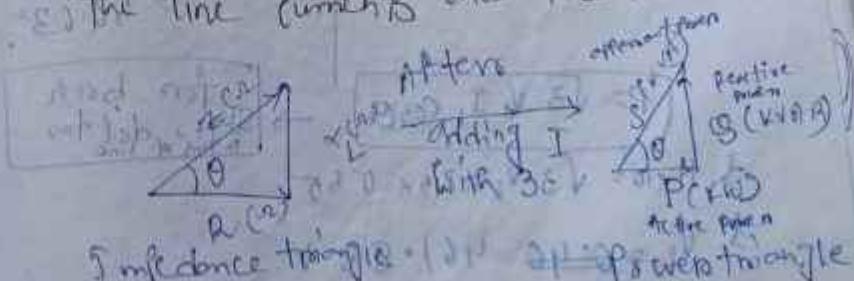- ① The load connected to a 3-ph supply comprises 3 similar coils connected in star. The line currents are 25 A and KVA and KW inputs are 20 and 11 respectively. Find the line and phase voltages, KVAR input and the resistance and reactance of each coil. Every coil is now connected in delta to this same 3-ph supply. Calculate the line currents and the powers taken.



$$V = \sqrt{P^2 + Q^2}$$

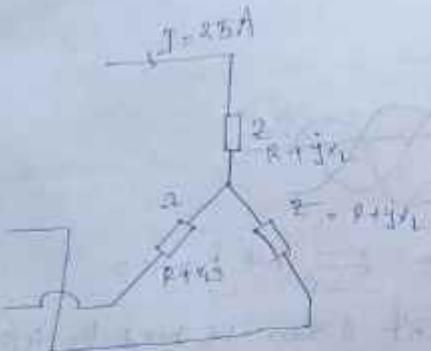

$$\begin{aligned} S &= I^2 \cdot Z \\ P &= I^2 \cdot R \\ Q &= I^2 \cdot X_L \end{aligned}$$

$$P = 11 \text{ kW}$$

$$S = 20 \text{ kVA}$$

$$\theta = \sqrt{S^2 - P^2} = 25^\circ$$

$$R = \frac{V}{I} = \frac{21}{2.5} = 8.4 \Omega$$

$$Q = I \cdot \sin \theta = 2.5 \cdot \sin 25^\circ = 1.06 \text{ kVAR}$$

at point 1, $\cos \theta = \frac{P}{S}$
 at point 2, $\cos \theta = \frac{P}{S}$
 at point 3, $\cos \theta = \frac{P}{S}$

$$P = \sqrt{3} V_L I_L \cos \theta$$

for both
start & del for
in terms of line

$$P = 11 \cdot 10^3 = \sqrt{3} V_L \cdot 2.5 \cdot 0.55$$

$$V_L = 6.46 \cdot 461.88 \text{ V}$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = 2.6667 \text{ V}$$

$$Z = \frac{V_{ph}}{I} = \frac{\sqrt{3} V_L}{2.5} = 21 \Omega$$

$$= \frac{2.6667}{2.5}$$

$$= 10.67 \Omega$$

$$R = 2 \cos \theta = 10.67 \times 0.55 = 5.87 \Omega$$

$$X_L = 2 \sin \theta = 10.67 \times 0.83 = 8.71 \Omega$$

$$\text{(ii) Point 2}$$

$$P_{ph} = \frac{P}{3} = \frac{3.6667}{3} = 1.22 \text{ kW}$$

$$= 3.6667 \text{ W}$$

$$= 366.67 \text{ mW}$$

$$P_{ph} = I_{ph}^2 \cdot R_{ph} \quad [R_{ph} = R]$$

$$366.67 \cdot (2.5)^2 \cdot R = 366.67 \text{ mW}$$


$$R = 5.87 \Omega$$

$$\frac{Q}{3} = Q_{ph} = \frac{(0.55 \times 10^{-3}) \times 2.5}{\sqrt{3}} = 38 \text{ mvar}$$

$$Q_{ph} = I_{ph}^2 \cdot X_L$$

$$16.7 \times 10^{-3} = (2.5)^2 \cdot X_L$$

$$X_L = 8.91 \Omega$$

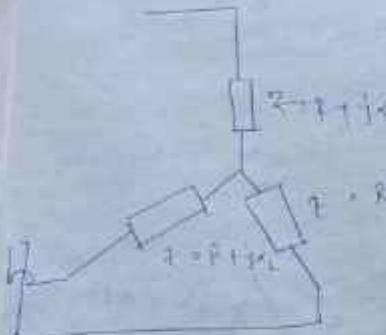

now, given line currents = 35A

$$I_B = I_A - I_C = 35A$$

Given, S = 20kVA
P = 11kW



$$\therefore \sqrt{S^2 - P^2} = 16.7 \text{ kVA P.D. (Ans)}$$

we have to get Φ line volt = V_{ph} , V_L

phase volt = $V_a, V_b, V_c = V_{ph}$

Now as E and Z are Smithsonians
all 3 coils are, the coils are
similar $V_a = V_b = V_c = V_{ph}$

$$V_{AB} = V_{BC} = V_{CA} = V_L$$

we have to find R, L

Now we know that

$$R = 3 \cos \theta, X_L = 3 \sin \theta$$

from Power triangle,

$$\tan \theta = \frac{S}{P} = \frac{16.7 \times 10^3}{11 \times 10^3}$$

$$\therefore \theta = 56.62^\circ$$

we know that $V_{ph} = ? \frac{10}{\sqrt{3}}$

we have to get V_{ph}
we also know that

$$P_L = \sqrt{3} V_{ph} I_L \cos \theta$$

Erased

$$\Rightarrow 11 \times 10^3 = \sqrt{3} \times V_L \times 2.5 \times 10^3 \quad (\text{Ans})$$

$$\therefore V_L = 461.72 \text{ V (Ans)}$$

$$V_L = \sqrt{3} V_{ph}$$

$$\therefore V_{ph} = \frac{V_L}{\sqrt{3}} \\ = 461.72 \text{ V}$$

$$V_{ph} = 266.57 \text{ V (Ans)}$$

$$\therefore 266.57 = 2 \times 25$$

$$\therefore t = 10.67 \text{ (Ans)}$$

$$R = 10.67 \times (0.3 + 0.67) \quad t_L = 10.67 \times 0.67 \\ = 5.8672 \Omega \quad = 8.952 \Omega$$

$\therefore I_{ph} = I_L$

For delta connection

$$\Rightarrow V_L = V_{ph} = 461.88 \text{ V}$$

$$I_{ph} = \frac{461.88}{Z} \quad [10 \angle 0^\circ]$$

$$= \frac{461.88}{10.67} = 43.28$$

$$I_L = \sqrt{3} \times 43.28 \quad [10 \angle 0^\circ]$$

$$= 74.97$$

$$= 75 \text{ A}$$

$$P = \sqrt{3} V_L I_L \cos \theta$$

$$= \sqrt{3} \times 461.88 \times 75 \times 0.55$$

$$= 32.09 \text{ kW}$$

(ii) $P_2 = 3 (I_{ph}^2 R)$ $\therefore P_2 = 3 P_{ph} = 3 (E_m^2 / Z)$

$$= 3 \times (43.28^2 \times 5.87)$$

$$= 33 \text{ kW}$$

Find the currents and power consumed by the unbalanced delta connection as shown

01/11/22



Power-factors = UPF, Lead, Lag
(PF)

$$\text{PF} = \cos \theta$$

$$= \frac{P}{S}$$

$$= \frac{P}{\sqrt{P^2 + Q^2}}$$

$$= \frac{P}{\sqrt{P^2 + (I^2 R)^2}}$$

$$= \frac{P}{I \sqrt{P^2 + I^2 R^2}}$$

$$= \frac{P}{I \sqrt{P^2 + V^2 / Z}}$$

$$= \frac{P}{V I}$$

is called unity PF

In Lag, $\theta = (V/I) \text{ rad} - 90^\circ$

$I = \frac{V}{2 \angle 0}$ (V is reference so the angle of V = 0
If $\theta > 90^\circ$ it will give negative)

In Lead, $\theta = -(\omega t) + 90^\circ$

Lead $\rightarrow I$ is leading V


$$\text{UPF} = 10^\circ, \text{Lag} = 10^\circ, \text{Lead} = 60^\circ$$

$$L = 1 - \cos \theta$$

$$= 1 - \cos 10^\circ$$

$$= 1 - 0.9848$$

$$= 0.0152$$

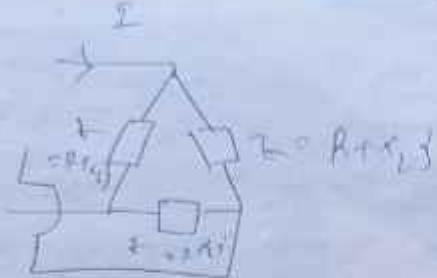

Everything will be same like

$$16.7 \text{ VAP}_2, 254.8 \Omega$$

but here $V_{ph} = V_L$ [as cos phi remain same]
 $V_L = 461.88$

$$V_{ph} = 461.88$$

Now, we know V_{ph} & I_{ph}

$$\text{Now } I_{ph} = I_{ph} \approx \sqrt{3}$$

$$\therefore I_{ph} = \frac{I_L}{\sqrt{3}} = \frac{254.8}{\sqrt{3}} = 144.3$$

$$\therefore 461.88 = 2 \times 144.3$$

~~2 - 32~~
we have to get line currents $I_a = I_b = I_c = ?$

and $P = ?$

i. We know that,

$$V_{ph} = 2 I_{ph}$$

$$\therefore \frac{461.88}{10.67} = I_{ph}$$

$$\therefore I_{ph} = 43.28 \text{ A}$$

$$\therefore I_L = \sqrt{3} \times 43.28 = 75 \text{ A (ans)}$$

$$\begin{aligned} P &= \sqrt{3} V_L I_L \cos \phi \\ &= \sqrt{3} \times 461.88 \times 75 \times \cos 60^\circ \\ &= 330 \text{ kW } \end{aligned}$$

$$I_R = 10 \angle -0.8^\circ = 10 \angle -36.87^\circ$$

$$I_y = 6 \angle 10^\circ \cos 10^\circ = 5 \angle 45.57^\circ$$

$$I_B = 7 \angle 0^\circ$$

at R, [As this connection is unbalanced so we can't apply KCL]

$$\begin{aligned} I_x &= -7 \angle 0^\circ + 10 \angle -36.87^\circ + 5 \angle 45.57^\circ \\ &= -7 + 8 - 6j \\ &= 1 - 6j \\ &= 6.08 \angle -80.5^\circ \end{aligned}$$

$$\begin{aligned} I_2 &= -I_x + I_y \\ &= 5 \angle 45.57^\circ - 10 \angle -36.87^\circ \\ &= 3.5 \angle 33^\circ - (8 - 6j) \end{aligned}$$

$$\begin{aligned} &= 3.5 \angle 33^\circ - 3.5j \\ &= 10.57 \angle 115.18^\circ \end{aligned}$$

$$\begin{aligned} I_3 &= I_B - I_y \\ &= 7 \angle 0^\circ - 5 \angle 45.57^\circ \\ &= 7 - (3.5 + 3.5j) \\ &= 3.5 - 3.57j = 4.9 \angle -0.21^\circ \end{aligned}$$

$$\begin{aligned} P_{A\text{phase}} &= |V_{AB}| |I_A| \cos \theta_A \\ &= 400 \times 10 \times \cos 0^\circ \\ &= 3200 \text{ W} \end{aligned}$$

[Magnitude of 5Ω] $\cos 0^\circ = 1$

$$\begin{aligned} P_{B\text{phase}} &= |V_{AB}| |I_B| \cos \theta_B \\ &= 400 \times 7 \times \cos 0^\circ \\ &= 1400 \text{ W} \end{aligned}$$


[$\cos 0^\circ = 1$] $\cos 0^\circ = 1$

$$\begin{aligned} P_{C\text{phase}} &= |V_{AB}| |I_C| \cos \theta_C \\ &= 400 \times 7 \times \cos 180^\circ \\ &= 2800 \text{ W} \end{aligned}$$

[As this unbalanced load is not in balance i.e. sum of the sum is not zero]

Total Power = $3200 + 1400 + 2800 = 7400 \text{ W}$

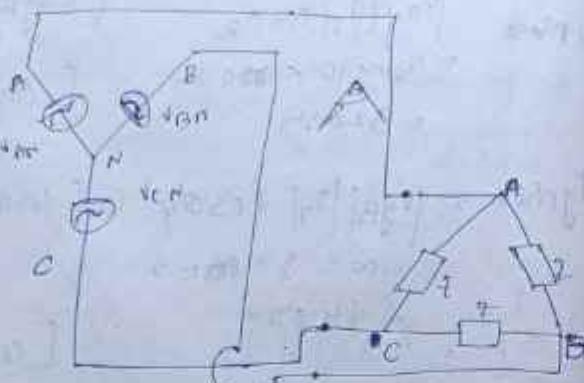- Q. One line voltage of a balanced star connected source is $V_{AB} = 240 \angle 0^\circ$. If this source is connected to a delta connected load of $20 \angle 40^\circ \Omega$. Find the phase and line currents. Assume A, B, C sequence.




$$V_{AB} = 240 \angle -20^\circ V$$

$$Z = 20 \angle 40^\circ \Omega$$

$$V_{BC} = 240 \angle -140^\circ V$$

$$V_{CA} = 240 \angle 100^\circ V$$

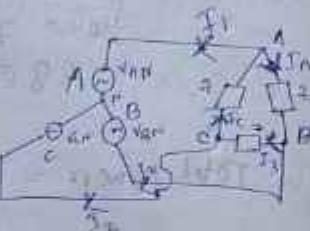

$$I_1 = \frac{V_{AB}}{Z} = \frac{240 \angle -20^\circ}{20 \angle 40^\circ} = 12 \angle -60^\circ A$$

$$I_{B2} = \frac{V_{BC}}{Z} = \frac{240 \angle -140^\circ}{20 \angle 40^\circ} = 12 \angle -180^\circ A$$

$$I_C = \frac{V_{CA}}{Z} = \frac{240 \angle 100^\circ}{20 \angle 40^\circ} = 12 \angle 60^\circ A$$

$$I_1 = I_C - I_A = 12 \angle 60^\circ - 12 \angle -60^\circ = 12 [1 \angle 60^\circ - 1 \angle -60^\circ] = 20.78 j = 20.78 \angle 90^\circ A$$

$$I_A = I_B$$

$$12 \angle -60^\circ = 12 \angle -180^\circ$$

$$= 6 \angle 10.39^\circ + j12 [1 \angle -120^\circ - 12]$$

$$= 20.78 \angle -30^\circ A$$

$$= 12 \sqrt{3} \angle -30^\circ A$$

(As 1 is balanced
So we can
apply
 $I_1 = 12 \angle 60^\circ$
as current
is
leading
by
30°)

$$I_3 = I_B - I_C$$

$$12 \angle -180^\circ - 12 \angle 60^\circ$$

$$= -12 - (6 + j10.39)$$

$$= -18 - 10.39 j$$

$$= -(18 + 10.39 j)$$

$$= -12 \sqrt{3} \angle 30^\circ A$$

$$= 12 \sqrt{3} \angle -150^\circ A$$

- ③ An unbalanced three-wire star connected load has balanced line voltages of 240 V. The load impedances are


$$Z_A = (10 + 3j) \Omega, Z_B = (3 - 8j) \Omega, Z_C = (10 + 4j) \Omega$$

Calculate the line currents, neutral current and the power in each phase. Phase sequence is A, C, B.

$$V_{AB} = 400 \angle 0^\circ$$

$$V_{BC} = 400 \angle +120^\circ \text{ (since } A-C, B)$$
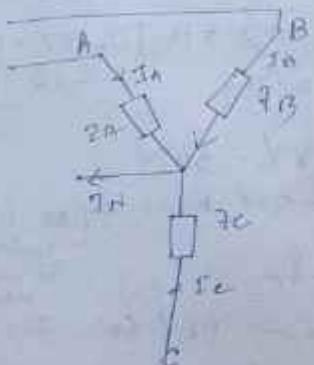
$$V_{CA} = 400 \angle -120^\circ \quad [A-B]$$




$$I_A = \frac{V_{AB}}{Z_A} = \frac{400}{\sqrt{3}} \angle -30^\circ \text{ (phase voltage)} \\ = 22.12 \angle -46.7^\circ \text{ A}$$

$$I_B = \frac{V_{BC}}{Z_B} = \frac{400}{\sqrt{3}} \angle +120^\circ - 30^\circ \\ = 22.12 \angle +150^\circ \text{ A}$$

$$I_C = \frac{V_{CA}}{Z_C} = 22.12 \angle 150^\circ + 30^\circ \text{ A}$$
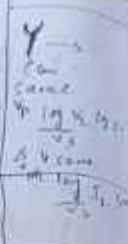
$$I_A = \frac{V_{CA}}{\sqrt{3} Z_A} = \frac{400}{\sqrt{3} Z_A} \angle 120^\circ - 30^\circ \\ = 22.12 \angle 21.8^\circ \text{ A}$$



$$I_N = I_A + I_B + I_C$$

$$= 22.12 \angle -46.7^\circ + 22.12 \angle 150^\circ + 22.12 \angle 21.8^\circ$$

$$= 15.17 \angle 16.1^\circ + 25.34 \angle 51.3^\circ$$

$$= 21.22 \angle 3.05^\circ$$

$$= 31.35 \angle 21.8^\circ \text{ in per phase}$$

$$= 30.5 \angle 21.8^\circ + 30.5 \angle 21.8^\circ$$

$$= 30.5 \angle 43.6^\circ \text{ total line current}$$

Power in each phase -

$$P_A = |I_A|^2 R_A = (22.12)^2 \times \frac{10}{3} = 4.832.9 \text{ W}$$

$$P_B = |I_B|^2 R_B = (22.12)^2 \times 3 = 2.2 \text{ kW}$$

$$P_C = |I_C|^2 R_C = (22.12)^2 \times 10 = 4.5 \text{ kW}$$

$$(a) P_A = V_{AB} |I_A| \cos \theta_A = \frac{400}{\sqrt{3}} \times 22.12 \times \cos(-46.7^\circ)$$

$$P_B = V_{BC} |I_B| \cos \theta_B = \frac{400}{\sqrt{3}} \times 22.12 \times \cos(150^\circ)$$

$$P_C = V_{CA} |I_C| \cos \theta_C = \frac{400}{\sqrt{3}} \times 22.12 \times \cos(21.8^\circ)$$

$$= 350.3 \text{ W}$$

$$= 5845.3 \text{ W}$$

$$= 10000 \text{ W}$$


$$I_A = 230 \times 22.12 \times \cos 16.7^\circ = 4.9 \text{ A}$$

$$P_A = 230 \times 22.12 \cos(60.45) = 22 \text{ W}$$

$$P_B = 230 \times 21.45 \cos(21.8^\circ) = 4.6 \text{ W}$$

H.W.

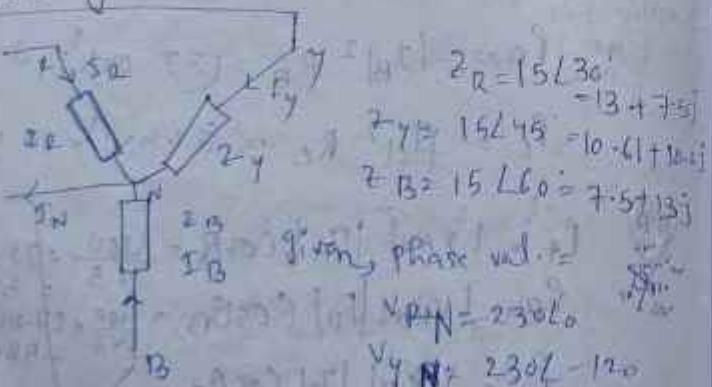- ① A 3-phase 4-wire system having a 230V phase voltage as the following loads connected between the respective lines and neutral $Z_R = 15L30^\circ \Omega$, $Z_Y = 15L45^\circ \Omega$, $Z_B = 15L60^\circ \Omega$. Calculate the current in the neutral wire and power taken by each load.



To calculate the currents I_{RN}, I_{YN}, I_{BN} (no header),
positive I_R, I_Y, I_B and P_{RN}, P_{YN}, P_{BN}

$$I_R = \frac{V_{PN}}{Z_R} = \frac{230L}{15L30} = 15.33L - 30^\circ$$

$$I_Y = \frac{V_{YN}}{Z_Y} = \frac{230L}{15L45} = 15.33L - 30^\circ$$

$$I_B = \frac{V_{BN}}{Z_B} = \frac{230L}{15L60} = 15.33L - 105^\circ$$

$$I_R = 15.33L - 105^\circ$$

$$I_B = \frac{V_{BN}}{Z_B} = \frac{230L}{15L60} = 15.33L - 105^\circ$$

$$I_R = 15.33L - 105^\circ$$

$$I_N = I_R + I_Y + I_B = 15.33L - 105^\circ + 15.33L - 30^\circ + 15.33L - 105^\circ = 45.99L - 105^\circ$$

$$= 6.135 + j0.51$$

$$= 6.135 + j0.51$$

$$P_{RN} = P_{RN} + P_{YN} + P_{BN}$$

$$\text{for Star connection } I_{RN} = I_R$$

$$I_{RN} = I_R = 15.33L - 105^\circ$$

$$I_{YN} = I_Y = 15.33L - 30^\circ$$

$$I_{BN} = I_B = 15.33L - 105^\circ$$


$$P_{RN} = P_{RN} + P_{YN} + P_{BN}$$

$$= |I_R|^2 \cdot P_R + (I_{RN})^2 \cdot P_R + (I_{RN})^2 \cdot R \cdot B$$

$$= (15.33)^2 \cdot P_R + (15.33)^2 \cdot P_Y + (15.33)^2 \cdot P_B$$

$$= (15.33)^2 [13 + 10.61 + 7.5] = 7.3420$$

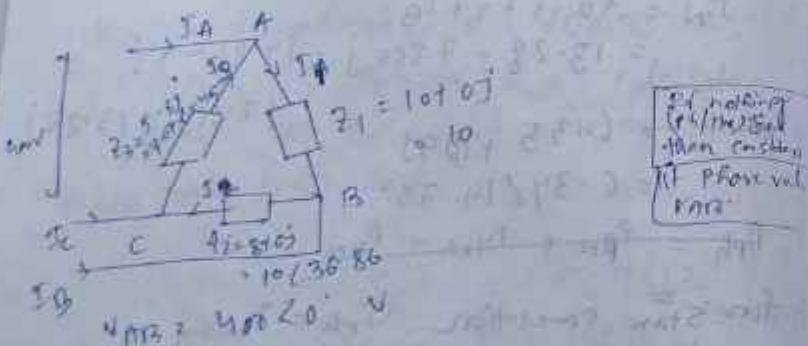(4) 3 impedances Z_1 , Z_2 and Z_3 are delta connected to a symmetrical 3-ph 400V source supply of phase sequence A-B-C. $Z_1 = 10 + j0 \Omega$ connected between lines A and B, $Z_2 = 8 - j0 \Omega$ connected between lines B and C and $Z_3 = 5 - j1.2 \Omega$ connected between line C and A. Calculate the phase and line currents and the total active power consumed. Draw the phasor diagram.



$$I_1 = \frac{V_{AB}}{Z_1} = \frac{400\angle 0^\circ}{10} = 40 \text{ A}$$

$$I_2 = \frac{V_{BC}}{Z_2} = \frac{400\angle -120^\circ}{8} = 50 \angle -136.86^\circ \text{ A}$$

$$I_3 = \frac{V_{CA}}{Z_3} = \frac{400\angle 120^\circ}{5 - j1.2} = 56.92 \angle 165^\circ \text{ A}$$

$$I_A = I_1 - I_3 = 40 - 56.92 \angle 165^\circ$$

$$I_B = I_2 - I_1 = 50 \angle -136.86^\circ - 40 \angle 0^\circ = 50 \angle -14.63^\circ \text{ A}$$

$$I_C = I_3 - I_2 = 56.92 \angle 165^\circ - 50 \angle -136.86^\circ = 56.92 \angle 111.57^\circ \text{ A}$$

$$= 56.92 \angle 14.63^\circ + 36.78 \angle 90^\circ - 115.73^\circ$$

$$= -17.87 + 30.37j$$

$$= 33.15 \angle 120.5^\circ \text{ A}$$

Total 3-ph Power

$$P_0 = (I_1)^2 R_A + (I_2)^2 R_B + (I_3)^2 R_C$$

$$P_0 = (40)^2 \cdot 10 + (50)^2 \cdot 8 + (56.92)^2 \cdot 5$$

$$= 1600 + 12800 + 14033.1$$

$$= 4343.73 \text{ kW}$$

(4)

Calculate
[If said, get the power then
by default calculate phase]

Note

(i) identify if nothing is said (whether by Laplace or by ac circuit)

(ii) AC cut \rightarrow AC source will be there
and will be given in the form of voltage, capacitor
and inductor will be given.

After Laplace transform \rightarrow there will not be
any AC source, there will be DC source.
The can be given like $-0.1F$, Inductances
will be given like $5H$. The terms those
are used in Laplace will be given there
is $u(t)$, $\delta(s)$, $v(t)$, $i(t)$, $u(s)$, $i(s)$, $I(t)$
etc. [Switch may be given]

③ for 3-phase, all the terms of 3-ph
like Star connection, Delta connection,
4-wire system, load, phase volt,
phase curr, line volt, line curr, neutral current,
power concn etc will term will be
there.

④ for 2-pants, you can easily identify
them by the term 7th & 8th of parameters
etc

EEA Previous year

Q1. Find the Laplace transformation of fig.



$$u(t) = 2R(U(t)) = 2R(t-3) + 2R(t-4)$$

$$u(t) = 2t u(t) = 2(t-1)U(t-1) - 2(t-3)$$

$$u(t) = 2(t-3) + 2(t-1)U(t-4)$$

Applying Laplace on both sides,

$$U(s) = 2 \left[\frac{1}{s} - 1 - \frac{1}{s-3} - \frac{1}{(s-1)^2} \right] e^{-5s}$$


$$U(s) = \frac{1}{(s-3)^2} e^{-5s} + \frac{1}{(s-1)^2} e^{-5s}$$

$$U(s) = \frac{2}{s^2} \left[\frac{1}{s} - 1 - \frac{e^{-5s}}{s-3} - \frac{e^{-5s}}{(s-1)^2} \right]$$

$$U(s) = \frac{2}{s^2} \left[\frac{1}{s} - 1 - \frac{e^{-5s}}{(s-3)(s-1)^2} \right]$$


$$U(s) = \frac{2}{s^2} \left[\frac{1}{s} - 1 - \frac{1}{(s-3)^2} e^{-5s} \right]$$
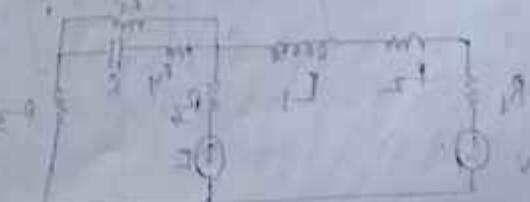
$$U(s) = \frac{2}{s^2} \left[\frac{1}{s} - 1 - \frac{1}{(s-3)^2} e^{-5s} \right]$$



$$= \frac{1}{(5-3)^2} e^{-3s} \cdot \frac{1}{s} + \frac{1}{(5-s)^2}$$

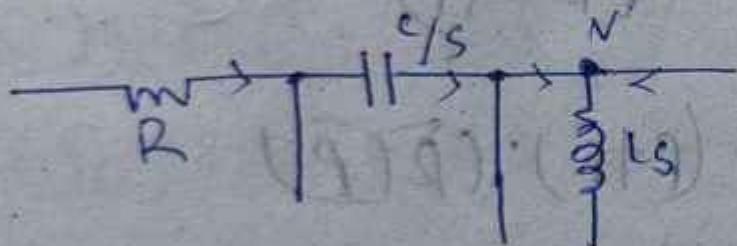Normal KCL will be applicable for a circuit
 for replace +. KCL will apply, but we will
 consider all resistance, inductance, capacitor.



$$\frac{V}{R + \frac{c}{s} L s}, \text{ since that}$$

$$\begin{aligned}
 & \cancel{P\bar{S} + P} + \cancel{P\bar{R} + \bar{S}} \\
 &= P\bar{S} + P\bar{R} + \cancel{P} + \cancel{(\bar{S}\bar{R})} \\
 &= (\cancel{P\bar{S} + P})(P\bar{S} + \cancel{(\bar{S}\bar{R})} + \cancel{P\bar{R} + P}) \\
 &\stackrel{*}{=} (\cancel{P\bar{S} + P}) \cdot (\cancel{P\bar{S} + P}) + (\cancel{P + \bar{P}}) \cdot (\cancel{\bar{R} + P}) \\
 &= (P + S) \cdot (\bar{S} + R) (\cancel{P + R}) + \cancel{R + P}
 \end{aligned}$$



State Dirichlet's conditions for a function to be expanded as a Fourier series.

Fourier series in general tends to converge slowly. In order for a function to be expanded properly, it must satisfy the following:

Dirichlet conditions: A piecewise function must be periodic with at most a finite number of discontinuities and/or a finite number of minima or maxima within one period.

(ii) Inc. mat.

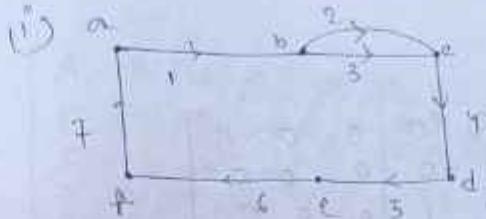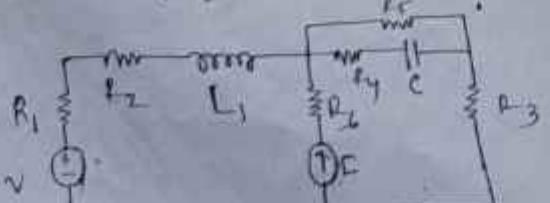- (i) For the cut shown in fig (i) draw the oriented graph and write the
 (ii) incidence matrix, (iii) f-cutset matrix,
 (iv) How many trees are possible from the graph of networks?



[the orientation is arbitrary]

Incidence matrix,

$$A = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 \\ a & +1 & 0 & 0 & 0 & 0 & -1 \\ b & -1 & +1 & +1 & 0 & 0 & 0 \\ c & 0 & -1 & -1 & +1 & 0 & 0 \\ d & 0 & 0 & 0 & -1 & +1 & 0 \\ e & 0 & 0 & 0 & -1 & +1 & 0 \\ f & 0 & 0 & 0 & 0 & 0 & -1 & +1 \end{bmatrix}$$

(ii) no. of trees possible $\det\{A(0,1)\}$

$$A = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & -1 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix}$$

$$A^T = \begin{bmatrix} 1 & -1 & 0 & 0 & 0 & 0 \\ 0 & 1 & -1 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 & 0 & 0 \\ 0 & 0 & 0 & 1 & -1 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \\ -1 & 0 & 0 & 0 & 0 & 1 \end{bmatrix}$$

$A \rightarrow PAJ_1$

$$A = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & -1 \\ -1 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & -1 & -1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & -1 & 1 & 0 \end{bmatrix}$$

$$\times \begin{bmatrix} 1 & -1 & 0 & 0 & 0 & 0 & 1 \\ 0 & 1 & -1 & 0 & 0 & 0 & 0 \\ 0 & 1 & -1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & -1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ -1 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & -1 & 0 & 0 & 0 & 0 & 1 \\ -1 & 1 & -1 & 0 & 0 & 0 & 0 \\ 0 & -1 & -1 & 1 & 0 & 0 & 0 \\ 0 & 0 & -1 & 1 & -1 & 0 & 0 \\ 0 & 0 & 0 & -1 & 1 & -1 & 0 \\ 0 & 0 & 0 & 0 & -1 & 1 & 0 \end{bmatrix}$$

$$= \begin{bmatrix} 2 & -1 & 0 & 0 & 0 & 0 & 1 \\ -1 & 3 & -2 & 0 & 0 & 0 & 0 \\ 0 & -2 & 3 & -1 & 0 & 0 & 0 \\ 0 & 1 & -1 & 2 & -1 & 0 & 0 \\ 0 & 0 & 0 & -1 & 1 & -1 & 0 \end{bmatrix}$$

$$= \begin{bmatrix} 2 & -1 & 0 & 0 & 0 & 0 & 1 \\ 0 & 5 & -4 & 0 & 0 & 0 & 0 \\ 0 & -2 & 3 & -1 & 0 & 0 & 0 \\ 0 & 0 & -1 & 2 & -1 & 0 & 0 \\ 0 & 0 & 0 & 1 & 2 & 0 & 0 \end{bmatrix}$$

$[P_2' = 2P_2 + P_1]$

→ next move of
this step

$$= \begin{bmatrix} 1 & -1 & 0 & 0 & 0 & 0 & 1 \\ -2 & 3 & -2 & 0 & 0 & 0 & 0 \\ -2 & -2 & 3 & -1 & 0 & 0 & 0 \\ 0 & 0 & -1 & 2 & -1 & 0 & 0 \\ 0 & 0 & 0 & -1 & 2 & 0 & 0 \end{bmatrix}$$

$[C_1 \leftarrow C_1 - C_2]$

$$= \begin{bmatrix} 1 & -1 & 0 & 0 & 0 & 0 & 1 \\ 0 & 5 & -2 & 0 & 0 & 0 & 0 \\ 0 & -4 & 3 & -1 & 0 & 0 & 0 \\ 0 & 0 & -1 & 2 & -1 & 0 & 0 \\ 0 & 0 & 0 & -1 & 2 & 0 & 0 \end{bmatrix}$$

$[P_2' = P_2 - 2P_1]$

$[P_3' = P_2 + 2P_1]$

$$= \begin{bmatrix} 5 & -2 & 0 & 0 & 0 & 0 & 1 \\ -4 & 3 & -1 & 0 & 0 & 0 & 0 \\ 0 & -1 & 2 & -1 & 0 & 0 & 0 \\ 0 & 0 & -1 & 2 & 0 & 0 & 0 \\ -2 & 5 & 0 & 0 & 0 & 0 & 0 \\ 3 & -4 & -1 & 0 & 0 & 0 & 0 \\ -1 & 0 & 2 & -1 & 0 & 0 & 0 \\ 0 & 0 & -1 & 2 & 0 & 0 & 0 \end{bmatrix}$$

$$\begin{bmatrix} -2 & 5 & 0 & 0 \\ -1 & -4 & 2 & -1 \\ 3 & -4 & 1 & 0 \\ 0 & 0 & -1 & -2 \end{bmatrix}$$

$$\begin{bmatrix} -1 & 0 & 2 & -1 \\ -2 & 5 & 0 & 0 \\ 3 & -4 & 1 & 0 \\ 0 & 0 & -1 & 2 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 0 & -2 & 1 \\ -2 & 5 & 0 & 0 \\ 0 & 4 & 1 & 0 \\ 0 & 0 & 1 & -2 \end{bmatrix}$$

$$\begin{aligned} R_2' &= R_2 - 2R_1 \\ R_3' &= R_3 + 3R_1 \end{aligned}$$

$$\begin{bmatrix} 1 & 0 & -2 & 1 \\ 0 & -5 & 4 & -2 \\ 0 & 4 & -5 & 3 \\ 0 & 0 & 1 & -2 \end{bmatrix}$$

$$\begin{bmatrix} -5 & 4 & -2 \\ 4 & -5 & 3 \\ 0 & 1 & -2 \end{bmatrix}$$

$$\begin{aligned} &= \begin{vmatrix} -5 & 4 & -2 & 1 \\ 0 & -5 & 4 & -2 \\ 0 & 4 & -5 & 3 \\ 0 & 0 & 1 & -2 \end{vmatrix} \\ &\text{using Sarrus rule} \end{aligned}$$

$$= -5(10 - 3) + 4(-8 - 0) - 2(4 - 0)$$

$$= -5 \times 7 + 4 \times 2 - 8$$

$$= -35 + 8 - 8$$

n no. of times one possible.




$$\begin{array}{c} \text{Let } C = \begin{pmatrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 \\ 0 & 1 & 0 & 0 & 0 & 0 & -10 \\ 0 & 0 & 0 & 0 & 0 & 0 & 11 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 11 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 10 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{pmatrix} \\ \text{and } B = \begin{pmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 11 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 10 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{pmatrix} \end{array}$$


this is the cut-set matrix

Qn-B

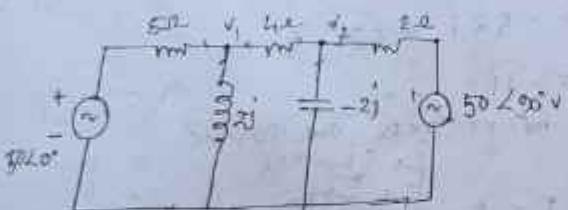2) what is super node in electrical circuit? In the network shown in the fig: find the node voltages v_1 and v_2 and current in the branch with the resistor 4Ω .



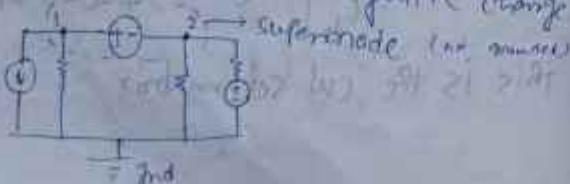* In cut theory, a supernode is a theoretical construct that can be used to solve a cut. This is done by viewing a voltage source on a wire as a point source voltage in relation to other point voltages located at various nodes in the cut, relative to a ground node assigned a zero or negative charge.



$$\frac{v_1 - 50\angle 0^\circ}{5} + \frac{v_1}{2j} + \frac{v_1}{4} = 0$$

$$\Rightarrow \frac{v_1 - 50}{5} + \frac{v_1}{2j} + \frac{v_1}{4} = 0$$

$$\therefore v_1 \left(\frac{1}{5} + \frac{1}{2j} + \frac{1}{4} \right) = \frac{50}{5} = 10$$

$$\therefore v_1 \left(0.45 + \frac{1}{2j} \right) = 10$$

$$\therefore v_1 \left(0.45 + 0.5j - j \right) = 10$$

$$\therefore v_1 = \frac{10}{0.45 - 0.5j}$$

$$= \frac{10}{0.67 - 0.48}$$

$$v_1 = 15\angle 48^\circ$$

$$v_1 = 10\angle 0^\circ + 14\angle 48^\circ$$

$$\frac{v_2}{4} + \frac{v_2}{-2j} + \frac{v_2 - 50\angle 90^\circ}{2} = 0$$


$$\therefore \frac{v_2}{4} + \frac{v_2}{-2j} + \frac{v_2 - 50j}{2} = 0$$

$$\therefore 2 \left(\frac{1}{4} - \frac{1}{2j} + \frac{1}{2} \right) = \frac{50j}{2} = \frac{50\angle 90^\circ}{2}$$


$$\therefore 2 \left(0.75 - \frac{1}{2j} \right) = 25\angle 90^\circ$$

$$\therefore 2 \left(0.75 + 0.5j - j \right) = 25\angle 90^\circ$$
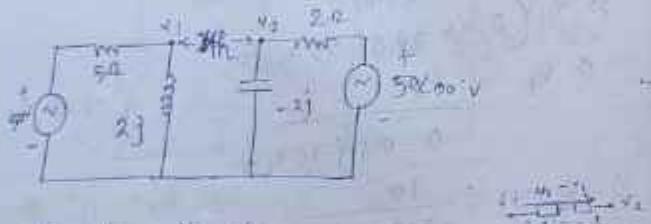
$$\begin{aligned} V_2 &= 2.6230^\circ \\ &= 0.95 + j0.5j \\ &= 2.6230^\circ \\ &= 0.95 + j0.5j \\ &= 27.78 \angle 56.31^\circ \\ &= 15.41 + j23.13 \end{aligned}$$


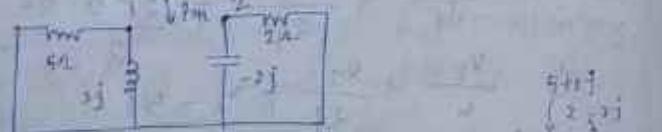
$$\begin{aligned} V_H &= V_{12} = V_1 - V_2 \\ &= (10.03 + j11.1j) - (15.41 + j23.10j) \\ &= -5.38 - j12.01j \\ &= -(5.38 + j12.01j) \end{aligned}$$



$$\begin{aligned} V_H &= (5 + 2j) + (2 - 2j) \\ &= 7\Omega \\ \therefore \text{Equivalent Ind.} & \quad [\text{Load resistance } -1\Omega] \\ & \quad \quad \quad \text{Inductance } 7\Omega \end{aligned}$$

$$\begin{aligned} I_L &= \frac{V_{12}}{Z_{L+2j}} \\ &= \frac{-(5.38 + j12.01j)}{4 + j7} \\ &= \frac{-29.78 / 56.31}{4 + j7} \\ &= -7.52 \angle 111.11^\circ \\ \text{Current } I_L &= -13.184 / 65.86^\circ \\ &= -1.19 \angle 65.86^\circ \\ &= 0.48 + j1.08 \end{aligned}$$

write the difference between independent and dependent voltage source.

Independent voltage source

1) Definition - done

2) It is denoted normally the middle symbol is the symbol for a specific type of inde-

1. S.

3) It is also termed as "Constant Source" or "Time Variant Source".

1) definition - done
or mentioned
2) It is denoted by diamond shape.

3) Here, there is no such term.

it has no types

Independent Current Source

- 1) Definition - done
- 2) The symbol of this is a circle with an arrow inside is the symbol to indicate the direction of the current flow.

- 3) It has no types



4) It has 2 types of dependent voltage source - CCVS, VCVS

Dependent Current Source

- 1) Definition - done
- 2) It is represented by diamond shape.

- 3) There have 2 types of dependent current source - CCVS, VCIS

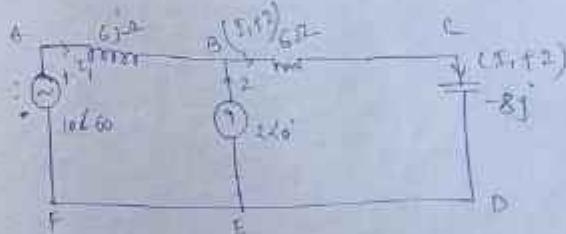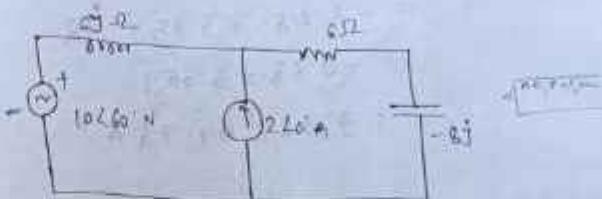3) b) Find the current through 6Ω resistor shown in Fig. using the mesh analysis. Here, voltage source is $10\angle 60^\circ$ V and current source is $2\angle 60^\circ$ A.



A B C D E F A, B, C,

$$6j + I_1 + 5(5I_1 + 2) + -8j(5I_1 + 2) = 10\angle 60^\circ$$

$$\Rightarrow 6j + I_1 - 8j + 5I_1 + 10\angle 60^\circ - 16j = 10\angle 60^\circ$$

$$\Rightarrow -25j + 6j + I_1 + 12 = 10\angle 60^\circ$$

$$\Rightarrow I_1(6-2j) + 12 - 16j = 10\angle 60^\circ$$

$$\Rightarrow I_1(6-2j) = 5 + 8j - 12 + 16j = 7 + 24j \angle 67^\circ$$

$$\Rightarrow I_1(6-2j) = \frac{7+24j}{6-2j} =$$

$$= 0.25 + j 105.84$$

$$0.322 - j 8.43$$

$$= 4.056 \angle 114.27^\circ$$


The current flowing 6.2 position

$$I_{12} = 4.056 / 174.22^\circ$$

$$= -2.28 + 3.35j \text{ A}$$

$$= -0.28 + 3.35j$$

$$= 3.30 \angle 94.78^\circ$$

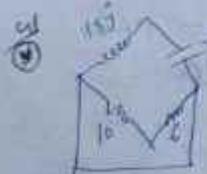

$$Z_{TH} = \frac{7.3 \times 14}{16.07j} = 7.186 \angle 102.1^\circ$$


$$= 12.46 \angle 23.02^\circ$$

$$= 2.56 + 5.37j$$



$$\text{The current through } (5\text{mH}) \text{ inductor} = \frac{151.78}{5 + 2.56 + 4.9 + 5.37j}$$

$$= \frac{151.78}{12.43 + 9.83j} = 12.43 \angle 23.02^\circ$$

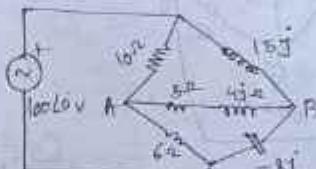Q1 State Thevenin's theorem. Find the current in the (5mH) -in inductor connected between A and B in the circuit shown in Fig. using Thevenin's theorem.




Q done

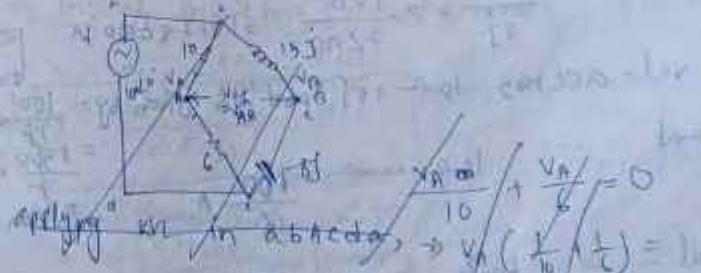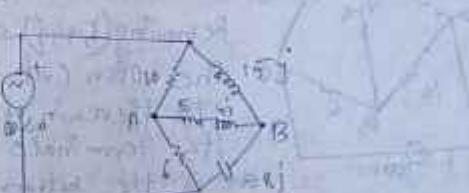

$$= 11.926 - 52.54j = 7.27 - 9.46j \text{ A}$$

Current in the branch between A and B in the circuit shown in Fig. using Thevenin's theorem

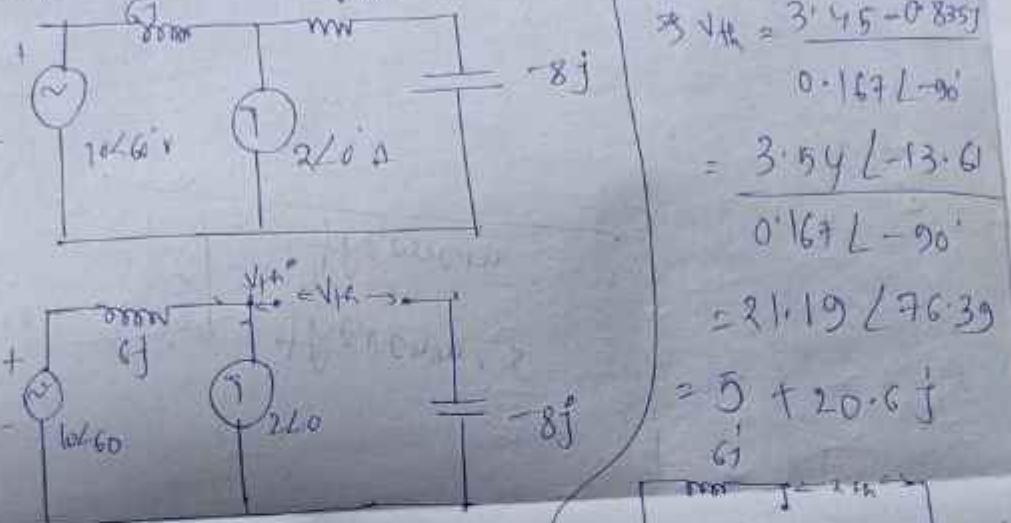Find the current through the two resistors using Thevenin's theorem



$$V_{th} = \frac{3.45 - 0.835j}{0.167 L - 90^\circ}$$

$$= 3.54 L - 13.6^\circ$$

$$0.167 L - 90^\circ$$

$$= 21.19 L 76.39^\circ$$

$$= 5 + 20.6j$$



$$\frac{V_{th} - 10\angle 60^\circ}{6j} = 2L_0$$

$$\Rightarrow V_{th} \left(\frac{1}{6j} \right) = 2L_0 + \frac{10\angle 60^\circ}{6j}$$

$$\Rightarrow V_{th} \left(\frac{1}{6jL_0} \right) = 2 + \frac{10\angle 60^\circ}{6jL_0}$$

$$\Rightarrow V_{th} \times 0.167 L - 90^\circ = 2 + 1.47 L - 30^\circ$$

$$\Rightarrow V_{th} \times 0.167 L - 90^\circ = 2 + 1.47 - 0.835j$$

$$\Rightarrow V_{th} \times 0.167 L - 90^\circ = 3.45 - 0.835j$$

$$I_L = 6j - 8j$$

$$= -2j$$

$$I_L = \frac{V_{th}}{6j + R}$$

$$= \frac{21.19 L 76.39^\circ}{6j + R}$$



$$= \frac{21.19 L 76.39^\circ}{6 - 2j}$$

$$= 21.19 L 76.39^\circ$$

$$= 6.32 L - 18.43^\circ$$

$$= 3.35 L 76.39^\circ$$
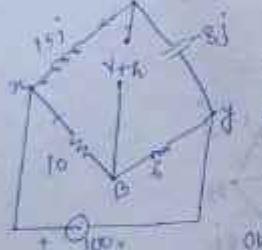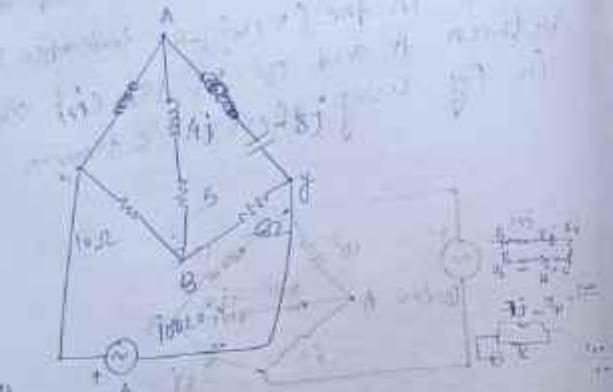
$$11.92 L - 52.54^\circ = 7.24 - 9.46 j A$$



Removing $(15\angle 0^\circ)$ load
the open cut voltage/
OTPV between vol. across
its terminals is being
obtained in the network of which

The current through $15\angle 0^\circ$ load is obtained as

$$\Rightarrow \frac{100}{7j} = \frac{100}{7+9j} = 14.28 \text{ A}$$

vol. across to $15\angle 0^\circ$ load is given by = $\frac{100}{7j+15j} = 10\angle -90^\circ$

$$(\text{current}) = 10\angle -90^\circ - \frac{100}{16} = \frac{100}{16} \angle -90^\circ = 6.25 \text{ A}$$

$$\text{vol. } = \frac{100}{16} = \frac{100}{16} \times 10 = \frac{1000}{16} = 62.5 \text{ V}_{AB}$$

$$\therefore V_{AB} = V_m - V_{B_N} = \frac{1500}{7} - \frac{1000}{16} = 151.78 \text{ V}$$

Ques Evaluate Laplace Transform of

$$\sin^3 t$$

$$\mathcal{L}[\sin^3 t] = \frac{1}{2j} [e^{j\omega t} - e^{-j\omega t}]$$

$$\therefore \sin^3 t = \frac{1}{2j} (e^{jt} - e^{-jt})$$

$$\text{Ques } \sin^3 t = \frac{1}{3}(1 - \cos 2t) = \frac{1}{3}[wt - \cos 2t]$$

$$\mathcal{L}[\sin^3 t] = \frac{1}{3} \left[\frac{1}{s} - \frac{s}{s^2 + 4} \right]$$

the Laplace transformation

$$\text{of } \sin^3 t = \frac{1}{3} \left[\frac{1}{s} - \frac{s}{s^2 + 4} \right] \quad [\because \cos wt = \frac{s}{s^2 + w^2}]$$



Ques

A series R-L circuit shown in fig experiences an exponential voltage $V = 10e^{-100t} \text{ V}$ after closing the switch $t=0$. Find the expression for current $i(t)$ using Laplace transform. Assume zero initial inductor current before switching.



Before switching $t=0^-$

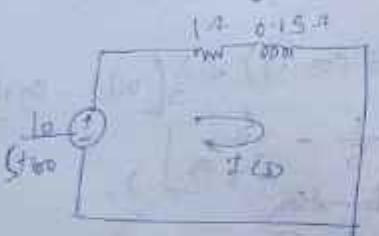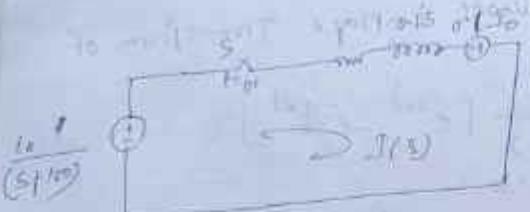$i(s)$ transforming the circuit into Laplace domain -



$$Y(s) = \frac{I_1}{(S110)(1 + S12)}$$

$$\text{Converting to time domain: } Y(t) = -1.11 e^{-1.11t} \quad (\text{from } S110)$$

$$Y(t) = \frac{I_1}{(S110)(1 + S12)} = \frac{100}{(S110)(S110 + S12)}$$

$$A = \frac{100 + S12}{(S110)(S110)} \quad B = \frac{100}{S110}$$

$$A = \frac{100 + (-1.11)}{(-1.11)(-1.11)} = -1.11$$

$$B = \frac{100}{-1.11} = -90$$

$$Y(s) = \frac{100}{(S110)(S110 + S12)} = \frac{100}{S110^2 + S110}$$

$$Y(t) = -1.11 e^{-1.11t} \quad (\text{from } S110)$$


$$Y(t) = -1.11 e^{-1.11t} \quad (\text{from } S110)$$

$$Y(t) = \frac{100}{(S110)(S110 + S12)} \quad |s = -1.11$$

$$Y(t) = \frac{100}{100} = 1.11$$

$$Y(t) = 1.11$$

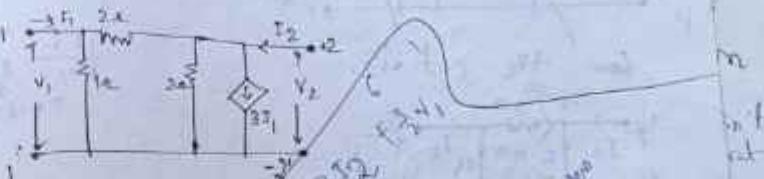Q: Why do we need two port networks?
For the network shown in the fig.
find Z-parameters.



This allows the response of the network to signals applied to signals at the ports to be calculated easily, without solving for all the internal voltages and currents in the network. It also allows similar circuits on devices to be compared easily.

→ This allows the whole line select previous line and others


→ This allows the whole line select previous line and others

→ This allows the whole line select previous line and others

→ This allows the whole line select previous line and others

→ This allows the whole line select previous line and others

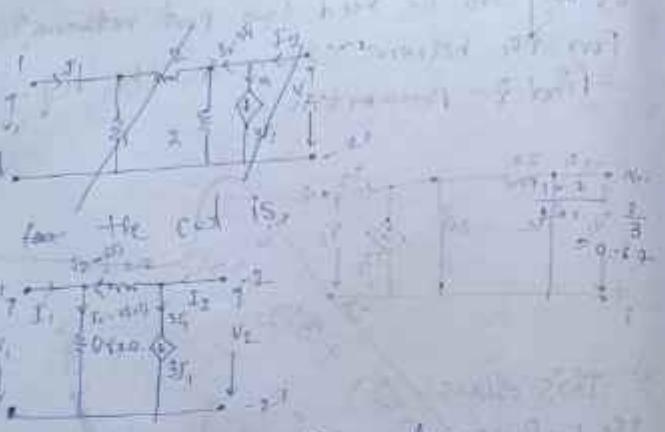→ This allows the whole line select previous line and others



defining α_{123} & γ Parameters,

$$(V_1, V_2, T_1, T_2)$$

$$V_1 = 2\alpha_{123}T_1 + T_2 \quad \text{--- (1)}$$

$$V_2 = 2\alpha_{123}T_2 + T_1 \quad \text{--- (2)}$$

$$V_1 = 0.67(T_2 - 2T_1) \quad \text{--- (3)}$$

$$V_1 = -1.34T_1 + 0.67T_2 \quad \text{--- (4)}$$

$$\begin{aligned} V_2 &= 2(T_2 - 2T_1) + 0.67(T_2 - 2T_1) \\ &= -(T_1 - 1.34T_1 + 2T_2 + 0.67T_2) \end{aligned}$$

$$V_2 = -1.34T_1 + 2.67T_2 \quad \text{--- (5)}$$

Comparing (1) and (4) we get

$$\begin{aligned} T_1 &= -1.34T_2, \quad T_2 = 0.67T_1 \\ \text{Comparing (4) and (5) we get,} \end{aligned}$$

$$\alpha_{123} = -1.34, \quad \alpha_{123} = 2.67 - 2$$

$$\begin{bmatrix} -1.34 & 0.67 \\ -1.34 & 2.67 \end{bmatrix}$$

$$\begin{aligned} &\frac{(V_1 - 3V_2)}{2} = \frac{V_1}{2} - 1.5V_2 \\ &V_1 - 3V_2 = -84 \\ &V_1 + 10V_2 = 360 \\ &V_1 = 7.2V_2 \\ &\frac{V_2}{10} = \frac{V_1}{7.2} = \frac{V_1}{V_2} = 5.2 \\ &V_2 - V_1 = 56 \\ &V_2 = 56 \\ &V_1 = 28 \\ &\text{Two Port Matrix} \end{aligned}$$


in
superposition
KVLvenn's theorem

in superposition
done by sum

$$I = \frac{2(6j)}{6 - 6j + 6j}$$

$$= \frac{2 \times 6(0)}{6} \\ = 0 + 2j$$
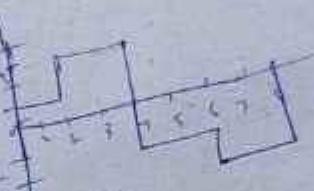
$$\frac{6(1 + 2j)}{(s+1)^2 + 1 + 1} \\ (s+1)^2 + 10(s+1)$$



For only \bar{R}_{TH} ?
we can't short any dependent vol.
source and remove any dependent
current source. Otherwise we
can do it.

$$V_s = I_{OL} + \frac{v_{OL}}{dr}$$

I EEN Pow yr in solve


(1)

→ W.A


Find the current in the resistor R_L using the principle of superposition in Fig. below.

[Superposition isn't in syllabus. I. not done by sin]

By Thevenin's theorem

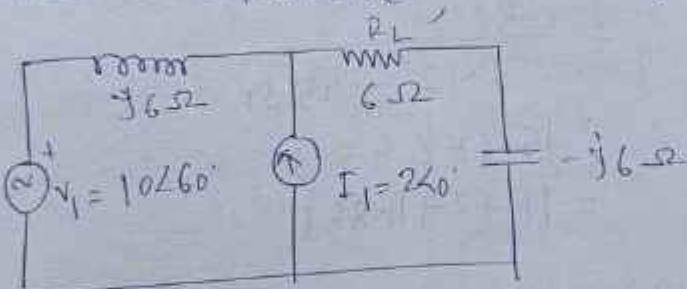

Short, v1

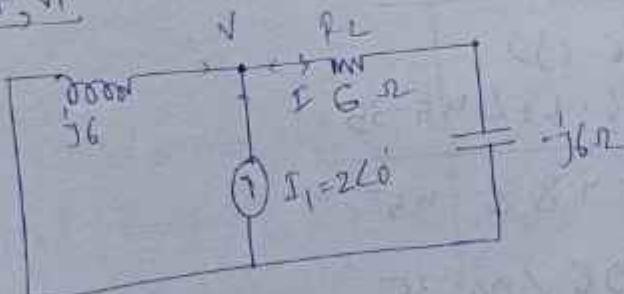

$$\frac{V}{6j} + \frac{V}{(6-j6)} = 2$$

$$\Rightarrow V \left[\frac{1}{6+j6} + \frac{1}{6-j6} \right] = 2$$

$$\Rightarrow V \left[\frac{1}{6(60)} + \frac{1}{8.48(-45)} \right] = 2$$

$$\begin{aligned} & \Rightarrow V = \frac{2}{0.157 - j0.118 + j0.157} = 2 \\ & \Rightarrow V = \frac{2}{0.083 + j0.083} \\ & = \frac{2}{0.083 - j0.083} \\ & = \frac{2}{0.12 - j0.35} \\ & = 16.67 - j4.35 \\ & \Rightarrow V = 11.72 + j0.86j \end{aligned}$$

$$I = \frac{16.67 - j4.35}{10 - j5}$$

$$= \frac{16.67 - j4.35}{8.48 - j4.5}$$

$$= 1.96 - j0.35$$

$$= -0.01 + j2$$

The current through $P_L = 1.96 - j0.35$

3) Distinguish between unilateral
of bilateral circuit elements.

Unilateral network

→ A circuit whose behavior is dependent on the direction of the current through various elements is called unilateral network.

Bilateral network

→ A circuit whose characteristics, behavior is same irrespective of the direction of current through various elements of it, is called bilateral network.



2) circuit consisting diodes
is good example of
unilateral circuit

2) circuit consisting
only resistors is
good example of
bilateral network.

3) The networks which have elements that allows the current to flow only in one direction.

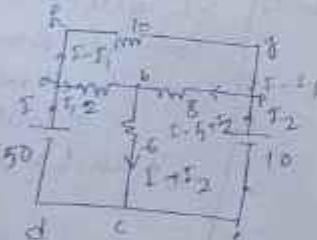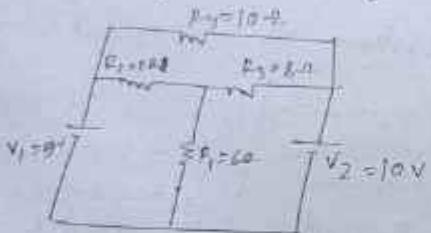3) The networks consist of elements that allows the current can flow in either direction.

⑥ Determine current through R_2 using mesh analysis shown fig.



abda + KVL

$$2I_1 + 6(I + I_2) = 50$$

$$2I_1 + 6I + 6I_2 = 50$$

$$3I + I_1 + 3I_2 = 25 \quad \text{---} ①$$

KGPbal - KVL

$$10(I - I_1) + 8(I - I_1 + I_2) - 2I_1 = 0$$

$$10I - 10I_1 + 8I - 8I_1 + 8I_2 - 2I_1 = 0$$

$$18I - 10I_1 + 8I_2 = 0$$

$$18I - 50I_1 + 8I_2 = 0$$

$$5I - 25I_1 + 4I_2 = 0$$

$$\rightarrow 9I - 10I_1 + 4I_2 = 0 \quad \text{---} ②$$

bfectb - KVL

$$-8(I - I_1 + I_2) - 6(I + I_2) = -10$$

$$-8(I - I_1 + I_2) + 6(I + I_2) = 10$$

$$4(I - I_1 + I_2) + 3(I + I_2) = 5$$

$$3I + 3I - 4I_1 + 4I_2 + 3I_2 = 5$$

$$\rightarrow 7I_1 - 1I_1 + 7I_2 = 5 \quad \text{---} ③$$

now from ①

$$7I_1 - 5I_2 = 7I_2$$

$$\rightarrow I = \frac{1}{7}(5 + 4I_2 - 7I_2) \quad \text{---} ④$$

$$\text{from } ① \text{ & } ④$$

$$\rightarrow \frac{9}{7}(5 + 4I_2 - 7I_2) = 0$$

$$\text{from } ③ \text{ & } ④$$

$$\rightarrow \frac{2}{7}(3 + 4I_1 - 4I_2) - 10I_1 + 4I_2 = 0$$

$$\rightarrow \frac{4I}{7} + \frac{3I}{7} = 1$$

$$\rightarrow 4I_1 - 13I_2 - 70I_1 + 28I_2 = 0$$

$$\rightarrow -34I_1 - 35I_2 + 45 = 0$$

$$\rightarrow 40I_1 + 35I_2 + 34I_1 - 45 = 0$$

$$\rightarrow 35I_2 + 45 - 34I_1 = 0 \quad \text{---} ⑤$$

$$\rightarrow I_2 = \frac{1}{35}(45 - 34I_1) \quad \text{---} ⑥$$

$$\frac{3}{35} \left\{ I_1 + 4I_2 - \frac{2}{35} (45 - 34I_1) \right\} + I_1 +$$

$$\frac{3}{35} \left\{ 45 - 34I_1 \right\} = 25$$

$$3 \left\{ (5 + 4I_1) \cdot 5 - 45 + 34I_1 \right\} + I_1 +$$

$$3 \left[25 + 20I_1 - 45 + 34I_1 \right] + \frac{35I_1}{3}$$

$$3 \left[(-20 + 54I_1) + \frac{35I_1}{3} + 45 - 34I_1 \right] = 25$$

$$3(54I_1 - 20) + 35I_1 + 45 - 34I_1 = 25$$

$$162I_1 - 60 + 35I_1 + 45 - 34I_1 = 25 - 35$$

$$105I_1 = 875 + 60 - 135 = 800 \quad I_1 = 8.75$$

the current through $R_2 = 8.75 A$.

$$500 \text{ V} / 8.75 A = 57.14 \Omega$$

$$50 \times 0.08 = 4 \text{ V}$$

then we can

$$I = \begin{bmatrix} I \\ I_1 \\ I_2 \end{bmatrix}, \quad A = \begin{bmatrix} 3 & 1 & 3 \\ 3 & -10 & 4 \\ 3 & -4 & 2 \end{bmatrix}, \quad B = \begin{bmatrix} 25 \\ 0 \\ 5 \end{bmatrix}$$

$$AI = B$$

$$A^{-1} =$$

$$\begin{vmatrix} 3 & 1 & 3 \\ 3 & -10 & 4 \\ 3 & -4 & 2 \end{vmatrix}$$

$$= 3(-70+16) - 1(63-24) + 3(-30+12)$$

$$= -102 - 35 + 102$$

$$= -35$$

$$A^{-1} = \left\{ \begin{vmatrix} -10 & 2 \\ -4 & 2 \end{vmatrix} \quad \begin{vmatrix} 10 & 4 \\ 2 & 2 \end{vmatrix} \quad \begin{vmatrix} 3 & 1 \\ 3 & 1 \end{vmatrix} \right.$$

$$\left. \begin{vmatrix} 1 & 3 \\ -1 & 2 \end{vmatrix} \quad \begin{vmatrix} 3 & 3 \\ 2 & 2 \end{vmatrix} \quad \begin{vmatrix} 3 & 1 \\ 3 & 1 \end{vmatrix} \right\} +$$

$$\begin{vmatrix} 1 & 3 \\ -10 & 2 \end{vmatrix} - \begin{vmatrix} 3 & 2 \\ 3 & 1 \end{vmatrix} - \begin{vmatrix} 3 & 1 \\ 3 & -10 \end{vmatrix}$$

$$= \left\{ \begin{array}{l} (-70+16) - (63-24) - (-30+12) \\ -(7+12) (21-21) - (-12-2) \\ (4+30) - (12-2) (-30-9) \end{array} \right\} T$$

$$= \begin{bmatrix} -54 & -19 & 34 \\ -19 & 0 & 19 \\ 34 & 19 & -39 \end{bmatrix} I$$

$$I = \frac{1}{-95} \begin{bmatrix} -54 & -19 & 34 \\ -35 & 0 & 19 \\ 34 & 19 & -39 \end{bmatrix}$$


$$= \frac{1}{95} \begin{bmatrix} 54 & 19 & -34 \\ 35 & 0 & -19 \\ -34 & -19 & 39 \end{bmatrix} \begin{bmatrix} 1 \\ 0 \\ 5 \end{bmatrix}$$

$$= \frac{1}{95} \begin{bmatrix} 1180 \\ 800 \\ -65 \end{bmatrix}$$


$$I_1 = \frac{800}{95} = 8.42 A$$

Ques (a) State Thevenin's theorem - done

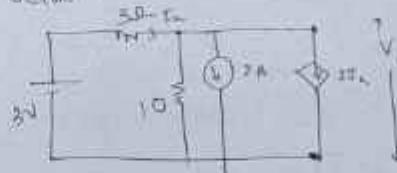(b) Find V_{th} and I_{th} for the circuit shown in fig below



by Thevenin's theorem

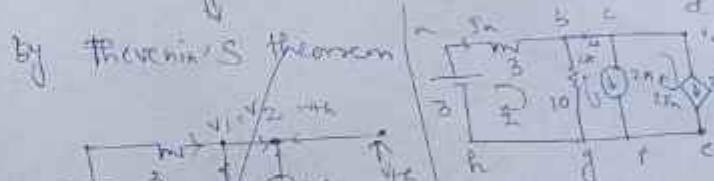

$$3 + 10I_{th} - 2 = 3$$

$$3 + 10I_{th} - 2 = 3$$

$$10I_{th} = 2$$

$$I_{th} = 0.2 A$$

$$2I_{th} = 2 \times 0.2 = 0.53 A$$

$$\begin{aligned} 10I_1 + 3V_1 - 3 &= 0 \\ 10I_1 + 3V_1 &= 3 \\ 10I_1 + 3 \cdot 0.2 &= 3 \\ 10I_1 &= 2.4 \\ I_1 &= \frac{2.4}{10} = 0.24 A \end{aligned}$$

$$I_{th} = \frac{3 - 0.24}{3} = 0.92 A$$

41

Find Laplace transform of $f(t) = \int_0^t e^{3t-s} \cos(5t) dt$

$\text{L}[f(t)] = \int_0^\infty e^{-st} f(t) dt = \int_0^\infty e^{-st} \int_0^t e^{3t-s} \cos(5t) dt dt$

Let the Laplace transformation of $f(t)$ is $L[f(t)] = F(s)$

By using first shifting rule,

If $L[e^{at} f(t)] = F(s)$, then $L[e^{at} f(t)] = F(s+a)$

$$\text{L}[\cos(5t)] = \frac{s}{s^2 + 25}$$

$$\therefore L[e^{3t} \cos(5t)] = \frac{s}{s^2 + 25 - 6s}$$


By applying the property of shifting

$$\begin{aligned} L[e^{-s} e^{3t} \cos(5t)] &= \frac{(s+3)}{(s+3)^2 + 25} \\ &= \frac{(s+3)}{s^2 + 6s + 34} \end{aligned}$$

Q) Consider the circuit shown in fig below. The switch was closed for a very long time and at $t=0$, the switch is opened. Find the expression of $v_c(t)$ for $t>0$



* Before switching,

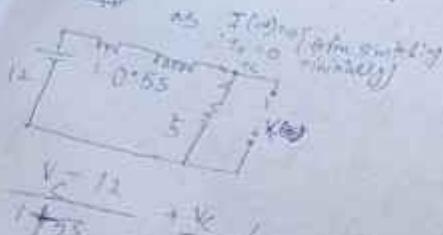

$$V_C = \frac{12}{1+0.55} + V_o$$

$$\frac{V_C}{0.55} + \frac{V_o}{5} = 0$$

$$3.4 \left[\frac{1}{0.55} + \frac{1}{5} \right] = \frac{12}{1+0.55}$$

$$3.4 \left[\frac{5+1}{1+0.55} \right] = \frac{12}{1+0.55}$$


$$3V_C = \frac{12}{1+0.55}$$

$$V_o = \frac{12}{1+0.55}$$

$$V_o = \frac{12}{1+0.55} \text{ before switching}$$

$$= \frac{12}{1+0.55}$$
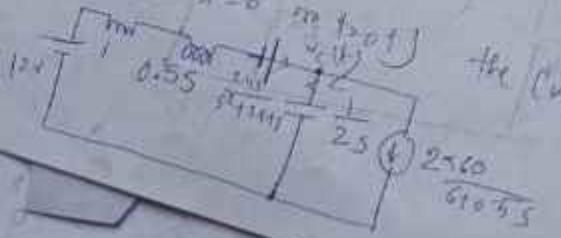
$$\text{After switching at } t=0 \text{ in } 10\mu s$$



$$V_o = \frac{12}{1+0.55}$$

$$= \frac{12}{1+0.55}$$

Now,

$$\frac{V_C - 12}{(1+0.55)} - \frac{2.4}{5(1+0.55)} + \frac{V_o}{2.5} = \frac{-12}{1+0.55}$$

$$\Rightarrow \frac{V_C}{(1+0.55)} - \frac{12}{1+0.55} - \frac{2.4}{5(1+0.55)} + \frac{V_o}{2.5} = \frac{-12}{1+0.55}$$

$$\Rightarrow \frac{V_C}{(1+0.55)} - \frac{12}{1+0.55} - \frac{2.4}{5(1+0.55)} + \frac{V_o}{2.5} = \frac{-12}{1+0.55}$$

$$\Rightarrow V_C \left[\frac{2}{(1+0.55)} + 2.5 \right] = \frac{-12}{1+0.55} + \frac{12}{1+0.55} + \frac{2.4}{5(1+0.55)}$$

$$\Rightarrow V_C \left[\frac{2+4.8+2.5^2}{2.5} \right] = \frac{-12}{1+0.55} + \frac{2.4}{5(1+0.55)}$$

$$\Rightarrow V_C \left[\frac{2.5^2 + 4.8 + 2}{2.5} \right] = \frac{-12}{1+0.55} + \frac{2.4}{5(1+0.55)}$$

$$\Rightarrow V_C \left[\frac{-26/10}{(1+0.55)} + \frac{12}{5(1+0.55)} \right] = \frac{-12}{1+0.55} + \frac{2.4}{5(1+0.55)}$$

$$\Rightarrow -10(5+2) = \frac{0.483(12+5)(5+1)^2}{(5+1)(5+2)} + \frac{12(5+1)(5+2)}{(5+1)(5+2)}$$

$$\Rightarrow -120 \cdot 4(5+2) = \frac{12(5+1)(5+2)}{(5+1)(5+2)}$$

$$\frac{120 \text{ (m)}_{\text{e}}}{\text{C}_6\text{H}_5\text{CH}_2} \cdot \frac{1/2}{(\text{S}+1)^2} \left[\frac{1/2}{(\text{S}+1)} \right]$$

$$\frac{120 \text{ (S+1)}}{(\text{S}+1)(\text{S}+2)} \cdot \frac{1/2}{(\text{S}+1)^2} + \frac{1/2}{(\text{S}+1)^2}$$

now

$\text{S}+1$

$$\frac{-120 \text{ (S+1)}}{(\text{S}+1)(\text{S}+2)} = \frac{A}{(\text{S}+1)^2} + \frac{B}{(\text{S}+1)}$$

$$A = \frac{-120 \text{ H}_2\text{C}_6\text{H}_5}{(\text{S}+1)(\text{S}+2)} \quad (\text{H}_2\text{C}_6\text{H}_5)$$

$$= -14.4(-\text{H}_2\text{C}_6\text{H}_5) \quad S = -1/2$$

$$= -14.4(-\text{H}_2\text{C}_6\text{H}_5)$$

$$B = \frac{12.00}{12/1} = 109.1$$

$$\frac{-120 \text{ (S+1)}}{(\text{S}+1)(\text{S}+2)} \cdot \frac{12.00}{12/1} = 109.1$$

$$= -10.91$$

$$C = \frac{-120 \text{ (C}_6\text{H}_5\text{CH}_2)}{(\text{S}+1)^2} \cdot \frac{1/2}{(\text{S}+1)}$$

$$\begin{aligned} &= -120 \cdot 1/2 \\ &= -10.91 \end{aligned}$$

$$\frac{-120 \text{ C}_6\text{H}_5\text{Y}}{(\text{S}+1)(\text{S}+2)} = \frac{109.1}{\text{S}+1} - \frac{10.91}{\text{S}+1} - \frac{10.91}{\text{S}+1}$$

$$= \frac{109.1}{\text{S}+1} - \frac{21.82}{\text{S}+1}$$

$$\frac{1/2}{(\text{S}+1)^2} = \frac{A}{(\text{S}+1)} + \frac{B}{(\text{S}+1)}$$

$$A = \frac{1/2 \cdot (\text{S}+1)}{(\text{S}+1)^2} \quad S = -1$$

$$= 1/2 - B$$

$$A = B = \frac{1/2 \cdot (\text{S}+1)}{\text{S}+1 \cdot (\text{S}+2)} \quad S = -1$$

$$\frac{1/2}{(\text{S}+1)^2} = \frac{1/2}{(\text{S}+1)^2} + \frac{1/2}{(\text{S}+1)^2}$$

$$Y(s) = \frac{10s_1}{s+2} + \frac{21s_2}{s+1} + \frac{12}{s+1} - \frac{7s_1}{s+2}$$

$$y(t) = \frac{10s_1 e^{-2t}}{s+2} + \frac{30e^{-t}}{s+1}$$

$$= [10s_1 e^{-2t} - 21s_2 e^{-t}] + \frac{30e^{-t}}{s+1}$$

~~or~~
or prove that $\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} sF(s)$

by find the Laplace transform of
the signal shown in Fig. below



$$f(t) = \begin{cases} 2 & 0 \leq t < T \\ 0 & T \leq t < 2T \\ 2 & 2T \leq t < 3T \\ 0 & 3T \leq t < 4T \\ \vdots & \end{cases}$$

$$(1) \quad f(t) = \frac{2}{T} u(t) - 2u(t-T) + 2u(t-2T) - \frac{2u(t-3T)}{T}$$

$F(s)$

$$= \frac{2}{T} \frac{1}{s+2} - 2 \left[e^{-Ts} \frac{1}{s+1} + e^{-2Ts} \frac{1}{s+1} + e^{-3Ts} \frac{1}{s+1} \right]$$

$$\Rightarrow \frac{2}{Ts+2} - \frac{2}{s+1} \left[e^{-Ts} + e^{-2Ts} + e^{-3Ts} \right]$$

$$= \frac{2}{Ts+2} - \frac{2}{s+1} \left[e^{-Ts} + e^{-2Ts} + e^{-3Ts} \right]$$

b) (a) Find inverse Laplace transform

$$\text{of } F(s) = \frac{s+2}{(s+1)^2(s+3)}$$

$$\frac{G(s)}{s+2} = F(s) = \frac{A}{(s+1)^2} + \frac{B}{s+3}$$

(s+3)

$$A = \frac{(s+2)(s+1)^2}{(s+1)^2(s+3)} \Big|_{s=-1} \quad B = \frac{(s+2)(s+3)}{(s+1)^2(s+3)} \Big|_{s=-1}$$

$$= \frac{1}{2} \quad B = -\frac{1}{4}$$

with also
cancel out
by the
term $+ \frac{2}{s+1}(1-s)$


$$\frac{P(s)}{P(s) - (n_1)} = \frac{1}{(s + C_{12})(s + C_{13})} = \frac{1}{s(C_{12})} - \frac{1}{s(C_{13})}$$

(A)

$P(s)$ current transform

$$= \frac{1}{2} [s e^{-t} - t e^{-t}]$$
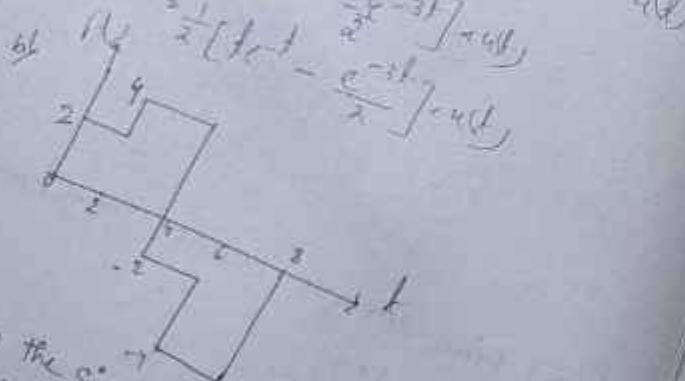
$$= \frac{1}{2} [s e^{-t} - t^2 e^{-t}] + \frac{1}{4} e^{-2t}$$





Consider the signal shown in fig. below
represent the signal in terms of unit step function
 $v(t) = 2u(t) + 2u(t-2) - 2u(t-3) + 0.6u(t-3) - 2u(t-4)$

Ques.

- (a) Derive the condition for reciprocity and symmetry for T-parameters.
Done

- (b) Derive \mathbf{h} -parameters, and \mathbf{T} -parameters in terms of \mathbf{y} -parameters.
Done

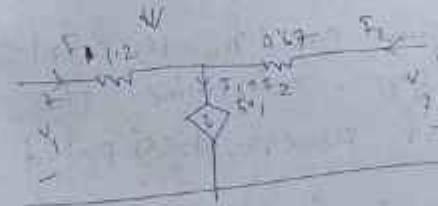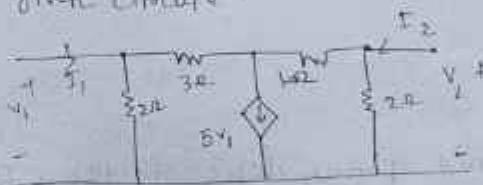- (c) Find open circuit impedance for the given circuit.



$$I_1 = 0,$$


$$\therefore I_2 = 5V_1$$

$$\therefore I_2 = 5V_1$$

$$\therefore \frac{V_1}{I_2} = \frac{1}{5} = 0.2 = Z_{12}$$

$$\therefore Z_{11} = 0.67 Z_{12}$$
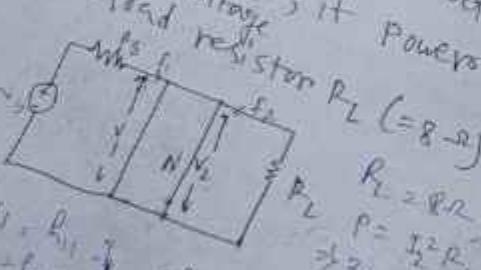
$$\therefore Z_{11} = 0.67 \times 0.2 = 0.134$$



Q(a) The hybrid parameters of the network shown in figure are: $h_{11} = 1.2$, $h_{12} = 0.67$, $h_{21} = 0.67$, $h_{22} = 0.67$. If $v_s = 5V$, determine the short circuit current i_s , if power dissipated in the load resistor $R_L (= 8\Omega)$ is 30W and $R_s = 20\Omega$.

$$P = \frac{I^2 R_L}{4} \Rightarrow 30 = \frac{I^2 \cdot 8}{4} \Rightarrow I^2 = 1.936 \text{ A}$$

$$I^2 = I_1^2 + I_2^2 \Rightarrow I_1^2 = 1.936 - 0.67^2 = 1.505 \text{ A}$$

$$I_1 = \sqrt{1.505} = 1.225 \text{ A}$$

$$I_2 = \sqrt{1.936 - 1.225^2} = 1.06 \text{ A}$$

$$\begin{aligned} v_s &= v_1 \\ &= h_{11}i_1 + h_{12}i_2 \\ &= 1.2i_1 + 0.67i_2 \\ &= 1.2 \cdot 1.225 + 0.67 \cdot 1.06 \\ &= 1.936 \text{ V} \end{aligned}$$

from (1),

$$\Rightarrow v_s = v_1 + i_1 R_s$$

$$\Rightarrow v_s = v_1$$


from (2)

$$\Rightarrow 1.936 = (-i_1) + v_1 + 20i_1$$

$$\Rightarrow 1.936 = v_1 + 19i_1$$

$$\Rightarrow v_s = 0.484 \text{ V}$$

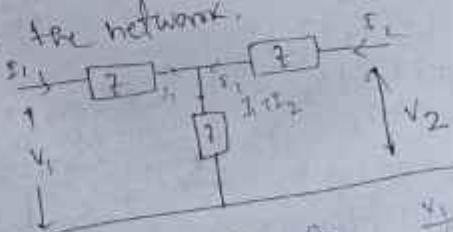Find the transmission parameters for the network.



$$\begin{aligned} v_1 &= Av_2 - Bi_2 \quad (1) \\ i_1 &= Cv_2 - Di_2 \quad (2) \end{aligned}$$

$$\begin{cases} v_1 = 0 \\ i_1 = A \end{cases} \Rightarrow \begin{cases} 0 = Av_2 - Bi_2 \\ A = Cv_2 - Di_2 \end{cases} \Rightarrow \begin{cases} v_2 = 0 \\ i_2 = B/A \end{cases}$$

Price Vol.

$$V_N = \frac{4\pi r^3 N}{3} = 300 \text{ cm}^3$$

$$\frac{V_{PN}}{2k} = \frac{q_{PN}}{\sqrt{3 + k^2}}$$

$$I_B = \frac{V_{BE}}{r_S} = \frac{0.01V - 0.50}{\sqrt{2}}$$

$$74 \times \frac{1470}{147} = \underline{\underline{400/00}}$$

$$T_N = \frac{2\pi}{k_B T} \ln \left(\frac{e^{\beta E_1} + e^{\beta E_2} + \dots}{N} \right)$$

$$R = 2.497 - 2.17j + 12.29j - 2.8 - 24.39 + 7.744j + 7.2979 + 7.05j - 20.4528 - 12.19j$$

$$V_N = \frac{12.51 - 9.8}{3.82 - 1.33} = \frac{2.614}{4.04 - 2.81} = 0.978$$

④ 5000 ft. x 1000 ft.
5000 ft. x 1000 ft.

25
1) Take an arbitrary subset of your choice (minimum 4 nodes). Draw oriented graph and select a tree. From there on express the following:

- thereon express the following:

 - Relation between incident matrix and branch current matrix.
 - Relation between \bar{f}_{sc} matrix and branch voltage matrix.
 - Relation among branch currents matrix, fundamental loop currents matrix and \bar{f}_{sc} matrix.

1818.12.20



Branch No. 36
Date 3-6

$$\begin{aligned} \lambda_1 &= \left\{ \begin{matrix} 3, & 2, & 1 \end{matrix} \right\} \\ \lambda_2 &= \left\{ \begin{matrix} 3, & 4, & 1 \end{matrix} \right\} \\ \lambda_3 &= \left\{ \begin{matrix} 2, & 1, & 1 \end{matrix} \right\} \end{aligned}$$

$$A \cdot a_2 - \beta - T_1 = 0$$

$$ab_3b_7 \left(x^2 - 5x + 2 \right) = 0 \quad \text{and} \quad x_3^2 + 6^{-2x} - b_2 = 0$$

$$M: 73 - 72 = 1$$

三

(2c)

$$\rightarrow \begin{bmatrix} -1 & 1 & 1 & 0 & 0 \\ -1 & 0 & 0 & 1 & -1 \\ 0 & -1 & 0 & 0 & -1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \end{bmatrix} = 0$$

$$\rightarrow [B] \cdot [I_b] = 0$$


Node matrix \times branch current matrix \Rightarrow

\therefore fundamental loop currents $=$ branch currents


~~matrix~~

(2)

by Thevenin's theorem,

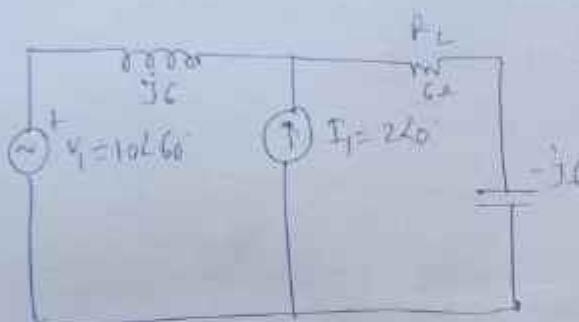

(3)

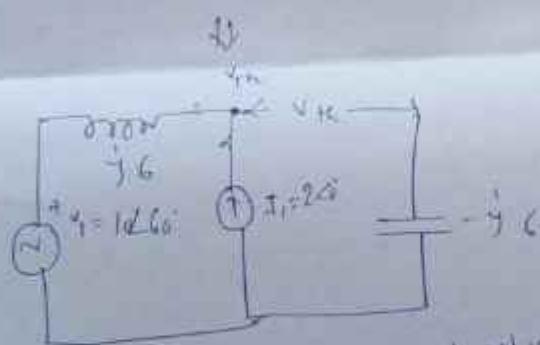


$$\frac{V_R - 10L60}{jC} = 2$$

$$\Rightarrow \frac{V_R}{jC} = 2 + \frac{10L60}{0.16j}$$

$$\Rightarrow \frac{V_R}{CL60} > 2 + \frac{10L60}{6L90}$$

$$\Rightarrow \frac{V_R}{CL60} = \frac{12L90 + 10L60}{CL90}$$
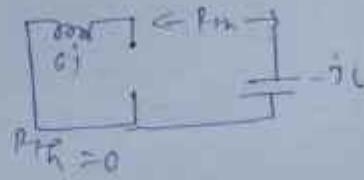
$$\begin{aligned} V_{TH} &= 0 + 12j + 5 + \\ &\quad 8.66j \\ &= 5 + 13.66j \\ &= 14.55L60 \cdot 8.9 \end{aligned}$$



(5)

$$T_{th} = \frac{14.55 - 169.89}{0 + 6}$$
$$= 2.4 \angle 69.89^\circ$$