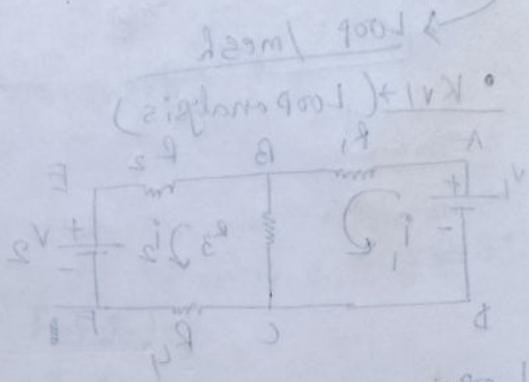


EE

3/3/22

- 1) 5 marks (Basics) [Electro Statics, magnetism]
- 2) DC N/W \rightarrow 15/20 marks
- 3) Single Phase AC
- 4) Rating - 230V - 50Hz
- 5) 1φ AC (Rating)
- 6) 110V DC (train fan)
 - $V = V_m \sin \omega t$
 - $I = I_m \sin \omega t$
- 7) $P_2 = VI \cos \phi$ (For AC)
- 8) $P_2 = VI$ (For DC)





8) Transformers (20 marks)

9) DC machines (1)

10) Induction m/c

EE EC8

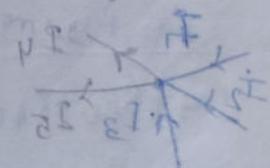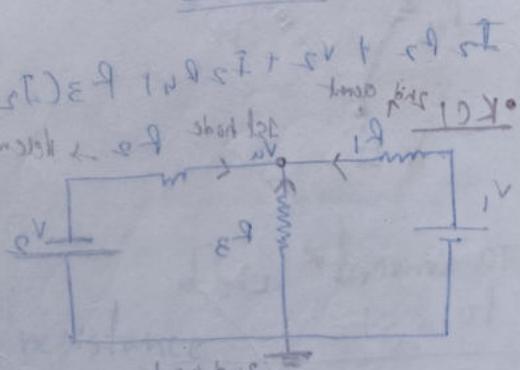

11) short of at neutral in 2 phases short low voltage


$$I_N = \frac{V}{R} + \frac{V - v_N}{R} + \frac{V - v_N}{R}$$

7/3/22

KVL and KCL
 $V = IR$

Loop / mesh

\bullet KVL + (Loop analysis)

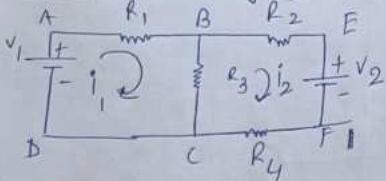

Loop 1



AB(CDA)

$$I_1 R_1 + R_3 (I_1 - I_2) - V_1 = 0$$

Loop 2

BEFCB
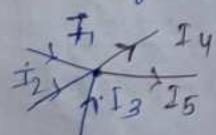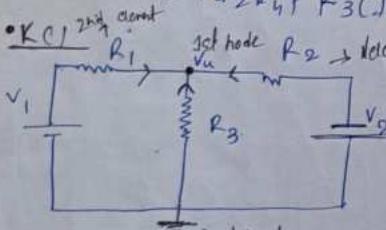
$$I_2 R_2 + V_2 + I_2 R_4 + R_3 (I_2 - I_1) = 0$$



For nodal analysis we have to go for RCL.

$$\frac{V_u - V_1}{R_1} + \frac{V_u - V_0}{R_3} + \frac{V_0 + V_2}{R_2} = 0$$

Nodal analysis
 $V_u ?$

Nodal
 V_u with SC

In steady state

then node's position

(initial) 3h vall

(final) 3h vall


$I_1 + I_2 \rightarrow$ resultant $\rightarrow V_1 - V_2$

$V_1(+), V_2(-) \rightarrow$ Resultant $V_1 + V_2$

\bullet KCL \rightarrow Nodal analysis

\bullet KVL \rightarrow Loop analysis (super mesh)

\bullet Current division rule

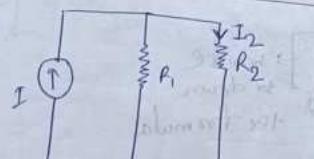

$$R_2(I_2) = ?$$

$$I_2(R_2) = ?$$

$$R_2(A_2) \quad I_2(R_2) \rightarrow \text{main current} \times \frac{\text{opposite Resistance}}{\text{Total Resistance}}$$

$$I_2(R_2) = J \times \frac{R_1}{R_1 + R_2}$$


\bullet Voltage division rule

Branch
 $v_d =$ main vol
 $r_d =$ same resistance


Total resistance $= R_d$

\bullet Source Transformation

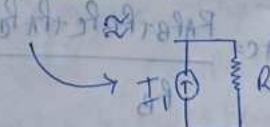$\frac{V_1}{R_1} \rightarrow$ [Equivalent Current Source]




Supermesh

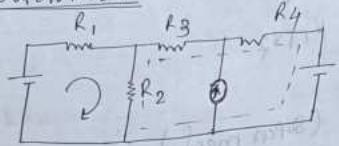


$$I(R_3) = ?$$

Assignment

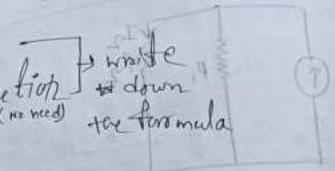- Star, delta connection
- Series and Parallel Connection



Delta, Star transformation

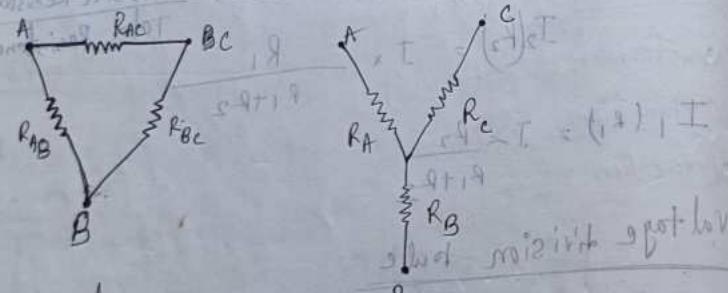

To convert a delta to a star

$$R_A = \frac{R_{AB} R_{AC}}{R_{AB} + R_{BC} + R_{AC}}$$

$$R_B = \frac{R_{AB} R_{BC}}{R_{AB} + R_{BC} + R_{AC}}$$

$$R_C = \frac{R_{BC} R_{AC}}{R_{AB} + R_{BC} + R_{AC}}$$

$$R_{AB} = \frac{R_A R_B + R_B R_C + R_A R_C}{R_C}$$

$$R_{BC} = \frac{R_A R_B + R_B R_C + R_A R_C}{R_A}$$

$$R_{AC} = \frac{R_A R_B + R_B R_C + R_A R_C}{R_B}$$

DC Network Theorem

10/3/22


1) Thevenin's theorem

2) Norton's theorem

3) Superposition theorem


4) Maximum Power Transformation theorem

5) [Tillegren's theorem] X

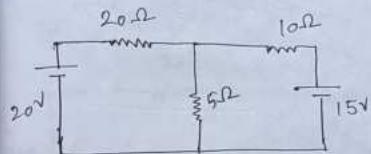


$$I(5\Omega) = ?$$

R_L → Load Resistance

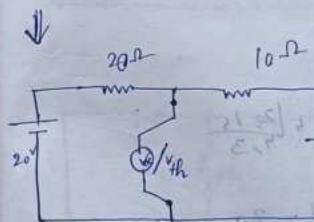

V_{th} = open circuit voltage

V_{th} = Thevenin's equivalent voltage

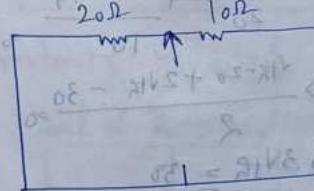


[This is not series, this is parallel]

[For thevenin's equivalent resistance]


To find out R_{th} voltage source should be short circuited with their internal resistance.

Current source should be open.

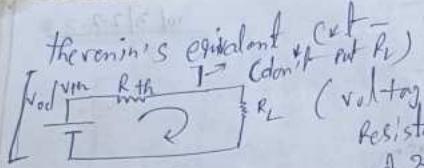measure total equivalent resistance of the circuit (R_{th}), viewed from the load terminal.



$$I_{th} = \frac{V_{th}}{R_{th} + R_L}$$

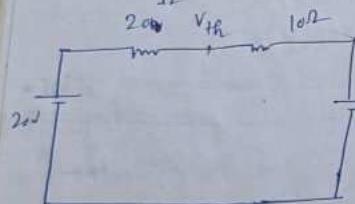

$$\frac{V_{th} - 20}{2\Omega} + \frac{V_{th} - 10}{10\Omega} = 0$$

$$\Rightarrow \frac{3V_{th} - 60 + 4V_{th} - 40}{20} = 0$$

$$\Rightarrow 7V_{th} - 100 = 0$$

$$\Rightarrow V_{th} = \frac{100}{7} V$$

$$R_{th} = \frac{20 \times 10}{20 + 70} = \frac{20}{9} \Omega$$


$$I_{th} = \frac{V_{th} - 20}{2\Omega} = \frac{\frac{100}{7} - 20}{2} = \frac{10}{7} A$$

$$I_{th} = \frac{10}{7} A$$

$$I_{th} = \frac{10}{7} A$$

$$I_{th} = \frac{10}{7} A$$

$$I_{th} = \frac{10}{7} A$$

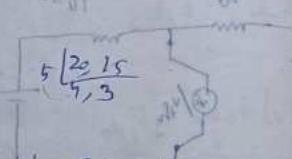

$$\frac{V_{th} - 20}{2\Omega} + \frac{V_{th} - 10}{10\Omega} = 0$$

$$\Rightarrow V_{th} - 20 + 2V_{th} - 30 = 0$$

$$\Rightarrow 3V_{th} = 50$$

$$\Rightarrow V_{th} = \frac{50}{3} V$$


$$R_{th} = \frac{20 + 10}{3} = \frac{30}{3} = 10 \Omega$$

$$I_{th} = \frac{V_{th} - 20}{2\Omega} = \frac{\frac{50}{3} - 20}{2} = \frac{10}{3} A$$


$$I_{th} = \frac{10}{3} A$$

$$I_{th} = \frac{10}{3} A$$

Norton's theorem

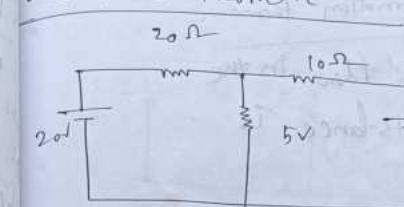

$$I(5\Omega) = ?$$

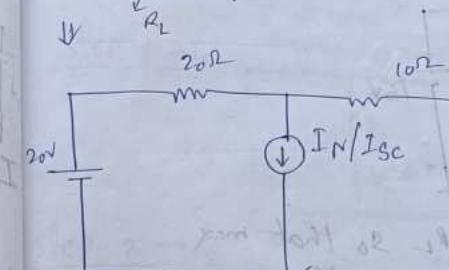


Identify R_L , then
short the R_L through
an ammeter,


redraw the Ckt
diagram, then
have to measure
 I_{sc} (short ckt
current),

findout R_{th} ,
redraw the
(Ckt diagram
with R_{th} in
voltmeter
in left side)

top - independent

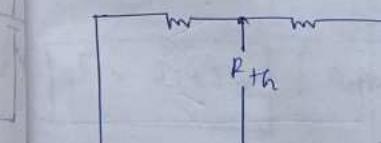


Norton's equivalent (Ckt)

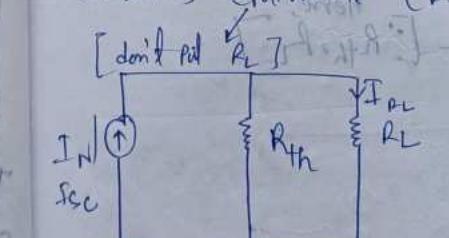


$$I_{RL} = \frac{I_{sc} \times R_{th}}{R_{th} + R_L}$$

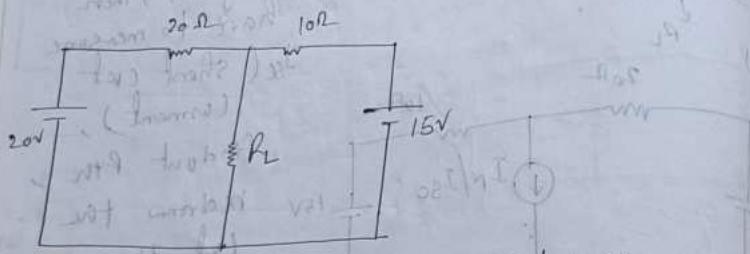- maximum Power transformation theorem
- Statement - max Powers will flow in the circuit when Load resistance is equal to the R_{th} .



Find out the value of R_L so that max Power will flow in that circuit?


Equivalent circuit

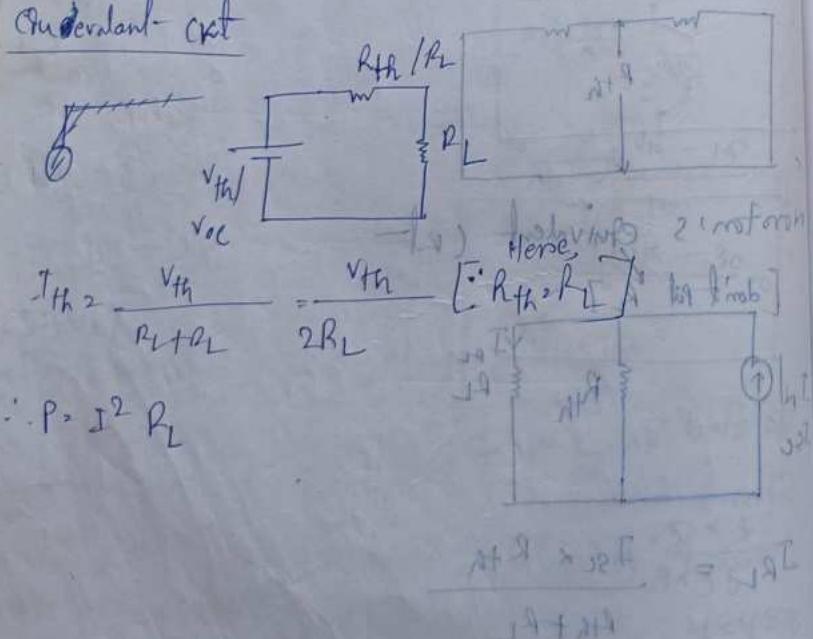

$$I_{th} = \frac{V_{th}}{R_{th} + R_L} = \frac{V_{th}}{2R_L}$$


$$\therefore P = I^2 R_L$$

• Superposition theorem

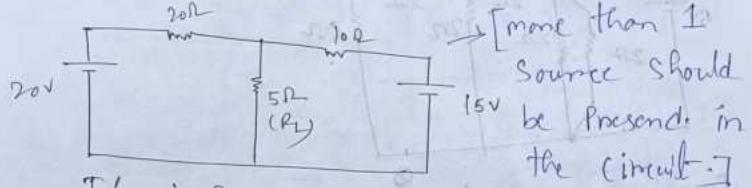


$$I(5\Omega) = ?$$

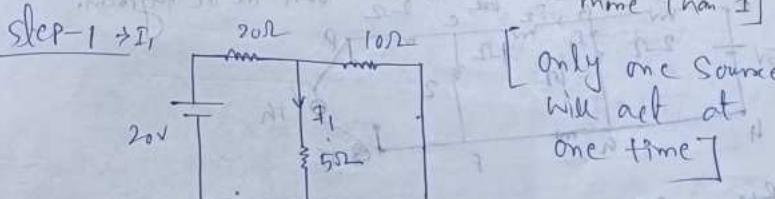[more than 1 Source should be present in the circuit]



[Voltage / current more than 1]

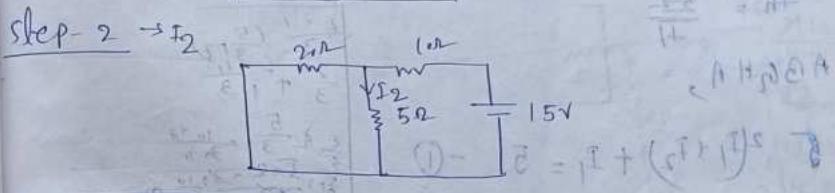


[only one source will act at one time]

$$I = I_1 + I_2$$

I = I₁ + I₂

[Superposition theorem]

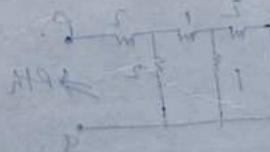

$$R_{th} = 2 + \frac{1}{\frac{1}{1} + \frac{1}{5}} = 2 + \frac{1}{\frac{6}{5}} = 2 + \frac{5}{6} = \frac{17}{6} \Omega$$



$$V_{oc} = 20 \times \frac{1}{\frac{17}{6}} = 20 \times \frac{6}{17} = \frac{120}{17} V$$

$$I = \frac{V_{oc}}{R_{th}} = \frac{\frac{120}{17}}{\frac{17}{6}} = \frac{120}{17} \times \frac{6}{17} = \frac{720}{289} A$$

$$P = I^2 R_L = \left(\frac{720}{289}\right)^2 \times R_L$$

$$P = \frac{518400}{83521} \times R_L$$

$$P = 6.21 R_L$$

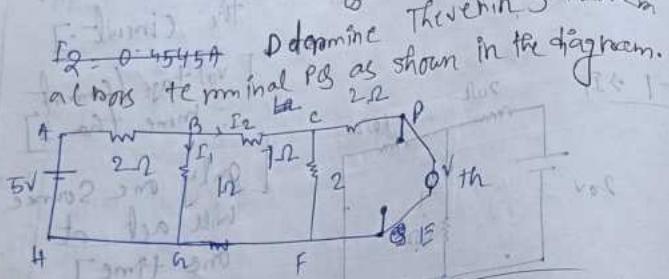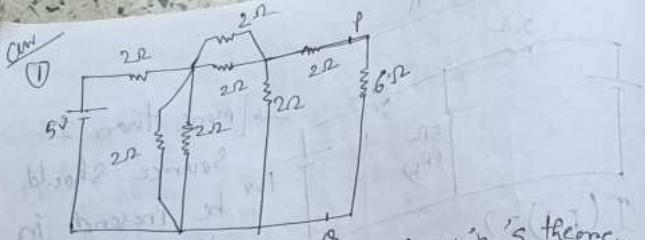

$$R_{Th} = \frac{2\Omega}{4}$$

ABGH A,

$$2(I_1 + I_2) + I_1 = 5 \quad \text{---(1)}$$

BCFGA B,

$$7I_2 + 2I_2 - I_1 = 0$$

$$\therefore 3I_2 = I_1$$

from, (1)

$$2(3I_2 + I_2) + 3I_2 = 5$$


$$\therefore 2 \times 4I_2 + 3I_2 = 5$$

$$\therefore 8I_2 + 3I_2 = 5$$

$$\therefore I_2 = \frac{5}{11} = 0.4545 \text{ A}$$



$$V_{Th} = 0.4545 \times 2 = \frac{10}{4} \text{ V}$$

$$\begin{aligned} & \left| \begin{array}{l} \frac{2}{3} + \frac{1}{3} \\ \frac{2}{3} + 1 \\ \frac{5}{3} \\ \frac{5}{3} + \frac{2}{3} = \frac{7}{3} \\ \frac{7}{3} + \frac{1}{3} = \frac{8}{3} \\ \frac{8}{3} + \frac{1}{3} = \frac{9}{3} \\ \frac{9}{3} + \frac{1}{3} = \frac{10}{3} \end{array} \right| \xrightarrow{\text{Simplifying}} \frac{10}{3} \\ & \left| \begin{array}{l} \frac{1}{3} + \frac{1}{3} \\ \frac{1}{3} + \frac{1}{3} \\ \frac{2}{3} \\ \frac{2}{3} + \frac{1}{3} = \frac{3}{3} \\ \frac{3}{3} + \frac{1}{3} = \frac{4}{3} \\ \frac{4}{3} + \frac{1}{3} = \frac{5}{3} \\ \frac{5}{3} + \frac{1}{3} = \frac{6}{3} \end{array} \right| \xrightarrow{\text{Simplifying}} \frac{6}{3} \end{aligned}$$

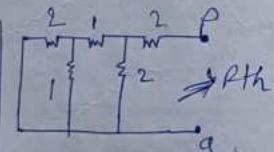

$$R_{Th} = 2\Omega$$

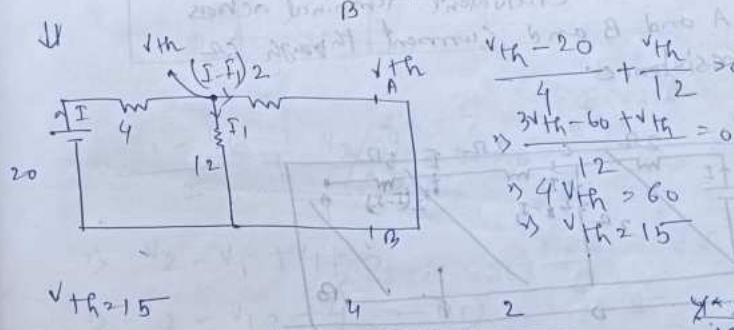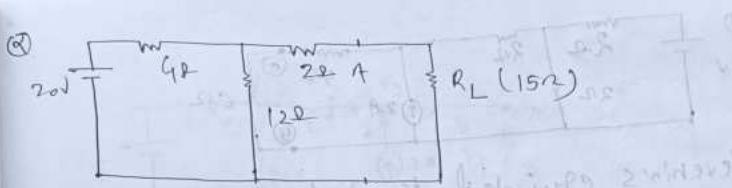
$$\begin{aligned} I_{Th} &= \frac{10}{11 \times (2\Omega) + 6} \\ &= \frac{10 \times 10}{11 \times 8\Omega} \\ &= \frac{100}{88} = 1.102 \text{ A} \end{aligned}$$



$$R_{Th} = \frac{10}{11}$$



$$\therefore I_{Th} = \frac{18 \times 7}{14} = 15$$

$$I_{Th} = \frac{15}{5 + 15}$$

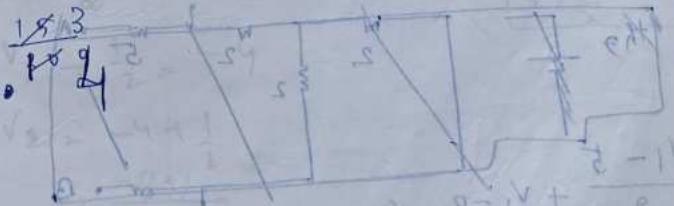

$$0 = \frac{5V - 1V + 1V + 2 - 1V}{8}$$

$$0 - 2V = 5V - 1V \quad \text{K}$$

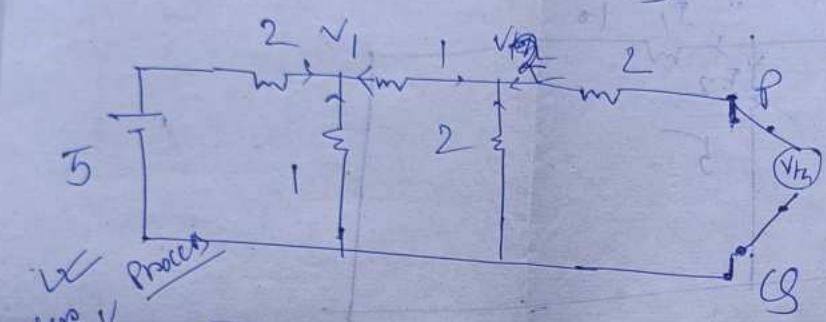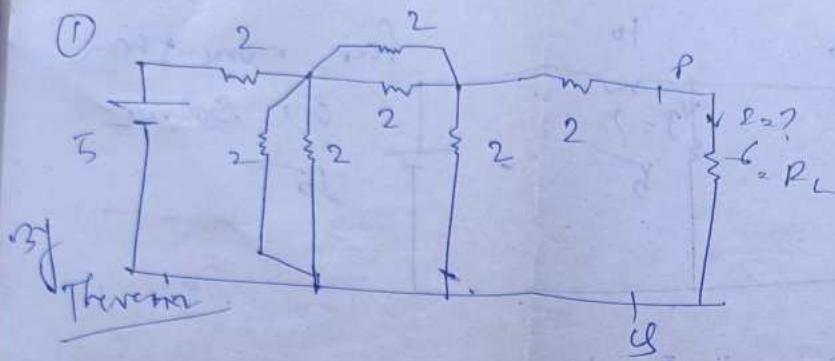

$$\frac{1-5}{2} + \frac{N_1}{1} + \frac{N_1 - N_2}{1} = 0$$

$$2\sqrt{1-5+2\sqrt{1+2\sqrt{1-2\sqrt{2}}}}=0$$

$$\therefore \sqrt{5}v_1 - 2v_2 = 5 \quad \text{--- (1)}$$


$$\frac{\sqrt{2}-\sqrt{2}}{1} + \frac{\sqrt{2}}{2} = \frac{5\sqrt{2}-2\sqrt{2}}{2} = \frac{3\sqrt{2}}{2}$$

$$\Rightarrow \frac{2\sqrt{2}}{2} - \sqrt{1} = \Rightarrow \sqrt{2} = \frac{10}{11}$$



$$2\sqrt{2} - 2\sqrt{1} + \sqrt{2} = 0 \Rightarrow \sqrt{2} = \frac{10}{11}$$

$$\Rightarrow -2x_1 + 3x_2 = 0 \quad \text{---(12) with}$$
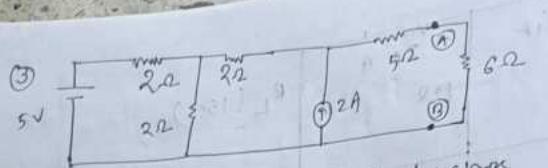
$$\frac{3\sqrt{2} + 2\sqrt{1}}{2} = \frac{3\sqrt{2}}{2}$$



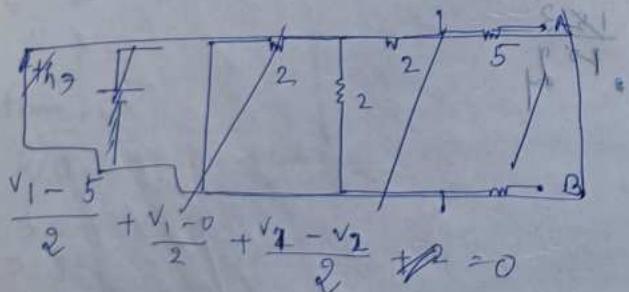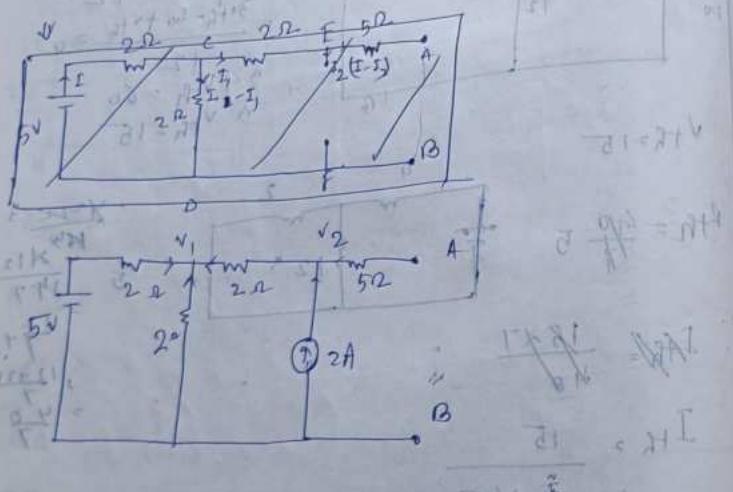
Thevenin's equivalent terminal across A and B and current through G2 resistance.



$$\frac{V_1 - 5}{2} + \frac{V_1 - 0}{2} + \frac{V_1 - V_2}{2} \neq 0$$

$$\Rightarrow V_1 - 5 + V_1 + V_1 - V_2 = 0$$

$$\Rightarrow 3V_1 - V_2 = 5 - 0$$

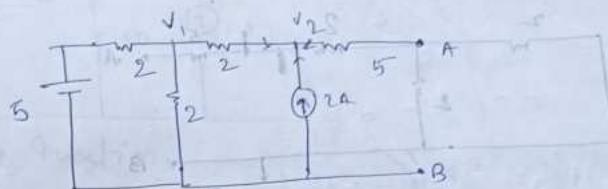

$$\frac{V_2 - V_1}{2} + \frac{V_2 - 0}{2} + 2 = 0$$

$$\begin{aligned} \Rightarrow V_2 - V_1 + 4 &= 0 \\ \Rightarrow V_2 - V_1 &= -4 \quad \text{--- (II)} \end{aligned}$$

$$3V_1 - V_2 = 5 \quad \text{--- (I)}$$

$$V_2 - V_1 = -4 \quad \text{--- (II)}$$

$$\Rightarrow 2V_1 = 1$$

$$\Rightarrow V_1 = \frac{1}{2}$$


$$\Rightarrow V_2 - \frac{1}{2} = -4$$

$$\begin{aligned} \Rightarrow V_2 &= -4 + \frac{1}{2} \\ &= -\frac{8+1}{2} \end{aligned}$$

$$\begin{aligned} &= -\frac{1}{2} \\ &= -3.5 \end{aligned}$$

$$V_{th} = V_2 = -3.5V$$

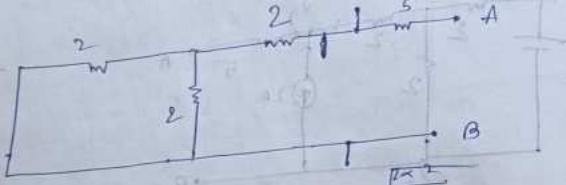
$$\begin{aligned} 3V_1 - V_2 &= 5 \\ V_1 + V_2 &= -4 \\ 3V_1 &= 1 \\ V_1 &= \frac{1}{2} \\ 3 \cdot \frac{1}{2} - V_2 &= 5 \\ \frac{3-10}{2} &= V_2 \\ -\frac{7}{2} &= V_2 \end{aligned}$$



$$R_{Th} = \frac{3 \times 5}{8} = \frac{15}{8} = 1.875 \Omega$$

$$I_{Th} = -\frac{3.5}{8+1.875} = -0.35 A$$

$$V = 10 - 1.875 = 8.125 V$$

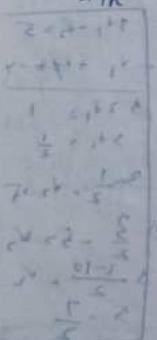


$$V = 1 - 1 = 0 V$$

$$\frac{1}{8} + N = 1.25 V$$

$$\frac{1}{8}$$

$$2 \cdot E = 2$$

$$V_E \cdot E = 1 - 0.25 = 0.75 V$$

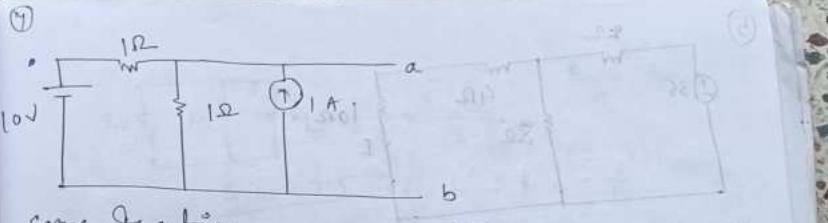

same question.

$$V_{Th} = 10 \quad I_{Th} = \frac{10}{2} = 5 A$$

$$V_{Th} = 0 \quad I_{Th} = \frac{0}{2} = 0 A$$

$$V_2 = 10 + 1 = 11 V$$


$$V_{Th} = 10 + V_{Th} = 0$$

$$2V_{Th} = 10$$


$$V_{Th} = \frac{10}{2} = 5 V$$

$R_{Th} = \frac{1}{2} \Omega$
current through 1Ω resistance

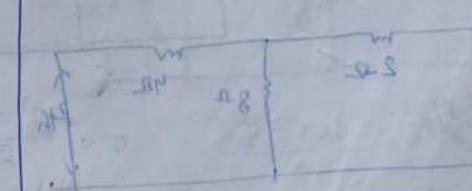
$$I_{Th} = \frac{5}{1/2 + 1} = \frac{10}{3} = 3.33 A$$



$$2 \cdot \beta = 11$$

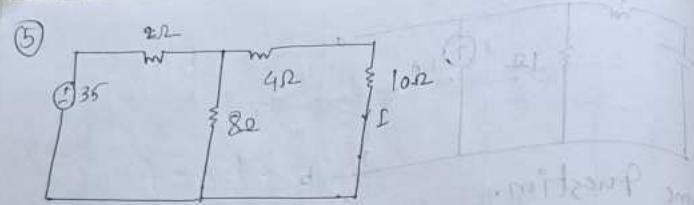

$I(10\Omega) = ?$ By Norton's theorem

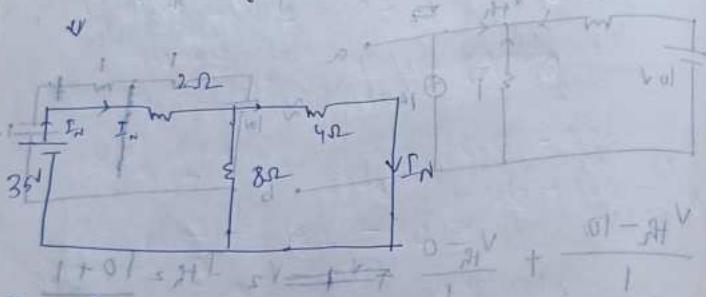


$$I_n = \frac{35}{R_{th}} = \frac{35}{8\Omega} = 4.375 A$$

$$V_o = 21 - \frac{1}{3}(21 - 10) = 14 V$$


$$\frac{1}{2} = \frac{1}{3} + \frac{1}{2}$$

$$\text{Norton's theorem}$$

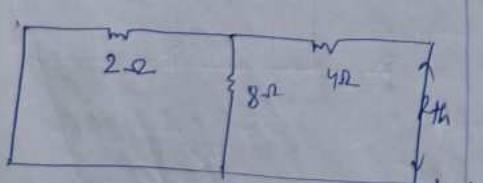


$$R_{th} = 6 \Omega$$
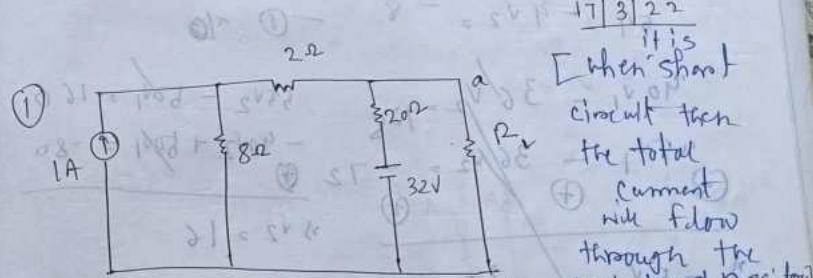
$$I = \frac{5.6 \times 7.5}{5.6 + 10} = 2.084 A$$



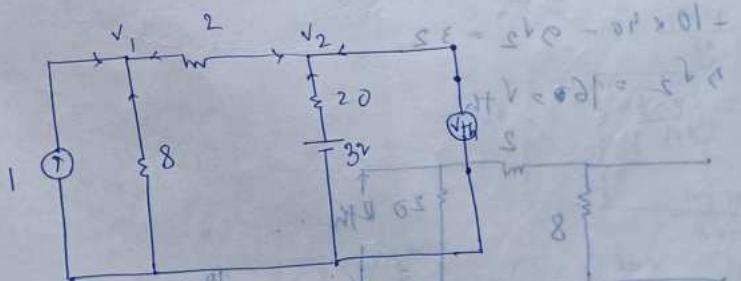Find thevenin and Norton's equivalent current as shown in the figure.



$$1 + \frac{\sqrt{1}}{8} + \frac{\sqrt{1} - \sqrt{2}}{2} = 0$$

$$\Rightarrow \frac{8 + \sqrt{1} + 4\sqrt{1} - 4\sqrt{2}}{8} = 0$$

$$\therefore 5\sqrt{1} - 4\sqrt{2} = -8 \quad \text{--- (1)}$$

$$\frac{\sqrt{2} - \sqrt{2}}{2} + \frac{\sqrt{2} - 32}{20} = 0$$


$$\frac{10\sqrt{2} - 10\sqrt{2} + \sqrt{2} - 32}{20} = 0$$

$$11\sqrt{2} - 10\sqrt{2} = 32 - 0$$

$$11\sqrt{2} - 10\sqrt{2} = 32 - 0$$

$$\begin{aligned} & 11\sqrt{2} - 10\sqrt{2} = 32 \\ & 10\sqrt{2} - 36\sqrt{2} = 128 \\ & 36\sqrt{2} = -72 \\ & \sqrt{2} = 16 \end{aligned}$$
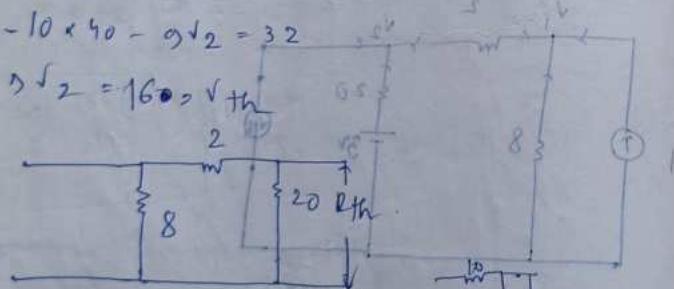
$$\begin{aligned} & 10 \times 40 - 9\sqrt{2} = 32 \\ & 10\sqrt{2} = 160 \end{aligned}$$



$$R_{th} = \frac{10 \times 20}{30}$$


$$\frac{20}{3}$$

$$10 - 8 = 2V_N - \frac{8}{10} V_Z$$


$$\begin{aligned} I_{th} &= \frac{160}{20 + 30} \\ &= \frac{160}{50} \\ &= \frac{16}{5} \text{ A} \end{aligned}$$


$$\begin{aligned} P_L &= P_{th} \times \frac{20}{30} \\ I_{th} &= \frac{280}{30} \\ &= \frac{28}{3} \\ &= \frac{6}{5} = 1.2 \text{ A} \end{aligned}$$

Norton's theorem

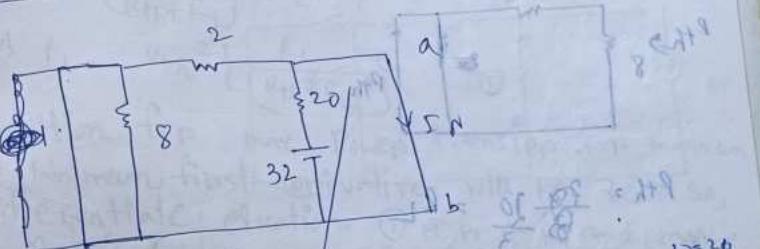
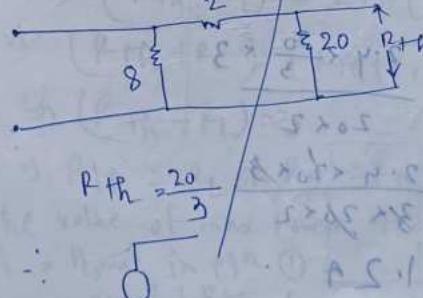
$$\begin{aligned} V_N &= \frac{16}{32+10} \times 10 \\ &= 4.8 \text{ A} \end{aligned}$$



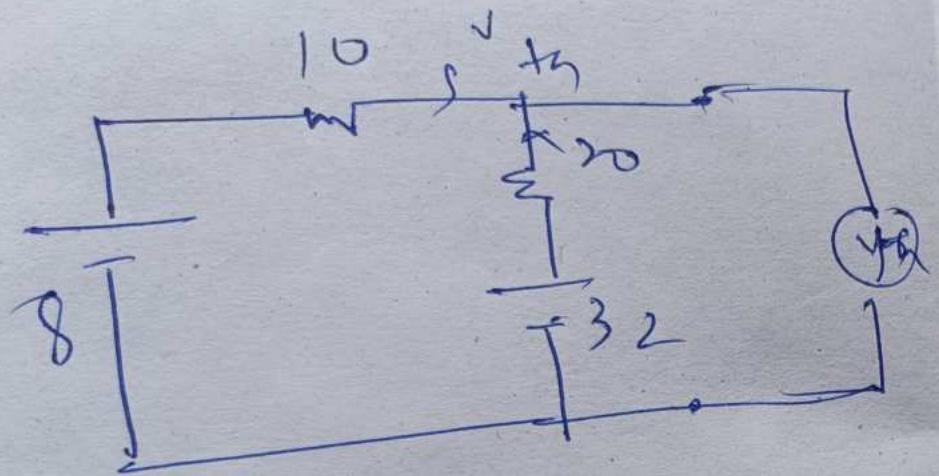


$$\frac{V_{TH} - 8}{10} + \frac{V_{TH} - 32}{20} = 0$$

$$\Rightarrow \frac{2V_{TH} - 16 + V_{TH} - 32}{20} = 0$$


$$\Rightarrow 3V_{TH} - 48 = 0$$

$$\Rightarrow V_{TH} = 16$$

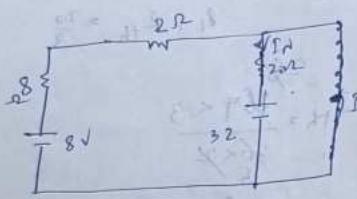


$$I_{th} = \frac{3/2 - 8}{10} = \frac{2}{10} = 0.2 \text{ A}$$

maximum 2 in shorting

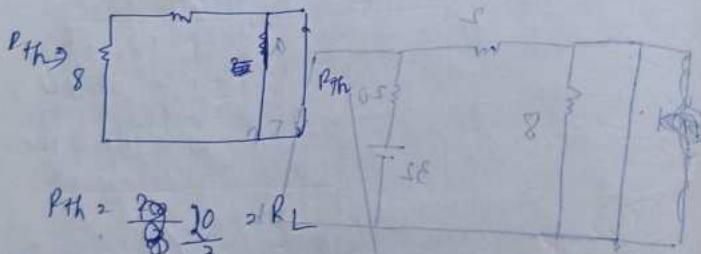
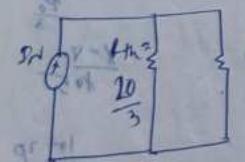
$$P_{th} = \frac{8^2}{8+3} = 1.6 \text{ W} = R_L$$




$$\therefore I_{th} = \frac{2 \cdot 4 \times \frac{20}{3} \times 3}{20+2} = 2 \cdot 4 \times \frac{20 \times 3}{3 \times 20 \times 2} = 1.2 \text{ A}$$

$$= \frac{2 \cdot 4 \times 20 \times 3}{3 \times 20 \times 2} = 1.2 \text{ A}$$

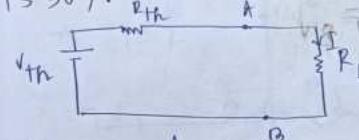2.1.2 A

Prove that $R_L = R_{th}$ in case of maximum power transfer theorem and also prove circuit deficiency is 50%.



The amount of power dissipated across the load resistors is $P_L = I^2 R_L$

Substitute $I = \frac{V_{th}}{R_{th}+R_L}$ in the above equation,

$$P_L = \left(\frac{V_{th}}{R_{th}+R_L} \right)^2 R_L$$

$$\Rightarrow P_L = V_{th}^2 \left\{ \frac{R_L}{(R_{th}+R_L)^2} \right\} \quad \text{--- (1)}$$

Condition for max Power transfer. For maximum or minimum first derivative will be zero. So, differentiate equation (1) w.r.t R_L and make it equal to '0'.

$$\frac{dP_L}{dR_L} = V_{th}^2 \left\{ \frac{(R_{th}+R_L)^2 - R_L \times 2(R_{th}+R_L)R_L}{(R_{th}+R_L)^4} \right\}_{R_L=0}$$

$$\Rightarrow (R_{th}+R_L)^2 - 2R_L(R_{th}+R_L) = 0$$

$$\Rightarrow (R_{th}+R_L)(R_{th}+R_L - 2R_L) = 0$$


$$\Rightarrow (R_{th}+R_L) = 0$$

$$\Rightarrow P_{th} = R_L \text{ or } R_L = R_{th} \text{ (Proved, 1st one)}$$

The value of max Power transfer, substitute $R_L = R_{th}$, $P_L = P_{max}$ in eqn (1).

$$P_{max} = V_{th}^2 \left\{ \frac{R_{th}}{(R_{th}+R_{th})^2} \right\} = \frac{V_{th}^2}{4R_{th}} \Rightarrow \frac{\sqrt{V_{th}}^2}{4R_{th}} \quad [\because R_L = R_{th}]$$
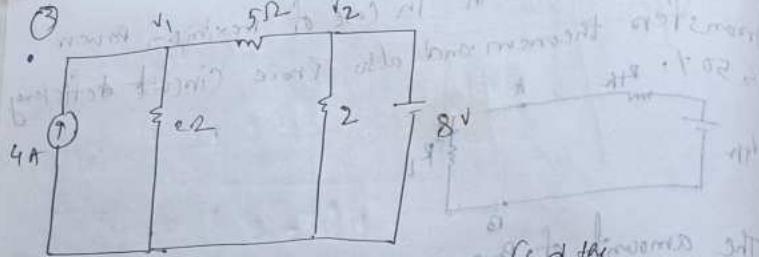
$$\text{Efficiency (h)} = \frac{\text{output}}{\text{input}} \times 100 = \frac{I_L^2 R_L / 2R_{th}^2 R_L}{I_{th}^2 R_{th}} \times 100 = 50\%$$



for the circuit showing figure find the node voltages v_1 and v_2 using the superposition theorem.

Step 1

$$0 \rightarrow \frac{4v_1}{2} + \frac{v_1 - v_2}{2} + \frac{v_1}{5} = 4$$

$$\frac{4v_1}{2} + \frac{v_1 - v_2}{2} + \frac{v_1}{5} = 4$$

$$40 + 5v_1 + 2v_1 - 2v_2 = 40$$

$$7v_1 - 2v_2 = 40 \quad (1)$$

Step 2

$$0 = (14 - 19 + 9) \Rightarrow 0 = -4 \Rightarrow 4 = 14 - 19 + 9$$

$$7v_1 - 2v_2 = -40 \quad (2)$$

Step 3

$$0 = (14 - 19 + 9) \Rightarrow 0 = -4 \Rightarrow 4 = 14 - 19 + 9$$

$$7v_1 - 2v_2 = -40 \quad (1)$$

$$7v_1 - 2v_2 = 40 \quad (2)$$

$$14v_1 - 8v_2 = 0$$

$$14v_1 = 8v_2$$

$$v_2 = \frac{14}{8}v_1$$

$$v_2 = \frac{7}{4}v_1$$

$$v_2 = 1.75v_1$$

$$v_2 = 1.75(14 - 19 + 9)$$

$$v_2 = 1.75(-4)$$

$$v_2 = -7$$

$$v_1 = 14 - 19 + 9$$

$$v_1 = -4$$

$$v_1 = 14 - 19 + 9$$

$$v_1 = -4$$

$$\rightarrow \frac{2\sqrt{2} - 2\sqrt{1} + 5\sqrt{2}}{10} = 0$$

$$\rightarrow 7\sqrt{2} - 2\sqrt{1} = 0 \quad (1)$$

$$7\sqrt{2} - 2\sqrt{1} = 0$$

$$\sqrt{2} = \frac{2\sqrt{1}}{7}$$

from (1),

$$[7v_1 - 2 \times \frac{2}{7}v_1 = -40] \text{ calculation}$$

$$\rightarrow 7v_1 - \frac{4v_1}{7} = -40$$

$$\rightarrow \frac{49v_1 - 4v_1}{7} = -40$$

$$\rightarrow 45v_1 = -40 \times 7$$


$$\rightarrow v_1 = \frac{-40 \times 7}{45}$$

$$= -6.22 \approx -6.2$$

$$= -6.22 \approx -6.2$$

$$v_2 = \frac{-2 \times 6.22}{7} \quad [7v_1 - 2v_2 = 0]$$

$$= 1.75 \times 6.22$$

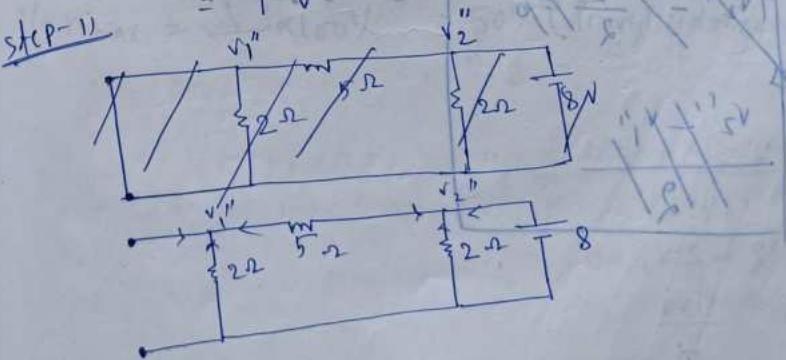

$$\begin{aligned}
 & \frac{V_1'' - V_2'' + V_2''}{5} = 0 \\
 & \Rightarrow \frac{2V_2'' - 2V_1'' + 5V_2''}{10} = 0 \\
 & \Rightarrow 7V_2'' - 2V_1'' = 0 \\
 & \Rightarrow V_2'' = \frac{2}{7}V_1'' \\
 & \therefore V_1'' = 1V, V_2'' = 3.5V
 \end{aligned}$$

$$\begin{aligned}
 & \frac{V_1''}{2} + \frac{V_1'' - V_2''}{5} = 0 \\
 & \Rightarrow 5V_1'' - 2V_2'' = 2V_1'' = 0 \\
 & \Rightarrow V_1'' = \frac{2}{3}V_2'' = \frac{2}{3} \cdot 3.5V = \frac{7}{3}V
 \end{aligned}$$

assignment

$$n_{\max} = \frac{P_{th,\max}}{P_S} \quad \text{--- (11)}$$

where,

$$P_S = I^2 R_{th} + I^2 R_L$$

$$\Rightarrow P_S = 2I^2 R_{th} \quad [\because R_L = R_{th}]$$

Substitute $I = \frac{V_{th}}{2R_{th}}$ in the above equation

$$P_S = 2 \left(\frac{V_{th}}{2R_{th}} \right)^2 R_{th}$$

$$\Rightarrow P_S = 2 \left(\frac{V_{th}^2}{4R_{th}^2} \right) R_{th}$$

$$= \frac{V_{th}^2}{2R_{th}}$$

from eqn (11)

$$n_{\max} = \frac{\left(\frac{V_{th}^2}{2R_{th}} \right)}{\left(\frac{V_{th}^2}{2R_{th}} \right)} = 1$$

$$n_{\max} = \frac{1}{2} \quad \text{--- (11)} \quad \therefore n_{\max} = \frac{1}{2} = 50\% \quad (\text{Proved, 2nd one})$$


$$0 = \frac{5V}{8} + \frac{1V}{2} - \frac{11 - 1V}{8}$$

$$0 = \frac{5V}{8} + \frac{4V}{8} - \frac{10V}{8}$$

$$0 = \frac{9V}{8} - \frac{10V}{8}$$


$$0 = \frac{-V}{8} \quad \text{--- (11)}$$

$$V = 8V$$

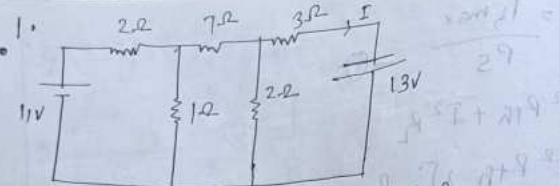

Determine the current through 3Ω resistor branch as shown in the figure using a) Thevenin's theorem.

b) Norton's theorem.

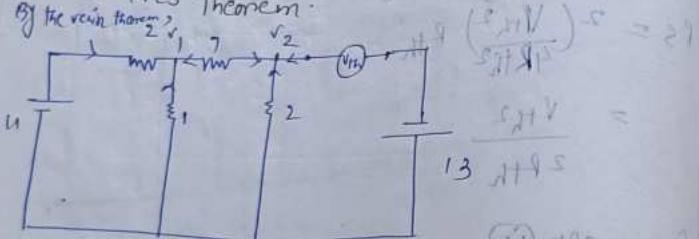

$$\frac{v_1 - 11}{2} + \frac{v_1}{1} + \frac{v_1 - v_2}{7} = 0$$

$$\frac{7v_1 - 77 + 14v_1 + 2v_1 - 2v_2}{14} = 0$$

$$23v_1 - 2v_2 = 77 \quad (1) \quad \frac{1}{c} = \text{NOM}$$

$$\frac{v_2 - V_{\text{parallel}}(v_1, v_2)}{7} + \frac{v_2}{2} = 0$$

$$\frac{2v_2 - 2v_1 + 7v_2}{14} = 0$$

$$9v_2 - 2v_1 = 0$$

$$v_1 = \frac{9v_2}{2}$$


from ①

$$23 \times \frac{9v_2}{2} - 2v_2 = 77$$

$$\frac{207v_2 - 4v_2}{2} = 77$$

$$203v_2 = 77 \times 2$$
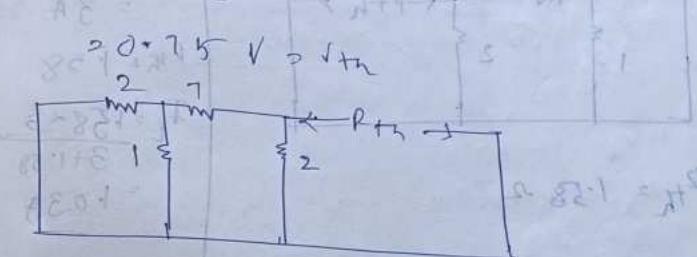
$$\sqrt{2} \times \frac{77 \times 2}{203} = \frac{E_{TH}}{R_{TH}}$$



$$R_{TH} = 1.58 \Omega$$

$$I_{TH} = \frac{0.75}{1.58 + 3}$$


$$= 0.163 A$$


$$V_{TH} = 9V$$

$$R_{TH} = 1.58$$

$$\therefore I_{TH} = \frac{9}{1.58 + 3}$$

$$= 1.06$$

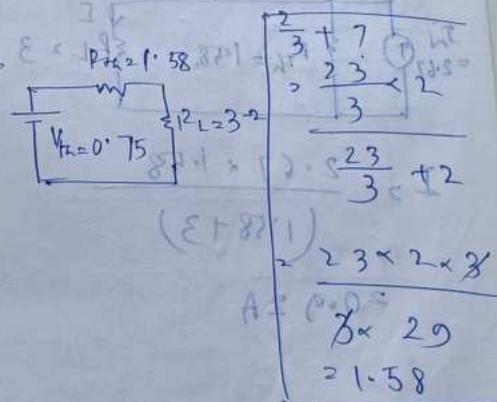

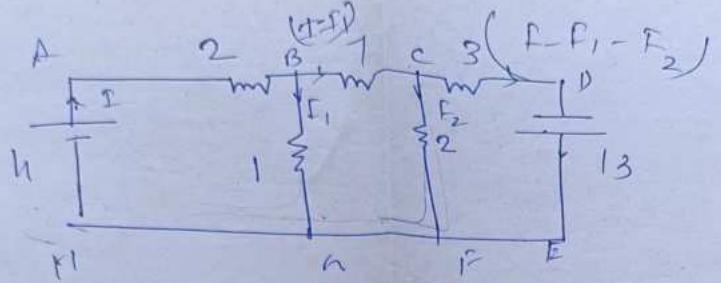

$$ABG_1(A), \quad \sqrt{t} \frac{3x^3}{t^2 - 9}$$

$$2I + I_1 = 11 \quad -\textcircled{1}$$

ADT HA,

$$2I + 1(I - I_1) + 3(I - I_1 - I_2) = 13 - 11$$

$$2I_1 + 3I_2 = 24$$

$$\begin{array}{l} \rightarrow 12I - 10I_1 - 3I_2 = 24 \\ \rightarrow I - 10I_1 - \frac{3}{2}(8I_1 - 7I) = 24 \\ \rightarrow 24I - 2 \end{array}$$

$$\Rightarrow 12I - 10I_1 - 5I_2 = 29$$

$$\Rightarrow 12I - 10I_1 - 3(8I_1 - 7I) = 29$$

$$\Rightarrow 24I - 20I_1 - 24I + 21I = 48$$

BL FRN,

$$24I_1 - 44I_1 = 48$$

$$\begin{aligned} f_2 &= \frac{1}{2}(x-1) + 2f_2 - f_1 = 0 \\ f_1 &= 11 \quad 2f_1 - 2f_2 = 0 \end{aligned}$$

$$\begin{array}{l} 2x + y = 1 \\ x - 3y = 0 \end{array}$$

~~115~~


$$88f + 44I_1 = 184$$

$$45I - 44f = 532$$


$$2I - f = 11$$

$$45I - 44f = 184$$


By Norton's theorem,

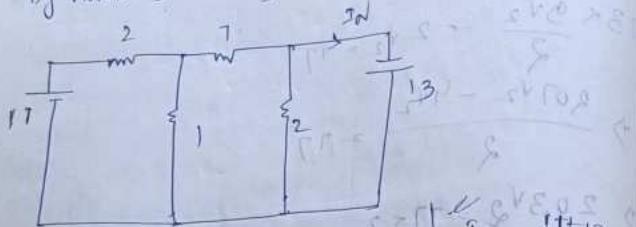
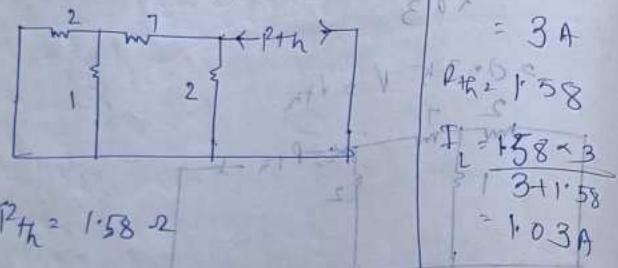
$$I_N = \frac{V}{R_{\text{eff}}} = \frac{11+13}{2+7} = 2.67 \text{ A}$$



$$R_{Th} = 1.58 \Omega$$

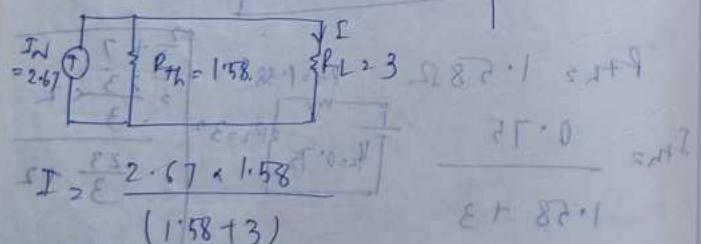

$$I_{Th} = \frac{11}{2+1.58} = 4.21 \text{ A}$$

$$\frac{V}{1.58+3} = 0.92 \text{ A}$$

$$0.92 \times 1.58 = 1.44 \text{ V}$$

$$1.44 + 11 = 12.44 \text{ V}$$

$$12.44 / 2 = 6.22 \text{ V}$$

$$6.22 - 11 = -4.78 \text{ V}$$

$$-4.78 / 1.58 = -3.02 \text{ A}$$

$$-3.02 \times 1.58 = -4.78 \text{ V}$$

$$-4.78 - 11 = -15.78 \text{ V}$$

$$-15.78 / 2 = -7.89 \text{ V}$$

$$-7.89 - 11 = -18.89 \text{ V}$$

$$-18.89 / 1.58 = -11.89 \text{ A}$$

$$-11.89 \times 1.58 = -18.89 \text{ V}$$

$$-18.89 - 11 = -29.89 \text{ V}$$

$$-29.89 / 2 = -14.9 \text{ V}$$

$$-14.9 - 11 = -25.9 \text{ V}$$

$$-25.9 / 1.58 = -16.1 \text{ A}$$

$$-16.1 \times 1.58 = -25.9 \text{ V}$$

$$-25.9 - 11 = -37 \text{ V}$$

$$-37 / 2 = -18.5 \text{ V}$$

$$-18.5 - 11 = -29.5 \text{ V}$$

$$-29.5 / 1.58 = -18.5 \text{ A}$$

$$-18.5 \times 1.58 = -29.5 \text{ V}$$

$$-29.5 - 11 = -40.5 \text{ V}$$

$$-40.5 / 2 = -20.25 \text{ V}$$

$$-20.25 - 11 = -31.25 \text{ V}$$

$$-31.25 / 1.58 = -19.8 \text{ A}$$

$$-19.8 \times 1.58 = -31.25 \text{ V}$$

$$-31.25 - 11 = -42.25 \text{ V}$$

$$-42.25 / 2 = -21.125 \text{ V}$$

$$-21.125 - 11 = -32.125 \text{ V}$$

$$-32.125 / 1.58 = -20.25 \text{ A}$$

$$-20.25 \times 1.58 = -32.125 \text{ V}$$

$$-32.125 - 11 = -43.125 \text{ V}$$

$$-43.125 / 2 = -21.5625 \text{ V}$$

$$-21.5625 - 11 = -32.5625 \text{ V}$$

$$-32.5625 / 1.58 = -20.25 \text{ A}$$

$$-20.25 \times 1.58 = -32.5625 \text{ V}$$

$$-32.5625 - 11 = -43.5625 \text{ V}$$

$$-43.5625 / 2 = -21.78125 \text{ V}$$

$$-21.78125 - 11 = -32.78125 \text{ V}$$

$$-32.78125 / 1.58 = -20.25 \text{ A}$$

$$-20.25 \times 1.58 = -32.78125 \text{ V}$$

$$-32.78125 - 11 = -43.78125 \text{ V}$$

$$-43.78125 / 2 = -21.890625 \text{ V}$$

$$-21.890625 - 11 = -32.890625 \text{ V}$$

$$-32.890625 / 1.58 = -20.25 \text{ A}$$

$$-20.25 \times 1.58 = -32.890625 \text{ V}$$

$$-32.890625 - 11 = -43.890625 \text{ V}$$

$$-43.890625 / 2 = -21.9453125 \text{ V}$$

$$-21.9453125 - 11 = -32.9453125 \text{ V}$$

$$-32.9453125 / 1.58 = -20.25 \text{ A}$$

$$-20.25 \times 1.58 = -32.9453125 \text{ V}$$

$$-32.9453125 - 11 = -43.9453125 \text{ V}$$

$$-43.9453125 / 2 = -21.97265625 \text{ V}$$

$$-21.97265625 - 11 = -33.97265625 \text{ V}$$

$$-33.97265625 / 1.58 = -20.25 \text{ A}$$

$$-20.25 \times 1.58 = -33.97265625 \text{ V}$$

$$-33.97265625 - 11 = -44.97265625 \text{ V}$$

$$-44.97265625 / 2 = -22.486328125 \text{ V}$$

$$-22.486328125 - 11 = -33.486328125 \text{ V}$$

$$-33.486328125 / 1.58 = -20.25 \text{ A}$$

$$-20.25 \times 1.58 = -33.486328125 \text{ V}$$

$$-33.486328125 - 11 = -44.486328125 \text{ V}$$

$$-44.486328125 / 2 = -22.2431640625 \text{ V}$$

$$-22.2431640625 - 11 = -33.2431640625 \text{ V}$$

$$-33.2431640625 / 1.58 = -20.25 \text{ A}$$

$$-20.25 \times 1.58 = -33.2431640625 \text{ V}$$

$$-33.2431640625 - 11 = -44.2431640625 \text{ V}$$

$$-44.2431640625 / 2 = -22.12158203125 \text{ V}$$

$$-22.12158203125 - 11 = -33.12158203125 \text{ V}$$

$$-33.12158203125 / 1.58 = -20.25 \text{ A}$$

$$-20.25 \times 1.58 = -33.12158203125 \text{ V}$$

$$-33.12158203125 - 11 = -44.12158203125 \text{ V}$$

$$-44.12158203125 / 2 = -22.060791015625 \text{ V}$$

$$-22.060791015625 - 11 = -33.060791015625 \text{ V}$$

$$-33.060791015625 / 1.58 = -20.25 \text{ A}$$

$$-20.25 \times 1.58 = -33.060791015625 \text{ V}$$

$$-33.060791015625 - 11 = -44.060791015625 \text{ V}$$

$$-44.060791015625 / 2 = -22.0303955078125 \text{ V}$$

$$-22.0303955078125 - 11 = -33.0303955078125 \text{ V}$$

$$-33.0303955078125 / 1.58 = -20.25 \text{ A}$$

$$-20.25 \times 1.58 = -33.0303955078125 \text{ V}$$

$$-33.0303955078125 - 11 = -44.0303955078125 \text{ V}$$

$$-44.0303955078125 / 2 = -22.01519775390625 \text{ V}$$

$$-22.01519775390625 - 11 = -33.01519775390625 \text{ V}$$

$$-33.01519775390625 / 1.58 = -20.25 \text{ A}$$

$$-20.25 \times 1.58 = -33.01519775390625 \text{ V}$$

$$-33.01519775390625 - 11 = -44.01519775390625 \text{ V}$$

$$-44.01519775390625 / 2 = -22.007598876953125 \text{ V}$$

$$-22.007598876953125 - 11 = -33.007598876953125 \text{ V}$$

$$-33.007598876953125 / 1.58 = -20.25 \text{ A}$$

$$-20.25 \times 1.58 = -33.007598876953125 \text{ V}$$

$$-33.007598876953125 - 11 = -44.007598876953125 \text{ V}$$

$$-44.007598876953125 / 2 = -22.003799438476562 \text{ V}$$

$$-22.003799438476562 - 11 = -33.003799438476562 \text{ V}$$

$$-33.003799438476562 / 1.58 = -20.25 \text{ A}$$

$$-20.25 \times 1.58 = -33.003799438476562 \text{ V}$$

$$-33.003799438476562 - 11 = -44.003799438476562 \text{ V}$$

$$-44.003799438476562 / 2 = -22.001899719238281 \text{ V}$$

$$-22.001899719238281 - 11 = -33.001899719238281 \text{ V}$$

$$-33.001899719238281 / 1.58 = -20.25 \text{ A}$$

$$-20.25 \times 1.58 = -33.001899719238281 \text{ V}$$

$$-33.001899719238281 - 11 = -44.001899719238281 \text{ V}$$

$$-44.001899719238281 / 2 = -22.00094985961914 \text{ V}$$

$$-22.00094985961914 - 11 = -33.00094985961914 \text{ V}$$

$$-33.00094985961914 / 1.58 = -20.25 \text{ A}$$

$$-20.25 \times 1.58 = -33.00094985961914 \text{ V}$$

$$-33.00094985961914 - 11 = -44.00094985961914 \text{ V}$$

$$-44.00094985961914 / 2 = -22.00047492980957 \text{ V}$$

$$-22.00047492980957 - 11 = -33.00047492980957 \text{ V}$$

$$-33.00047492980957 / 1.58 = -20.25 \text{ A}$$

$$-20.25 \times 1.58 = -33.00047492980957 \text{ V}$$

$$-33.00047492980957 - 11 = -44.00047492980957 \text{ V}$$

$$-44.00047492980957 / 2 = -22.000237464904785 \text{ V}$$

$$-22.000237464904785 - 11 = -33.000237464904785 \text{ V}$$

$$-33.000237464904785 / 1.58 = -20.25 \text{ A}$$

$$-20.25 \times 1.58 = -33.000237464904785 \text{ V}$$

$$-33.000237464904785 - 11 = -44.000237464904785 \text{ V}$$

$$-44.000237464904785 / 2 = -22.000118732452392 \text{ V}$$

$$-22.000118732452392 - 11 = -33.000118732452392 \text{ V}$$

$$-33.000118732452392 / 1.58 = -20.25 \text{ A}$$

$$-20.25 \times 1.58 = -33.000118732452392 \text{ V}$$

$$-33.000118732452392 - 11 = -44.000118732452392 \text{ V}$$

$$-44.000118732452392 / 2 = -22.000059366226196 \text{ V}$$

$$-22.000059366226196 - 11 = -33.000059366226196 \text{ V}$$

$$-33.000059366226196 / 1.58 = -20.25 \text{ A}$$

$$-20.25 \times 1.58 = -33.000059366226196 \text{ V}$$

$$-33.000059366226196 - 11 = -44.000059366226196 \text{ V}$$

$$-44.000059366226196 / 2 = -22.000029683113098 \text{ V}$$

$$-22.000029683113098 - 11 = -33.000029683113098 \text{ V}$$

$$-33.000029683113098 / 1.58 = -20.25 \text{ A}$$

$$-20.25 \times 1.58 = -33.000029683113098 \text{ V}$$

$$-33.000029683113098 - 11 = -44.000029683113098 \text{ V}$$

$$-44.000029683113098 / 2 = -22.000014831565049 \text{ V}$$

$$-22.000014831565049 - 11 = -33.000014831565049 \text{ V}$$

$$-33.000014831565049 / 1.58 = -20.25 \text{ A}$$

$$-20.25 \times 1.58 = -33.000014831565049 \text{ V}$$

$$-33.000014831565049 - 11 = -44.000014831565049 \text{ V}$$



$$-44.000014831565049 / 2 = -22.000007415782524 \text{ V}$$

$$-22.000007415782524 - 11 = -33.000007415782524 \text{ V}$$


$$-33.000007415782524 / 1.58 = -20.25 \text{ A}$$

$$-20.25 \times 1.58 = -33.000007415782524 \text{ V}$$


$$-33.000007415782$$

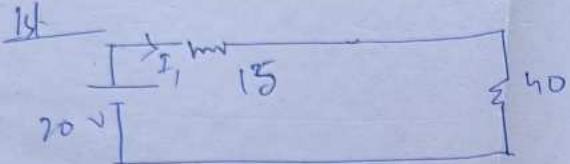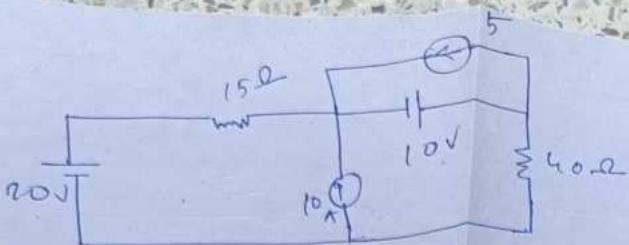

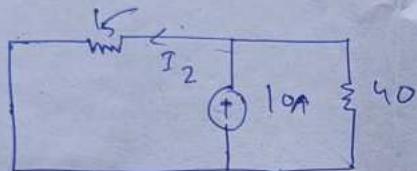
$$I_1 = \frac{20}{15 + 40} = 0.363 \text{ A}$$


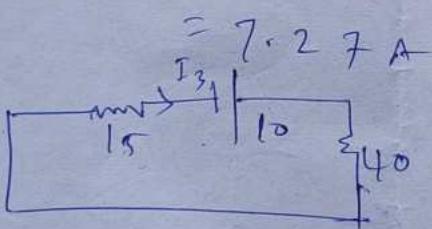
$$I_2 = \frac{10 \times 40}{15 + 40} \quad \therefore V_{15} = 6.727 \times 15 \\ = 100 \text{ V}$$




$$I_3 = \frac{10}{15 + 40}$$

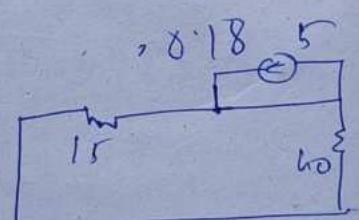

Ans : If 13 statement
current
is 0.18
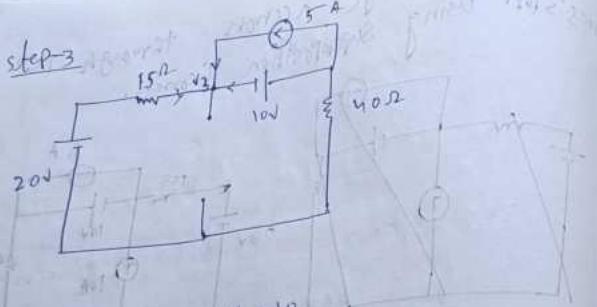
$$\therefore I = 0.363 - 7.27 + 0.18 \\ = -6.727$$




$$V_3 - \frac{20}{15} + 5 + \frac{V_3 + 10}{40} = 0$$

$$\Rightarrow \frac{8V_3 - 160 + 600 + 3V_3 + 30}{120} = 0$$

$$\Rightarrow 11V_3 = -970$$

$$\Rightarrow V_3 = -87.2V$$

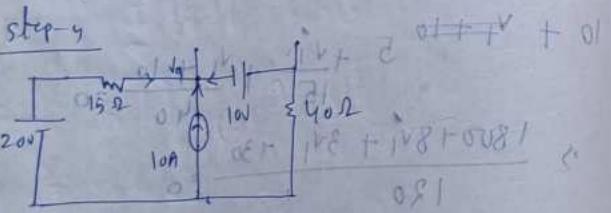


$$\frac{V_4 - 20}{15} + \frac{V_4 + 10}{40} + 10 = 0 \Rightarrow V_4 = -11V$$

$$\Rightarrow \frac{8V_4 - 160 + 3V_4 + 30 + 120}{120} = 0 \Rightarrow V_4 = -11V$$


$$\frac{V_4 + 20}{15} + 11V_4 = 1070$$

$$\Rightarrow V_4 = -87.2V$$

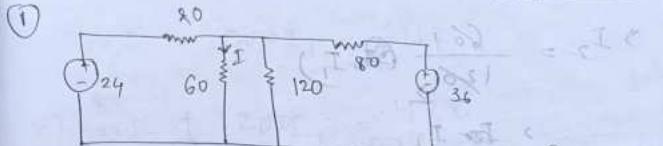Total Nodal voltage = $166 + 149 + 42.7 + 97.2$
 $V_{Nodal} = 455V$



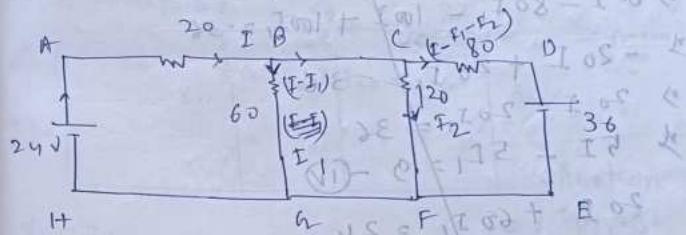In the circuit shown in the figure determine the current through 60Ω resistor using mesh analysis.



For Loop A-B-C-D applying mesh analysis

$$20I_1 + 60(I_1 - I_2) = 24$$

$$\Rightarrow 20I_1 + 60I_1 = 24 \Rightarrow I_1 = 0.2A$$

For loop B-C-D-E applying mesh analysis

$$120I_2 + 80(I_2 - I_1 - I_3) = -36$$

$$\Rightarrow 80I_2 - 80I_1 - 80I_2 - 120I_2 = -36$$

$$\Rightarrow 80I_2 - 200I_2 = -36 \Rightarrow I_2 = 0.18A$$

For loop C-D-E-B applying mesh analysis

$$120I_2 - 60(I_2 - I_1) = 0$$

$$\Rightarrow 120I_2 = 60I_1 \Rightarrow I_2 = \frac{60}{120}I_1$$

$$\rightarrow I_2 = \frac{60I_1}{136} \quad (1)$$

$$\rightarrow \frac{20I_1}{2} - (1) \quad (2)$$

from (1)

$$80I - 80I_1 - \frac{100}{200} (I - I_1) - 36$$

$$\rightarrow 80I - 80I_1 - 100I + 100I_1 = -36$$

$$\rightarrow -20I + 20I_1 = -36$$

$$\rightarrow 20I - 20I_1 = 36$$

$$\rightarrow 5I - 5I_1 = 9 \quad (3)$$

$$20I + 60I_1 = 24$$

$$\rightarrow 5I + 15I_1 = 6 \quad (4)$$

$$\rightarrow 5I - 5I_1 = 9 \quad (5)$$

$$\rightarrow 20I_1 = -3$$

$$\rightarrow I_1 = -\frac{3}{20} A$$

$$(1) \rightarrow 80I - 80I_1 - 100I + 100I_1 = -36$$

$$\rightarrow 80I - 80I_1 - 200 \times \frac{I_1}{2} = -36$$

$$\rightarrow 80I - 80I_1 - 100I_1 = -36$$

$$\rightarrow 80I - 180I_1 = -36 \quad (6)$$

$$\rightarrow 5I + 15I_1 = 18 \quad (7)$$

$$\rightarrow I_1 = 0.314 A$$


$$400f - 500I_1 = -180$$

$$\rightarrow 400I + 1200I_1 = 480$$

$$\rightarrow -2100I_1 = -660$$

$$\rightarrow I_1 = 0.314 A$$

Nodal analysis

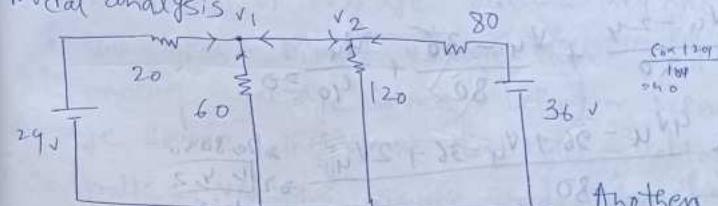

another

process

$$\frac{v_1 - 24}{20} + \frac{v_1}{60} = 0 + \frac{v_1 - v_2}{120} \quad v_2 = 0.81 \text{ V}$$

$$\rightarrow \frac{3v_1 - 72 + v_1}{60} = 10 \quad v_1 = 14.4 \text{ V}$$

$$\rightarrow \frac{(v_1 - 14.4) + 2v_1 + v_1 - v_2}{120} = 0 \quad v_2 = 14.4 \text{ V}$$


$$\rightarrow 9v_1 - v_2 = 144 \quad (1)$$

$$\rightarrow v_2 = 14.4 \text{ V}$$

$$\rightarrow 9v_1 - 144 = 144 \quad (2)$$

$$\rightarrow v_1 = 32 \text{ V}$$
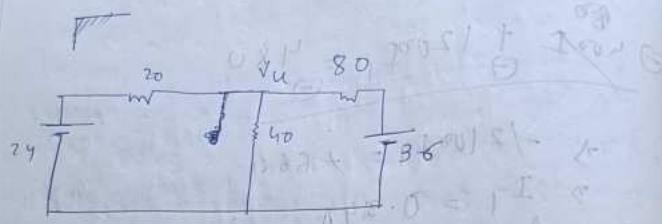
$$\rightarrow 9(32) - 144 = 144 \quad (3)$$



$$\frac{V_u - 24}{20} + \frac{V_u - 36}{80} + \frac{V_u}{40} = 0$$

$$\therefore \frac{4V_u - 96 + V_u - 36 + 2V_u}{80} = 0$$


$$\therefore 7V_u = 132$$

$$\therefore V_u = 18.85V$$

$$\therefore I_u = \frac{18.85}{40}$$

$$= 0.47A$$

NOW

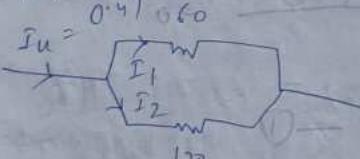

$$I_{1,2} = \frac{0.47 \times 120}{18.85}$$

$$= 0.314A$$

answering

① Classification of voltage and current Source.

② Dependent Current Source and voltage Source Independent symbol, CKD diagram.


③ Classification of voltage Source - They are of two types - Direct Voltage Source and Alternating voltage Source. Dependent dependent voltage source : they are two types - Voltage Controlled Voltage Source and Current Controlled Voltage Source.

Classification of current Source - Current Source is a circuit element which delivers energy with a specified current through it. If such a source maintains constant current for any voltage then it is called as an ideal current source. An ideal current source has infinite resistance (or impedance) across it.

④ Dependent Current Source - In the theory of electrical networks, a dependent source is a voltage source or a current source whose value depends on a voltage or current elsewhere in the network. Dependent sources are useful, for example, in modeling the behavior of amplifiers.


Symbol - Ideal dependent & voltage sources represented by a diamond-shaped symbol. are dependent on, and are proportional to an external controlling voltage or current I . The multiplying constant, M , for a $V_C V_S$ has no units, while the multiplying constant μ for a $C_V S$ has units of ohm's.

Circuit diagram -

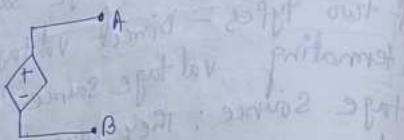

Independent voltage source - An independent voltage source is an idealized circuit component that fixes the voltage in a branch respectively, to a specified value.

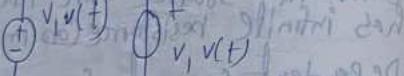Symbol - The middle symbol is the symbol for a specific type of independent voltage source known as a battery.




Dependent current source - In the theory of electrical networks, a dependent source is a voltage source or a current source whose value depends on a voltage or current elsewhere in the network. Dependent sources are

useful, for example, in modelling the behaviour of amplifiers.

Symbol - Ideal dependent & current sources represented by a diamond-shaped symbol. A circle with an arrow inside is the symbol to indicate the direction of current flow.


Circuit diagram -

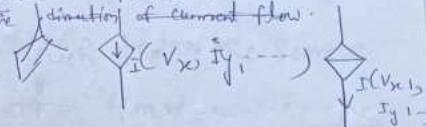


Independent current source - An independent current source is an energy source that pushes a constant flow of electrons through an electrical circuit regardless of the load presented to it. In other words, a 1 amp current source will maintain a current flow of 1 amp through its terminals if it has an open circuit or short circuit as a load.

Symbol - A circle with an arrow inside is the symbol to indicate the direction of the flow of the current.

Circuit diagram -

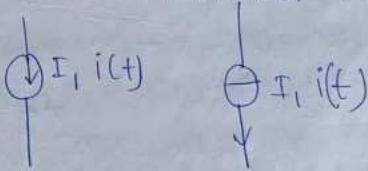

(2)

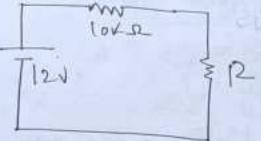

for the circuit shown above

It has 3 Part-

Part A - determine R such that the source delivers a power of 4mW.Part B - Determine R that results in $10k\Omega$ resistor to absorb ≈ 1.6 mW of PowerPart C = Replace R by a voltage source that will cause no power to be absorbed by any resistor.

Point-A

$$\frac{P_2}{R} \frac{V^2}{12}$$

$$P_2 = \frac{V^2}{R} = \frac{V^2}{12} = \frac{4 \times 10^{-3}}{12} = 3.33 \times 10^{-4} \text{ W}$$

$$\Rightarrow 4 \times 10^{-3} = \frac{(12)^2}{R}$$

$$\Rightarrow R = \frac{(12)^2}{4 \times 10^{-3}} = 3.6 \times 10^5 \Omega$$

$$\Rightarrow R + 10 \times 10^3 = 3.6 \times 10^5 \Omega$$

$$\Rightarrow R = 5 \times 10^4 \Omega$$

A- try

Part-B

$$P = \frac{V^2}{R} = \frac{V^2}{10 \times 10^3 + R}$$

$$\Rightarrow V^2 = 1.6 \times 10^{-9} \Omega$$

$$\Rightarrow 1.6 \times 10^{-9} \Omega + 1.6 \times 10^{-9} \Omega = V^2$$

$$\Rightarrow V^2 = 1.28 \times 10^{-9} \Omega$$

Power remains same always

$$1 \cdot 6 \times 10^6 = (16.5 \times 10^3)^2$$

$$\begin{aligned} P &= 10 \times 10^3 \\ \Rightarrow P &= 1.6 \times 10^6 \\ \Rightarrow R &= 10 \times 10^3 / 1.6 \times 10^6 = 0.9375 \text{ k}\Omega \end{aligned}$$

Part C: Showed that I am not able to do it.

If the diagram is a model of a system

$$+ \frac{12V}{12\sqrt{2} \text{ k}\Omega} \text{ and } -12V \text{ on ground line. Then } V_{AB} = 12V$$

$$\text{Then } V_{AC} = 12 - 12 = 0$$

$$\text{So } P = \frac{V^2}{R} = \frac{0}{10 \times 10^3} = 0 \text{ W}$$

No power can be absorbed by any resistor.

Part - B

$$I^2 \times 10 \times 10^3 = 1.6 \times 10^6$$

$$\Rightarrow I^2 = 12.64$$

$$P = V^2 / R$$

$$V = \sqrt{12^2 + 12^2} = \sqrt{2 \times 12^2} = 12\sqrt{2}$$

$$P = V^2 / R = 12\sqrt{2} \times 10 \times 10^3 = 1.6 \times 10^6$$

$$P = \frac{V^2}{R} = \frac{(12\sqrt{2})^2}{10 \times 10^3} = 10 \text{ k}\Omega$$

Ques

AC Signal

22/3/22

L N (Line and Neutral)


$P = VI \cos \phi$ [Angle between voltage and current ϕ]

$$P = VI (\text{DC})$$

1φ, 50 Hz

(Single Phase)

Pure DC

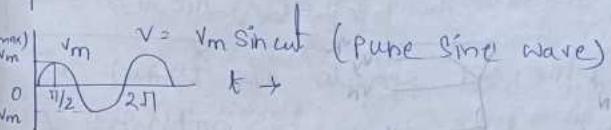


$$\begin{aligned} V_R &= V_m \sin \omega t \\ V_Y &= V_m \sin(\omega t - 120^\circ) \\ V_B &= V_m \sin(\omega t - 240^\circ) \end{aligned}$$

(P.E) $V_A = V_B$

(N.E) $V_B = V_A$

(P.E) $V_B = V_A$


(N.E) $V_B = V_A$

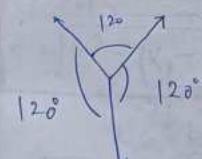

Rating = $444 \sqrt{3}$ (3-phase rating)

Line Voltage - If we connect a voltmeter between 2 lines then what voltage we will get that is line voltage: (3 Phase lines), V_{AB} , V_{BC} , V_{CA} .

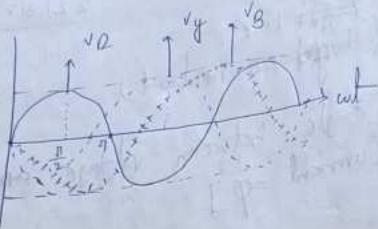Phase Voltage = V_{RN} , V_{YN} , V_{BN} , The voltage difference between line and neutral is called Phase voltage.




VCtors sum of V_x, V_y, V_z at any particular is '0'.

$$\begin{aligned} & \text{Dots} \\ & LV = PV \quad (3\phi) \\ & I_L = \sqrt{3} I_{ph} \end{aligned}$$

$$\begin{aligned} & \text{Star, } (3\phi) \\ & LV = \sqrt{3} PV \\ & I_L = I_{ph} \end{aligned}$$

Definitions:-

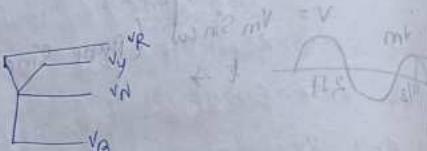1 Define waveform, P.C value, average value, frequency, time period, rms value, form factor, the relation between average and rms value, the relation between rms and average value, and normal value, phase, Phase sequence (ex).



Pure resistors

$$I = I_m \sin \omega t$$

Pure Inductors

$$I = I_m \sin(\omega t - \frac{\pi}{2})$$

In inductive crt the current is always lagging, the current will stay behind the voltage.

[$I \downarrow \rightarrow v$] (Phase diagram) in retarding

Pure Capacitor,

$$I = I_m \sin(\omega t + \frac{\pi}{2})$$

The current will always lead w.r.t. Voltage in capacitor crt. The current will stay upper the voltage. [$I \uparrow \rightarrow v$]



$$(a) L, X_L = 2\pi f L$$

$$(b) X_C = \frac{1}{2\pi f C}$$

$$R = \sqrt{R^2 + (X_L - X_C)^2}$$

$X_L > X_C \rightarrow$ inductive crt

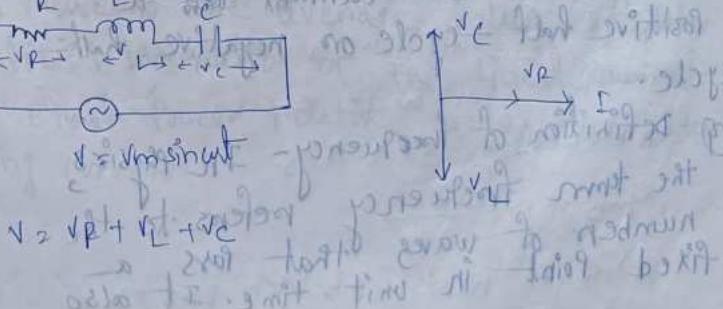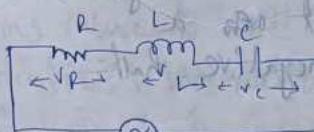$X_C > X_L \rightarrow$ capacitive resistance



- ① Definition of waveform - a usually graphic representation of the shape of a wave that indicates its characteristics (such as frequency and amplitude) - called also wave-shape.
- ② Definition of PIC value - the polymorphism information content (PIC) value is often used to measure the informativeness of a genetic marker for linkage studies. The PIC value was first derived for the case of a rare dominant disease, when one of the parents is affected and is a function of the particular mode of disease inheritance.
- ③ Definition of average value - The average value of alternating current is defined as the average of all values of current over a positive half-cycle or negative half-cycle.
- ④ Definition of frequency - In physics, the term frequency refers to the number of waves that pass a fixed point in unit time. It also
- describes the number of cycles or vibrations undergone during one unit of time by a body in periodic motion.
- ⑤ Definition of time period - The time period is the time taken by a complete cycle of the wave to pass a point.
- ⑥ Definition of rms value - The rms value is the effective value of a varying voltage or current. It is the equivalent steady DC (constant) value which gives the same effect. For example, a lamp connected to a 6V RMS AC supply will shine with the same brightness when connected to a steady 6V DC supply.
- ⑦ Form factor - In electronics or electrical engineering, the form factor of an alternating current waveform is the ratio of the RMS value to the average value. It identifies the ratio of the direct current of equal power relative to the given alternating current.

⑧ phase - A simple description is that a phase is a region of material that is chemically uniform, physically distinct, and (often) mechanically separable.

⑨ Phase sequence - phase rotation or phase sequence is the order in which the voltage waveforms of a polyphase AC source reach their respective peaks. For three-phase system, there are only two possible phase sequences: 1-2-3 and 3-2-1. Corresponding to the two possible directions of alternator real rotation.

Example - Clockwise rotation. Phase sequence $\rightarrow 1-2-3 \rightarrow$ counter clockwise rotation. Phase sequence: 3-2-1.

⑩ The RMS value is the square root of the mean (average) values of the squared function of the instantaneous values.

$$e_{rms} = e_{avg} \sqrt{\frac{\pi}{2}}$$

It is the relation between RMS and average value.

⑪ The relation between RMS value and normal value - $e_{rms} = \frac{e_0}{\sqrt{2}}$

⑫ The relation between average value and normal value - $e_{avg} = \frac{2e_0}{\pi}$

$$\begin{aligned} e_{avg} &= \frac{1}{(\frac{\pi T}{2})} \int_0^{\frac{\pi T}{2}} e_0 \sin \omega t dt \\ &= \frac{2}{T} \int_0^{\frac{\pi T}{2}} e_0 \sin \omega t dt \\ &= \frac{2e_0}{T} \left[-\frac{\cos \omega t}{\omega} \right]_0^{\frac{\pi T}{2}} \\ &= \frac{2e_0}{T \omega} \left[-\cos \frac{\omega T}{2} + 1 \right] \\ &= \frac{2e_0}{2\pi} \left[1 - \cos \frac{2\pi}{2} \right] \quad \left\{ T = \frac{2\pi}{\omega} \right\} \\ &= \frac{2e_0}{2\pi} \end{aligned}$$

$$\begin{aligned} e_{rms} &= \left[\frac{1}{T} \int_0^T e_0^2 dt \right]^{\frac{1}{2}} \\ e^2_{rms} &= \frac{1}{T} \int_0^T e_0^2 \sin^2 \omega t dt \quad [e^2 = e_0^2 \sin^2 \omega t] \\ &= \frac{e_0^2}{2T} \int_0^T 2 \sin^2 \omega t dt \\ &= \frac{e_0^2}{2T} \int_0^T (1 - \cos 2\omega t) dt \\ &= \frac{e_0^2}{2T} \left[t - \frac{\sin 2\omega t}{2\omega} \right]_0^T \end{aligned}$$

$$= \frac{e_0^2}{2T} \left[T - \frac{\sin 2\omega t}{2\omega} \right]$$

$$= \frac{e_0^2}{2T} \left[T - \frac{\sin 4\pi}{2\omega} \right] \quad [f: T = \frac{2\pi}{\omega}, WT = 2\pi]$$

$$= \frac{e_0^2}{2T} \times T$$

$$= \frac{e_0^2}{2}$$

$$e_{\text{rms}} = \frac{e_0}{\sqrt{2}}$$


• Sinusoidal Superposition Theorem —

In a linear bilateral network containing more than one independent source, the voltage across or the current that flows through any branch is algebraic sum of individual voltages or current produced by each independent source acting separately with all other independent sources being replaced by their internal resistance.


$$T = \left[\frac{1}{2\omega C} + \frac{1}{R} \right] \frac{1}{2\omega}$$

Ex —

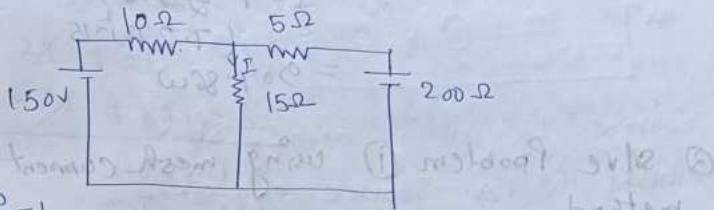- ① Using the principle of superposition, find the current through 15Ω resistor in the circuit shown in the fig. Also prove that superposition is not valid for power responses.




Step - I

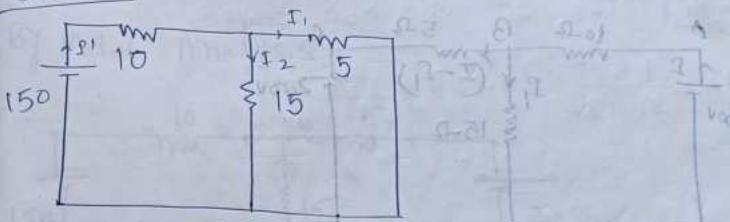

$$I'_1 = \frac{150}{13.75} = 10.91 \text{ A}$$

$$I'_2 = \frac{10.91 \times 5}{20} = 2.7275 \text{ A}$$

Step - II

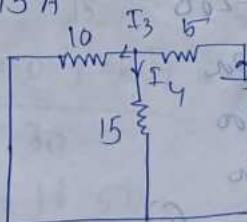


$$I'' = \frac{200}{110} = 18.18 \text{ A}$$

$$I'_3 = \frac{18.18 \times 10}{25} = 7.272 \text{ A}$$

$$I = I' + I'' = 2.7275 + 7.272 = 10 \text{ A}$$

right method - power supplied by the source - $I^2 R = (10)^2 \times 15 = 1500 \text{ W}$
 wrong method - power supplied by the source is $I_a^2 R + I_b^2 R$
 $= (2.728)^2 \times 15 + (7.272)^2 \times 15$
 $= 904.86 \text{ W}$

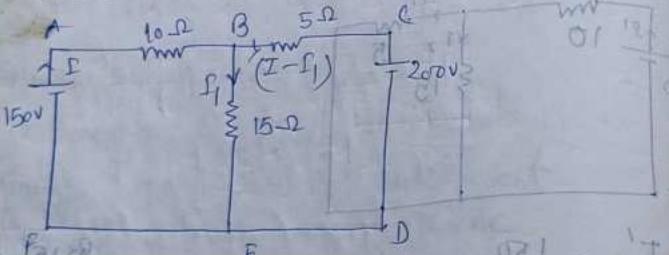② solve Problem ① using mesh current method.



Loop ABEFA,

$$10I + 15I_1 = 150 \quad \text{--- (1)}$$

Loop BCDEB,

$$5(I - I_1) - 15I_1 = -200 \quad \text{--- (2)}$$

$$\Rightarrow -5(I + I_1) + 15I_1 = 200$$

$$\Rightarrow 5I + 5I_1 + 15I_1 = 200$$

$$\Rightarrow 5I + 20I_1 = 200 \quad \text{--- (3)}$$

$$\Rightarrow -5I + 20I_1 = 200 \quad \text{--- (4)}$$

$$\begin{aligned} 10I + 15I_1 &= 150 \\ -5I + 20I_1 &= 200 \end{aligned} \quad \text{--- (1)} \quad \text{--- (4)}$$

$$A.0 = 2I + 3I_1 = 30 \quad \text{--- (5)}$$

$$-I + 4I_1 = 40 \quad \text{--- (6)}$$


By (1) $\times 4$ and (2) $\times 2$ we get

$$\begin{aligned} 8I + 12I_1 &= 120 \\ -3I + 12I_1 &= 80 \end{aligned}$$

$$\begin{aligned} 2I + 3I_1 &= 30 \\ -2I + 8I_1 &= 80 \end{aligned}$$

$$\begin{aligned} 11I_1 &= 110 \\ \Rightarrow I_1 &= 10 \text{ A} \end{aligned}$$

By Nodal Analysis,

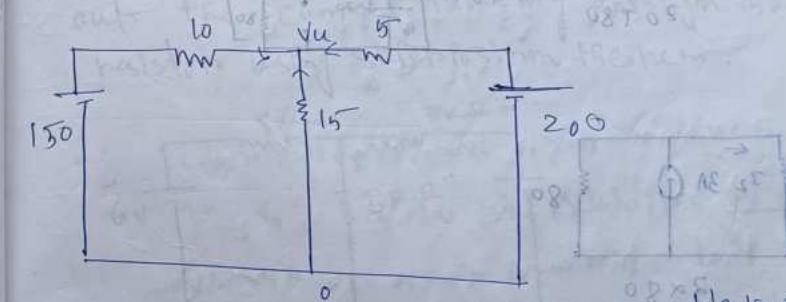

$$\frac{V_u - 150}{10} + \frac{V_u - 200}{15} + \frac{V_u - 0}{5} = 0$$

$$\Rightarrow \frac{3V_u - 450 + 2V_u + 6V_u - 1200}{30} = 0$$


$$\Rightarrow 11V_u = 1650$$

$$\Rightarrow V_u = 150 \text{ V}$$

$$A.0 = \frac{0.1}{0.08705} = 8 \text{ A}$$



$$I = \frac{150}{15} = 10 \text{ A}$$

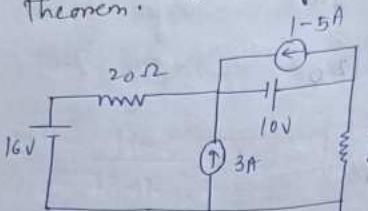- ! ③ Determine the voltage across 20Ω resistance in the circuit shown in the fig, using superposition theorem.




Source 16V acting alone; short circuit the 10V source and open circuit the 3A and 1.5A sources.

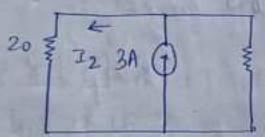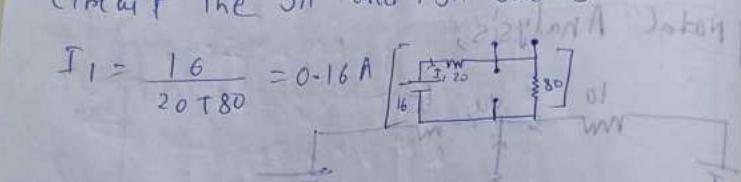
$$I_1 = \frac{16}{20+80} = 0.16 \text{ A}$$


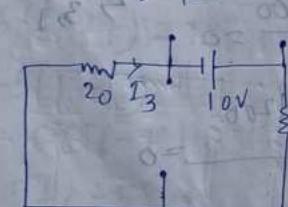
$$I_2 = \frac{3 \times 80}{80+20} = 2.4 \text{ A}$$



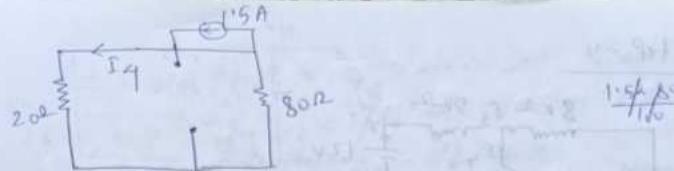
$$I_3 = \frac{10}{20+80} = 0.1 \text{ A}$$




Now $I_4 = 0$, since the current source 1.5A is short circuited. The current through 20Ω resistor is $0.16 - 2.4 + 0.1 = 2.14 \text{ A}$. The current 2.14 A flows from right to left. The voltage across 20Ω resistance is $2.14 \times 20 = 42.8 \text{ V}$.

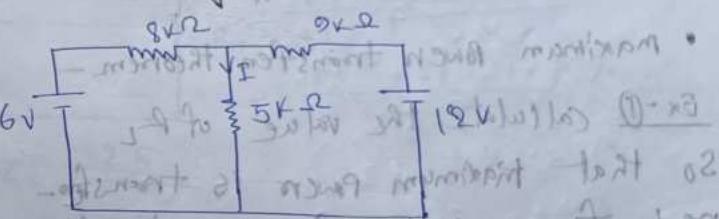- ④ For the circuit shown in the figure find out the current flowing through $5\text{k}\Omega$ resistor using superposition theorem.




Step-1

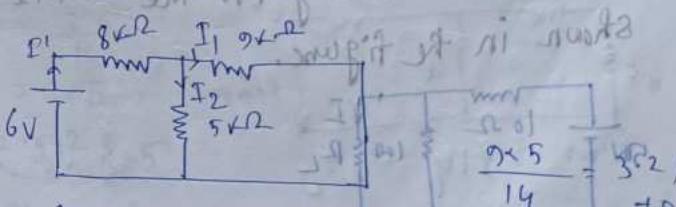

$$I_1 = \frac{6}{11.2 \times 10^3} = 5.35 \times 10^{-4} \text{ A}$$

$$I_2 = \frac{12 - 6}{14 \times 10^3} = 3.44 \times 10^{-4} \text{ A}$$

Step - 11

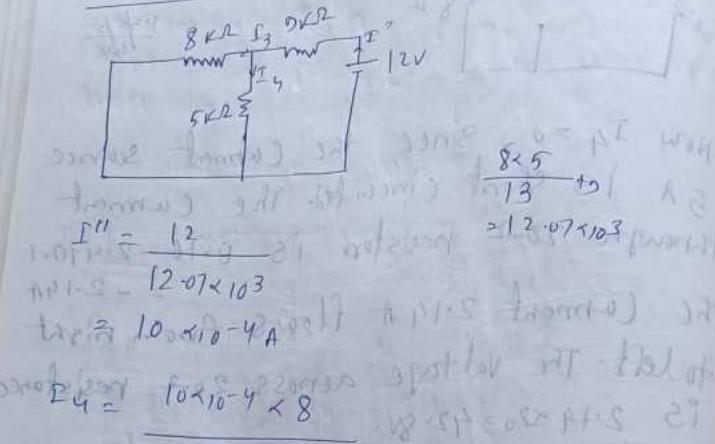

$$\text{With } 1.2 \text{ A} \text{ in } 10\Omega \text{ branch, } I_{\text{out}} = 1.2 \text{ A}$$


$$I_{\text{out}} = (3.4 + 6.2) \times 10^{-4} \text{ A}$$

$$= 10 \times 10^{-4} \text{ A}$$


• Maximum Power transfer theorem -

Ex - ① Calculate the value of R_L

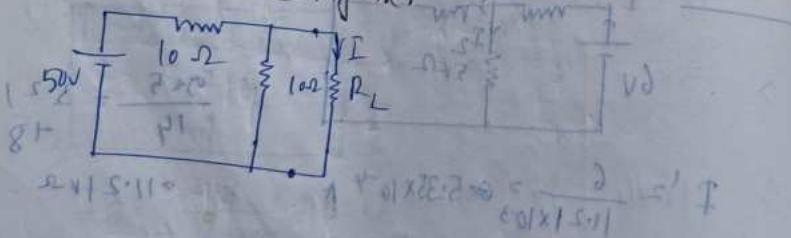So that maximum power is transferred from battery for the circuit shown in the figure.



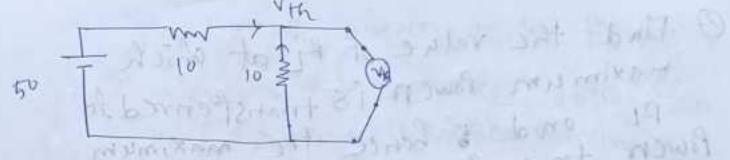
$$A.P.E = \frac{P}{P.M.E} = \frac{250}{100} = 2.5$$



$$\frac{V_{th} - 5}{10} + \frac{V_{th}}{10} = 0$$

$$2V_{th} = 50$$

$$\Rightarrow V_{th} = 25 \text{ V}$$

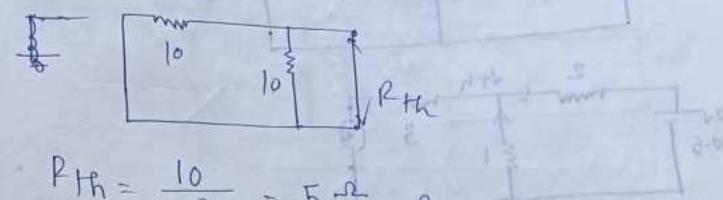


$$R_L > 5$$

$$R_L > \frac{50}{5} = 10 \Omega$$

$$I_{th} = \frac{25}{5+5} = \frac{25}{10} = 2.5 \text{ A}$$

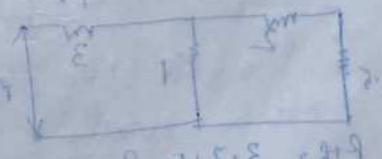
$$P = (2.5)^2 \times 5 = 31.25 \text{ W}$$



$$\frac{P.M.E}{P.M.E + P.th} = \frac{P.M.E}{P.M.E + P.th}$$

$$W.P.D = P.M.E > 100 \times 2.5 = 250 \text{ W}$$

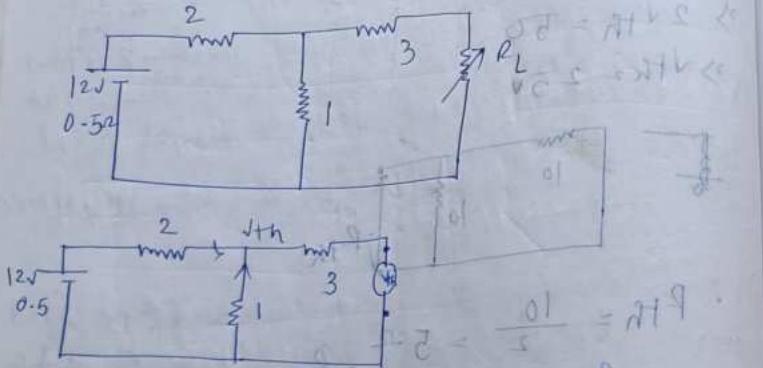② Find the value of R_L at which maximum power is transferred to R_L and hence the maximum power transferred to R_L in the circuit shown in fig.



$$\text{V}_{th} = \frac{\text{V}_{th} - 12}{2 + 0.5} + \frac{\text{V}_{th}}{1} = 0$$

$$\Rightarrow \text{V}_{th} - 12 + 2.5\text{V}_{th} = 0$$

$$\Rightarrow 3.5\text{V}_{th} = 12$$


$$\Rightarrow \text{V}_{th} = 3.4V$$

$$R_{th} = 3.715 \Omega$$

$$I_{th} = \frac{3.4}{3.715 + 3.715} = 0.375A$$

$$\therefore P = (0.375)^2 \times 3.715 = 0.78W$$

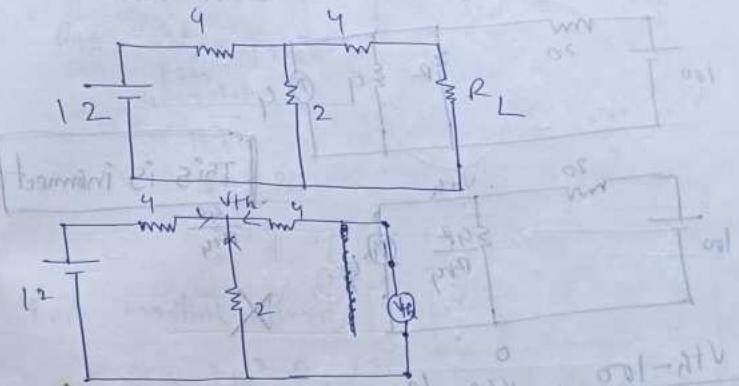③ For the circuit shown in the figure find out (a) the value of R_L to transfer maximum power and (b) the maximum power.



$$\frac{\text{V}_{th} - 12}{4} + \frac{\text{V}_{th}}{2} = 0$$

$$\Rightarrow \frac{\text{V}_{th} - 12 + 2\text{V}_{th}}{4} = 0$$

$$\Rightarrow 3\text{V}_{th} - 12 = 0$$

$$\Rightarrow \text{V}_{th} = 4V$$


$$R_{th} = 5.33 \Omega$$

$$P_{th} = \frac{4^2}{5.33 \times 2} = 0.75W$$

$$I_{th} = \frac{4}{5.33 \times 2} = 0.375A$$

$$P_2 = (0.375)^2 \times 5.33 = 0.75W$$

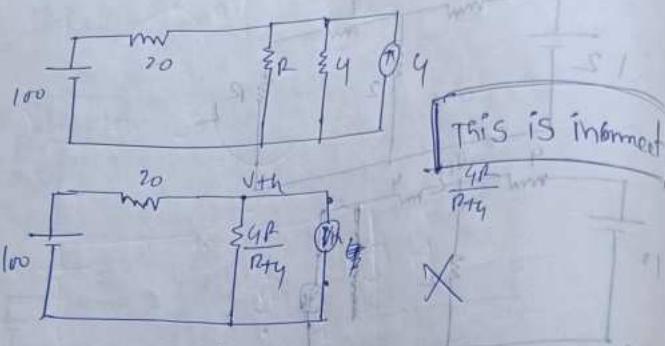Q) For the circuit shown in the figure, find out the value of R for maximum power transfer and also find out the maximum value of powers.



$$\frac{V_{th} - 100}{20} + \frac{V_{th} \times (R_{th})}{4R} = 0$$

$$\Rightarrow R(V_{th} - 100) + 5V_{th}(R_{th}) = 0 \quad \text{--- (1)}$$

$$\Rightarrow R(V_{th} + 5R_{th}) = 100R \quad \text{--- (2)}$$

$$\Rightarrow R \times V_{th} - 100R + 5V_{th}R + 20V_{th} = 0 \quad \text{--- (3)}$$

$$\Rightarrow 6V_{th}R - 100R + 20V_{th} = 0$$


$$\Rightarrow V_{th}(6R + 20) = 100R$$

$$\Rightarrow V_{th}^2 = \frac{100R}{6R + 20}$$

$$V_{th} = \frac{100R}{3R + 10}$$

$$= \frac{100}{3 + 10/R}$$

$$= 10 \text{ V}$$

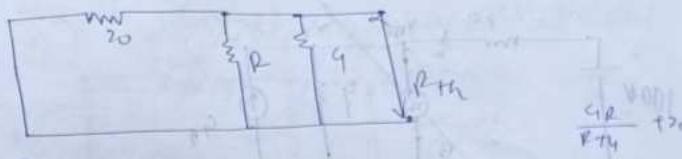

$$P_{th} = \frac{4R}{R_{th} + 20} + 20$$

$$= \frac{4R}{4R + 20R + 80}$$

$$> \frac{24R + 80}{R + 4}$$

For maximum power,

$$P_{max} = I_{th}^2 R_L$$

$$= \left(\frac{V_{th}}{2R} \right)^2 \times R_L = \frac{(V_{th})^2 \times R_L}{(R_L + R_{th})^2}$$

$$= \frac{V_{th}^2 \times R_L}{(R_L + R_{th})^2}$$


$$\frac{dP_{max}}{dR_L} = \frac{1}{4} \cdot \frac{R_L}{R_L + R_{th}}$$

$$\frac{dP_{max}}{dR_L} = \frac{\frac{V_{th}^2}{4} \left\{ (R_L + R_{th})^2 - R_L \cdot 2(R_L + R_{th}) \right\}}{(R_L + R_{th})^4} > 0$$


$$\Rightarrow (R_L + R_{th})^2 - 2R_L(R_L + R_{th}) = 0$$

$$\Rightarrow (R_L + R_{th})^2 - (R_{th} - R_L) = 0$$

$$R_{th} = R_L$$

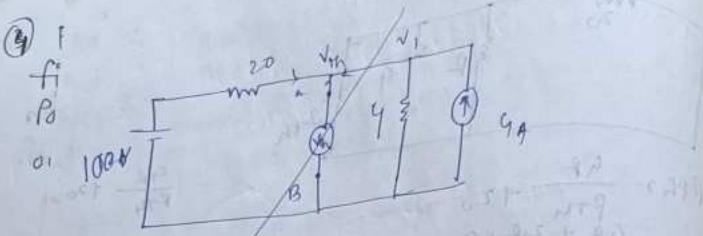
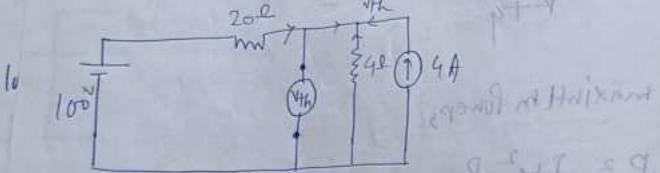
$$10 \cdot \frac{V_{th} - 100}{20} + \frac{V_{th}}{4} + 4 = 0$$



$$\frac{V_{th} - 100}{20} + \frac{V_{th}}{4} + 4 = 0$$

$$\therefore V_{th} = 100 + 5V_{th} + 80$$

$$\therefore 6V_{th} - 20 = 0$$

$$\therefore V_{th} = \frac{20}{6} = 3.33$$





$$R_{th} = \frac{20 \times 4}{24} = 3.33 \neq R$$

$$\therefore I_{th} = 3.33$$

$$P = (0.5)^2 \times 3.33 = 0.8325 \text{ W}$$

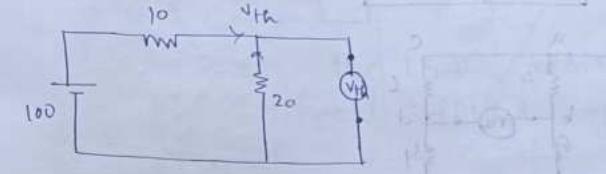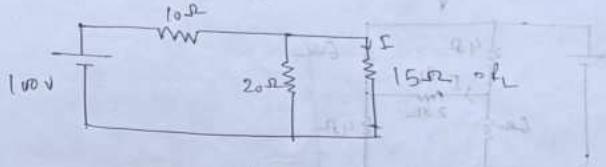• EX-① Using Thevenin's theorem find the current through the 15Ω resistor.




$$\frac{V_{th} - 100}{10} + \frac{V_{th}}{2} = 0$$

$$\therefore \frac{2V_{th} - 200 + V_{th}}{20} = 0$$

$$\therefore 3V_{th} = 200$$


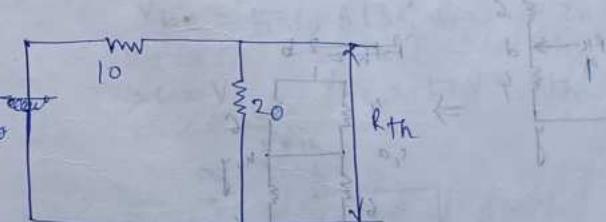
$$\therefore V_{th} = \frac{200}{3} = 66.67 \text{ V}$$




$$R_{th} = \frac{20 \times 10}{30} = \frac{20}{3} \Omega$$

$$\therefore I_{th} = \frac{66.67}{\frac{20}{3} + 15} = 3.07 \text{ A}$$

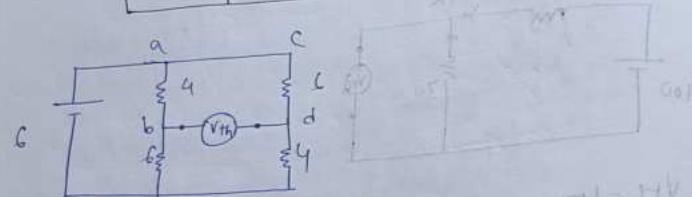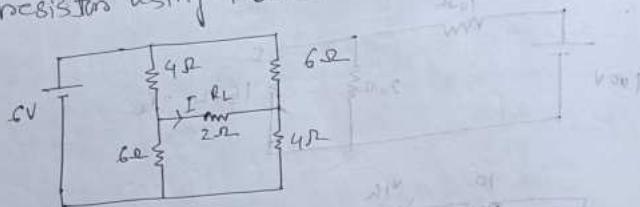② find the current through 2Ω resistor using Thevenin's theorem.



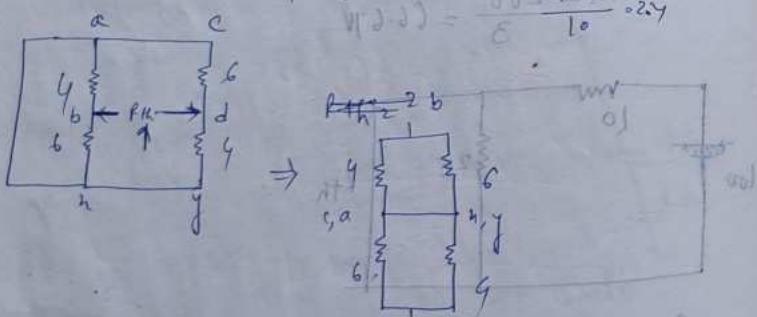
$$\begin{aligned} V_{th} &= V_{bd} = V_{ed} - V_{ab} \\ &= 6 \times \frac{6}{10} - 6 \times \frac{4}{10} \quad \text{branch rd} = 1.5 \Omega \\ &= \frac{36 - 24}{10} \quad \text{main val + same R} \\ &= 1.2 \text{ V} \end{aligned}$$




$$R_{th} = 2.4 + 2.4 = 4.8 \Omega$$

$$I_{th} = \frac{1.2}{4.8 + 2} = 0.176 \text{ A}$$

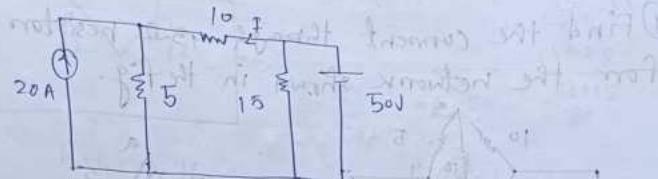③ Find the current through 10Ω resistance in the fig.



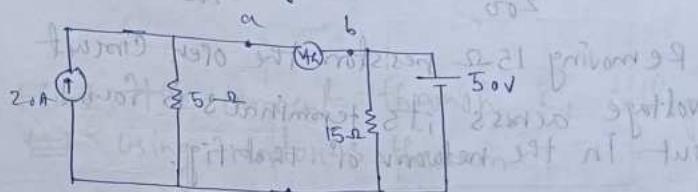
The voltage across the 15Ω resistor is due to the current supplied by the voltage source only.



∴ Voltage across the 15Ω resistor is 50V

Hence $V_{bc} = 50V$, Also, $V_{ac} = 20 \times 5 = 100V$

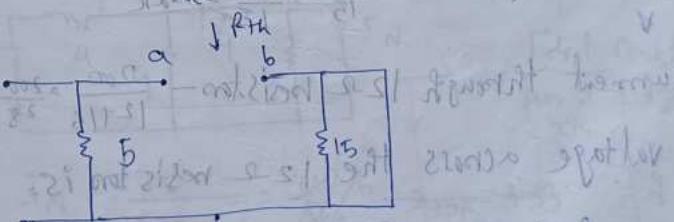
$$\therefore V_{abc} = V_{dc} - V_{bc} = 50V = V_{th}$$



$R_{th} = 5\Omega$ the internal resistance of the network as view from open circuited terminals is 5Ω (as 15Ω resistor is short circuit)

$$\textcircled{1} \quad I_{Th} = \frac{50}{5+10} = \frac{50}{15} = 3.33 \text{ A}$$

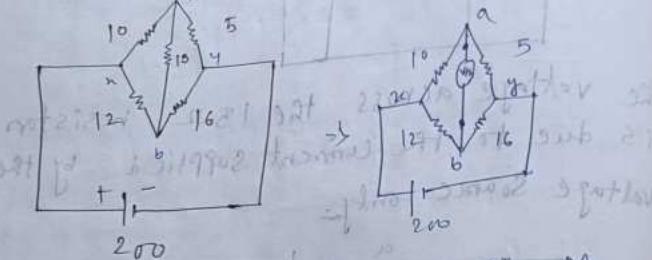- \textcircled{4} Find the current through 15Ω resistor for the network shown in the fig.



Removing 15Ω resistor the open circuit voltage across its terminals is found out in the network of that fig.

The current through 10Ω resistor is obtained as $\frac{200}{200} = 1 \text{ A}$

Voltage across the 10Ω resistor is given by $V = 10 \times \frac{200}{15} = \frac{2000}{15} = 133.33 \text{ V}$

Current through 12Ω resistor $= \frac{200}{12+16} = \frac{200}{28} = 7.14 \text{ A}$


Voltage across the 12Ω resistor is:

$$V_{ab} = \frac{200}{28} \times 12 = \frac{2400}{28} \text{ V} = V_{bn}$$

$$V_{ab} = V_{tb} - V_{ta} = V_{bn}$$

$$I_{ab} = \frac{2400}{28} + \frac{2000}{15} = \frac{2400}{28} + \frac{2000}{15} = \frac{2400}{28} + \frac{2000}{15}$$

$$= 47.62 - V_{th}$$

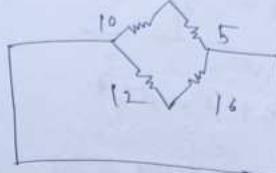



$$\frac{15}{15+28} \times 28 = \frac{15 \times 28}{43} = \frac{420}{43} = 9.76 \text{ V}$$

$$R_{th} = 9.76 \Omega$$

$$I_{Th} = \frac{47.62}{9.76+15}$$

$$= 34.87 \text{ A} = 1.92 \text{ A}$$

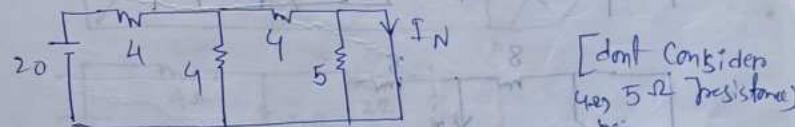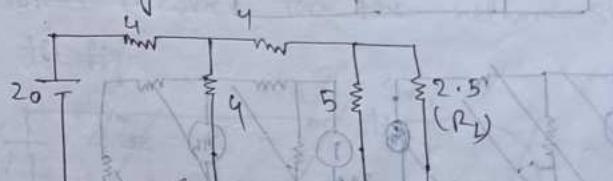- \textcircled{5} Find the current through R_L in fig. using Norton's theorem.




[don't consider 4Ω , 5Ω resistance]

$$I_N = \frac{20}{4+16} = \frac{20}{20} = 1 \text{ A}$$

$$R_{th} = 2.73 \Omega$$




Q

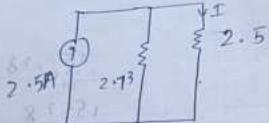

$$I_N = \frac{3.34 - 2.73}{2.5 + 2.73} = 1.71 A$$



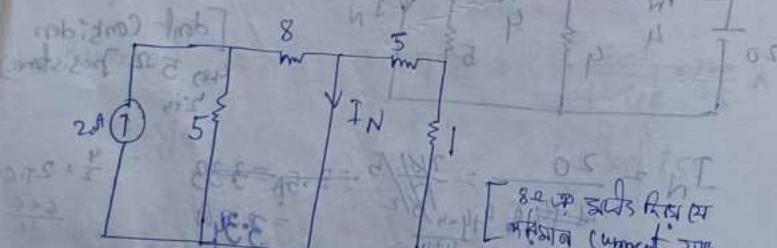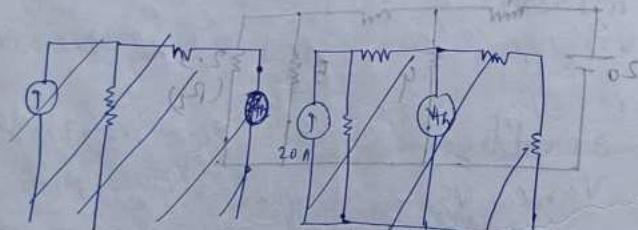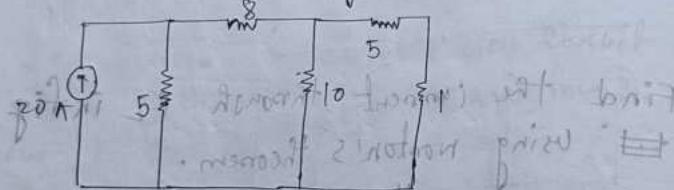
Q) Find the current through 10Ω resistor in the circuit using Norton's theorem.




$$I_N = \frac{2.5 \times 5}{8 + 5} = 1.69 A$$

[By current division rule]

doubt


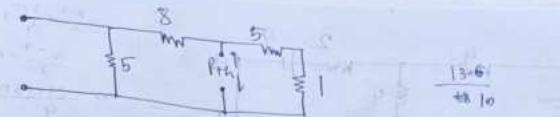



$$R_{th} = 4.1 \Omega$$

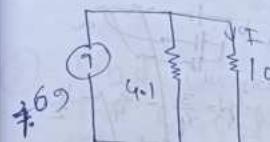

$$I = \frac{7.69 \times 4.1}{10 + 4.1} = 2.23 A$$

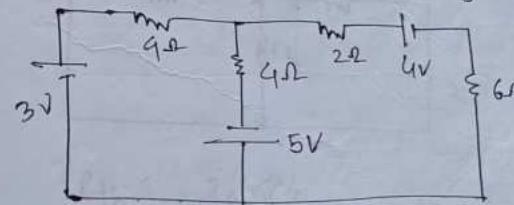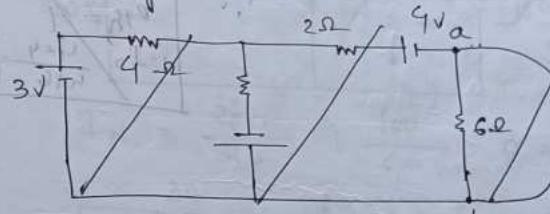Q) Find the current in 6Ω resistor using
• Norton's theorem for the network shown
in the fig..



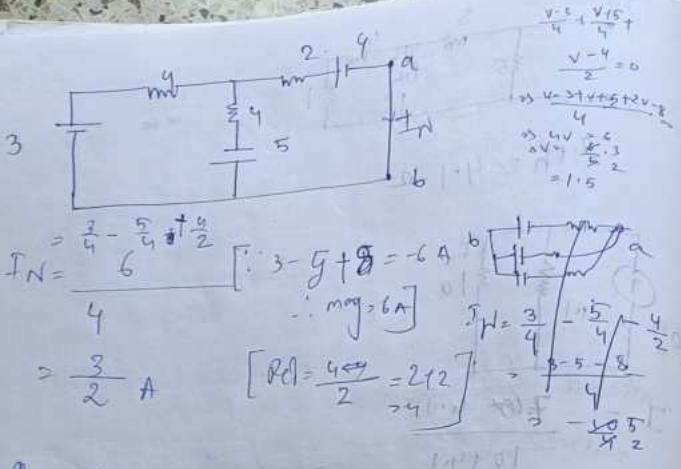



$$P_{th} = 4$$

$$\therefore I = \frac{3 \times 4^2}{2(4\pi)} = \frac{3 \times 4}{4\pi} = 0.6 \text{ A}$$


work written not correct

$\pi r^2 \frac{3}{4} \frac{5}{4} + \frac{1}{2}$
$\frac{8+8}{9}$
$\pi r^2 \frac{4}{9} + \frac{1}{2}$
$r_{th} = 4$
$\therefore I_2 = \frac{4 \times 4}{4\pi \cdot 6} = \frac{16}{10 \pi}$

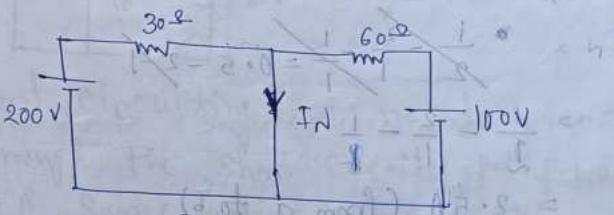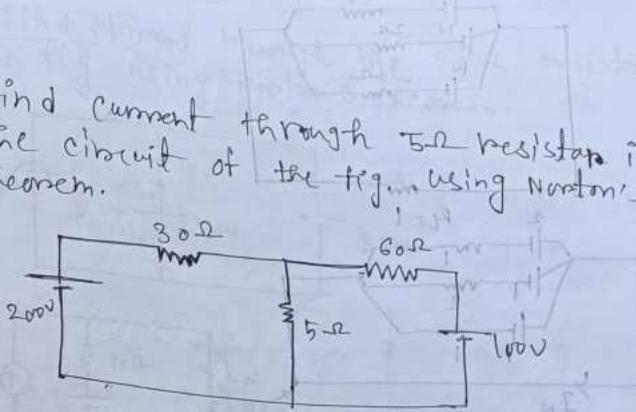(8) Find current through 5Ω resistor in the circuit of the fig., using Norton's theorem.




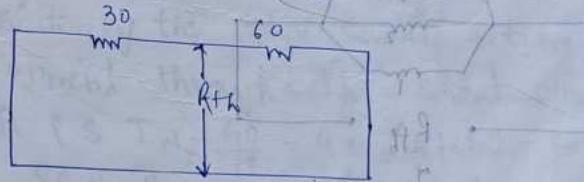
$$I_N = \frac{200}{30} + \frac{100}{60} = 8.33 A$$



$$R_{th} = \frac{30 \times 60}{90} = 20 \Omega$$


$$J = \frac{835 \times 20}{25} = 6.664 A$$

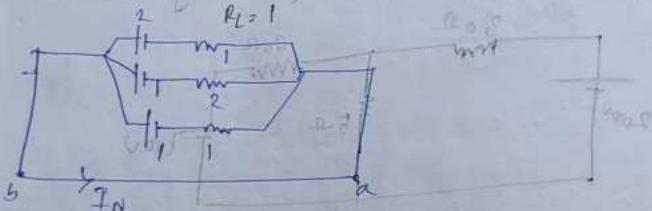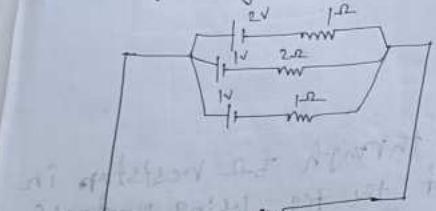(9) Find the current through R_L in the fig using Norton's theorem.



$$I_N = \frac{1}{2} - \frac{2}{1} = 0.5 - 2 = -1.5$$
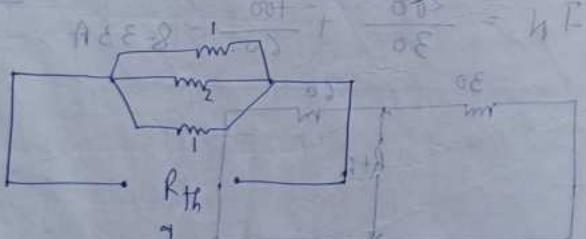
$$= 2.5A \text{ (from } a \text{ to } b)$$



$$\frac{1}{R_{Th}} = \frac{1}{1} + \frac{1}{2} + \frac{1}{1}$$

$$= 2 + \frac{1}{2}$$

$$= \frac{5}{2}$$



$$R_{Th} = \frac{2}{5} = 0.4\Omega$$

$$I = \frac{2.5 \times 0.4}{0.4 + 1}$$

$$= 0.714A$$



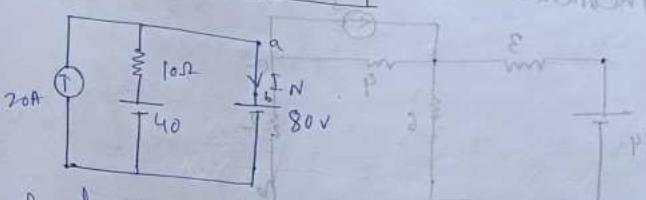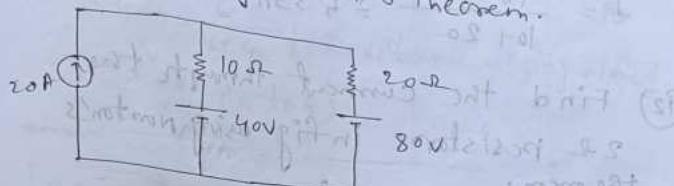(10) Find current through the 20Ω resistor in fig using Norton's theorem.




Short circuiting 20Ω resistor, the current through the short circuit path due to $20A$ Source acting alone is $I_{N1} = 20A$ from a to b .

Considering the $40V$ Source acting alone the current through the short circuited path is $I_{N2} = \frac{40}{10} = 4A$ (at b). Considering the $80V$ Source acting alone the current through the short circuited path is $I_{N3} = \frac{80}{20} = 4A$ (at a).

16 (from a to b)


by $\frac{1}{2}$ min

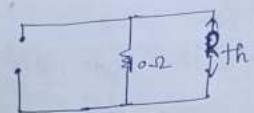



$$R_{th} = 10 + 20 = 30 \Omega$$

$$I = \frac{16}{30} = 0.533 A$$

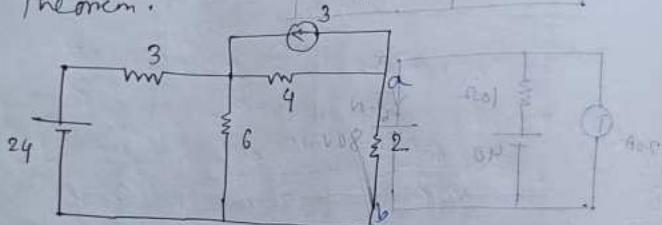(12) Find the current through the 2 ohm resistor in fig using Norton's theorem.



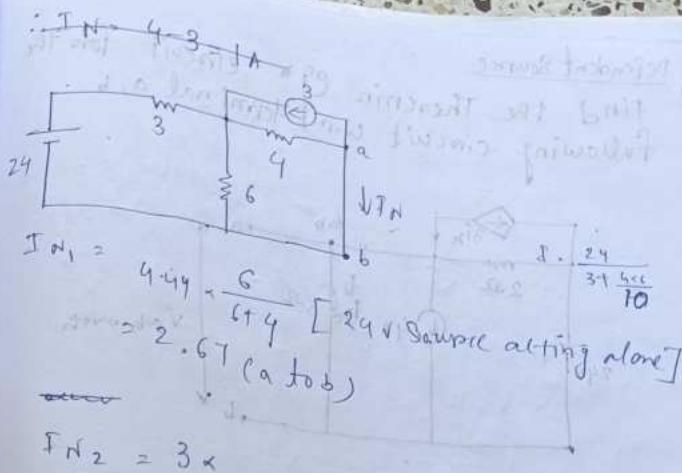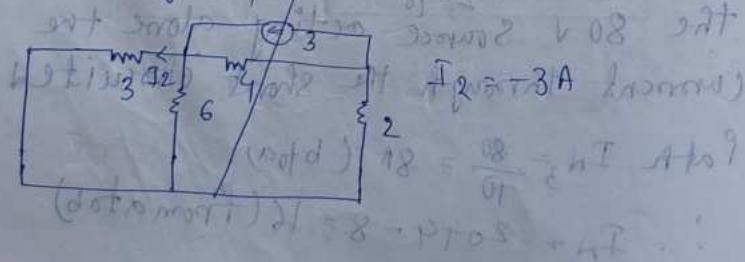From Source 24 acting alone: short open
at circuit the 3A source. At present
the 3A source is removed. A 0.5
A current flows in the 3 ohm resistor.
b) Find the total apparent current at
points P1 and P2 = $\frac{24+4}{6+4} A = 3 A$



$$I_{N_1} = \frac{4-4}{6+4} [24] \text{ Source acting alone}$$

$$= 2.67 \text{ A (at } b)$$

$$I_{N_2} = 3 \times$$

$$0.5 \text{ (parallel)} \frac{12 - 3A}{2} + \frac{3A}{2}$$

$$\frac{12}{8} \text{ (parallel)} \frac{8 - 4A}{2} + \frac{4A}{2}$$

$$R_{th} = \frac{3 \times 6}{3+6+3C - 4A - 3A} = 2$$

$$= 6 \Omega$$

$$V^2 = 2 \times 8 = 16$$

$$R_{th} = 16 = 4 \Omega$$




$$V_{th} = \frac{8 \times 4}{6+4} = 4 V$$

$$\frac{4}{3} = 1.33$$

Ex ① Dependent Source

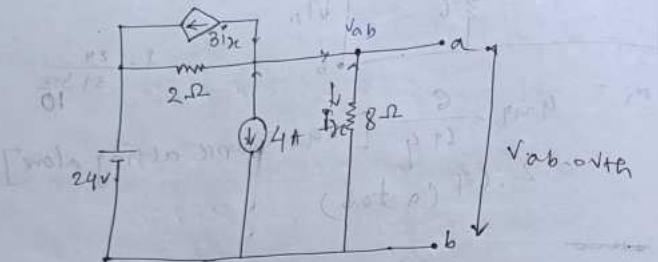Dependent Source
Find the Thevenin equivalent circuit for the following circuit w.r.t terminal a, b




$$\frac{V_{ab}}{8} + \frac{V_{ab} - 24}{2} + 3in + 4 = 0$$

$$\Rightarrow \frac{V_{ab}}{8} + \frac{V_{ab}-24}{2} + \frac{3 \cdot V_{ab}}{8} + 4 = 0 \quad \left[T_h = \frac{V_{ab}}{8} \right]$$

$$\Rightarrow \frac{v_{ab} + 4v_{cb} - 96 + 3v_{cb} + 32}{20} = 0$$

$$\Rightarrow 8v_{ab} = 64$$
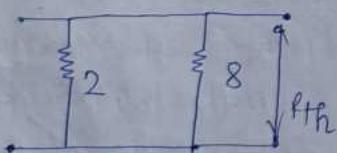
$$\Rightarrow V_{ab} = gV \rightarrow \sqrt{t_h}$$




$$R_{th} = \frac{258}{10} = 1.6V$$

$$\text{A} \times 7 = \frac{8}{1.6}$$

1

① Single phase - AC circuit

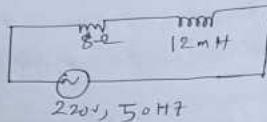

- Find (a) the current
(b) voltage drop across each element (c) power factors and (d) power consumed

$$V = 220V, f = 50 \text{ Hz}, R = 8, L = 12 \times 10^{-3}$$

$$\begin{aligned} Z &= \sqrt{(R^2 + (2\pi f L)^2)} \\ &= 8.84 \Omega \end{aligned}$$

$$\text{a) } I = \frac{220}{8.84} = 24.8A$$

$$\text{b) } V_R = 24.8 \times 8 = 198.4 \text{ V}$$

$$V_L = 24.8 \times 2\pi f L = 24.8 \times 12 \times 10^{-3} = 93.49 \text{ V}$$

$$\text{c) } \cos \phi = \frac{R}{Z} = \frac{8}{8.84} = 0.904$$

? d) Power consumed =

- True Power - The power which is consumed or utilized by an AC circuit is called true power or active power.

- Reactive Power - The reactive power is not useful for a circuit since it flows back and forth in the circuit.

The reactive power is given by -


voltage \times current as out-of-phase with voltage =

$V I \sin \phi$ KVAR or mvar,

- Apparent Power - The total power is given by $V I$ VA or mVA.

(True Power)² / Apparent Power

$$\text{KVA} = \sqrt{(P^2 + Q^2)}$$

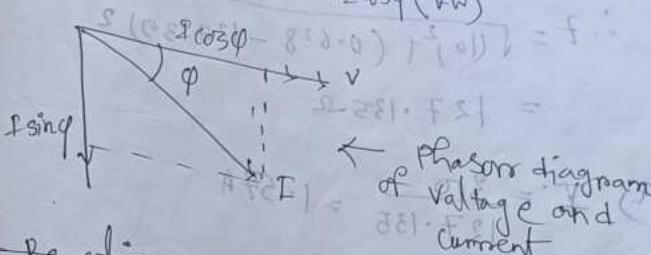

• Reactive Power - The reactive power is not used.

• Active Component of Current - The current component which is in-phase with voltage is called active or wattful or in-phase component of current. It contributes to active power of the circuit.

• Reactive Component of Current - The current component which is in quadrature with voltage is

Called reactive and wattless component
on current. It contributes reactive
power of the circuit.

- Q) A 200V, 50Hz supply is applied
to an RLC circuit of $10\ \Omega$ resistance,
 2mH inductor and $25\mu\text{F}$ capacitor. Find
the (a) input current and (b) voltage across
each element.

$$X_L = 314 \times 2 \times 10^{-3} = 0.628$$


$$X_C = \frac{1}{314 \times 25 \times 10^{-6}} = 127.39$$

$$\therefore Z = \sqrt{(10)^2 + (0.628 - 127.39)^2}$$
$$= 127.135\ \Omega$$

(a) $I = \frac{200}{127.135} = 1.57\text{A}$

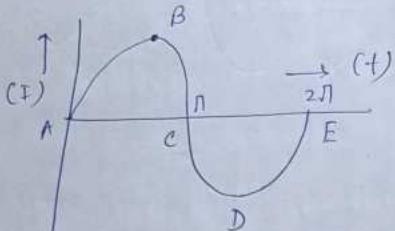
(b) $V_R = I R = 1.57 \times 10 = 15.7\text{V}$
 $V_L = I X_L = 1.57 \times 0.628 = 0.985\text{V}$
 $V_C = I X_C = 1.57 \times 127.39 = 200\text{V}$

- Sinusoidal Alternating Quantity —
The instantaneous value of current
is $I = I_m \sin \theta$



Sinusoidal AC

- AC Fundamentals and Circuits —

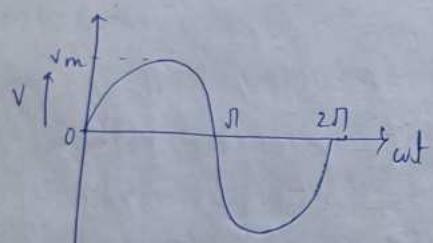

A sinusoidal wave

The expression for AC voltage is —

$$V = V_m \sin \omega t$$

[V_0 = Instantaneous value
 V_m = max value]

The expression for alternating current
is —

$$I = I_m \sin \omega t$$

[I_0 = Instantaneous
value
 I_m = max value]


ω = Angular velocity of the coil


- Instantaneous value — The value of alternating quantity at any particular instant is called instantaneous value. It is denoted by lower case letters such as e for emf, i for current, v for voltage.

• Amplitude — The amplitude of a sine wave is the maximum vertical distance reached in either direction from the current center line of the wave. As a sine wave is symmetrical about its center line, the amplitude of the wave is half of the peak-to-peak value.

• Peak-to-peak value — The peak-to-peak value is the vertical distance between the top and bottom of the wave. volts for a voltage waveform.

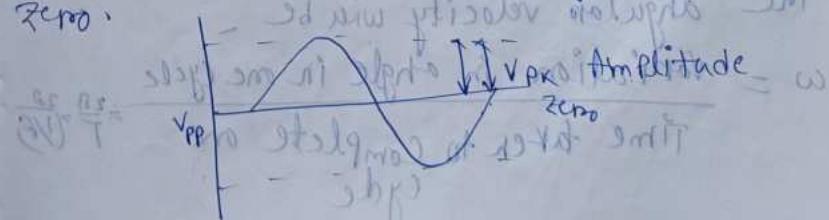• Peak value — The peak value of the wave is the highest value the wave reaches above a reference value. The reference value normally used is zero.



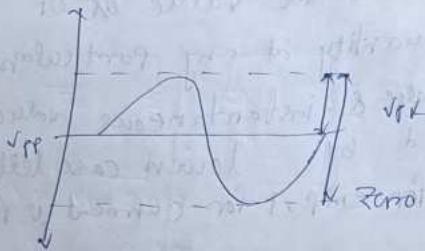


- Cycle and Alternation - when an alternating quantity completes one complete set of positive and negative values, it is called one cycle, whereas when it completes only one set of either positive or negative values, that is, half a cycle, then it is called one alternation. One alternation corresponds to 180° or π rad while one cycle is 360° or 2π rad.

- Angular Frequency or Angular velocity - An alternating quantity completes one cycle by 2π rad. The angular velocity will be -
- $\omega = \frac{\text{Variation in angle in one cycle}}{\text{Time taken to complete one cycle}} = \frac{2\pi}{T} = \frac{2\pi}{f}$

$= 2\pi f$ electrical rad/s in it/s

Graphically -
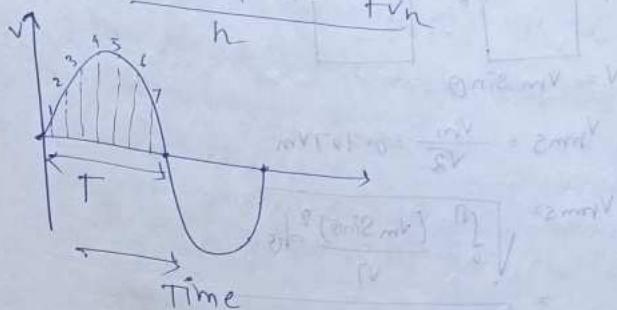
$$V_{av} = \frac{1}{2} V_m + \frac{1}{2} h$$



Analytically -


$$\text{Area of half cycle voltage wave} = 2Vm$$

$V_{av} = \text{Height of the equivalent rectangle having the same base} \times \frac{\text{Area}}{\text{base}}$

$$V_{av} = \frac{2Vm}{\sqrt{2}} = 0.637 V_m$$

$$I_{av} = \frac{2I_m}{\sqrt{2}} = 0.637 I_m$$

• Analytical determination of rms -

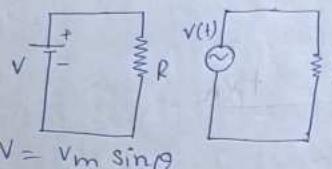

$$V = V_m \sin \theta$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} = 0.707 V_m$$

$$\begin{aligned} V_{rms} &= \sqrt{\frac{1}{T} \int_0^T (V_m \sin \theta)^2 d\theta} \\ &= \sqrt{\frac{V_m^2}{T} \int_0^T (\sin \theta)^2 d\theta} \end{aligned}$$

$$\begin{aligned} V_{rms} &= \sqrt{\frac{V_m^2}{T} \int_0^T \left[\frac{1 - \cos 2\theta}{2} \right] d\theta} \\ &\text{Step 2: } \int_0^T \left[\frac{1 - \cos 2\theta}{2} \right] d\theta = \frac{1}{2} T \end{aligned}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \left[\theta - \frac{\sin 2\theta}{2} \right]_0^\pi} = \frac{V_m \pi}{\sqrt{2}} = V_r V$$

$$\begin{aligned} &= \sqrt{\frac{V_m^2}{2\pi} \left[(\pi - 0) - \frac{(\sin 2\pi - \sin 0)}{2} \right]} = V_r I \\ &\text{Step 2: } \sqrt{\frac{V_m^2}{2\pi} \cdot \pi} \end{aligned}$$

$$= \frac{V_m}{\sqrt{2}}$$

$$\boxed{V_{rms} = 0.707 V_m \\ I_{rms} = 0.707 I_m}$$

- ① An alternating Voltage of 50Hz has a peak value of 230V. write down the expression for its instantaneous value.

$$V_m = 230, f = 50 \text{ Hz}$$

$$V = V_m \sin \omega t$$

$$\Rightarrow V_m \sin 2\pi ft \quad [\omega = 2\pi f]$$

$$\Rightarrow 230 \sin 2\pi \times 50t$$

$$\Rightarrow 230 \sin 314t$$

- ② An alternating current is represented by $I = 12 \sin 314t$. Find (a) frequency (b) instantaneous value at $t = 4 \text{ ms}$, (c) time taken to attain a value of 10A for first time after passing through zero. Given $I = I_m \sin \theta$

$$(a) \omega = 2\pi f$$

$$\Rightarrow 314 = 2\pi f$$

$$\Rightarrow f = \frac{314}{2\pi} = \frac{50}{\pi} \text{ Hz} = 15.9 \text{ Hz}$$

$$(b) t = \frac{4}{10^{-3}} = 4 \times 10^{-3} \text{ s} \quad [\because I_m \sin \theta = 12 \sin 314t]$$

$$I = I_m \sin \theta$$

$$= 12 \sin 314 \times 4 \times 10^{-3}$$

$$= 10.8 \text{ A}$$

The initial current is 10.8 A.

$$\text{Q) } I = I_m \sin \omega t$$

$$\Rightarrow I_0 = 12 \sin 314t$$

$$\Rightarrow t = 0.0179 \text{ s}$$

③ An alternating current having frequency of 50Hz has peak value of 15.5. How much time will it require for the current to attain values of 10 A and 12A starting from zero?

$$I_m = 15.5$$

$$f = 50 \text{ Hz}$$

$$I_0 = 15.5 \sin 2\pi \times 50t$$

$$\Rightarrow t = 0.127 \text{ s}$$

④ Instantaneous current is given by the relation $I = 20 \sin 314t$. Find rms and average value of A.C.

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2}} = \frac{20}{\sqrt{2}} = 14.142 \text{ A}$$

$$I_{\text{av}} = \frac{2 \times 20}{\sqrt{2}} = 28.28 \text{ A} \quad | I_{\text{av}} = \frac{2 I_m}{\sqrt{T}} = \frac{2 \times 20}{\sqrt{\pi}} = 12.73 \text{ A}$$

⑤ An AC has frequency of 50Hz and rms current of 25A. Write eqn of instantaneous current and find (a) Current at time 0.0025s and (b) time at

which current is 14.14 A.

$$f = 50, I_{\text{rms}} = 25 \text{ A}$$

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2}}$$

$$\Rightarrow I_m = 25\sqrt{2} = 35.35 \text{ A}$$

$$I = 35.35 \sin 2\pi \times 50 \times 0.0025$$

$$= 0.484$$


$$14.142 \cdot 35.35 \sin 2\pi \times 50t$$

$$\Rightarrow t = 0.075 \text{ s}$$

⑥ Calculate the rms and average of a square wave shown in fig. If the current is passed through 2Ω resistor, find out average power absorbed by it.

$$I_{\text{rms}}^2 = \frac{1}{T} \int_0^T I(t)^2 dt = \frac{1}{T} \int_0^T I_m^2 dt$$
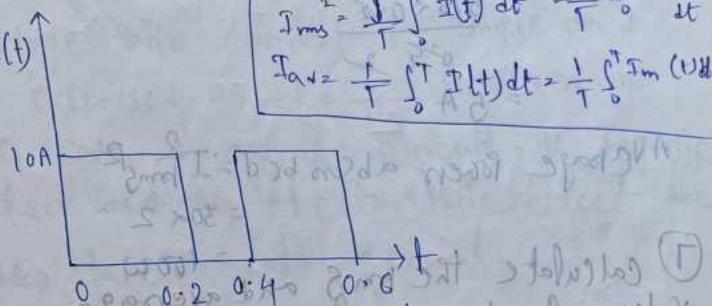
$$I_{\text{av}} = \frac{1}{T} \int_0^T I(t) dt = \frac{1}{T} \int_0^T I_m dt$$



For the time interval $0 < t < 0.2$, $I = 10 \text{ A}$ and for $0.2 < t < 0.4$, $I = 0 \text{ A}$. Time period of the current waveform, $T = 0.4$, The rms value is given by

$$I_{\text{rms}}^2 = \frac{1}{T} \int_0^T I^2 dt = \frac{1}{0.4} \left[\int_0^{0.2} 10^2 dt + \int_{0.2}^{0.4} 0^2 dt \right]$$

$$= \frac{1}{0.4} \left[\int_0^{0.2} 100 dt \right]$$

$$= \frac{100}{0.4} [0.2 - 0] = \frac{100}{0.4} \times 0.2$$

$$= \frac{100 \times 50}{0.4 \times 2}$$

$$I_{rms} = \sqrt{50} = 7.071A$$

$$I_{av} = \frac{1}{T} \int_0^T I(t) dt$$


$$= \frac{1}{0.4} \left[\int_0^{0.2} 10 dt + \int_{0.2}^{0.4} 0 dt \right]$$

$$(1) \frac{10}{0.4} \times \frac{1}{7} = \frac{5}{0.4} \times 0.2$$

$$(2) \frac{10}{0.4} \times \frac{1}{7} = \frac{5}{0.4} \times 2$$

Average power absorbed = $I_{rms}^2 R$
 $= 50 \times 2$
 $= 100W$

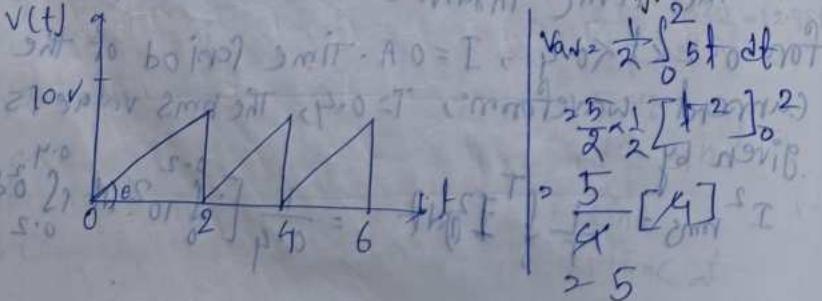⑦ calculate the I_{rms} and average value for the waveform shown in Fig.



From the given triangular waveform, it is observed that $V = 5t$, for $0 < t < 2$ and the time period is 2. The rms value is -

$$\begin{aligned} V_{rms}^2 &= \frac{1}{T} \int_0^T V^2 dt \\ &= \frac{1}{2} \int_0^2 (5t)^2 dt \end{aligned}$$

$$= \frac{1}{2} \times \frac{25}{3} [t^3]_0^2$$

$$= \frac{25}{6} [8 - 0]$$


$$\begin{aligned} \text{Average current} &= \frac{25 \times 8}{6 \times 3} \\ &= 3 \times \frac{5 \times 2}{\sqrt{3}} = \frac{10}{\sqrt{3}} \end{aligned}$$

- For a DC circuit, the relationship between voltage and current is simple and is expressed as, $I = \frac{V}{R}$. However, in the case of an AC circuit, the magnetic effect and the electrostatic effect are also taken into account.

Pure Resistance

The circuit which contains a pure resistance, or has negligible inductance is called pure resistance circuit.
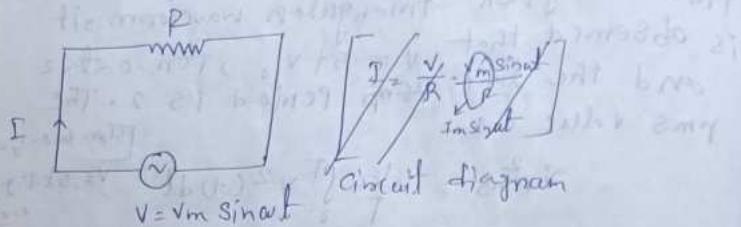
$$[2m \text{ mm}^2 \times \frac{10^{-6}}{S^2} \times \frac{10^3}{S^2} = 10]$$



for pure resistances

$$\text{the circuit is } I = \frac{V}{R} = \frac{V_m \sin \omega t}{R} = \frac{V_m}{R} \sin \omega t$$

$$I = I_m \sin \omega t \quad \text{---(1)}$$

$\left[\because \text{resistor}, I_m = \frac{V_m}{R} \right]$

The current will be maximum if $\sin \omega t = 1$ and $\sin \omega t = 1$, therefore

$$I_{\max} = \frac{V_m}{R}$$


By placing I_{\max} in eqn (1) we get

$$I = I_{\max} \sin \omega t$$

The average power of a pure resistance

$$\text{circuit is } P_{av} = \frac{V_{\max} I_{\max}}{2} = V_{\text{rms}} I_{\text{rms}} = \frac{V^2}{R} \quad \text{---(2)}$$
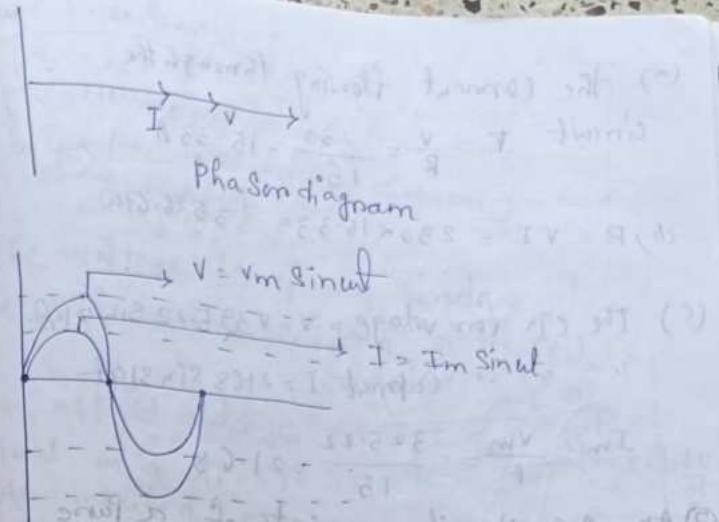
$$\left[\because \frac{V_{\max}}{\sqrt{2}} \times \frac{I_{\max}}{\sqrt{2}} = V_{\text{rms}} I_{\text{rms}} \right]$$



- Ex-1 A 230V (rms), 50Hz voltage source is connected in series with a pure resistance of 15Ω. Determine (a) the current flowing in the circuit, (b) the power absorbed by the circuit and (c) the equation for the voltage and the current.

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}} = \frac{V_m}{\sqrt{2}} \times \sqrt{2} = V_m = 325 \sin 30^\circ$$

$$\therefore V_m = 230 \times \sqrt{2} = 325 \text{ V}$$

$$f = 50, R = 15$$

$$I_m = \frac{V_m}{R} = \frac{325}{15} = 21.67 \text{ A}$$

$$\therefore I = 21.67 \sin 30^\circ \text{ A}$$

(a) the current flowing through the circuit

$$I = \frac{V}{R} = \frac{230}{15} = 15.33 A$$

$$(b) P = VI = 230 \times 15.33 = 3526.67 W$$

(c) the emf for voltage $V = V_m \sin \omega t$
" " Current $I = I_m \sin \omega t$

$$I_m = \frac{V_m}{R} = \frac{325.22}{15} = 21.68$$

Q An AC circuit consists of a pure resistance of 20Ω and is connected across $220V$ AC supply. Calculate (a) the current, (b) the power consumed and (c) the equation for the voltage and the current. (a) Ans (b) $220W$ (c) $I = I_m \sin \omega t$

Given $V_m = 220 \sqrt{2} V$, $f = 50 \text{ Hz}$, $\omega = 2\pi f = 314 \text{ rad/s}$. Then $I_m = \frac{V_m}{R} = \frac{220 \sqrt{2}}{20} = 31.12 A$

$$\text{Ans} I_m = \frac{V_m}{R} = \frac{31.12}{20} = 1.555 A$$


$$\text{by } I = \frac{V}{R} = \frac{220}{20} = 11 A$$

$$\text{by } P = VI = 11 \times 220 = 2420 W$$

$$\text{c) } V = V_m \sin \omega t = 31.12 \sin 314t$$

$$I = I_m \sin \omega t = 1.555 \sin 314t$$

Pure Inductance

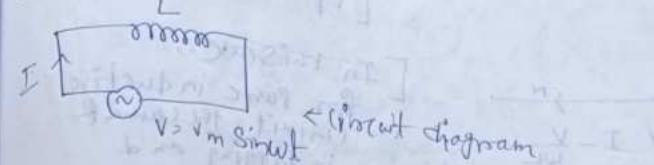

The voltage is $V = V_m \sin \omega t$
The self-induced emf of the coil is

Now, applied voltage is equal and opposite to self-induced emf. Therefore, $V = V_m \sin \omega t = -(-L \frac{dI}{dt}) = L \frac{dI}{dt}$

$$\Rightarrow \int dI = \int \frac{V_m}{L} \sin \omega t dt \quad \left| \begin{array}{l} \text{as for pure inductance} \\ R = 0 \\ I = 0 \\ \frac{dI}{dt} = 0 \end{array} \right.$$

$$\Rightarrow I = \frac{V_m}{WL} \cos \omega t \quad \left| \begin{array}{l} \text{Ans} \\ \omega = \frac{2\pi f}{L} \end{array} \right.$$

$$\Rightarrow I = \frac{V_m}{WL} \left(\sin \left(\omega t - \frac{\pi}{2} \right) \right)$$

The current I will be maximum when

$$\sin \left(\omega t - \frac{\pi}{2} \right) = 1 = (+) \text{ at } \omega t = \frac{\pi}{2}$$

$\Rightarrow \omega t = \frac{\pi}{2} \Rightarrow \frac{\pi}{2} = \omega t \Rightarrow \omega = \frac{\pi}{2t} = \frac{\pi}{2 \times 50} = \frac{\pi}{100} \text{ rad/s}$

$$\therefore I_m = \frac{V_m}{WL}$$

$$\therefore I = I_m \sin \left(\omega t - \frac{\pi}{2} \right)$$


Hence, the current flowing through the inductor lags behind the applied voltage by $\frac{\pi}{2}$ rad.

[Ex 4]

$$I = \frac{V}{\omega L}$$

Phasor diagram

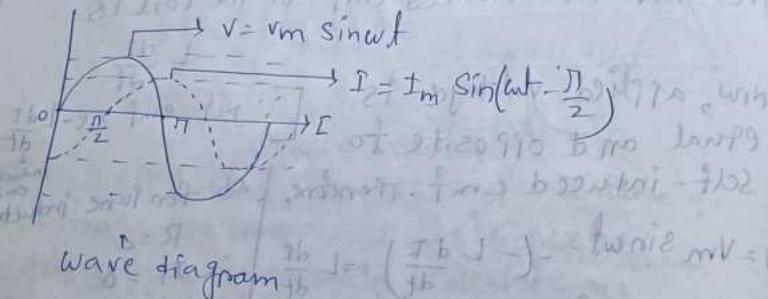In this case, for pure inductive circuit the current is lagging and the voltage is leading]



Wave diagram

- The inductive reactance (or inductive opposition)

$$X_L = \omega L$$

$$\therefore I_m = \frac{V_m}{\omega L} = \frac{V_m}{X_L} = \frac{V_m}{\omega L}$$

- The average power absorbed over a complete cycle in pure inductor is zero i.e. $P_{av} = 0$

Ex-③

The voltage $v(t) = 15 \sin(50t + 45^\circ)$ is applied to a 0.3 H inductor. Find the current flowing through the inductor.

$$\left[\frac{V}{(\omega - \omega_0)} \right] \text{ rad } m^2 \cdot C = I$$

$$v(t) = 15 \sin(50t + 45^\circ)$$

$$L = 0.3, \omega = 50, V_m = 15, \phi = 45^\circ$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} = 10.61 \text{ V}$$

$$\therefore I = \frac{V_{rms}}{\omega L} = \frac{10.61}{50 \times 0.3} = 0.61 \text{ A} \quad [\text{Ans}]$$

Hence, the current of 1 A will lag behind the applied voltage by 45° .

- (4) An inductor of 0.5 H is connected in series with a voltage source of $220 \text{ V}, 50 \text{ Hz}$. Find (a) the rms value of current. (b) the power and (c) the equation for voltage and current.

$$V_{rms} = 220 \text{ V}, f = 50 \text{ Hz}, L = 0.5 \text{ H} \quad [I = I_{rms}]$$

$$a) I_{rms} = \frac{V_{rms}}{\omega L} = \frac{220}{50 \times 2\pi \times 0.5} = 1.40 \text{ A}$$

$$b) P = VI = 220 \times 1.40 = 308.2 \text{ W}$$


$$c) V_m = V_{rms} \sqrt{2} = 220 \sqrt{2} = 311.12 \text{ V}$$

$$I_m = \frac{311.12}{314 \times 0.5} = 1.98 \text{ A}$$

$$V = 311.12 \sin 314t \quad [m^2 \cdot C = I]$$

$$I = 1.98 \sin(314t - \frac{\pi}{2})$$

• Pure capacitor

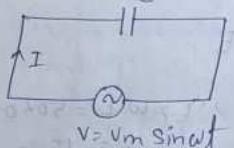

Circuit diagram

$$V = V_m \sin \omega t$$

the applied voltage is,

$$V = V_m \sin \omega t$$

The charge stored in the capacitor is

$$q = CV = C V_m \sin \omega t \quad (1)$$

$$\text{Now } I = \frac{dq}{dt} = \frac{d}{dt} [C V_m \sin \omega t] = C V_m \cos \omega t$$

$$\Rightarrow I = C V_m \cos \omega t \quad \text{or} \quad I = \frac{V_m}{(1/\omega)} \cos \omega t$$

$$\Rightarrow I = \frac{V_m}{(1/\omega)} \sin(\omega t + \frac{\pi}{2})$$

$$\text{or } I = \frac{V}{(1/\omega)} = \frac{V}{\omega} = V \omega \quad (2)$$

Now, I will be maximum, when

$$\sin(\omega t + \frac{\pi}{2}) = 1 \quad \text{or } \omega t = \frac{\pi}{2}$$

$$\therefore \omega t = \frac{\pi}{2} \quad \text{or } t = \frac{\pi}{2\omega}$$

$$\therefore I_m = \frac{V_m}{1/\omega} = V_m \omega = V_m \cdot \frac{\omega}{1} = V_m \cdot \frac{2\pi f}{1} = V_m \cdot 2\pi f \cdot 10^3 = V_m \cdot 2\pi \times 10^3 = V_m \cdot 6283 \approx 6.283 V_m$$

$$\therefore I = I_m \sin(\omega t + \frac{\pi}{2})$$

$$(I = I_m \sin(\omega t + \frac{\pi}{2}))$$


$$(I = I_m \sin(\omega t + \frac{\pi}{2}))$$

Hence the current flowing through the capacitor leads the applied voltage by $\pi/2$. The capacitive reactance is

$$X_C = \frac{1}{\omega C}$$


$$I_m = \frac{V_m}{1/\omega C} = \frac{V_m}{X_C}$$

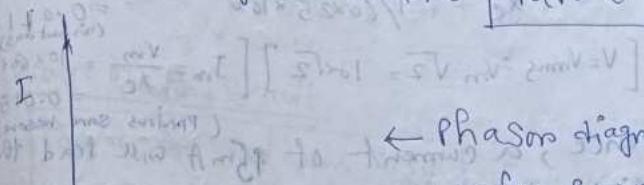The average power absorbed over a complete cycle is zero $[P_{av} = 0]$



Phasor diagram

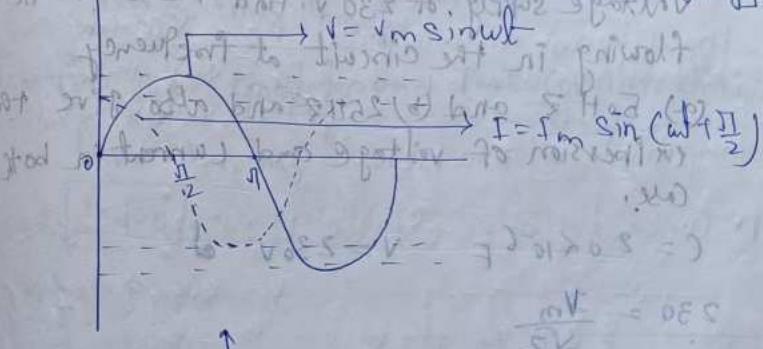for pure capacitance the current is leading and the voltage is lagging



Wave diagrams $V = V_m \sin \omega t$

$I = I_m \sin(\omega t + \frac{\pi}{2})$

$$\frac{V}{I} = \frac{V_m \sin \omega t}{I_m \sin(\omega t + \frac{\pi}{2})} = \frac{V_m \sin \omega t}{I_m \cos \omega t} = \frac{V_m}{I_m} \tan \omega t$$

$$\frac{V}{I} = \frac{V_m}{I_m} \tan \omega t = \frac{V_m}{I_m} \tan 2\pi f t$$

$$\frac{V}{I} = \frac{V_m}{I_m} \tan 2\pi f t = 2\pi f V_m \tan 2\pi f t$$

Ex-5 An AC circuit consisting of a capacitor of capacity of 25 nF is connected in series with applied voltage $v(t) = 10 \sin(60t + 45^\circ)$. Find out the current through the capacitor.

$$v(t) = 10 \sin(60t + 45^\circ)$$

$$C = 25\text{ nF} = 25 \times 10^{-9}\text{ F}, V_m = 10, \omega = 60, \phi = 45^\circ$$

$$I_m = \frac{V_m}{X_C} = \frac{10\sqrt{2}}{1/60 \times 25 \times 10^{-9}} = 10\sqrt{2} \times 60 \times 25 \times 10^{-6} \text{ A}$$

$$[V = V_{rms} = V_m \sqrt{2} = 10\sqrt{2}] \quad [I_m = \frac{V_m}{X_C} = \frac{10}{10 \times 60 \times 25 \times 10^{-6}} = 0.0157 \text{ A}]$$

Hence, a current of 0.0157 A will lead the applied voltage by 45° .

⑥ A capacitor of 20 nF is connected to a voltage supply of 230 V . Find the current flowing in the circuit at frequency

(a) 50 Hz and (b) 25 Hz and also give the expression of voltage and current in both cases.

$$C = 20 \times 10^{-9}\text{ F}, V = 230\text{ V}$$

$$230 = \frac{V_m}{\sqrt{2}}$$

$$\therefore V_m = 230\sqrt{2} = 325.26 \text{ V} \therefore V = 325.26 \sin 314t$$

$$\text{a) } f_1 = 50\text{ Hz} \Rightarrow C = 20 \times 10^{-9}\text{ F}$$

$$\therefore I_m = \frac{V_m}{X_C} = \frac{V_m}{1/\omega C} \Rightarrow$$

$$\therefore 325.26 = V_m \times 314 \times 20 \times 10^{-9}$$

$$\therefore I_m = 325.26 \times 314 \times 20 \times 10^{-9} = 2.04\text{ A}$$

$$\therefore I = 2.04 \sin(314t + \frac{\pi}{2})$$

$$\text{b) } f_2 = 25\text{ Hz}$$

$$V_m = 325.26$$

$$\therefore V = 325.26 \sin 314t$$

$$I_m = 325.26 \times 25 \times 2\pi \times 20 \times 10^{-9}$$

$$= 1.02\text{ A}$$

$$\therefore I = 1.02 \sin(314t + \frac{\pi}{2})$$

Powers of AC circuit

$$P_{av} = V_{rms} I_{rms} \cos \phi$$

[ϕ - phase difference between V and I]

(i) for pure resistance circuit, $\phi = 0$

$$P_{av} = V_{rms} I_{rms}$$

(ii) for pure conductor and pure capacitor circuit

$$P_{av} = V_{rms} I_{rms} \sin \phi$$

(iii) $P_{av} > 0$

$$P_{av} = P_{max} \sin^2 \theta$$

$$\rightarrow P_{av} = \frac{1}{2} P_{max} = \frac{1}{2} \times 230 \times 50 \times 25 \times 20 \times 10^{-9}$$

$$= 21.44\text{ A}$$

$$I_2 = 230 \times 25 \times 2\pi \times 20 \times 10^{-9}$$

$$= 0.722\text{ A}$$


মাত্রায় বলা না
মাত্রায় max
value consider
বরে মাত্র বল
মাত্রায় rms value consider

class

Transformers

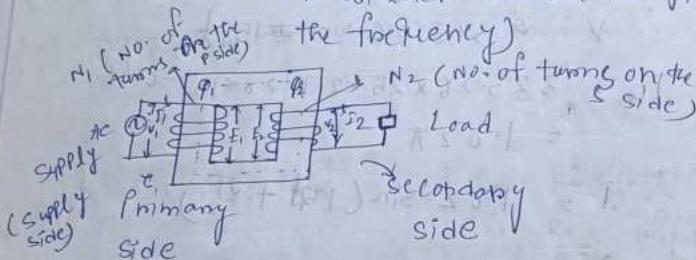28.3.22

(static device that can transform the val / current w.r.t from one to another without changing the frequency)




In Basic principle of transformer → Primary winding, secondary winding, primary current, secondary current, primary voltage, secondary voltage, primary emf, secondary emf, & n of single phase

transformers, The relation between V_1 and V_2 and E_1 and E_2 , how the transformer ratio in KVL is

$$\begin{aligned} I_1 &= \text{Primary current} \\ I_2 &= \text{Secondary current} \\ V_1 &= \text{Primary voltage} \\ V_2 &= \text{Secondary voltage} \\ E_1 &= \text{Primary emf} \\ E_2 &= \text{Secondary emf} \\ E_1 &= \text{Self induction} \\ E_2 &= \text{Mutual Inductance} \end{aligned}$$

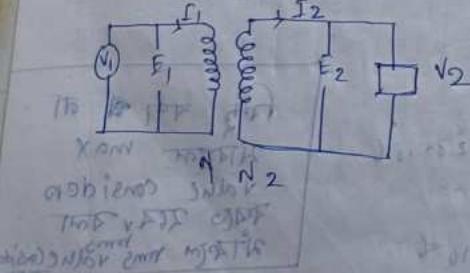• Representation of single phase AC transformer-




$$V_1 = 4.44 f \Phi_m N_1$$

$$V_2 = 4.44 f \Phi_m N_2$$

$$E_1 = 4.44 f \Phi_m N_1$$
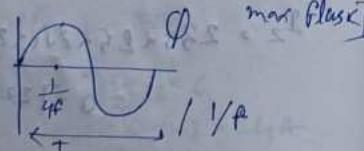
$$E_2 = 4.44 f \Phi_m N_2 \quad [\Phi_m = \text{max flux}]$$



• Transformation -


$$\frac{E_2}{E_1} = \frac{V_2}{V_1} = \frac{I_1}{I_2} = \frac{N_2}{N_1} = K$$

$$V_1 I_1 = V_2 I_2$$

$$\Rightarrow V_1 = \frac{V_2 I_2}{I_1}$$

If we supply DC then the winding get heated as the same current will flow in primary side and the primary side will get heated.

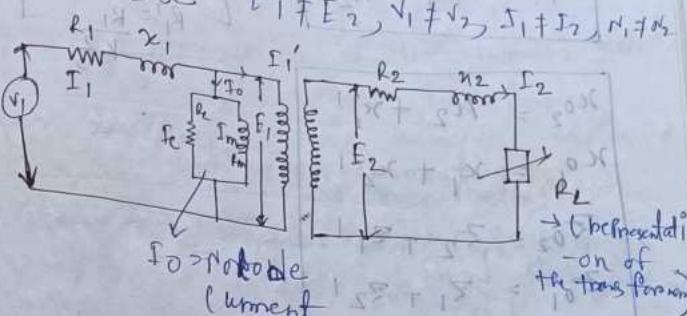• In ideal Case, $I_1 = I_2, V_1 = V_2, I_1 = I_2, N_1 = N_2$
In real Case, $E_1 \neq E_2, V_1 \neq V_2, I_1 \neq I_2, N_1 \neq N_2$




vector sum of I_0 and I_m .

$I_c =$ Core loss component of the current
 $I_m =$ Magnetic component of the current

$$\begin{aligned} I_0 &= \sqrt{I_c^2 + I_m^2} \\ I_1 &= I_0 + I_m \end{aligned}$$

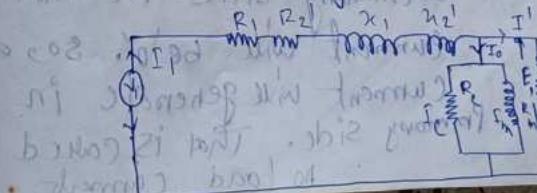If we want to shift the parameters of primary side to secondary side



31/3/22

R_{02} (Total eq. resistance referred to secondary) $R_2 + R_1'$

$$R_{01} = R_1 + R_2'$$

$$R_2' = k^2 R_2$$

$$R_1' = \frac{R_1}{k^2}$$


$$x_{02} = x_2 + x_1'$$

$$x_{01} = x_1 + x_2'$$

$$z_{02} = z_2 + z_1'$$

$$z_{01} = z_1 + z_2'$$

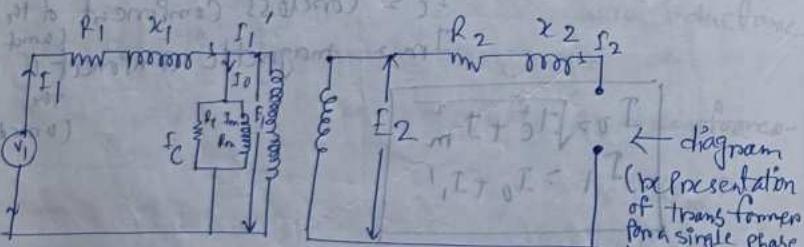• No load operation for a single phase transformer



As there is no load in secondary side the secondary current will be '0'. So, a current will generate in primary side. That is called no load current.

• On load operation for a single phase transformer


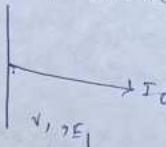


Diagram (representation of transformers for a single phase transformer)

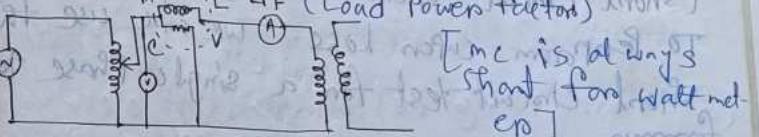① What is the wattmeter connection? [LPF (Load Power Factor)]



$K = k_i S$ Wattmeter constant [V = rated voltage]

$$K = \frac{V_s I_s}{\text{Full Scale deflection}}$$


V_s , Voltage selected
 I_s , Current selected

② Open Circuit Phase for single phase transformer (details)

Here we will get a small amount of current that is called no load current (I_0) when we will give a rated voltage (230V) as the secondary side is disconnected so the I_0 current will be present in primary

side.

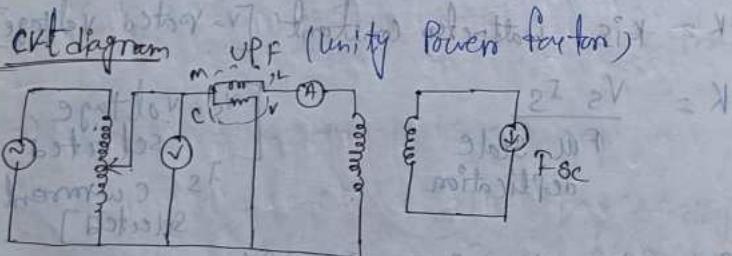- No load component - I_{no}
- on load operation for single phase transformer (short circuit operation - \dots). To perform open loss we will use the short circuit test for a single phase transformer.



Here we will give rated current and the value of rated current is 45A.


To know more about
Transformer based on
(a) no load loss
and (b) short circuit loss
and (c) total loss
and (d) efficiency
and (e) power factor

Phasor diagrams


[$B = \text{hysteresis angle}$]

[at time $t = 0$, V_1 and I_1 are max negative]


[Let the trans ratio = 1:1 here]

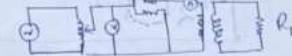

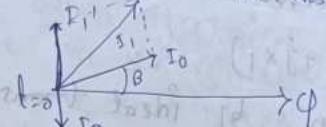(Loading is 3 types,
capacitive, inductive,
resistive loading)




[For ideal
case Phasor
diagram]

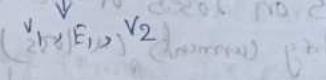


[For capacitive
loading Phasor
diagram]



[For inductive
loading Phasor
diagram]

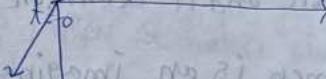

[For resistive
loading Phasor
diagram]

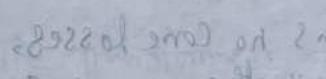

[For resistive
loading Phasor
diagram]



[For resistive
loading Phasor
diagram]

• Demagnetising effect -

$I_2' = I_1'$	I_1' is just opposite direction of I_2'
$I_1' = I_0 + I_1'$	emphasized account
$I_2 = I_1'$	

assignment

① Some phasor diagrams for non-ideal case of ideal type transformers.

Hint: $E_1 = V_1 + I_1 (R_1 + jX_1)$

- ② What do you mean by ideal transformers?
 ③ Write short notes on losses of the transformers. (Iron loss, eddy current loss, cu. loss)

④ At what condition transformers will give maximum efficiency? $[n = \frac{V_2 I_2 \cos \phi_2}{V_1 I_1 (\cos \phi_1 + R_1 + jX_1^2)}$

⑤ Define it. ⑥ full load, half load operation
 [iron loss is constant] transformer, ⑦ short circuit test circuit \rightarrow transformer
 [Copper loss is variable and it depends on I^2]

⑦ An ideal transformer is an imaginary transformer which does not have any loss in it, means no core losses, copper losses and any other losses in transformer. Efficiency of this transformer is considered as 100%.

⑧ Iron loss - This is defined as the loss that is caused due to the alternating flux in the core of the transformer.

As the loss occurs in the core, therefore the iron loss is also known as core loss. There are two types of iron losses, and they are eddy current loss and hysteresis loss.

Cu loss - It is the term often given to heat produced by electrical currents in the conductors of transformer windings or other electrical devices. Copper losses are an undesirable transfer of energy, as are core losses, which result from induced currents in adjacent components.

Eddy current losses - Eddy current losses are the result of Faraday's law, which states that, "Any change in the environment of a coil of wire will cause a voltage to be induced in the coils regardless of how the magnetic change is produced." Thus, when a motor changes its core is rotated in a magnetic field, a voltage, or EMF, is induced in the coils.

⑨ The transformer will give the maximum efficiency when their copper loss is equal to the iron loss.

$$P_c = P_i = P_{Cu} \left[\frac{P_{Fe} \text{ Iron loss}}{P_{Cu} \text{ Copper loss}} \right]$$

$$⑤ n = \frac{\sqrt{2} I_2 \cos \varphi_2}{\sqrt{2} I_2 \cos \varphi_2 + I_1 + I_{cu}}$$

$$h = \frac{\sqrt{2} T_2 \cos \phi_2}{\rho}$$

$$\sqrt{2} I_2 \cos q_2 + p_i + (I_1^2 r_1 + I_2^2 r_2)$$

$$h_2 = \frac{v_2 T_2 \cos \phi_2}{v_2 T_2 \cos \phi_2 + f_1 + I_2 \cdot \rho_2}$$

$$n = \frac{\sqrt{2} I_2 \cos \phi_2}{m}$$

$$\frac{dn}{dT_2} = 0 \Rightarrow T_2 = \frac{1}{2} \left(T_1 + \frac{R_{\text{air}}}{C_p} \right)$$

$$\text{Now, } n = \frac{(\sqrt{2} I_2 \cos \varphi_2)}{(\sqrt{2} I_2 \cos \varphi_2 + I_1^2 + I_2^2 \rho_{\varphi_2})}$$



$$\frac{dn}{dI_2} = \frac{d}{dI_2} \left[\frac{\sqrt{2} I_2 \cos \varphi_2}{\sqrt{2} I_2 \cos \varphi_2 + I_1^2 + I_2^2 \rho_{\varphi_2}} \right] = 0$$


$$2. \quad (\sqrt{2} I_2 \cos \varphi_2 + P_1 + I_2^2 R_{02}) \frac{d}{dI_2} (\sqrt{2} I_2 \cos \varphi_2) \\ = (\sqrt{2} I_2 \cos \varphi_2) \cdot \frac{d}{dI_2} (\sqrt{2} I_2 \cos \varphi_2 + P_1 + I_2^2 R_{02}), \\ (\sqrt{2} I_2 \cos \varphi_2 + P_1 + I_2^2 R_{02}) (\sqrt{2} \cos \varphi_2) + (\sqrt{2} I_2 (\cos \varphi_2)) (\sqrt{2} f_2)$$

Cancelling $(v_2 \cos \theta_2)$ from both terms we get,

$$\begin{aligned} & V_2 I_2 C_0^3 p_2 + p_i + I_2^2 R_{02} - V_2 I_2 q_2 - I_2^2 R_{02} = 0 \\ \therefore & p_i - I_2^2 R_{02} = 0 \\ \Rightarrow & p_i = I_2^2 R_{02} = P_{Cu} \end{aligned}$$

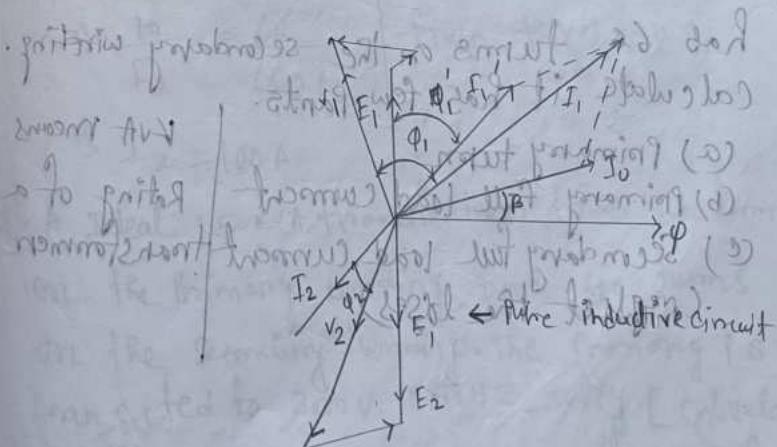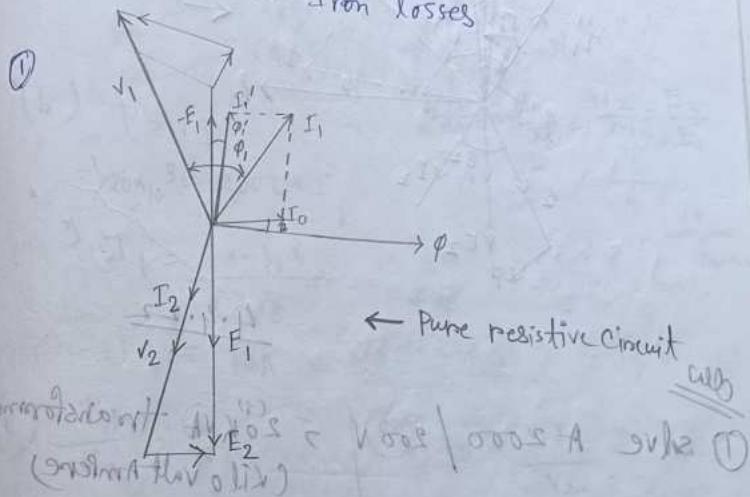So condition to achieve maximum efficiency
is that, copper losses = iron losses



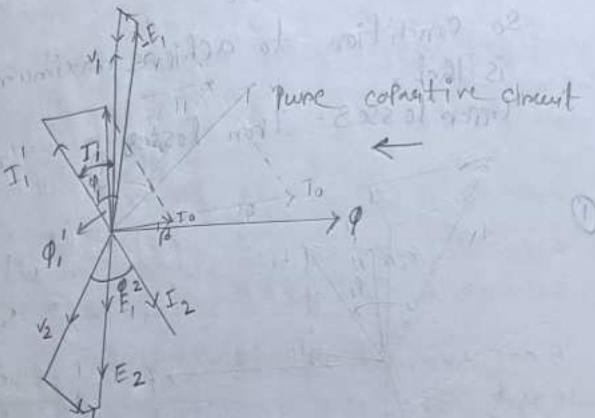

4.4.22

Q solve A 2000 / 200 V \Rightarrow 20 kVA transformer
(Kilo volt Amperes)

has 66 turns on the secondary winding.
calculate it has few turns.

- | | |
|---------------------------------|-------------|
| (a) Primary turn | KVA means |
| (b) Primary full load current | Rating of a |
| (c) Secondary full load current | transformer |
| (neglect the losses) | |

$$N_2 > 66, E_2 = 200, E_1 = 2000 \text{ V}$$

$$(a) \frac{E_2}{E_1} = \frac{N_2}{N_1}$$

$$\Rightarrow \frac{200}{2000} = \frac{66}{N_1}$$

$$\therefore N_1 = \frac{2000 \times 66}{100}$$

$$= 660$$

$$(b) P = \sqrt{I} \cdot V$$

$$\Rightarrow 20 \times 10^3 = 2000 \times I$$

$$\therefore I_1 = \frac{20 \times 10^3}{2000}$$

$$= 10A$$

$$(c) \frac{I_1}{I_2} = \frac{N_2}{N_1}$$

$$\Rightarrow \frac{10}{I_2} = \frac{66}{660/10}$$

$$\therefore I_2 = 100A$$

$$(m) I_2 = \frac{V_1 I_1}{V_2}$$

from this eqn (ii)

- 2) A Ideal 25 kVA transformer has 500 turns on the primary winding and 40 turns on the secondary winding. The primary is connected to 3000 V / 50 Hz supply. [calculate i) primary and secondary currents on full

load

(ii) secondary EMF.

(iii) The minimum core flux

$$\phi > 25 \times 10^{-3}, N_1 = 500, N_2 = 40, V_1 = 300 \text{ V}$$

$$(i) 25 \times 10^{-3} = 3000 \times I_1$$

$$\therefore I_1 = \frac{25 \times 10^{-3}}{3000}$$

$$= 83.33 \text{ A}$$

$$\frac{I_1}{I_2} = \frac{N_2}{N_1}$$

$$\therefore \frac{83.33}{I_2} = \frac{4\phi}{500}$$

$$\therefore I_2 = \frac{83.33 \times 500}{4}$$

$$= 108.33 \text{ A}$$

$$(ii) \frac{N_1}{N_2} = \frac{V_1}{V_2}$$

$$\therefore \frac{N_2}{N_1} = \frac{V_2}{V_1}$$

$$\therefore \frac{40}{500} = \frac{V_2}{300}$$

2nd method

$$\frac{40}{500} = \frac{V_2}{300}$$

2nd method

$$\frac{40}{500} = \frac{V_2}{300}$$

2nd method

$$\frac{40}{500} = \frac{V_2}{300}$$

$$\text{stability condition: } E_1 = 4.44 \phi_m N_1 \Rightarrow E_1 > 4.44 \times 50 \times \phi_m N_1$$

$$\text{and } 2300 = 4.44 \phi_m \times 50 \times 50$$

$$\Rightarrow \phi_m = \frac{30}{5 \times 4.44 \times 50} = 0.027$$

(3) A 230/2300 volt transformer takes no load current of 5 amp, of 0.25 power factor lagging. Find (i) Iron loss (I_C)

(ii) magnetising loss component of current (I_m)

$$V_1 = 230 \text{ V}, V_2 = 2300 \text{ V}, I_0 = 5 \text{ A}, \cos \phi = 0.25$$

$$I = I_C + I_m$$

(i) Iron loss component of the current is

$$I_C = I_0 \cos \phi_0$$

$$I_C = 5 \times 0.25 = 1.25$$

$$(ii) I_m = I_0 \sin \phi_0$$

$$I_m = I_0 \sin \phi_0$$

$$= 5 \times 0.96$$

$$= 4.84$$

④ A 10 kVA single phase transformer has 200 turns in one winding and 100 turns in the other winding, 50 Hz, if the induced EMF in a primary side is 250 V find the value of -

- max flux density if the core area is 64×10^{-4}

$$(P = 10 \times 10^3, N_1 = 200, N_2 = 100, f = 50)$$

$$\frac{100}{200} = \frac{E_2}{250}$$

$$E_2 = 125$$

$$E_2 = 4.44 f \Phi_m N_2$$

$$\Rightarrow 125 = 4.44 \times 50 \Phi_m \times 100$$

$$\Rightarrow \Phi_m = 5.6 \times 10^{-3}$$

$$\text{max flux density} = \frac{\Phi_m}{A} = \frac{5.6 \times 10^{-3}}{64 \times 10^{-4} \text{ m}^2} = 87.5$$

$$= 0.875$$

⑤ A 20 kVA, 2000/200 V transformer at full load, the iron and Cu losses are found to be 400 W and 450 W respectively. Calculate the efficiency at (i) full load, (ii) half load.

In case of full load, $n = 1$

$$P = 20 \times 10^3, V_1 = 2000, V_2 = 200$$

$$P_i = 400 \text{ W}, P_{Cu} = 450$$

$$(i) n_1 = \frac{O/P}{O/P + P_i + \eta^2 P_{Cu}}$$

$$n = \frac{1.2 \times 0.34}{\eta^2 + 0.34 + 1.2 \times 0.34} = 1$$

$$20 \times 10^3 = \frac{20 \times 10^3}{20 \times 10^3 + 400 + (0.875)^2 \times 450}$$

At half load, KVA will be $\frac{1}{2} \times 20 = 10 \text{ kVA}$. Iron loss remains same, but $P_{Cu} = \frac{1}{4} \times 450 = 112.5$

$$\text{In case of half load, } n = \frac{0.96}{O/P + P_i + \eta^2 P_{Cu}}$$

$$= \frac{20 \times 10^3 \times \frac{1}{2}}{20 \times 10^3 + 400 + (\frac{1}{2})^2 \times 450}$$

$$= 0.9512$$

⑥ A single-phase 2200/250 V, 50 Hz transformer has a net core area of 36 cm^2 and a maximum flux density of 6 Wb/m^2 . Calculate the numbers of turns of (a) the primary and (b) the secondary.

$$V_1 = 2200 \text{ V}, V_2 = 250 \text{ V}, f = 50 \text{ Hz}$$

$$\frac{36 \times 8 \times 2 \times 10^{-6}}{6} = \frac{\Phi \text{ m}}{10^{-4}} = 1.9$$

$$\Rightarrow \Phi_m = 6 \times 36 \times 10^{-4} = 1.1 \text{ m} \quad (i)$$

$$E_1 = 4.44 f \Phi_m N_1 = 90$$

$$\Rightarrow 2200 = 4.44 \times 50 \times 6 \times 36 \times 10^{-4} N_1$$

$$\Rightarrow N_1 = 450 \text{ turns}$$

$$E_2 = 4.44 f \Phi_m N_2$$

$$250 = 4.44 \times 50 \times 36 \times 6 \times 10^{-4} N_2$$

$$\Rightarrow N_2 = 52 \text{ turns}$$

$$(m) \frac{E_2}{E_1} = \frac{N_2}{N_1}$$

$$\Rightarrow \frac{250}{2200} = \frac{N_2}{450}$$

$$\Rightarrow N_2 = 52 \text{ turns}$$

⑦ A 230/2300 V transformer takes no-load current of 5 A at 0.25 Power factor lagging. Find (a) iron loss and (b) magnetizing loss component of current.

$$V_1 = 230, V_2 = 2300, I_0 = 5, P = 0.25$$

done

$$\text{iron loss} = 5 \times \frac{0.25}{\pi} = 1.9$$

$$\text{magnetizing loss} = 5 \times \frac{0.25}{3} = 0.41$$

$$P = 1 \times \frac{0.25}{\pi} = 0.04$$

$$P = 1 \times \frac{0.25}{3} = 0.08$$

④ The emf per turn of 3300/300, 50 Hz, single-phase core type transformer is 6V. The maximum flux density is 1.2 T. Find the number of turns in the primary and secondary windings. Also find the hot core-sectional area of the core.

$$V_1 = 3300, V_2 = 300, f = 50$$

$$\frac{E_1}{N_1} = 6$$

$$\therefore \frac{3300}{6} = N_1 = 550 \text{ turns}$$

$$\frac{E_2}{N_2} = 6$$

$$\therefore \frac{300}{6} = N_2 = 50 \text{ turns}$$

$$\frac{\rho_m}{A} = 1.2$$

$$\therefore \phi_m = 1.2 A$$

$$\therefore 300 = 4.44 \times 50 \times 1.2 \times A \times 50$$

$$\therefore A = 225.2 \text{ cm}^2$$

⑤ A 1 kVA, 200/400 turns, single-phase transformer is fed with a 220V, 50 Hz supply at the low-voltage end. Assuming ideal condition, calculate the maximum flux density if the area of cross-section of the core is 5 cm².

$$P = 1 \text{ kVA}, N_1 = 200, N_2 = 400, V_1 = 220 \text{ V}, f = 50 \text{ Hz}$$

$$A = 5 \text{ cm}^2, \Phi_m = ?$$

$$220 = 4.44 \times 200 \times 50 \times 10^{-4} \times A \times 50$$

$$220 = \frac{103}{200} \times 5 \times 10^{-4} \times A \times 50$$

$$A = \frac{220}{103} \times \frac{200}{5} \times 10^{-4} \text{ m}^2$$

$$A = 1.126 \times 10^{-4} \text{ m}^2$$

$$\therefore \text{flux density} = \frac{\Phi_m}{A} = \frac{1.126 \times 10^{-4}}{5 \times 10^{-4}}$$

$$= 0.2252 \text{ T}$$

- (10) A 50 kVA, 5000/500 V, bolted single-phase transformer is given as 900 W. Find the efficiency of the transformer at full load and 0.8 power factor lagging. It has the high and low-voltage winding resistance of 8 Ω and 0.04 Ω respectively. The no-load loss of the transformer is $n = \frac{\text{output}}{\text{no-load loss}}$.
 $P = 50 \times 10^3$, $V_1 = 5000$, $V_2 = 500$, $f = 50$

The no-load loss is same as the core loss or iron loss $= P_i = 900$ W. Full load loss is the copper loss which equals

$$P_{cu} = I_2^2 R_2 \quad [R_1 = K^2 R_2]$$

Now, for $K = 1/10$

$$R_2 = R_2 + K^2 R_1 = R_2 + \left(\frac{V_2}{V_1}\right)^2 R_1 \\ = R_2 + \left(\frac{500}{5000}\right)^2 \times R_1$$

$$= 0.04 + \left(\frac{1}{10}\right)^2 \times 8 \\ = 0.12 \Omega$$

The current is $I_2 = \frac{50 \times 10^3}{500} = 100$ A

$$P_{cu} = (100)^2 \times 0.12 = 12000 \text{ W}$$

So, total loss at full load $= P_i + P_{cu} = 1200 + 900 = 2100$ W

At 0.8 power factor, the full load output P is $50 \times 0.8 = 40$ kW. So, efficiency $\eta = \frac{40}{42.1 \times 100} = 95\%$.

- (11) Determine the minimum of rating of a circuit breaker for single-phase transformer with 3% impedance derived from 400 V, 50 Hz source.

Normal full-load Current is -

$$I_L = \frac{VA}{V_L} \rightarrow \frac{10,000}{400} = 25 \text{ A}$$

max. short-circuit ampere is given by -

Full-load ampere	$\frac{1}{\% \text{ Impedance}}$
------------------	----------------------------------

$$\frac{\text{Full-load ampere}}{\% \text{ Impedance}} = \frac{25}{0.03} = 833.3 \text{ A}$$

So the breaker used would have minimum interrupting rating of 833.3 A.

[NOTE - The secondary side voltage is not used in the calculation because in a transformer the primary circuit is the only winding to be interrupted]

% Impedance = 14.5

$$= 225 \cdot 2 \text{ cm}^2$$

$$P_2 = 50 \times 10^3$$

$$f = 50, R_1 = 8, E_1 = 500, R_2 = 500$$
$$\cos \phi = 0.8, P_1 = 900,$$

$$P_1 = 900$$

$$P_{in} = I_2^2 R_2$$

$$R_2 = R_2 + \beta' R_1$$

$$= 0.047 \left(\frac{500}{5000} \right)^2 \text{ gaw}$$

$$I_2 = \frac{50 \times 10^3}{500} = 0.12 \text{ A}$$
$$P_{in} = \left(\frac{100}{200} \right)^2 (100) \text{ gaw}$$

no load loss of 0.048 respectively
transformer
 $P = 50 \times 10^3$ [$n = \frac{\text{output}}{\text{input}}$]

output = $50 \times 10^3 \times 1 \times 0.8$
 $= 40 \text{ kW}$

take 2100 W
 $\rightarrow 2.1 \text{ kW}$

$$n = \frac{40}{42.1} \times 100 \\ \approx 96\%$$

$$\frac{(500)^2}{5000} \times R_1 \\ = 0.04 + \left(\frac{1}{10}\right)^2 \times 8$$

$$\text{At } 0.02 \text{ total loss at } 10.10 \text{ is } 105.3$$

(12) A 50 kVA, 6000/250 V transformer has 52 turns on the secondary winding. Determine the primary number of turns. Also calculate primary and secondary currents.

$$P = 50 \times 10^3 \quad V_1 = 6000, \quad V_2 = 250$$

$$N_2 = 52$$

$$\frac{250}{6000} = \frac{52}{N_1}$$

$$\therefore N_1 = 1248$$

$$50 \times 10^3 = 6000 \times I_1 \rightarrow I_1 = 1000$$

$$\therefore I_1 = 8.33$$

$$\frac{250}{6000} = \frac{8.33}{I_2}$$

$$\therefore I_2 = 200$$

other side of the core - 370 A
current through it is 200 A
then current through it is 200 A
induced at primary side is 200 A

(13) A single-phase, 50 Hz transformer has 350 turns on the primary and 800 turns on the secondary windings. The primary voltage is 400 and the cross-sectional area of the core is 750 mm^2 . Determine (a) the emf induced in the secondary and (b) the maximum value of flux density.

$$f = 50, \quad N_1 = 350, \quad N_2 = 800, \quad V_1 = 400, \\ A = 750 \times 10^{-6} = 7.5 \times 10^{-4}$$

$$(a) \quad E_2 = \frac{800}{400} \times 350$$

$$E_2 = 714.2 \text{ V}$$

$$(b) \quad 400 = 4.44 \times 50 \times \frac{\Phi_m}{7.5 \times 10^{-4}} \times 350 \\ \therefore \Phi_m = 5.1 \times 10^{-3} \text{ Wb}$$

$$\text{max flux density} = \frac{5.1 \times 10^{-3}}{7.5 \times 10^{-4}}$$

$$= 6.86 \text{ Vs/m}^2$$

(14) A 440/220 V transformer takes a current of 0.2 A open circuit at a power factor of 0.18. Find the magnetizing and iron loss component of current.

$$N_1 = 440; V_2 = 220; \text{ for } 0.2 \text{ A} \cos \phi = 0.18$$

$$I_C = I_o \cos \phi$$

$$= 0.2 \times 0.18$$

$$= 0.036 \text{ A}$$

$$I_m = I_o \sin \phi$$

$$= 0.2 \times \sqrt{1 - (0.18)^2}$$

$$= 0.1967 \text{ A}$$

$$\therefore \text{Efficiency} = 0.82 \quad (d)$$

$$\text{Power Factor} = 0.18$$

$$\text{Efficiency} = \text{Output Power} / \text{Input Power}$$

$$= 0.82$$

(15) Determine the % efficiency of single-phase 20 kVA, 2200/120 transformer at full load 0.8 pf and half full load 0.4 pf. Given: Full load iron loss = 400 W, iron loss = 350 W.

$$P_r = 20 \times 10^3 \quad V_1 = 2200 \quad I_2 = 20$$

Rated kVA = 20, iron loss = 350 W, full-load copper loss = 400 W.

To find % efficiency at full load 0.8 pf:
Fraction of the load (x) = 1. Therefore,

$$\text{Output} = \text{Rated kVA} \times 1000 \times \text{pf} \times x$$

$$= 20 \times 10^3 \times 0.8 \times 1$$

$$= 16000 \text{ W}$$

$$\begin{aligned} \text{Total loss} &= (\text{iron loss}) \times 2 + (\text{copper loss}) \\ &= 350 + (1)^2 \times 400 \end{aligned}$$

$$= 750 \text{ W}$$

$$\text{Input} = \text{Output} + \text{Total loss}$$

$$= 16000 + 750 = 16750 \text{ W}$$

$$\% \eta = \frac{\text{Output}}{\text{Input}} \times 100$$

$$= \frac{16000}{16750} \times 100$$

$$= 95.52\%$$

$$= 95.52\% = 0.9552$$

$$= 0.9552 \times 100 = 95.52\%$$

To find 1. efficiency at full load, 0.4 pf. & half

$$(12) \quad x = \frac{1}{2}$$

$$\therefore \text{output} = 25 \times 10^3 \times \frac{1}{2} \times 0.4 = 4000 \text{ W}$$

$$\text{total loss} = 350 + (0.5)^2 \times 400 = 450 \text{ W}$$

$$\text{input} = 4000 + 450 = 4450 \text{ W}$$

$$1.\eta = \frac{4000}{4450} \times 100 = 89.88\%$$

(b) In a 25 kVA, 2000/200 V transformer the iron and copper losses are 350 and 400 W, respectively. calculate the percent efficiency on unity pf at (a) full load, (b) half load

and (c) determine the load for maximum efficiency and the iron and copper losses in this case.

$$P = 25 \times 10^3 \quad V_1 = 2000, V_2 = 200$$

$$P_i = 350, P_{cu} = \frac{400}{100} + \frac{400}{200} = 1.5 \text{ W/W}$$

$$(a) \quad x = 1, \text{pf} = 1$$

$$\therefore \text{output} = 25 \times 10^3 \times 1.5 \text{ W}$$

$$\text{Total loss} = 25 \times 10^3 \text{ W}$$

$$\text{input} = 750 + 25 \times 10^3 = 25750$$

$$1.\eta = \frac{25 \times 10^3}{25750} \times 100 = 97.08\%$$

$$(b) \quad \text{pf} = 1, x = \frac{1}{2}$$

$$1.\eta = \frac{25 \times 10^3 \times \frac{1}{2} \times 1}{25 \times 10^3 \times \frac{1}{2} + 350 + 400 \times (\frac{1}{2})^2} \times 100 \\ = 96.52\%$$

(c) The load at which maximum efficiency will occurs is -

$$\sqrt{\frac{350}{400}} \times 25 \times 10^3 = 23.38 \text{ kVA}$$

and the losses are each 350 W

The load at which max. efficiency will occurs - $\sqrt{\frac{P_i}{P_{cu}}} \times P$
losses are each $= P_i$

$$12.52 \text{ kVA} \left[\begin{array}{l} \left(\frac{1}{2} - \frac{1}{1.5} \right) \text{ pf} = 0.25 \\ \left(1 - \frac{1}{1.5} \right) \text{ pf} = 0.2 \\ \left(\frac{1}{2} - \frac{1}{1.5} \right) \text{ pf} = 0.08 \end{array} \right]$$

②

Ques 11/9/22
 (1) A resistance of 10Ω is connected in series with a 50mH inductance across 230V , 50Hz supply. Calculate (i) Current flowing in the circuit. (ii) The phase angle of the current.

$$R = 10\Omega, V = 230\text{V}, f = 50\text{Hz}, L = 50 \times 10^{-3}\text{H}$$

$$(i) I = \frac{V}{R} = \frac{230}{10} = 23\text{A}$$

$$(ii) I_m = \frac{V_m}{X_L} = \frac{V_m}{\omega L}$$

$$V_m = \frac{V_m \sin 90^\circ}{\sqrt{2}}$$

$$3 V_m = 230 \times \sqrt{2}$$

$$= 325.2\text{V}$$

$$\therefore I_m = \frac{325.2}{2\pi \times 50 \times 50 \times 10^{-3}} = 10.7\text{A}$$

$$I = I_m \sin(\omega t - \frac{\pi}{2})$$

$$= 20.7 \sin(2\pi \times 50t - \frac{\pi}{2})$$

$$> 20.7 \sin(314t - \frac{\pi}{2})$$


$$\tan \phi = \frac{X_L}{R} = \frac{2\pi \times 50 \times 50 \times 10^{-3}}{10} = 2fL = 57.51^\circ$$

$$\therefore \phi = 2fL = 57.51^\circ$$

$$I = \frac{23}{2} = 12\text{A}$$

\therefore The phase angle is $\frac{\pi}{2}^\circ$ and the current is lagging.

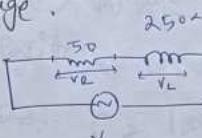(2) The resistance of 5Ω is connected in series with a pure inductor of 250mH . The circuit is connected to a 50Hz sinusoidal supply and the voltage across the resistance is 150V . (i) Calculate the supply voltage.



$$R = 5\Omega, L = 250 \times 10^{-3}\text{H}, f = 50\text{Hz}$$


$$\sqrt{R^2 + X_L^2} = \sqrt{5^2 + (2\pi \times 50 \times 250 \times 10^{-3})^2} = 150$$

$$\therefore I = \frac{VR}{R} = \frac{150}{5} = 3\text{A}$$


$$V_L = IX_L = 3 \times 2\pi \times 50 \times 250 \times 10^{-3}$$

$$= 235.6\text{V}$$
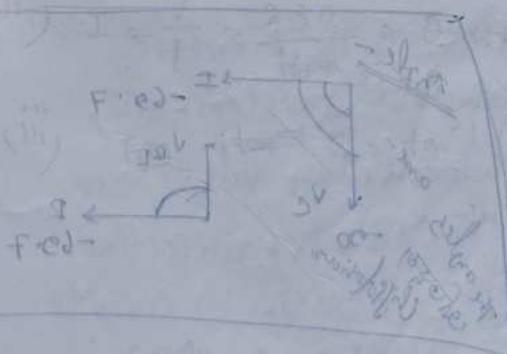
$$\therefore \text{Supply voltage} = \sqrt{V_R^2 + V_L^2} = \sqrt{150^2 + 235.6^2} = 385.6\text{V}$$



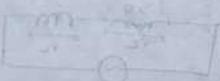(i) A bulb of 25W is connected in series with a resistor of 10 ohms. If voltage across the bulb is 20V, find the current through the bulb.



$$P = V^2 / R \Rightarrow 25 = 20^2 / R \Rightarrow R = 16 \Omega$$

$$V = 20V$$


$$I = P / V = 25 / 20 = 1.25A$$

$$E = V + IR \Rightarrow E = 20 + 1.25 \times 16 = 32V$$

$$V = 32V$$

$$I = 1.25A \rightarrow 1.25A - \text{current flow}$$

$$V = 32V$$

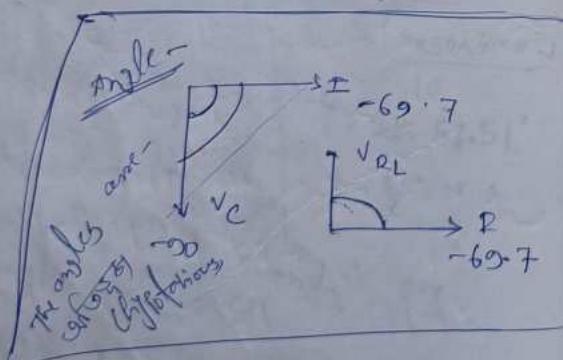

(ii) A 10Ω resistor is connected in series with a $100\mu F$ capacitor to a 230V 50Hz supply. Find (i) Impedance

(ii) Current (iii) Power factor (iv) Phase angle (v) Voltage across resistor and the capacitor.

$$R = 10\Omega, C = 100 \times 10^{-6} F, V = 230, f = 50$$


$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 100 \times 10^{-6}} = 31.8 \times 10^3 \Omega$$

$$(i) Z = \sqrt{(X_C)^2 + R^2} = \sqrt{(31.8 \times 10^3)^2 + (10)^2} = 31.8 \times 10^3 \Omega$$

$$(ii) I = \frac{V}{Z} = \frac{230}{31.8 \times 10^3} = 0.014A = 1.4mA$$

$$(iii) \cos \phi = \frac{R}{Z} = \frac{10}{31.8 \times 10^3} = \tan^{-1} \left(\frac{X_C}{R} \right) = \tan^{-1} \left(\frac{31.8 \times 10^3}{10} \right)$$
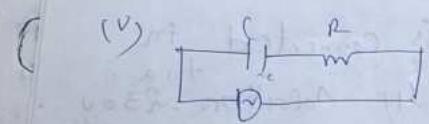
$$\therefore \cos \phi = 0.029 \quad \text{[1st get the angle from } \cos \phi, \text{ then calculate tan]} \\ (iv) \text{Phase angle } \phi = 17.2^\circ$$



$$C = 100 \times 10^{-6} F$$

$$I = 6.89$$

The voltage across capacitor = 6.89×31.8
~~100~~
 $= 219.1 V$

The voltage across the resistance =

$$6.89 \times 10$$

$$68.9 V$$

- (vi) A choke coil of resistance 8Ω and inductance of $0.15 H$ is connected in series with a capacitor of capacitance $125 \mu F$ across $230V, 50Hz$. Supply calculate (i) the inductive reactance (ii) capacitive reactance (iii) Impedance (iv) current (v) voltage across the coil and the capacitor respectively.
- (vi) Phase difference between the current and the supply voltage.

$$R = 8 \Omega, L = 0.15 H, C = 125 \times 10^{-6} F$$

$$f = 50, V = 230 V$$

$$(i) X_L = 2\pi f L = 0.15 = 47.12 \Omega$$

$$(ii) X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 125 \times 10^{-6}} = 25.46 \Omega$$

$$(iii) Z = \sqrt{(X_L - X_C)^2 + R^2}$$

$$= \sqrt{(47.12 - 25.46)^2 + (8)^2}$$

$$Z = 23.09 \Omega$$

$$(iv) I = \frac{V}{Z} = \frac{230}{23.09} = 9.96 A \text{ at an angle } = -69.7^\circ$$

$$(v)$$

$$\text{The voltage across coil } = I(X_L)$$

$$= 9.96 \times 47.12 = 247.12$$

$$= 2469.39 V, \text{ angle} = 10.66^\circ$$


$$\text{Capacitor } = I \times X_C$$

$$= 9.96 \times 25.46$$

$$= 253.58 V, \text{ angle} = 159.7^\circ$$

$$(vi) \tan \phi = \frac{(X_L - X_C)}{R}$$

$$= \frac{47.12 - 25.46}{8} = 14.8$$

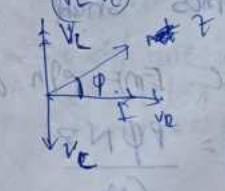


$$\phi = 69.72^\circ$$

The phase diff. is 69.72° (we consider a minus angle with V_C [i.e., 2469.39 is 69.72°])

The value of impedance is 23.09 at an angle of 69.72° .

13/4/22

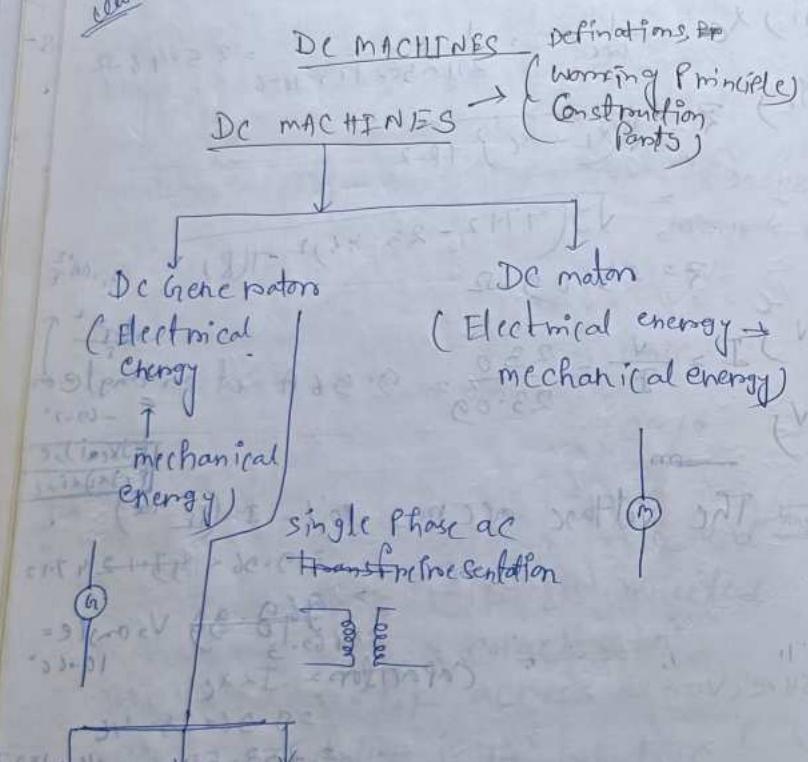


In the EMF eqn of DC Generators.

$$E_g = \frac{P\phi N Z}{60A}$$

P = no of poles
 A = no of parallel path
 N = speed
 Z = no of conductors
 ϕ = flux

The winding of conductors \rightarrow LAP, A=1
 \rightarrow H.A.V.E A=2

• Series Generators

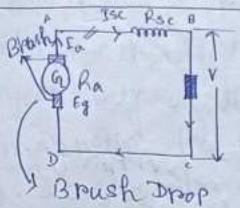

- [R_{sc} = series resistance]
- [R_a = armature resistance]
- [I_a = Armature current]
- [I_{sc} = series field current]
- [V = Terminal voltage drop]

ABC DA Loop,


$$BCD + I_a R_a + I_{sc} R_{sc} = E_g \quad \Rightarrow \frac{V}{R_a} +$$

$$\Rightarrow V + BCD + I_a (R_a + R_{sc}) = E_g$$

$$\Rightarrow E_g = V + I_a (R_a + R_{sc}) + BCD$$

BCD = Brush Contact drop

• Shunt Generators

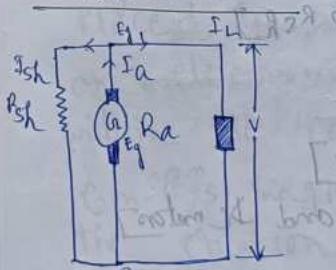

- [R_{sh} = Shunt resistance]
- [R_a = armature resistance]
- [I_L = Load / line current]

$$I_a = I_L + I_{sh}$$

$$\frac{E_g}{R_{sh}} + \frac{E_g}{R_a} + (E_g - V) = 0$$

$$\Rightarrow E_g \left(\frac{1}{R_{sh}} + \frac{1}{R_a} + \frac{1}{R_{sh}} \right) = V$$

$$\Rightarrow E_g = (R_a + R_{sh}) + E_g - P_a R_{sh} - V R_a R_{sh} \rightarrow$$


$$\Rightarrow E_g = R_a + R_{sh}$$

$$E_g = V + I_a R_a + BCD$$

$$R_{sh} = \frac{B f_m V}{f_{sh}}$$

H/W

• Compound Generators

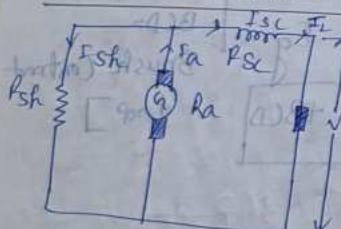

[When it is compound then Ra and Rsc are in series and this will be parallel to Rsh]

[Graphs Ia vs Q
N vs Ia]

[DC Generator Characteristics]

[Principle of DC Generators and

[Numericals]



$$R_2 f + jL = nT$$

$$0 = (n - p_f) + \frac{P^2}{n^2} + \frac{B^2}{R_2^2}$$

$$0 = j2\pi n \left(V - C_f \right) + j2\pi f p_f + j2\pi n / p_f \times R$$

Definition

① DC motors - A DC motor is any of a class of rotary electrical motors that converts direct current electrical energy into mechanical energy. The most common types rely on the forces produced by magnetic fields.


② DC generators - A direct-current (DC) generator is a rotating machine that supplies an electrical output with unidirectional voltage and current. The basic principle of operation are the same as those for synchronous generators.

③ DC generators operates on the principle of the dynamically induced electromagnetic force. When a conductor is placed in a varying magnetic field, an electromotive force gets induced within the conductor. This induced e.m.f's magnitude is measured using the equation of the electromotive force of a generator. This is the working principle of dc generator.

(4) Working principle of DC motor -
when rest in a magnetic field,
a current-carrying conductor
gains torque and develops a
tendency to move. In short, when
electric fields and magnetic
fields interact, a mechanical
force arises. This is the
principle on which the DC motor
works.

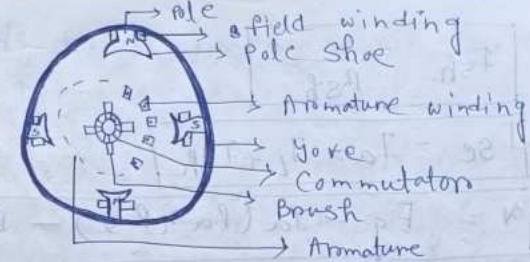(5) Construction of DC motor -


There are two main parts
of DC motor. The rotating part
is the armature and the static
part is their stationary part. The
armature coil is connected
to the DC Supply. The armature
coil consists the commutators
and brushes.



(6) Compound Generators - In a Compound generator there are two sets of
the field winding on each pole.
one of them is connected in series
having few turns of thick wire,
and the other is connected in
parallel having many turns of fine
wire with the armature windings.
This is divided into 2 types -

- 1) Long Shunt Compound Generators
- 2) Short "

1) Long shunt Compound Generators -

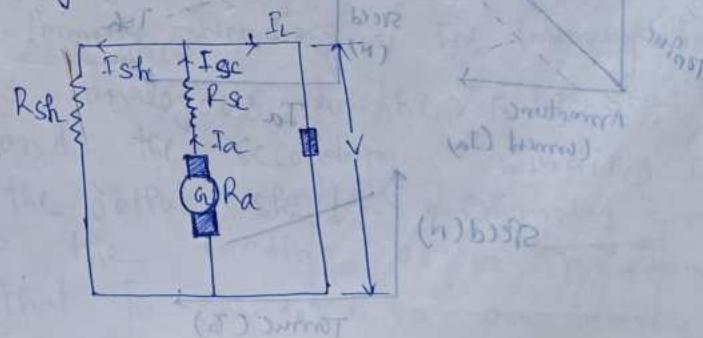


$$f_{sh} = \frac{V}{R_{sh}}$$

$$I_{se} = I_a = I_L + f_{sh}$$

$$V = E_g - I_a (R_a + R_{se}) - B S D$$

(1)

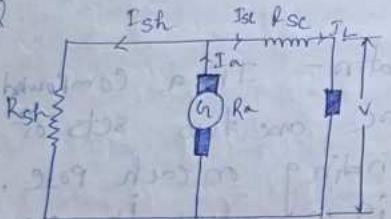


$$I_{se} = I_L$$

$$f_{sh} = \frac{V + I_L R_{se}}{R_{sh}}$$


$$\frac{E_g - I_a R_a}{f_{sh} + I_L R_{se}}$$

$$V = E_g + I_a R_a + I_L R_{se} + B S D$$

(2)

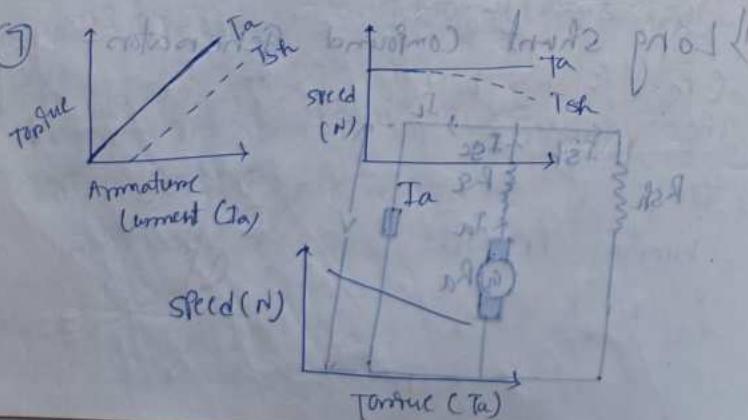

(3) speed v/s torque graph

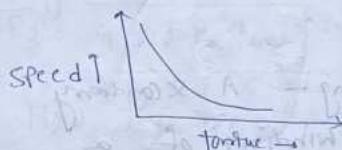

(4) characteristics of DC generators

- (i) open circuit characteristic (o.c.c)
- (ii) internal or total characteristic
- (iii) external characteristic

(5) Basic principle of transformer

The transformer works on the principle of Faraday's law of electromagnetic induction and mutual induction. There are usually two coils primary coil and secondary coil on the transformer core. The core laminations are joined in the form of strips.

(6) Primary winding → The primary winding is analogous to the input shaft and the secondary winding to the output shaft. A primary winding is the winding part of a transformer that is connected to and receives

(i) Energy from an external source
of electrons.

③ Secondary winding - A secondary winding is the winding of a transformer that receives its energy by electromagnetic induction from the primary winding.

(3) Emf E_m of single phase
Ac transformer -

We know that - $E_1 = \frac{N \frac{d\phi}{dt}}{\mu_0 A}$

$$F_{p(\max)} = N \cdot w \cdot q_m$$

Rms Value is given by, $F_r = \frac{F_1(\max)}{\sqrt{2}}$

Putting the value of $E_{1(\max)}$ in above equation, we get

$E = \frac{1}{2} m f^2$ (vibrations) $\omega = 2\pi f$

Similarly, we get,

$$F_2 = 4.49 \text{ N} \cdot \text{m}$$


(14) How the transformer is rated in kVA = Transformer are rated in kVA because the losses occurring in the transformer are independent of Power factors. kVA is the unit of apparent power. It is a combination of real power and reactive power.

(13) What is wattmeters connections?

The dynamo-mie the current coil is connected in series with the load hence it carries the circuit current. The potential coil is connected across the load so it carries current proportional to the voltage.

21/4/22

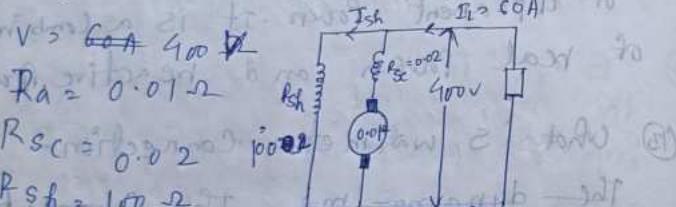- (1) Pole cone
 ① A ~~sh~~ 100² shunt generator supp Neg
 60A at a terminal voltage of 400V.
 the armature resistance is 0.01Ω. the
 series field resistance is 0.02Ω and
 the shunt field resistance is 100Ω.
 Find the generated emf taking the
 BSD at 1V per brush. Neglect
 the armature reaction drop.



$$\begin{aligned}
 I_a &= I_{sh} + I_L \\
 &= 4 + 60 \\
 &= 64A \\
 E_g &= V + I_a(R_{sh} + R_{sc}) + BSD \\
 &= 400 + 64(0.01 + 1) = 401.6V
 \end{aligned}$$

$$I_a = I_{sh} + I_L$$

$$= 4 + 60$$


$$= 64A$$

$$\begin{aligned}
 E_g &= V + I_a(R_{sh} + R_{sc}) + BSD \\
 &= 400 + 64(0.01 + 1) = 401.6V
 \end{aligned}$$

$$\begin{aligned}
 E_f &= V + I_a(R_{sc} + R_a) + BCD \\
 &\Rightarrow 401.64 = (0.02 + 0.01) + 1 \\
 &\Rightarrow 403
 \end{aligned}$$

- ② A 20kW, 200V dc shunt generators has armature and field resistance of 0.05Ω and 150Ω respectively. Determine the total armature power developed when the machine works as a generator delivering 20kW output.
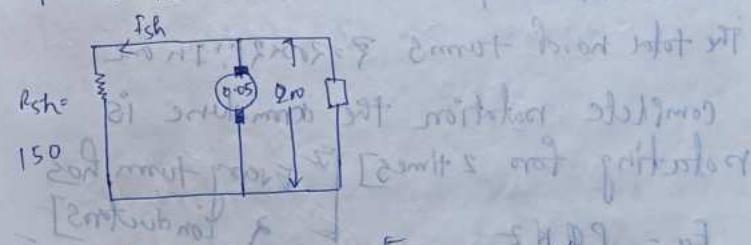
$$\begin{aligned}
 V &= 200V & N_d &= 1000 \\
 R_a &= 0.05\Omega & P &= 20kW \\
 R_{sh} &= 150\Omega & 200 &= 1000 \times 200 \\
 P &= 20 \times 10^3 W & 1000 &= h
 \end{aligned}$$



$$\begin{aligned}
 I_a &= I_{sh} + I_L \\
 &= \frac{200}{150} + 1000 \\
 &= 1.33 + 1000 = 101.33A
 \end{aligned}$$

$$\begin{aligned}
 E_g &= V + I_a(R_{sh} + R_{sc}) \\
 &= 200 + 101.33 \times 0.05 \\
 &= 205.06V
 \end{aligned}$$

(12)

$$P_a = 20.5 \cdot 0.6 \times 101.33 \quad [R_a = E_g I_a]$$

$$= 20.78 \times 10^3 \text{ W}$$

$$\begin{aligned} A &= p (\text{lap wound}) \\ A &= 2 (\text{wave wound}) \end{aligned}$$

- (3) A 4 pole lap wound dc shunt generator
has useful flux per pole of 0.08 weber.
The armature winding consists of 200 turns
with total resistance of 0.8Ω.

Calculate the terminal voltage when running
at 1000 rpm. If the armature current is
15 A.

$$\begin{aligned} P &= q \\ A &= p = 4 \\ \phi &= 0.08 \text{ wb} \\ N &= 1000 \text{ rpm} \end{aligned} \quad \begin{aligned} I_a &= 15 \text{ A} & V_{0.5} &= V \\ \text{number of turns (n)} &= 200 = 50 \\ R_a &= 0.8 \Omega & 200 &= 2 \times 100 = 200 \\ 200 &= 2 \times 100 = 200 & 200 &= 2 \times 100 = 200 \end{aligned}$$

The total no. of turns $\frac{200}{4} = 50$ in one complete rotation the armature is rotating for 2 times] Every turn has 2 conductors

$$E_g = \frac{P\phi N}{60A} \quad \begin{aligned} &I + \frac{dI}{dt} = \frac{dV}{dt} \\ &= 9 \times 0.08 \times 1000 \times 200 = 144000 \end{aligned}$$

$$\begin{aligned} [AEg \cdot 16014] &= 1533.33V \\ &E_g = 0.08 \times 1700 \end{aligned}$$

$$\begin{aligned} \frac{dV}{dt} &= 0.08 \times 1700 + 1000 = 144000 \\ &V = 0.08 \times 1700 = 1360 \end{aligned}$$

$$R_a = 0.8 \Omega$$

since there are four parallel paths,
each path has the resistance of $0.8/4 = 0.2 \Omega$

The equivalent resistance of the four parallel paths of 0.2Ω in each parallel path will be $0.2/4 = 0.05 \Omega$

$$V = E_g - I_a R_a$$

$$\begin{aligned} &= 533.33 - 15 \times 0.05 \\ &= 530.83V \end{aligned}$$

$$\begin{aligned} &(b) \text{ now } n = 1000 \\ &\text{so } V = 530.83V \end{aligned}$$

$$0.08 \times 200 = \frac{E - 0.05 \times 200}{0.05}$$

$$E = 1000$$

and counter emf becomes 530.83Ω
which is right hand emf

so terminals voltage is $530.83 - 0.05 \times 200 = 510.83$

current $E - 0.05 \times 200 = 510.83$

$I = \frac{510.83}{0.05} = 10216.6$

(i) A 4 Pole wave wound dc generator has 50 slots and 34 conductors per slot. The flux per pole is 10 mwb. Determine the induced emf in the armature if it is rotating at speed of 600 rpm.

$$P = 4$$

$$Z = 24 \times 50 = 1200$$

$$\Phi = 10 \times 10^{-3} \text{ Wb}$$

$$N = 600 \text{ rpm}$$

$$A = 2 \quad (\because \text{it is a wave wounded})$$

$$E_g = \frac{P \times N \times Z}{60A}$$

$$= \frac{4 \times 10 \times 10^{-3} \times 600 \times 1200}{60 \times 2}$$

$$= 240 \text{ V}$$

(ii) A 6 Pole wave wound armature has 780 conductors and a flux of 12 mwb. Find the speed of the ~~the~~ armature when generated emf is 400 v. What will be the speed when it is lap wound.

wave wound
 $E_g = 400 \quad \Phi = 12 \times 10^{-3}$

$$P = 6$$

$$A = 2$$

$$Z = 780$$

(iii)

$$400 = \frac{6 \times 12 \times 10^{-3} \times N_1 \times 780}{60 \times 2}$$


$$\Rightarrow N_1 = 8.54 \times 10^4 \text{ rpm}$$

$$(iv) 400 = \frac{6 \times 12 \times 10^{-3} \times N_2 \times 780}{60 \times 6}$$

$$\Rightarrow N_2 = 2.56 \times 10^5 \text{ rpm}$$

Types of generator

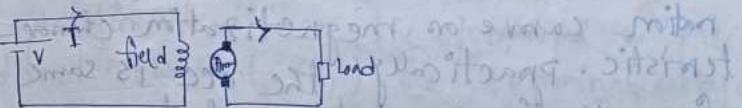1) Separately excited generator - In this type of generators, the field magnets are energized from an external DC source.



2) Self excited generator - In these generators the field is excited by the current induced in the generator itself. These are classified into 3 types of generators -

a) Shunt-wound generator

b) Series-wound generator

c) Compound wound generator

i) Long-Shunt compound ,

ii) Short-Shunt compound ,

• The armature magnetic field has two effects-

1. It demagnetizes or weakens the main flux.
2. It cross-magnetizes or distorts the flux.

main

• DC generator's characteristics

1) Open circuit characteristic - [The curve between the no-load generated emf (E_0) and the field current (I_f) at constant speed is known as open-circuit characteristics (OCC) of a DC generator]. If it is otherwise known as no-load saturation curve or magnetization characteristic. Practically the OCC is same for all the generators whether separately or self-excited. The data for OCC curve are obtained experimentally by varying the field current at a constant speed and recording the change in terminal voltage for the corresponding field currents.

2) Internal or total characteristic (E/I_a):

It gives the relation between the generated emf on load (E) and the armature current (I_a). The Emf E is the emf generated after deducting the voltage drop due to the demagnetizing effect of armature reaction. Therefore, this curve lies below the OCC curve. The internal characteristic can be obtained from external characteristic if winding resistances are known.

$$E = E_0 - \text{Armature reaction drop}$$

3) External characteristic (V/I_L) - It gives the relation between the terminal voltage (V) and load current (I_L). The terminal voltage V becomes available across the external circuit after deducting the voltage drop due to the armature reaction drop, due to the armature resistance and voltage drop from the total emf generated (E_0). Therefore this curve lies below the internal characteristic. This characteristic is very important in determining the suitability of a generator for a given purpose.

$$V = E_g - \text{Armature reaction drop}$$

$$V = E - I_a R_a$$

where I_a is the armature current and R_a is the armature resistance.

↳ voltage regulation - The voltage regulation of a generator generally refers to the change in output voltage for any change in load. It is usually expressed as the change in voltage

from a no-load condition to a full-load condition and is expressed as a percentage of full load. It is expressed mathematically in the following way -

$$\% \text{ regulation} = \frac{E_{\text{no load}} - E_{\text{full load}}}{E_{\text{full load}}} \times 100$$

where $E_{\text{no load}}$ is the no-load terminal voltage which is same as E_g and $E_{\text{full load}}$ is the full-load terminal voltage of the generator.

Some applications of generators are:

- Generating power for industrial purposes.
- Generating power for domestic purposes.
- Generating power for railway traction.
- Generating power for aircrafts.
- Generating power for ships.
- Generating power for space vehicles.

• Applications of DC generators -

1) DC Shunt generator - Because of its slightly drooping characteristics, the shunt generator is suited for charging batteries and also for parallel operation. It is also used for lighting and power supply purpose.

2) DC series generator - Because of its raising characteristics, it is widely used as boosters (railway service). It is also used for supplying the field current for regenerative breaking of DC locomotives.

3) DC Compound generator - They are used to supply power to railway circuits, elevator motors, incandescent lamps, etc. Differentially compound generator is used as an arc welding generator.

(1) A DC long shunt compound generator delivers a load current of 200A at 500V. The resistance of the armature, series field and shunt field are 0.03Ω , 0.015Ω and 150Ω . Calculate the emf induced in the armature. Allow a brush contact drop of $1V/\text{brush}$.

$$I_L = 200A, V = 500V, R_a = 0.03\Omega,$$

$$R_{se} = 0.015\Omega, R_{sh} = 150\Omega, B_{SD} = 2V$$

$$F_{sh} = I_a + I_{sh} + I_L$$

$$F_{sh} = \frac{V}{R_{sh}} = \frac{500}{150} = 3.33A$$

$$I_{sh} = 3.33 + 200 = 203.33A$$

$$E_g = V + I_a(R_a + R_{se}) + B_{SD}N$$

$$= 500 + 203.33(0.03 + 0.015) +$$

$$= 511.15V$$

(2) An 8-pole lap wound DC generator has 450 armature turns. It operates at 0.02wb flux per pole on 2 rounds at 1000 rpm at no load. Find the emf induced by it.

$$A = P = 8$$

$$Z = 450 \times 2 \quad [\text{Every turn has 2 conductors}]$$

$$\text{1 pole} \rightarrow \Phi = 0.02$$

$$8 \rightarrow 0.02 \times 8$$

$$N = 1000$$

$$E_g = \text{constant} \times N \times \Phi = 2 \times 1000 \times 0.02$$

(3) A separately-excited DC generator develops an induced emf of 220V while running at 500 rpm and with a flux of 0.05 wb/pole . What would be the required speed if the emf of 200V is to be generated with a flux of 0.045 wb ?

$$E_g = 220V, N_1 = 500, \Phi_1 = 0.05$$

$$E_g = \frac{N_1 \Phi_1}{60}$$

$$E_g = 200V, N_2 = ?, \Phi_2 = 0.045$$

$$\frac{220}{200} = \frac{500 \times 0.05}{N_2 \times 0.045} \Rightarrow N_2 = 500 \text{ rpm}$$

Q) A 6-pole 10P wound DC generator has 720 conductors. A flux of 80m wb/pole is driven at 1000 rpm. Find the generated emf.

$$A = P = 6, Z = 720, \phi = 80 \times 10^{-3}$$

$$N = 1000$$

$$E_g = \frac{6 \times 1000 \times 720 \times 80 \times 10^{-3}}{60 \times 6} = 9600$$

To a 48-pole DC generator has 500 conductors and a useful flux of 0.05 wb. What will be the emf generated if it is lap connected and runs 1200 rpm? What must be the speed at which it is to be driven to produce the same emf if it is wave wound?

$$A = P = 48, \phi = 0.05, Z = 500 \times 2 \\ N = 1200$$

$$E_g = \frac{48 \times 0.05 \times 500 \times 1200}{60 \times 48} = 500 V$$

$$b) A = 2, P = 8, \phi = 0.05, E_g = ? \\ Z = 500, N = ?$$

$$E_g = 500 = \frac{48 \times 0.05 \times N \times 500}{60 \times 2}$$

$$N = \frac{120}{48 \times 0.05} = 600 \text{ rpm}$$

• Principle of DC motor

Motors change electrical energy to mechanical energy. Whenever a current carrying conductor is placed in a magnetic field, a force (F) will act on the conductor whose magnitude is given by -

$$F = B I L \sin \theta \text{ Newton}$$

$$B = \text{flux density (wb/m}^2)$$

$$l = \text{length (m)}$$

$$I = \text{current (A)}$$

$$\theta = \text{angle between conductor and field}$$

* Direction of the force is given by Fleming's left-hand rule.

Sem-II (Last year) EENUGLE 301

- (i) Distinguish between mesh and loop of a network.
- loop \oplus is encountered more than once.
- loop is any closed path through a circuit where no node more than one is encountered
- To find a loop, start at a node in the circuit from this node, move back to the same node along a path to ensure that no node is encountered again.
- 6) An electric iron is rated power 240W. Find the current drawn and resistance of the heating element.

$$P = 1000 \text{ W}, V = 240 \text{ V}$$

$$\begin{aligned} & P = VI, \text{ where } I \text{ is current} \\ & 1000 = 240 \times I \\ & I = \frac{1000}{240} = 4.16 \text{ A} \end{aligned}$$

(ii) Define i) charge ii) electric current

(iii) Power (iv) network.

(i) Charge - Electric charge is the physical property of matter that causes it to experience a force when placed in an electromagnetic field. The fundamental electrical property to which mutual attractions or repulsions between electrons or protons is attributed.

- 1) A mesh is a close path in a circuit with no other paths inside it.
- 2) In other terms, a loop with no other loops inside it.

(ii) Electric current - An electric current is a flow of electrical charge, electric charge flows when there is voltage present across a conductor.

(iii) Power - The rate of doing work or the rate of using energy is called Power.

(iv) network - A network is a collection of points or nodes joined by lines or edges.

d) Write some applications of maximum power transfer theorem, Radio communications, audio systems.

e) Why a single phase induction motor does not self start?

Ans - The produced stator flux is alternating in nature and at the starting, the two components of this flux cancel each other and hence there is no net torque.

$$\text{Power factor} = \frac{\text{Active Power}}{\text{Total Power}} = \frac{P}{S}$$

S = Total Power of Generators Consumed,


P = Power Consumed in the load
(Active Power)

Q = Reactive power stored in magnetic field - are wasted powers.

- (i) Power factor will be max. when either a.c. circuit is pure resistive or circuit is in resonance condition.
- (ii) min. when a.c. circuit is either pure inductive or pure capacitive or a combination of two.
- (iii) Can DC be applied to transformers?

No. If we supply DC then same current will move round in primary side, so the winding side (primary side) will get heated. So we cannot use DC to transformers.

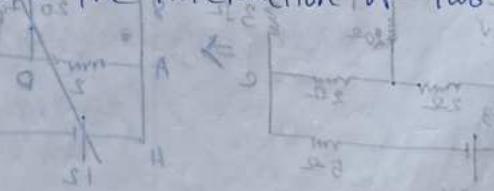- 1) Give some applications of D.C. motors.
Elevators, steel mills, rolling mills, locomotives, and excavators, like auto roti rotating machines > D.C. motors result from the interaction of two magnets.



- f) Give two basic speed control schemes of D.C. Shunt motor?
- Flux control - To control the flux, a rheostat is added in series with the field winding.
- Armature control - Speed control of a D.C. motor is directly proportional to the back EMF E_b and $E_b = V - I_a R_a$. That means, when supply voltage V and constant, then the speed is directly proportional to armature current I_a .
- g) Define Power factor. State the conditions under which it is (i) maximum (ii) minimum.

In electronics and electrical it will be max. when $\phi = 0^\circ$ and will be min. when $\phi = 90^\circ$.

Power factor is the ratio of ACTIVE POWER to the TOTAL POWER
(Apparent Power)

(12)

Q - current with - not out comes
 2 resistors
 (current entering to every left + 2
 total at terminals + 9
 current with)

J) determine the power factors of a
 RLC series circuit with $R = 50\ \Omega$

$$X_L = 80\ \Omega, X_C = 12\ \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\sqrt{50^2 + (80 - 12)^2}$$


$$= 84.40\ \Omega$$

$$\cos \phi = \frac{R}{Z} = \frac{50}{84.40} = 0.59$$

The power factor is $\cos \phi = 0.59$.


2) a) Determine current in $5\ \Omega$ resistor

by any one method.

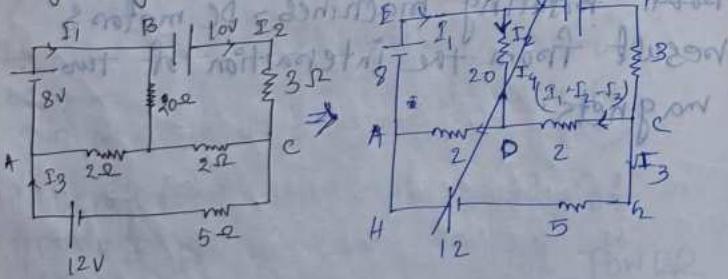


- I_1
 - I_2

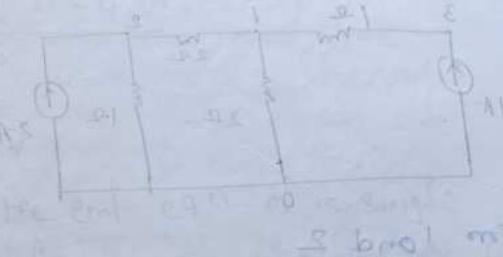total current at terminals (d)
 electric load is connected to



→ total net

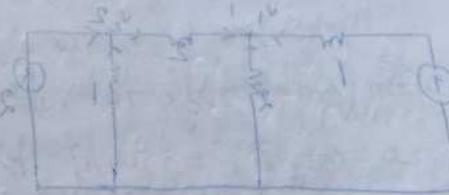

$$0 = R + \frac{V - sV}{s} + \frac{V - sV}{s}$$

$$0 = R + sV + V - sV$$


$$0 = sV - V + V + sV$$

$$0 = sV - V + V + sV$$


$$0 = sV - V + V + sV$$

$$0 = sV - V + V + sV$$

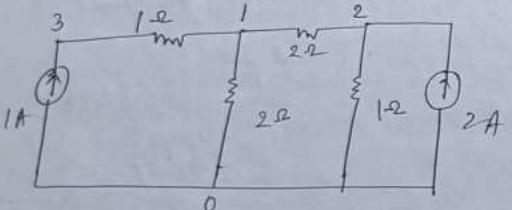(b) Determine the voltages 1 and 2 of the network by nodal analysis.



From 1 and 2

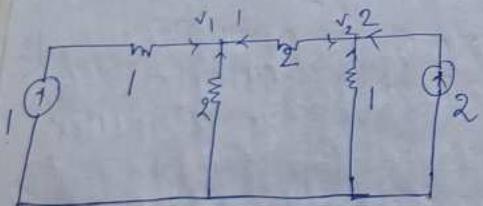

$$1 + \frac{v_1}{2} + \frac{v_1 - v_2}{2} = 0 \quad | \quad \frac{v_2 - v_1}{2} + \frac{v_2}{1} + 2 = 0$$

$$\Rightarrow 2 + v_1 + v_1 - v_2 = 0 \quad | \quad \Rightarrow v_2 - v_1 + 2v_2 + 4 = 0$$

$$\Rightarrow 2v_1 - v_2 = -2 \quad \text{---(I)} \quad | \quad \Rightarrow -v_1 + 3v_2 = -4 \quad \text{---(II)}$$

$$2v_1 - v_2 = -2 \quad \text{---(I)} \times 1$$

$$-v_1 + 3v_2 = -4 \quad \text{---(II)} \times 2$$

$$\begin{array}{l} 2v_1 - v_2 = -2 \\ -2v_1 + 3v_2 = -8 \end{array} \quad | \quad \begin{array}{l} (1) \times 2 \\ (2) \times 1 \end{array}$$

$$\Rightarrow 5v_2 = -10 \quad | \quad \begin{array}{l} (1) \times 2 \\ (2) \times 1 \end{array}$$

$$\Rightarrow v_2 = -2$$

$$\text{mag } v_2 = 2\text{V}$$

$$\begin{array}{l} 2v_1 - v_2 = -2 \quad \text{---(I)} \times 3 \\ -v_1 + 3v_2 = -4 \quad \text{---(II)} \times 1 \end{array}$$

$$\begin{array}{l} 6v_1 - 3v_2 = -6 \\ -v_1 + 3v_2 = -4 \end{array} \quad | \quad \begin{array}{l} (1) \times 1 \\ (2) \times 1 \end{array}$$

$$5v_1 = -10$$

$$\Rightarrow v_1 = -2$$

$$\text{mag } v_1 = 2\text{V}$$

3) a) Derive the emf eqn of a single phase transformer.

q; fm sinus
By faraday's law of electromagnetic induction emf induced is for a single turn.

$$e = -\frac{d\Phi}{dt}$$

For N no of turns.

$$e = N \left\{ -\frac{d\Phi}{dt} (\text{fm sinus}) \right\}$$

$$= -N \cos \omega t \cdot \Phi_m$$

$$e = -\phi_m N \cos(\omega t)$$

$$\Rightarrow q_m n \cdot 2\pi f \cdot \sin(wt - \frac{\pi}{2})$$

$$t_{\max} \text{ such that } \omega t - \frac{\pi}{2} = \frac{\pi}{2}, \text{ i.e. } \sin(\omega t - \frac{\pi}{2}) = 1$$

$$\therefore e_{\max} = \varphi_m \cdot n \cdot 2\pi f$$

$$From s = \frac{l_{max}}{\sqrt{2}} = 4.49 N \varphi mf$$

Primary induced emf

E1

$$F_2 = 4.44 f \Phi_m N_2$$

b) A $200/50\text{ V}$, 50 Hz single phase transformer is connected to a 200 V , 50 Hz supply with secondary air-tight pen.

(i) What is the value of max flux through the core, if the primary winding has 400 turns?

(ii) What is the peak value of flux if the primary voltage is 200 V , 25 Hz and what happens to no load current? [Data missing]

$$V_1 = 200 \text{ V} \quad f_s = 50 \text{ Hz}$$

$$F_1 = 4.49 \cdot f(\rho_m N)$$

$$\text{vii) } \Rightarrow q_m = \frac{200}{4.44 + 50 + 410} \\ \Rightarrow 2.25 \times 10^{-3} \text{ Nm}$$

ii) $E_1 = 200 \text{ V}$, $f = 25 \text{ Hz}$

$$q_m = \frac{200}{444 \times 252400} e^{-0.125} = 1.08 \times 10^{-3} \text{ A}$$

$$T_0 = T_c + T_m$$

$$= I_0 \cos \varphi + I_0 \sin \varphi$$

No load current is independent of flux or max flux. i.e. there is no relation between flux and no load current. So it will remain unchanged.

4) a) sketch the o.c. c of DC generation done (Previous)

b) A series RLC circuit has 3 ohm resistance, 2 mH inductance and 25.14F capacitance and is connected to 220V, 60Hz supply. Find i) the current ii) the Power factor, iii) the voltage drop across each element.

$$R = 3\Omega, L = 2 \times 10^{-3} \text{ H}, C = 25.14 \text{ F}$$

$$V = 220 \text{ V}, f = 60$$

$$XL = 2\pi f L = 2 \times 10^{-3}, XC = \frac{1}{2\pi f C} = 10.568 \Omega$$

$$Z = \sqrt{R^2 + (XL - XC)^2} = \sqrt{3^2 + (10.568 - 0.75)^2} = 10.913 \Omega$$

$$(i) I_L = \frac{220}{10.913} = 2.01 \text{ A}$$


$$(ii) \cos \phi = \frac{R}{Z} = \frac{3}{10.913} = 0.27$$

$$(iii) V_R = IR = 2.01 \times 3 = 6.03 \text{ V}$$


$$V_L = IX_L = 2.01 \times 0.75 = 1.507 \text{ V}$$

$$V_C = XC = 2.01 \times 10.568 = 21.24 \text{ V}$$

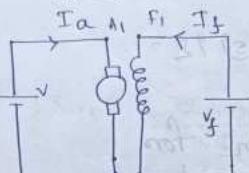
5) a) Draw the circuit for various types of DC motor.



(a) Separately excited

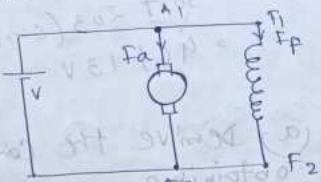

(b) Shunt

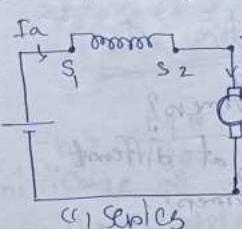

(c) Series

b) A DC long shunt compound generator delivers a load current of 200 A at 450 V. The resistance of the armature, series field and shunt field are 0.03Ω, 0.015Ω and 150Ω. Calculate the emf induced in the armature. Allow a brush drop of 1V/brush.

$$I_L = 200 \text{ A}, V = 450, R_a = 0.03 \Omega, R_{sh} = 0.015 \Omega$$

$$R_{sf} = 150 \Omega, B_{SD} = 2 \text{ V}$$

$$I_{sh} = \frac{450}{150} = 3 \text{ A}$$

$$I_a = I_{sh} = I_L + I_{sh} = 200 + 3 = 203 \text{ A}$$

$$\begin{aligned} f_2 &= V + I_a R_{\text{load}} + B S D \\ &= 950 + 203(0.03 + 0.015) + 2 \\ &= 961.13 \text{ V} \end{aligned}$$

6) (a) Derive the condition for obtaining max Power from a Source to resistive load.
done (Previous)

(b) What is an ideal transformer?
Draw phasor diagram at different loads for an ideal transformer.
done.

7) (a) Write short notes on RMS values of AC waveforms.
done

(b) An alternating voltage is given by $V = 230 \sin 314t$. Calculate (i) frequency (ii) maximum value (iii) average value
(iv) RMS value.

$$\begin{aligned} \text{(i)} \quad f &= \frac{314}{2\pi} = 50 \text{ Hz} \\ \text{(ii)} \quad V_m &= 230 \text{ V} \\ \text{(iii)} \quad V_{\text{rms}} &= \frac{V_m}{\sqrt{2}} = \frac{230}{\sqrt{2}} = 162.63 \text{ V} \end{aligned}$$

$$\text{(iii)} \quad V_{\text{av}} = \frac{2 \times 230}{\sqrt{2}} = 166.42 \text{ V}$$

$$\begin{aligned} \text{(iv)} \quad V_{\text{rms}} &= \frac{230}{\sqrt{2}} \\ &= 162.63 \text{ V} \end{aligned}$$

DC motors

[13] 5/22


$$E_b = \frac{P \phi N Z}{60 A}$$

- significance of back emf, running principle, definitions, classification, characteristics, torque etc., speed control.

[
P = Pole
 ϕ = flux
N = speed
Z = no. of conductor
A = no. of parallel path]

- If I_a is changed what will be the effect over back emf (E_b)?

series motor

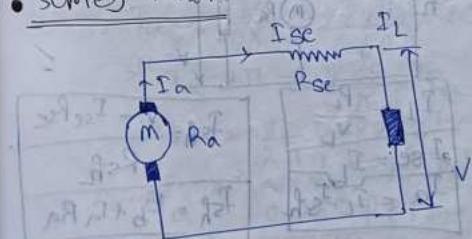

I_a = Armature current
 I_{se} = Series field current


$B \& D$ = Brush control drop
 V = terminal voltage, R_a = armature resistance

$$\begin{aligned} E_b &= V - I_a(R_a + R_{se}) - B \& D \\ I_a &= I_{se} > I_L = \frac{R_a}{V} \end{aligned}$$

$$F_b = I_L(R_a + R_{se}) + V - BCD$$

$$F_b = V - BCD - I_a(R_a + R_{se})$$

- DC Shunt motors

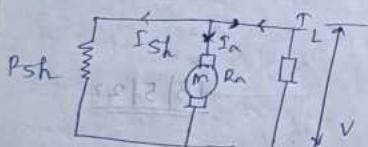


R_{sh} Shunt field resistance
 I_{sh} = shunt field current


$$I_{sh} = \frac{V}{R_{sh}}$$

$$\begin{aligned} E_b &= V - I_a R_a - BCD \\ I_a &= I_{sh} + I_L - I_h \end{aligned}$$

- Compound motors

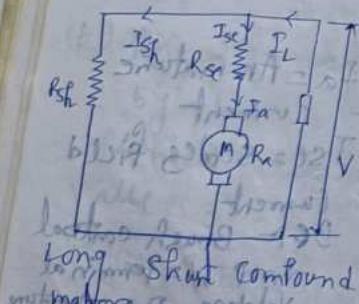

Long shunt compound

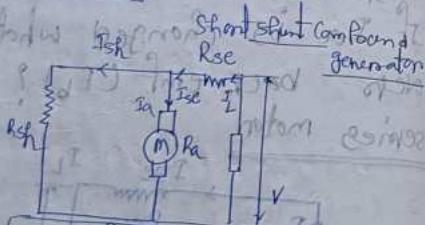

$$\begin{aligned} I_L &= \frac{P_L}{V_L} \\ I_{se} &= I_L - I_a \\ I_a &= I_L - I_{sh} \end{aligned}$$

$$\begin{aligned} I_a &= I_L - I_{sh} \\ I_{sh} &= \frac{N}{R_{sh}} \\ F_b &= V - I_a R_a - I_{sh} R_{se} - BCD \end{aligned}$$

$$\begin{aligned} I_a &= I_L - I_{sh} \\ I_{se} &= I_a \end{aligned}$$

$$\begin{aligned} E_b &= V - I_a R_a - I_{sh} R_{se} - BCD \\ &= V - I_a (R_a + R_{se}) - BCD \end{aligned}$$

- Derive the torque equation for dc motors.

- Ammature torque

Torque = force \times distance = $F \times R$ Nm

$$\text{Work done} / \text{sec} = F \times (2\pi R) \times \frac{N}{60}$$

- w/sec or power developed is given by

$$P_m = w T_a$$

$$\Rightarrow P_m = T_a \times \frac{2\pi N}{60} \text{ W/s or W}$$

Also, the electrical equivalent of mechanical

- Speed control of dc motors

Power developed in the armature is $F_b I_a$ watts

$$T_a \times \frac{2\pi N}{60} = F_b I_a$$

$$\text{whereas } E_b = \frac{\phi Z NP}{60A} V$$

$$T_a \times \frac{2\pi N}{60} = \frac{Z \phi NP}{60A} \times I_a$$

$$\Rightarrow T_a \times 2\pi = \frac{\phi Z P}{A} \times I_a$$

$$\Rightarrow T_a = \frac{1}{2\pi} \cdot \frac{\phi Z P}{A} I_a$$

$$T_a = 0.159 \frac{\phi Z P}{A} I_a = \left(\frac{0.159 Z P}{A} \right) \phi I_a$$

This implies that, $F_b T_a \propto \phi I_a$

For a series motor, before saturation, as the field winding carries armature current we have $\phi \propto I_a$

- Speed control of DC motors - The speed of a motor is given by

$$N = \frac{E_b(60A)}{P\phi^2} = \frac{V - I_a R_a}{P\phi^2} \cdot \left(\frac{C_o A}{P}\right) = K \frac{V - I_a R_a}{\phi^2}$$

where K is a constant, V is the supply voltage, I_a is the armature current, R_a is the armature resistance and ϕ is the flux per pole. we can control the speed of DC motors by varying:

1. Flux per pole ϕ (flux control)
2. Armature resistance control
3. voltage control

Characteristics of DC motors

A motor has both electrical and mechanical characteristics. There are three important characteristics worth noting:

1. Armature torque versus armature current is T_a/I_a . This is also called electrical characteristic.
2. Speed versus armature current (N/I_a).
3. Speed versus armature torque (N/T_a). This is also called mechanical characteristic. The following relation are to be discussed while discussing the characteristics of motors:
 1. $T_a \propto \phi I_a$
 2. $N \propto \frac{E_b}{R_a}$
 3. ϕ is constant for shunt motors.

4. ϕ is proportional to I_a for a series motor, before saturation.

1. T_a/I_a char-

2. N/I_a char-

3. N/T_a char-

(for series motor)

Applications of DC motors

i) Shunt motor application - Since shunt motor has approximately constant speed, it can be used for lathe line-shaft drives, pumps, machine tools, fans, wood working machines etc.

ii) Series motor applications - Since series motor has high starting torque, it can be used for electric traction, trams, cars, railway cars, elevators etc.

iii) Cumulative compound motor application - Since this motor has high starting torque, it can be used for rolling mills, elevators, gears, power fans etc.

(1) Significance of back emf - Back emf is very significant in the working of a dc motor. The presence of back emf makes the d.c. motor a self regulating machine i.e., it makes the motor to draw as much armature current as is just sufficient to develop the torque required by the load.

(2) Classification of dc motor-

i) series motor

ii) shunt motor

iii) compound motor

long shunt field short shunt field compound motor (cumulative/differential)

(3) If I_a changed what will be the effect upon E_b ?

As the armature speed increases, the back emf E_b also increases and causes the armature current I_a to decrease. The motor will stop accel-

erating when the armature current is just sufficient to produce the reduced torque required by the load.

(1) A 250V DC shunt motor takes 40A at full load. The resistance of the armature and shunt field winding are 0.5Ω and 250Ω respectively. Determine the back emf at full load.

$$V = 250V, I_L = 40A, R_a = 0.5\Omega$$

$$R_{sh} = 250\Omega$$

$$I_a = I_L - I_{sh} \left[F_{sh} = \frac{V}{R_{sh}} \right]$$

$$= 40 - 1 \left[\frac{250}{250} = 1 \right]$$

$$= 39A$$

$$\therefore E_b = 250 - 39 \times 0.5$$

$$= 230.5V$$

(2) A 250V DC series motor has an armature resistance of 0.05Ω and series field resistance of 0.02Ω. It is running at a speed of 200 rpm taking a current of 30A. Determine its speed when it takes current of 23A.

$$V = 250V, R_a = 0.05, R_{sf} = 0.02, I_1 = 30A$$

$$\therefore I_{sh} = \frac{250}{0.02} = 12500A$$

$$f_a = 30 \Rightarrow I_{sc} = I_L$$

$$E_b = 250 - 30(0.02 + 0.05)$$

$$\therefore 247.9 \text{ volt } \text{base } 20 \text{ V.D.C}$$

When, $I_a = 25 = I_{sc}$, $E_L = 25 \text{ V.D.C}$

$$E_b = 250 - 25 \times 0.07$$

$$\frac{E_b}{E_{b2}} = \frac{n_1}{n_2} \times \frac{F_1}{F_2} \left[\because \frac{E_b}{E_{b2}} = \frac{P\phi N}{60A} \right]$$

$$\therefore \frac{247.9}{248.25} = \frac{300}{n_2} \times \frac{25}{50}$$

$$\therefore n_2 = \frac{300 \times 25}{304.247.9} \times 1 - 0.07$$

$$= 751.05 \text{ rpm}$$

We have $2.0 > 2.5 - 0.2^2 = 2.3$

$$\frac{N_2}{n_1} = \frac{E}{E_b} \times F_1$$

$$\therefore \frac{N_2}{n_1} = E_2 \times F_1 / k_N$$

$$\therefore n_2 = \frac{E_b}{E_2} \times F_2 \text{ and base } 20 \text{ V.D.C}$$

$$\text{given } n_2 = 248.25 \times 30 + 9 \text{ rpm}$$

$$\therefore \frac{E_b}{E_2} = \frac{247.9 \times 25}{125 + 9} \text{ turns/wire}$$

$$60C = 125 \times 25 \times 30 + 9 \text{ turns/wire}$$

$$60C = 1081 \text{ rpm}$$

$$60C = 1080 \times 30 + 9 \text{ turns/wire}$$

$$60C = 32409 \text{ turns/wire}$$

$$60C = 1080 \times 30 + 9 \text{ turns/wire}$$

• emf eqn of fm dc generators

ϕ = flux per pole, P = pole no.

N = Spced

Z = no. of conductors

A = No. of Parallel Paths

(where $A > 2$ (Wave Wound))

$A = P$ (lap Wound)

E_g = generated emf

We know, $d\phi = P \times \phi \text{ Wb}$

Time taken to complete one revolution -

$$dt = \frac{\pi}{60} \text{ sec} = \frac{60}{\pi} \text{ sec}$$

We know that, emf generated per conductor

$E_g / \text{Per conductor}$, [According to the law of electro-magnetic induction]

$$= \frac{d\phi}{dt}$$

$$= \frac{P\phi}{(\pi/60)} = \frac{P\phi}{60/\pi} = \frac{P\phi N}{60}$$

No. of conductors / Parallel Path = $\frac{Z}{A}$

\therefore generated emf = $(E_g / \text{Per conductor}) \times (E_g)$

$(\text{No. of Conductors})$

$\text{Parallel Path})$

$$E_g = \frac{P\phi Z N}{60A}$$